

Unit 2 YouTube references

Current and Resistance

In the laboratory, solid copper rods are used to carry large currents. Current flows from a section with a diameter of 4.00 cm to a section with a diameter of 1.00 cm.

You measure that the potential difference across a 2.00 m segment of the bigger section of the rod is 13.4 mV.

- What is the potential difference across a 1.00 m segment of the smaller section of the rod?
- Compare the speed of the electrons in the smaller and in the bigger section of the rod.


The resistivity of copper

is $\rho_{\text{copper}} = 1.69 \times 10^{-9} \Omega\text{m}$.

The number of charge carriers per unit of volume for copper is

$n_{\text{copper}} = 8.49 \times 10^{28} \text{ (e}^- \text{)}/\text{m}^3$.


You Tube: <http://youtu.be/4I-QvEmOPUc>

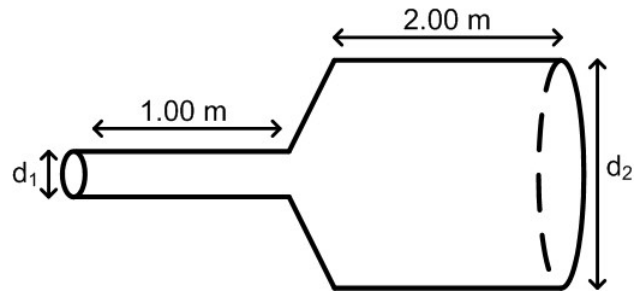

Resistors in series and in parallel

Consider the circuit below. All resistors are 20 Ω .

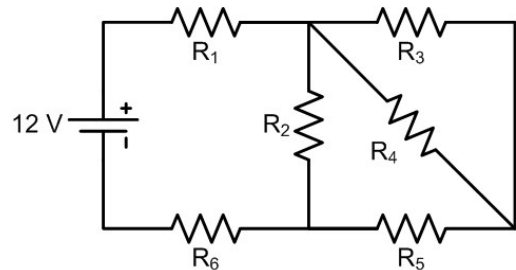- What is the equivalent resistance of this circuit?
- Find the potential difference across all resistors, and what is the current through the resistors



You Tube: <http://youtu.be/YsvAtGHHHWI>

Circuits, example 1

Consider the following circuit:


- What is the current in this circuit?

What is the power used by the resistors?

What is the power provided by or used by the batteries ?

What is the potential difference V_{AC} ?


YouTube: <http://youtu.be/CfoCqhdVpaU>

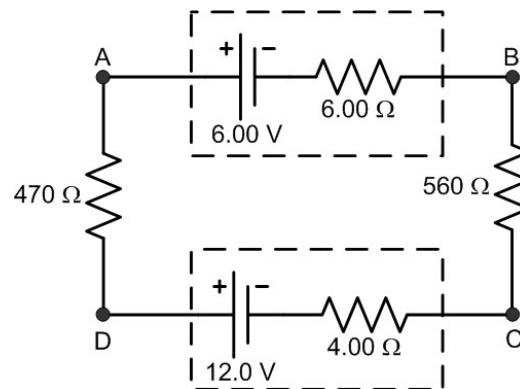

Multi-loop circuit

Consider the circuit below. Find all the currents in the circuit.

You Tube: <http://youtu.be/0vwe1XLZsCo>

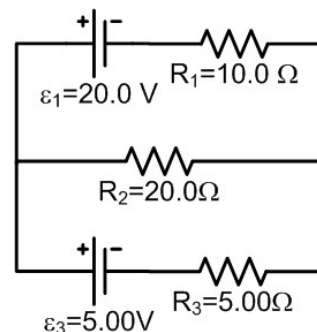


Multi-loop circuit and power in an electric circuit

The following circuit contains a battery with an emf of 25 V that delivers 25 W of power. The battery delivers an unknown amount of current that is less than 2.0 A.

How much power does the unknown battery deliver or use?

YouTube: http://youtu.be/YWAuoy_qleU

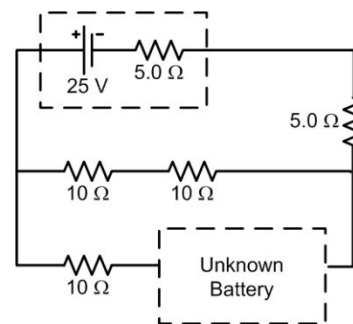

Capacitors

The plates of an air-filled parallel plate capacitor are 1.00 cm apart.


- How big would the plates have to be for the capacitor to have a capacitance of 1.00 μF ?
- Dielectric breakdown in air occurs when the electric field is greater than 3.00 MV/m. What is the maximum charge that can be placed on the 1.00 μF capacitor?
- How big would the capacitor have to be if we put a slab of ceramic between the plates? ($\kappa = 173$ – a very high value)
- Do you think that the ceramic-filled capacitor can carry as much charge as the air-filled capacitor?

YouTube: <http://youtu.be/q8qDg8kDS3Y>

Capacitors in series and in parallel

Consider the following arrangement of capacitors.

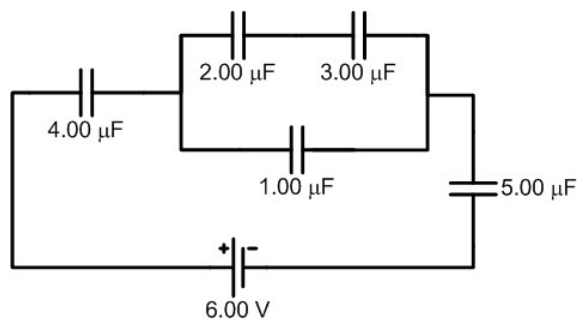- Find the total capacitance of the circuit.
- Find the charge on each capacitor as well as the potential difference across each capacitor



YouTube: http://youtu.be/CfloCOQ2_1U

Reconnected capacitors

A $5.00 \mu\text{F}$ capacitor is charged to 10.0 V , and a $10.0 \mu\text{F}$ capacitor is charged 5.00 V .


- How much energy is lost or gained when the capacitors are reconnected positive plate to positive plate?
- How much energy is lost or gained when the capacitors are reconnected positive plate to negative plate?

YouTube: <http://youtu.be/3iH5vs-2rN0>

Capacitors in circuits

The following circuit diagram is a simplified version of the flash circuit inside a disposable camera. The user charges the capacitor by pressing on a button (switch 1), and when the user snaps a picture, the shutter presses switch 2 which allows the capacitor to discharge quickly through the flash bulb.

- What is the time constant of the circuit when the capacitor is charging?
- What is the potential difference across the capacitor after one time constant?
- The flash bulb requires an initial potential difference of 350 V in order to 'flash'. How much time does it take to accumulate this potential difference across the capacitor?
- What is the time constant of the circuit when the capacitor is discharging?
- What is the potential difference across the flash bulb after one time constant?
- How long does it take for the potential difference across the capacitor to drop to 10.0 V ?

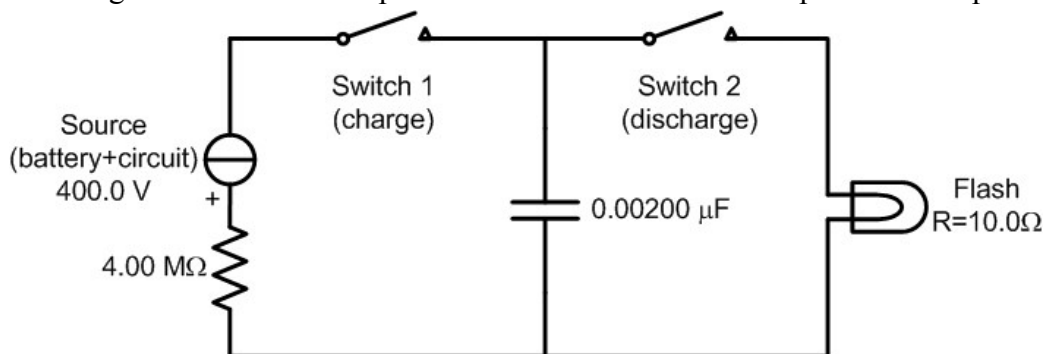


YouTube: <http://youtu.be/9fRIW6ZN6n0>

RC Circuit

Consider the following circuit (the capacitor is initially uncharged):

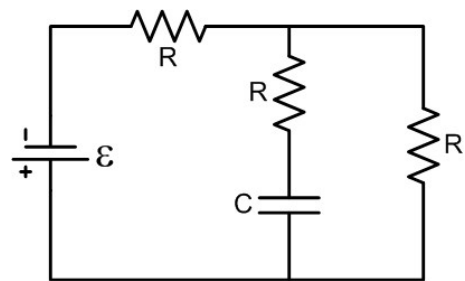- What is the initial current through the circuit?
- After a long, long time what is the current through the circuit?
- What is the maximum potential difference across the capacitor?



YouTube: <http://youtu.be/C1zmDdPvzcM>