

LAKSHYA JEE

LAKSHYA KO HAR HAAL ME PAANA HAI



Electric Potential & Capacitance

-Er. Rohit Gupta



Today's GOALS!

symmetric circuits





Symmetry circuit


1

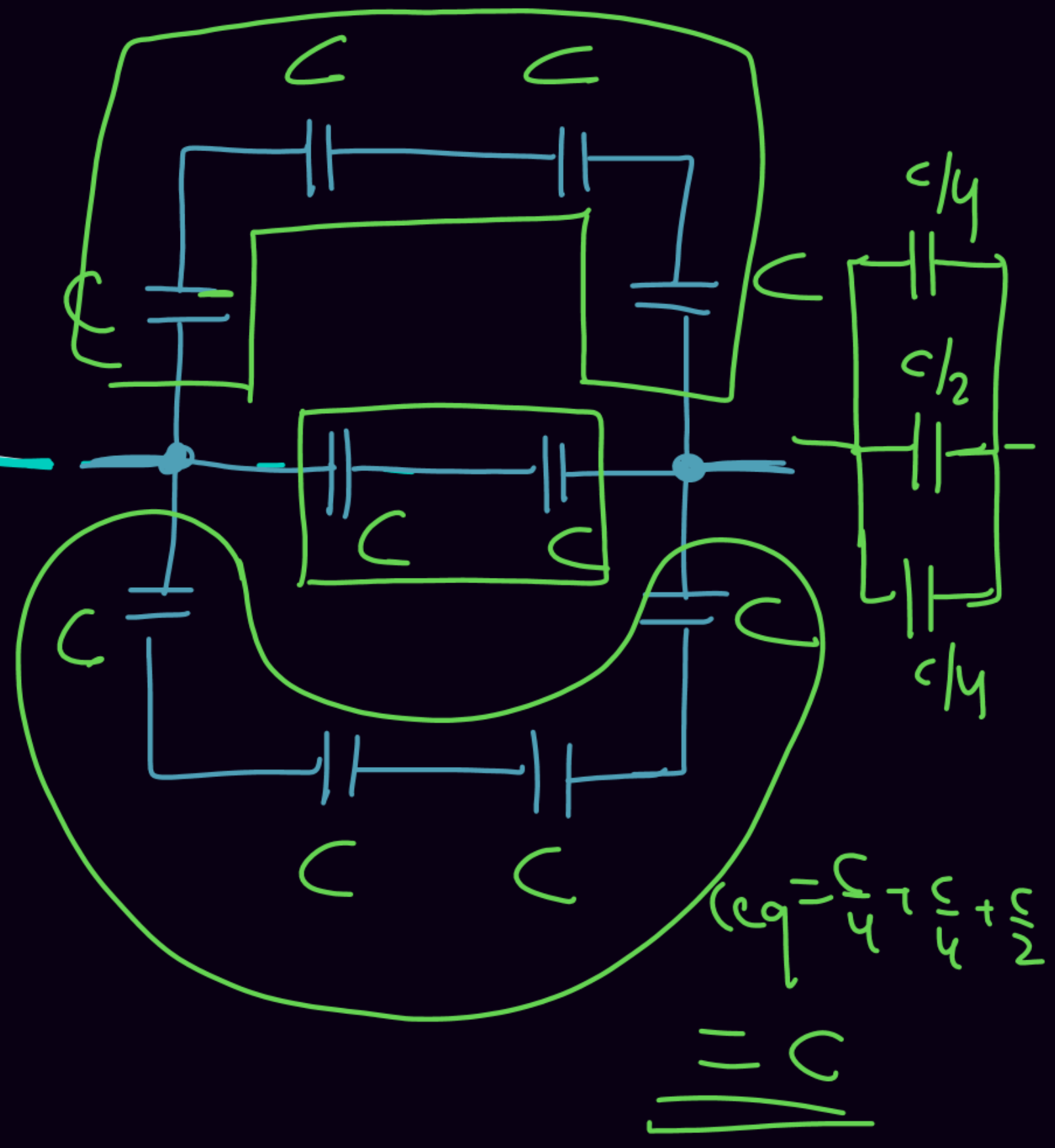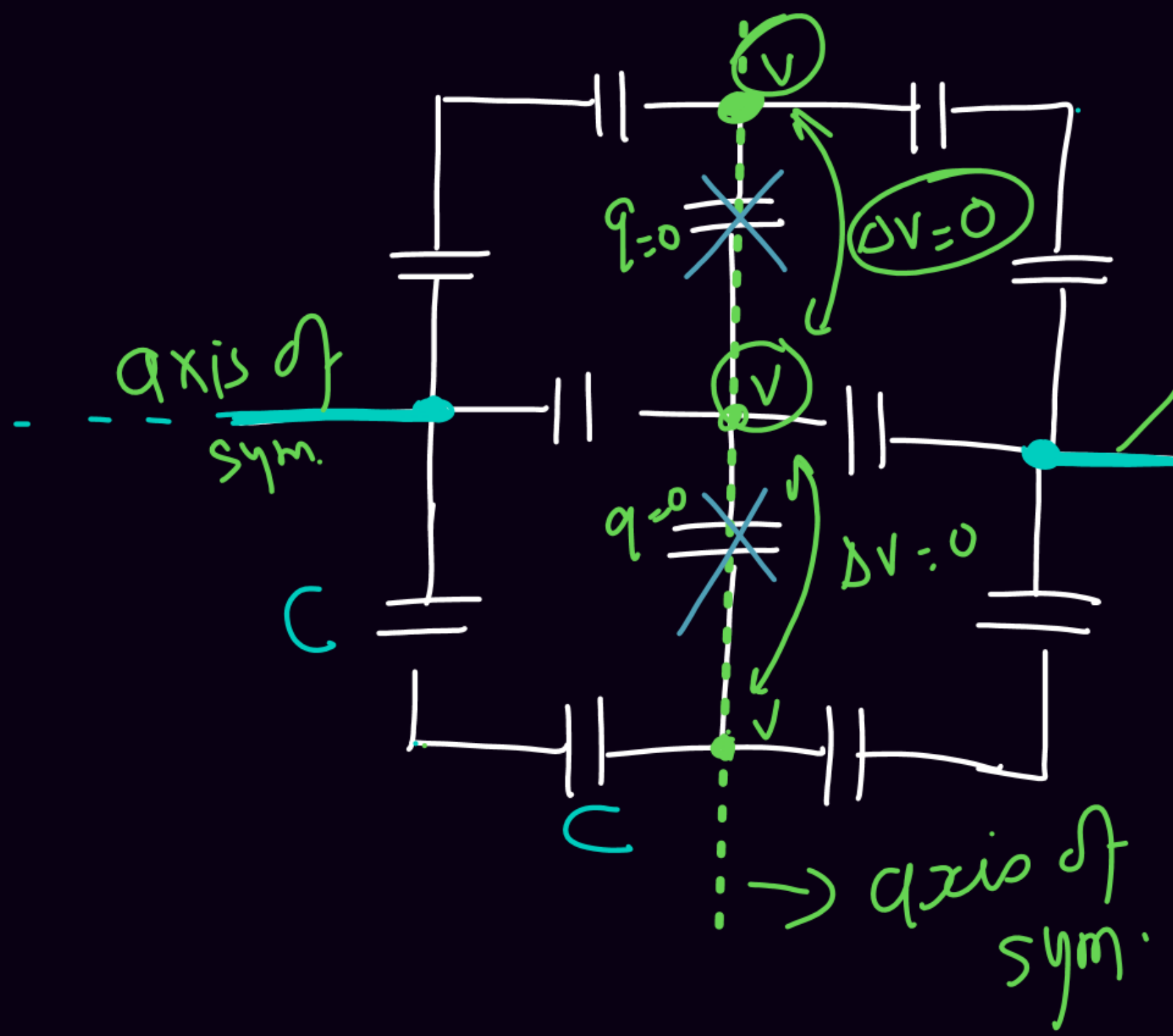If the line joining the terminals becomes axis of symmetry then the perpendiculars drawn on it will carry equipotential junctions.






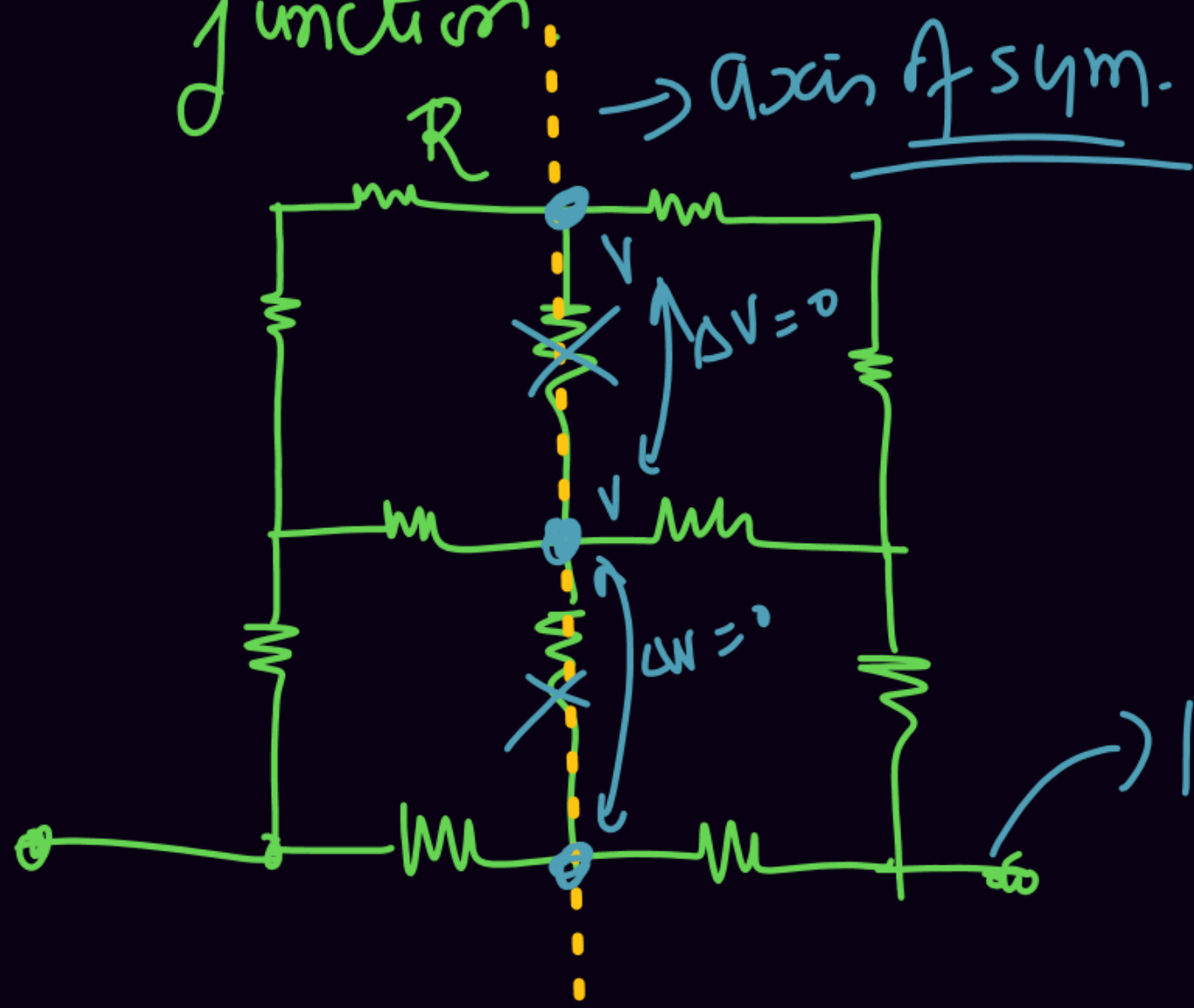2 If the \perp bisector to the line joining the terminals becomes axis of symmetry then this \perp bisector will carry equipot. junction.



\equiv

Not an axis of sym.

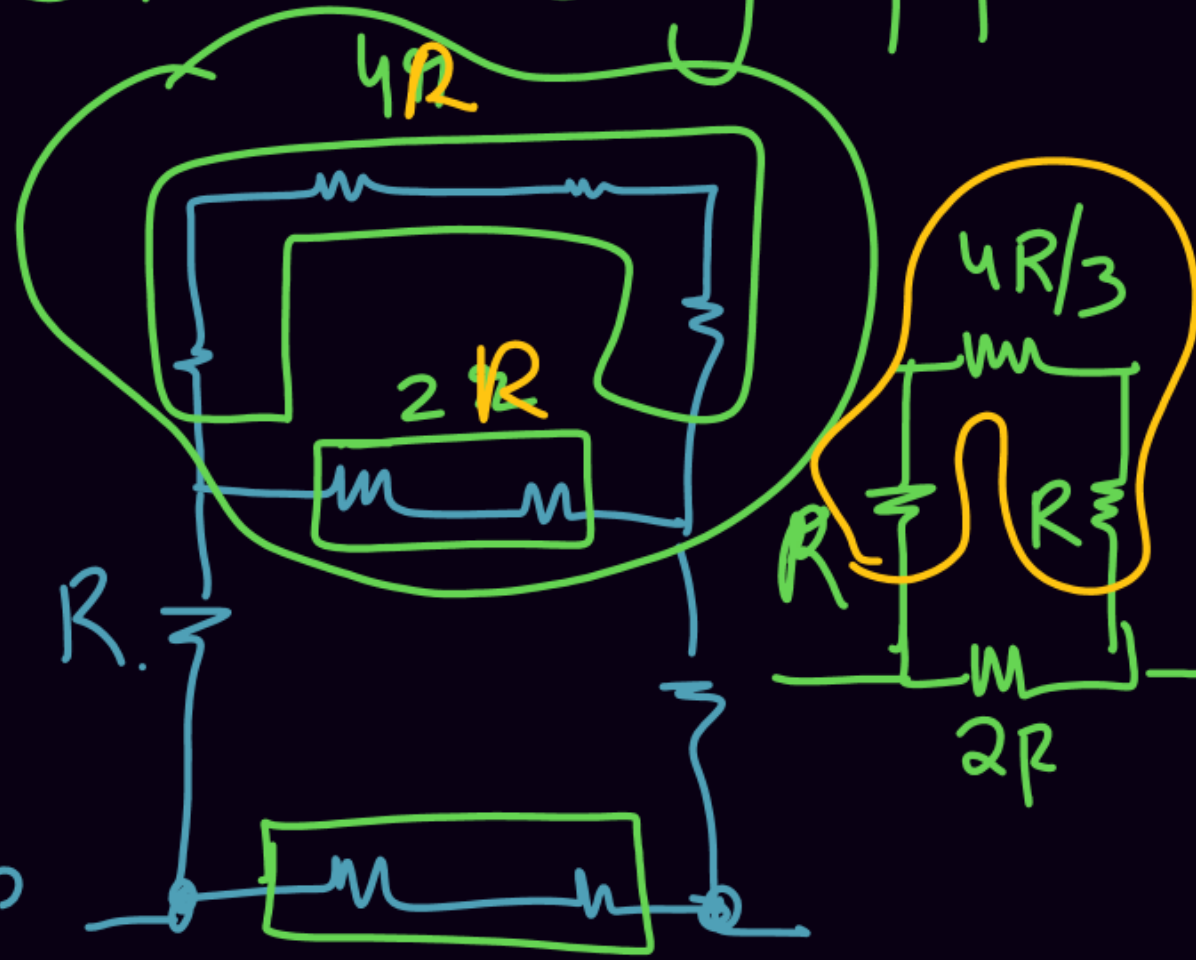

$$\left(\frac{4R}{3} + 2R \right) \parallel 2R$$


$$\left(\frac{4R}{3} + 2R\right) \parallel 2R$$

$$\frac{10R}{3} \parallel 2R$$


$$\frac{\frac{10R}{3} \times 2R}{\frac{10R}{3} + 2R}$$

$$= \frac{20R}{\cancel{3} / 16}$$

$$= \frac{5R}{5}$$

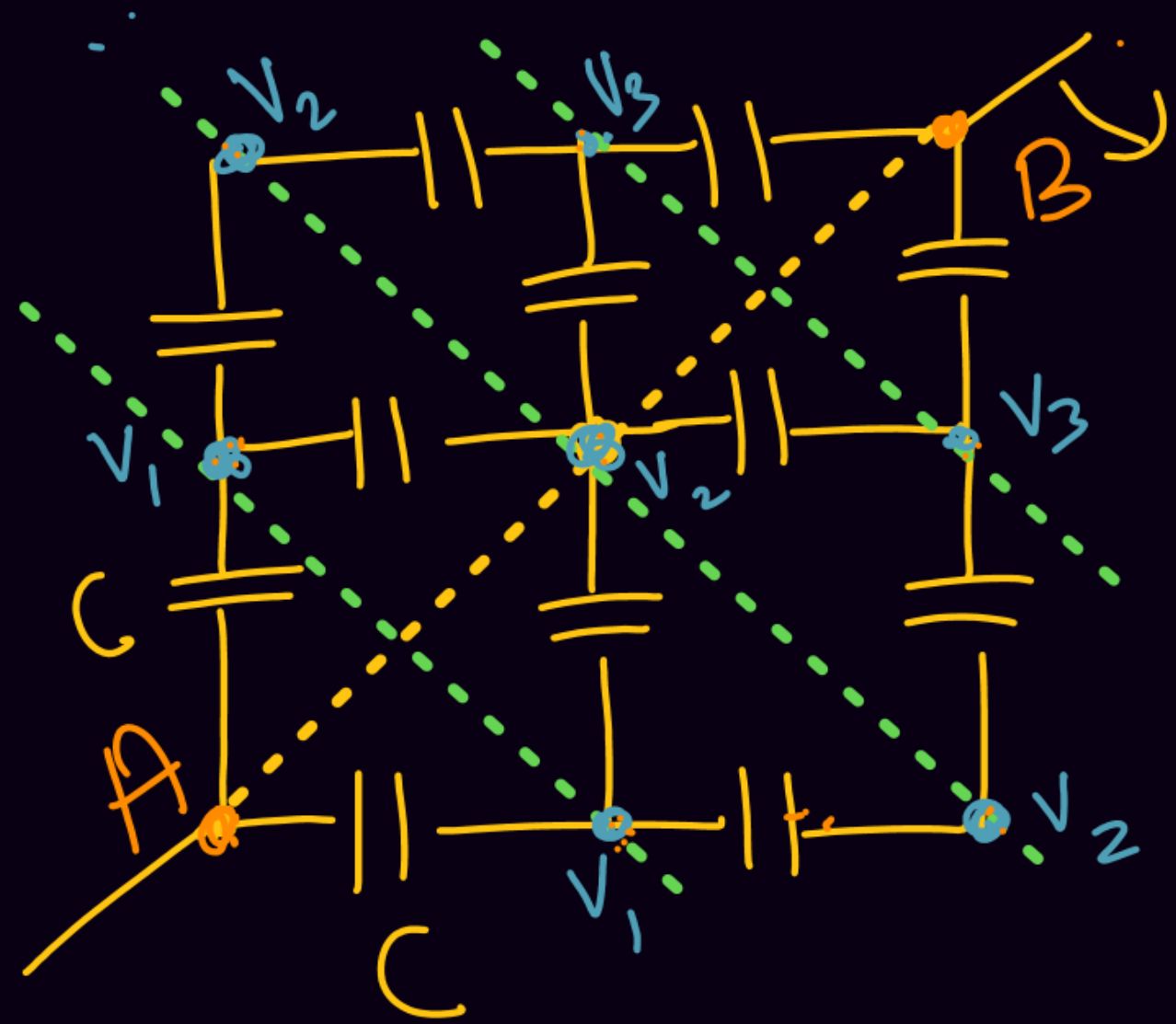

axis of sym

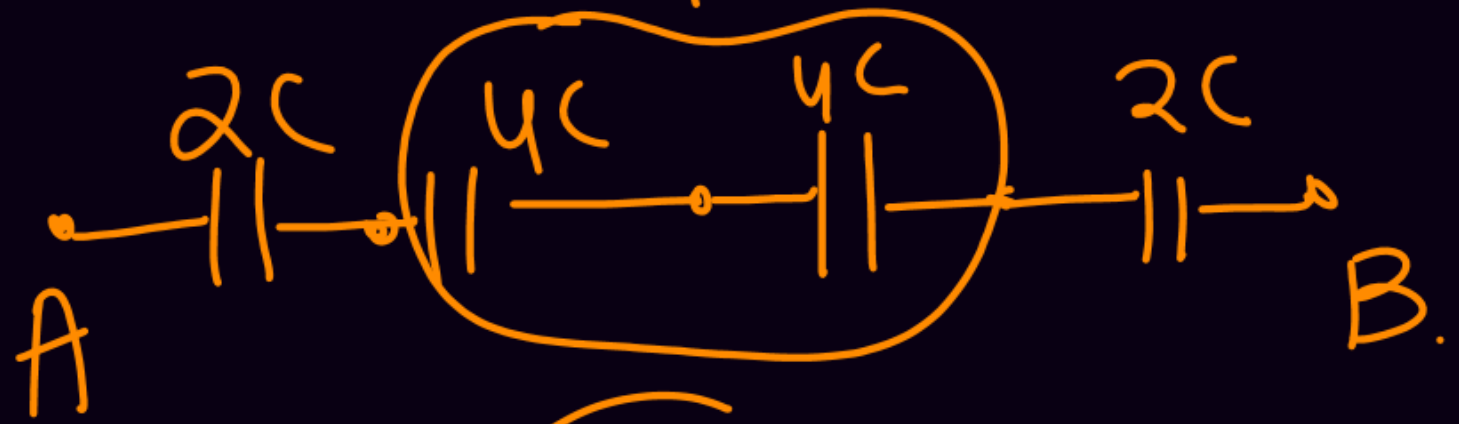

$$\frac{2C}{3}$$



Ans

2



Find C_{eq} ?

$$C_{eq} = 3C$$

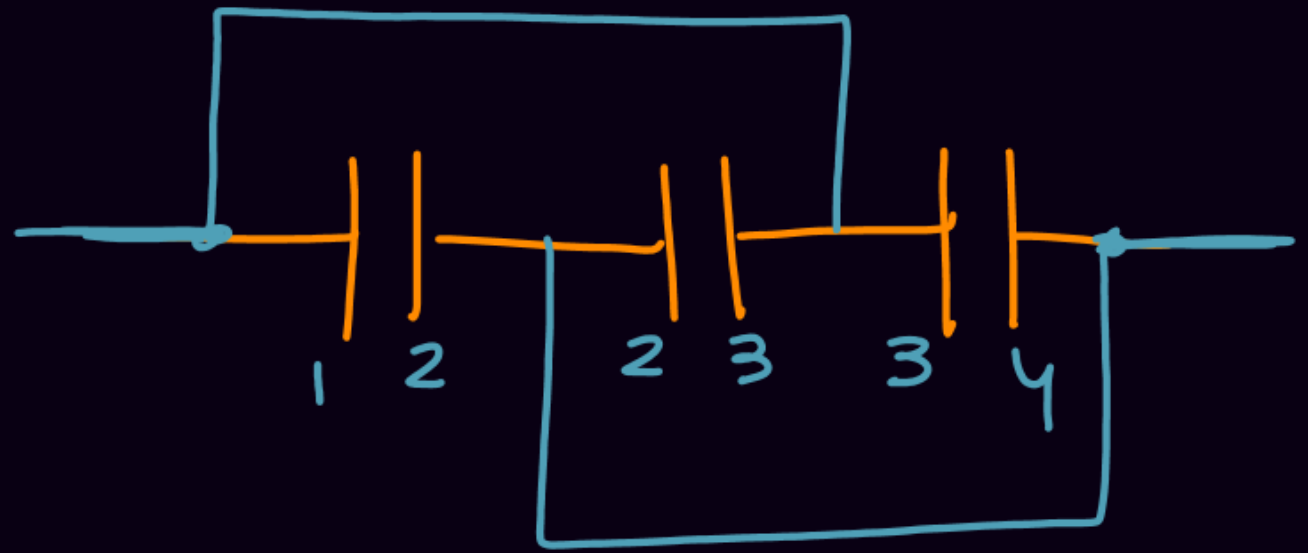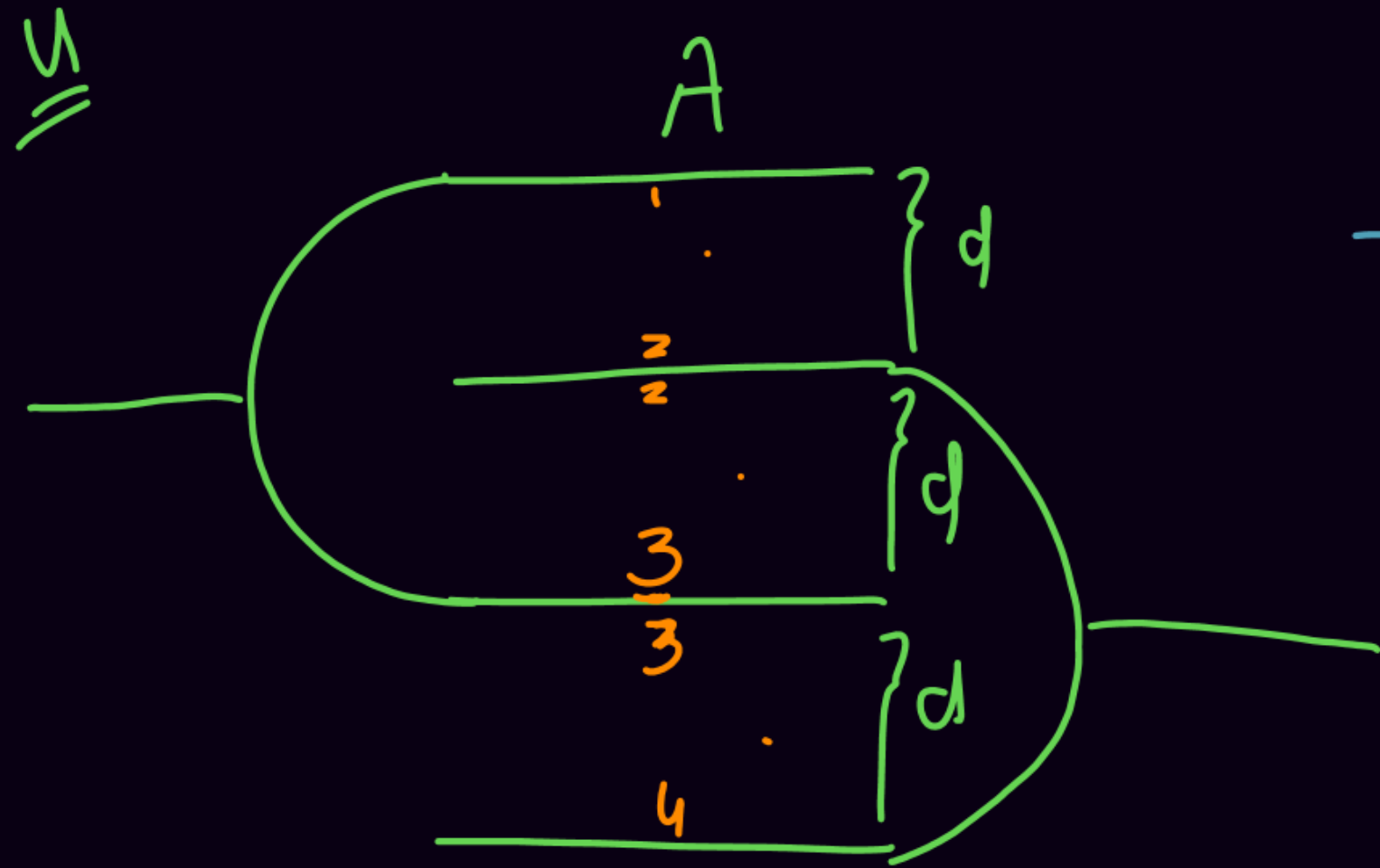


Ans 3C


$$\boxed{\frac{3\epsilon_0 A}{d}}$$

5

Wheatstone bridge

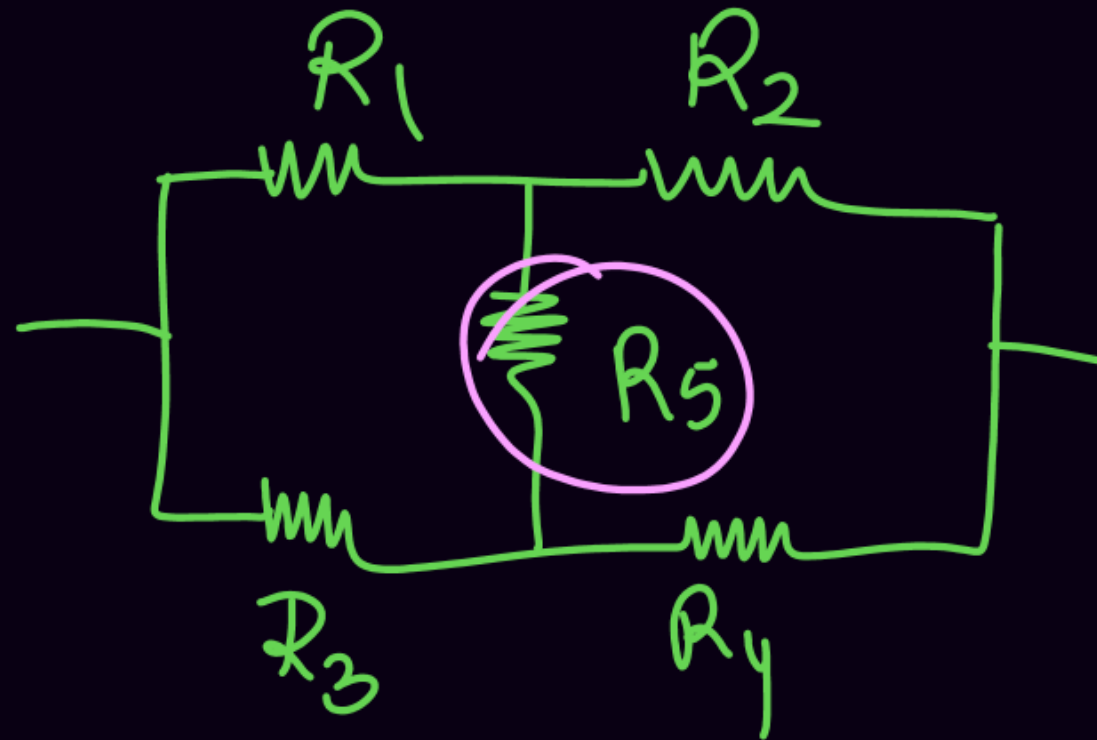


$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$

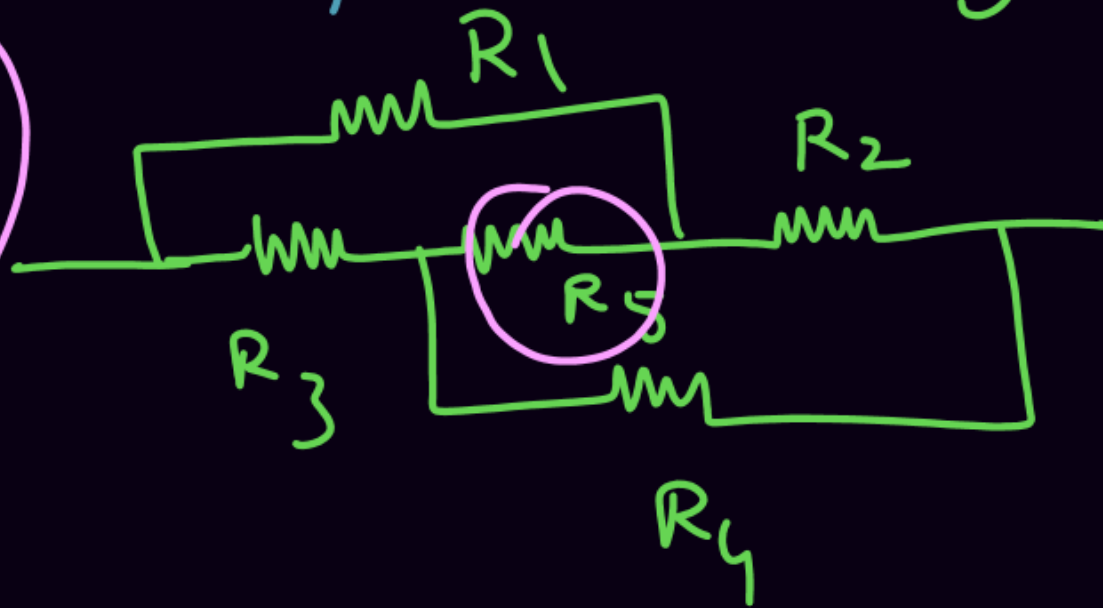


6

Extended wheatston bridge

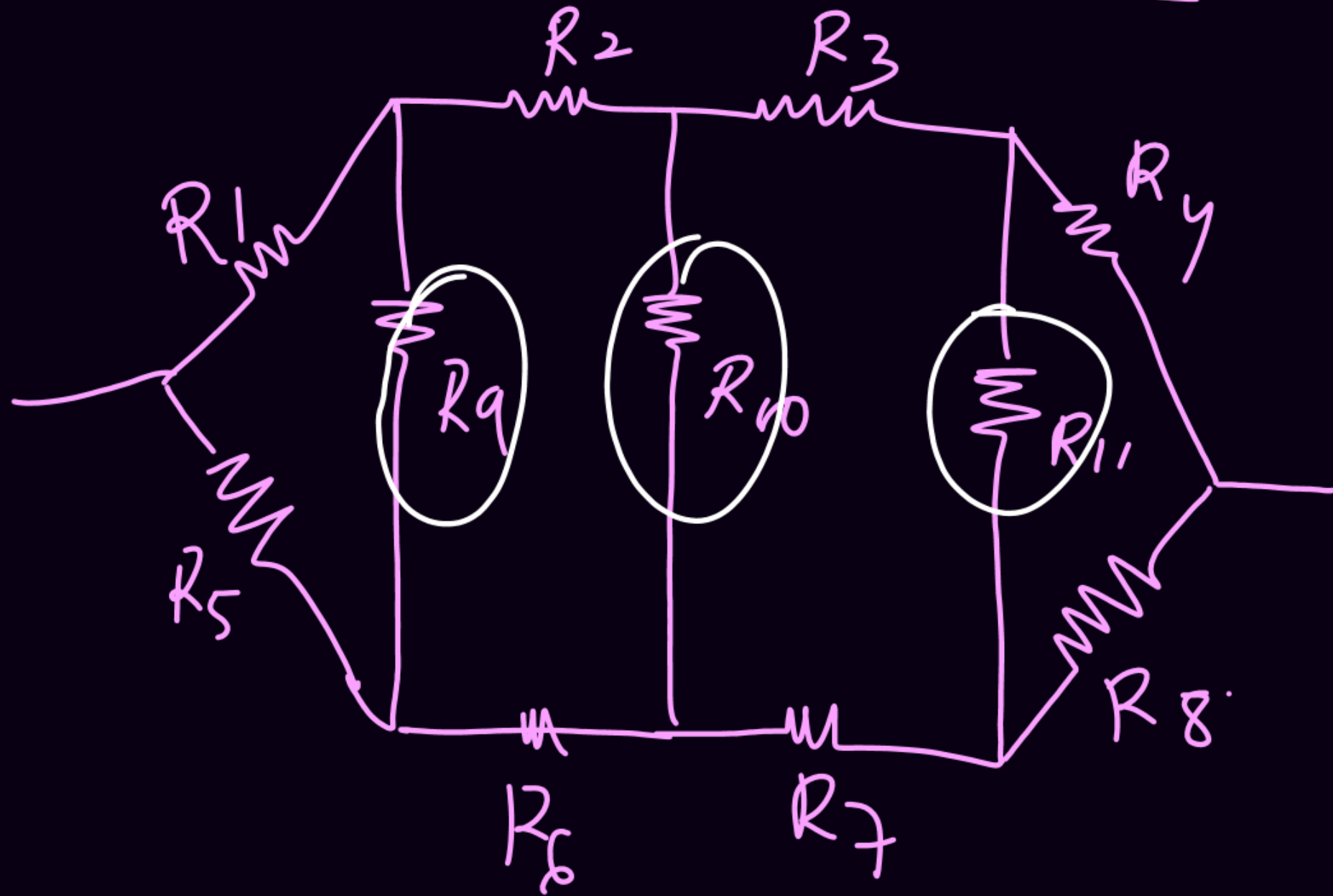

$$\frac{R_1}{R_5} = \frac{R_2}{R_6} = \frac{R_3}{R_7} = \frac{R_4}{R_8}$$

R_9, R_{10}, R_{11}
will be removed.

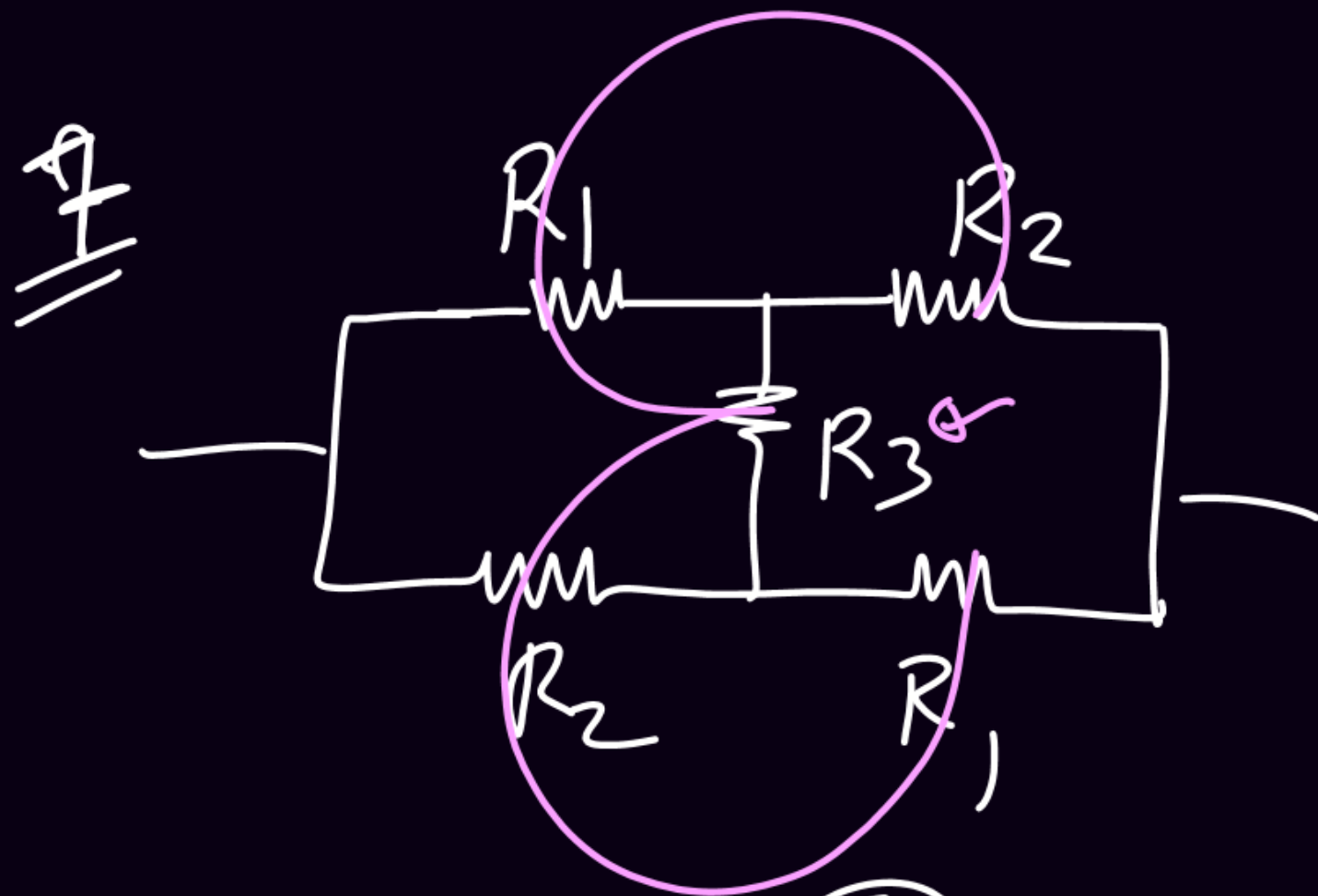

$$\frac{R_1}{R_2} \neq \frac{R_2}{R_1}$$


$$R_{eq} = \frac{R_2 R_1 + R_1 R_3 + R_3 R_2 + R_2 R_1}{R_2 + R_1 + 2R_3}$$



$$R_{eq} = \frac{2 + 5 + 10 + 2}{2 + 1 + 2 \times 5} = \frac{19}{13} \Omega$$

8

Cube

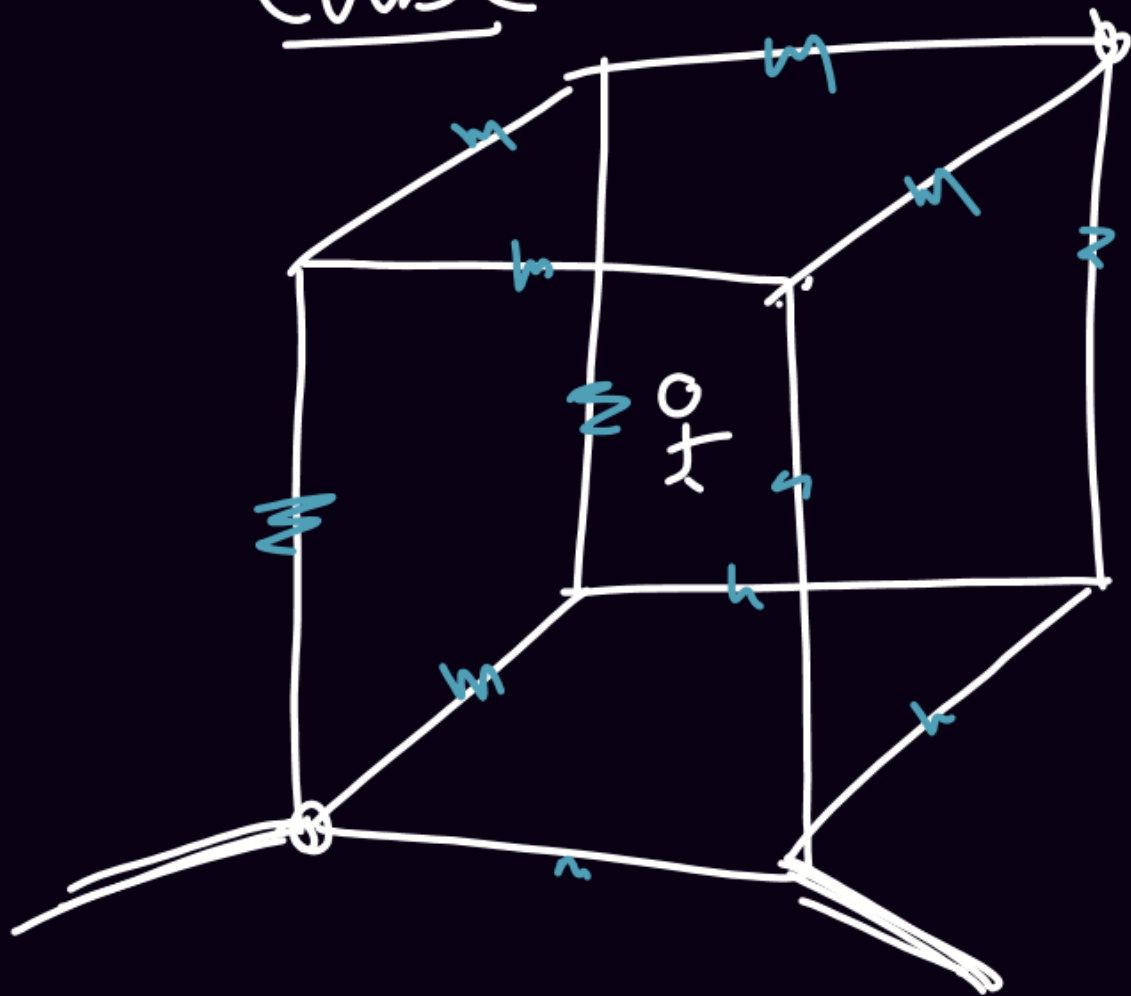

	Edge	Face diag.	Body diag.
Res.	$\frac{7}{12} R$	$\frac{9}{12} R$	$\frac{10}{12} R$
Cap.	$\frac{12}{7} C$	$\frac{12}{9} C$	$\frac{12}{10} C$

Face diag.

$$\frac{3R}{9}$$


$$\frac{5R}{6}$$

Body diag.

$$\frac{5R}{6}$$


$$\frac{5R}{6}$$

9 Infinite ladder

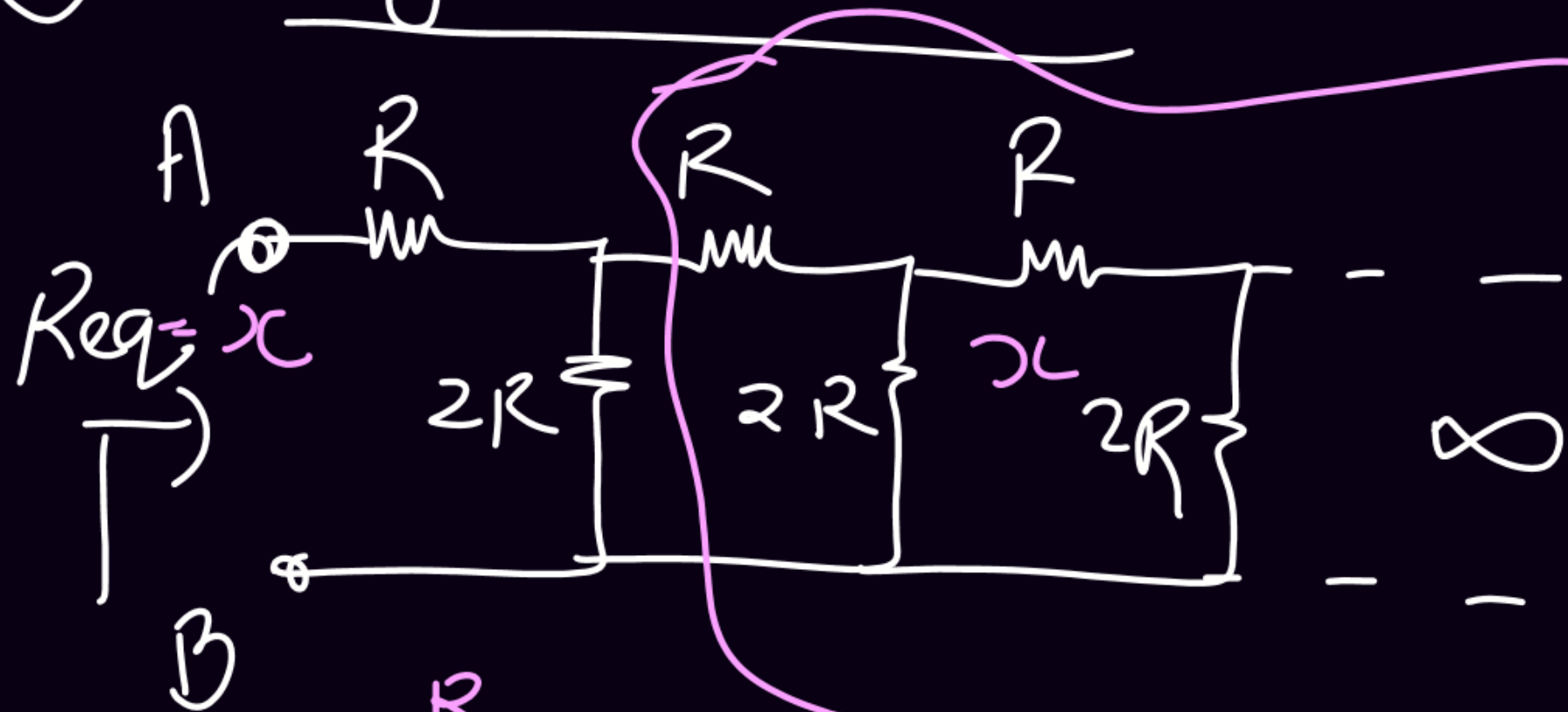


Req = x

$$y = 6 + \frac{1}{y}$$

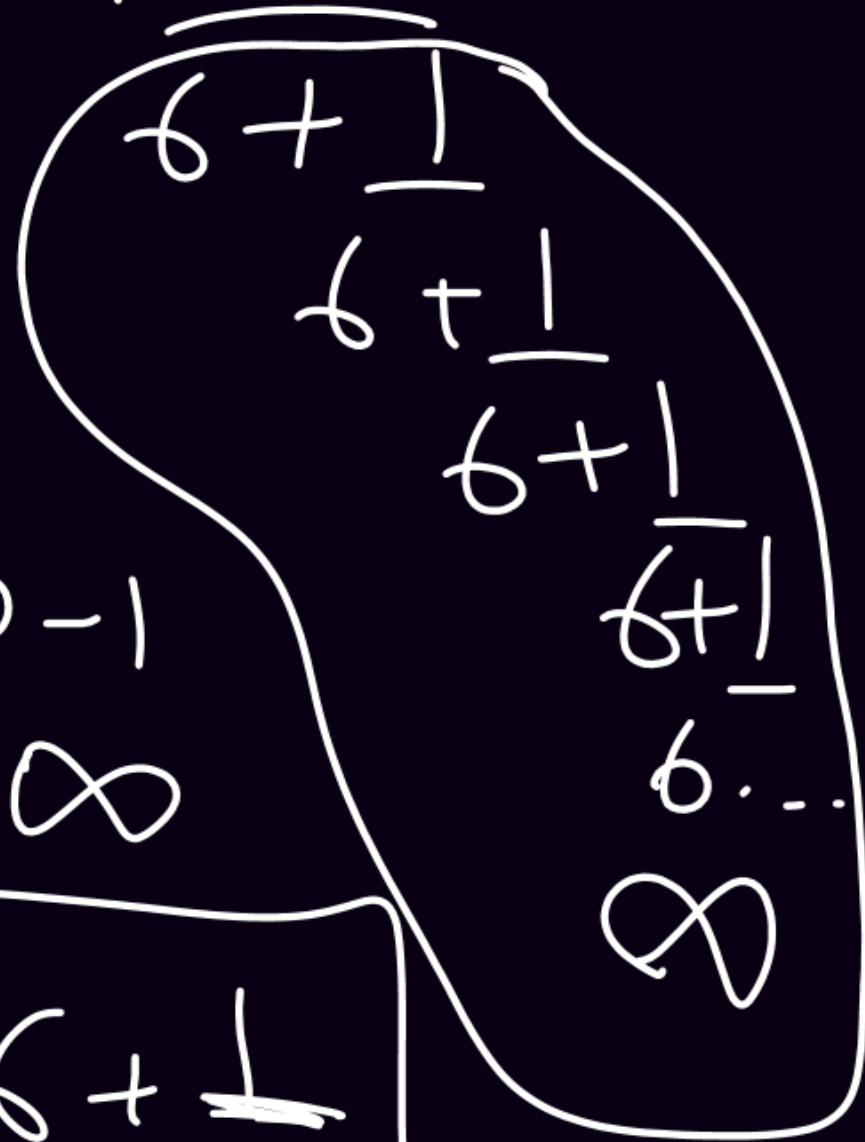

$$\infty - 1 = \infty$$

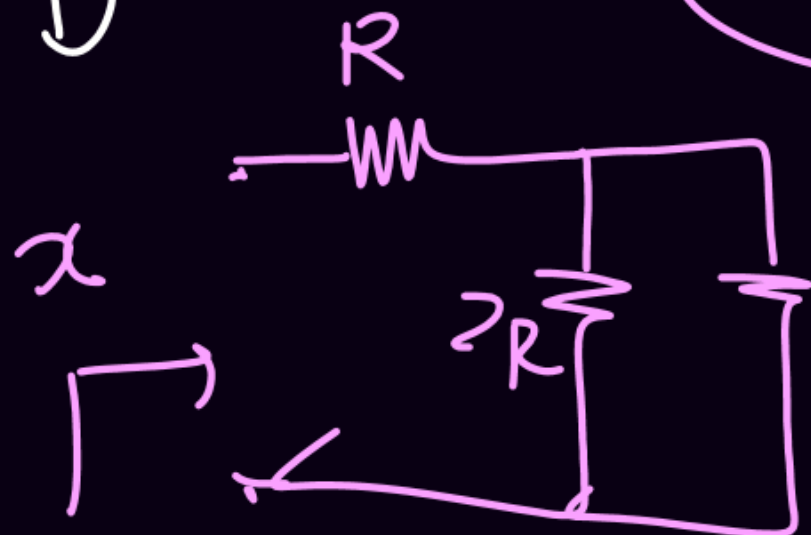

$$(2R \parallel x) + R = x$$

$$\frac{2Rx}{2R+x} + R = x$$

$$2Rx + 2R^2 + Rx = 2Rx + x^2 \Rightarrow x^2 - Rx - 2R^2$$

$$y = 6 + \frac{1}{y}$$



Thank You Lakshyians