

# LAKSHYA JEE

LAKSHYA KO HAR HAAL ME PAANA HAI



## Electric Potential & Capacitance

-Er. Rohit Gupta




# Today's GOALS!

## Capacitors



# Spherical capacitors

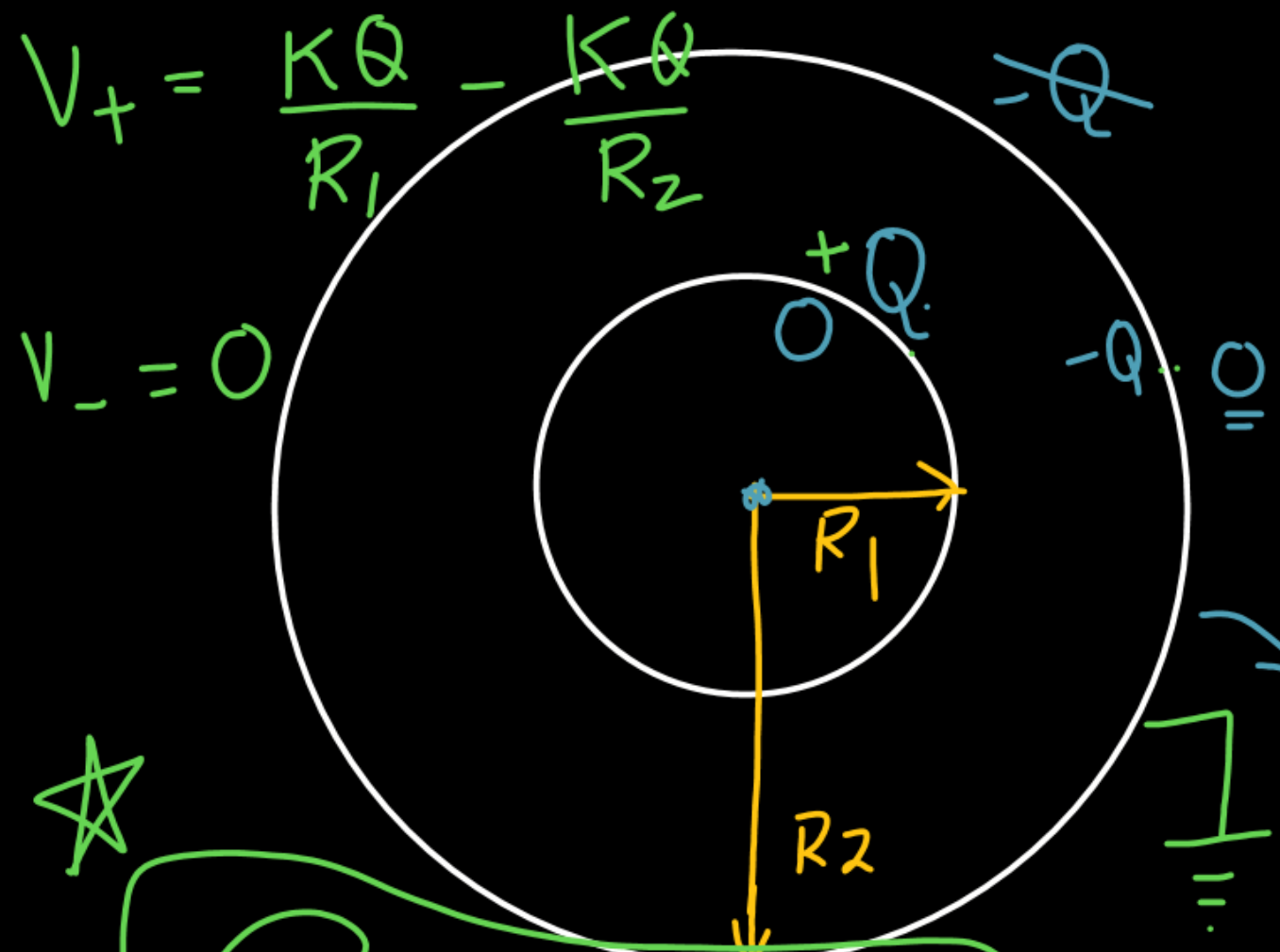

$$V_+ = kQ \left( \frac{1}{R_1} - \frac{1}{R_2} \right)$$

$$V_- = 0$$

$$\Delta V = V_+ - V_-$$

$$\Delta V = \frac{kQ}{R_1} - \frac{kQ}{R_2}$$

$$C = \frac{Q}{\Delta V} = \frac{Q}{kQ \left( \frac{1}{R_1} - \frac{1}{R_2} \right)} = \frac{R_1 R_2}{k(R_2 - R_1)}$$

$$C = \frac{4\pi\epsilon_0 R_1 R_2}{R_2 - R_1}$$




$$C = \frac{Q}{\Delta V}$$




$$\Delta V = V_+ - V_- = \frac{Q}{C}$$

$$C = \frac{Q}{\Delta V}$$

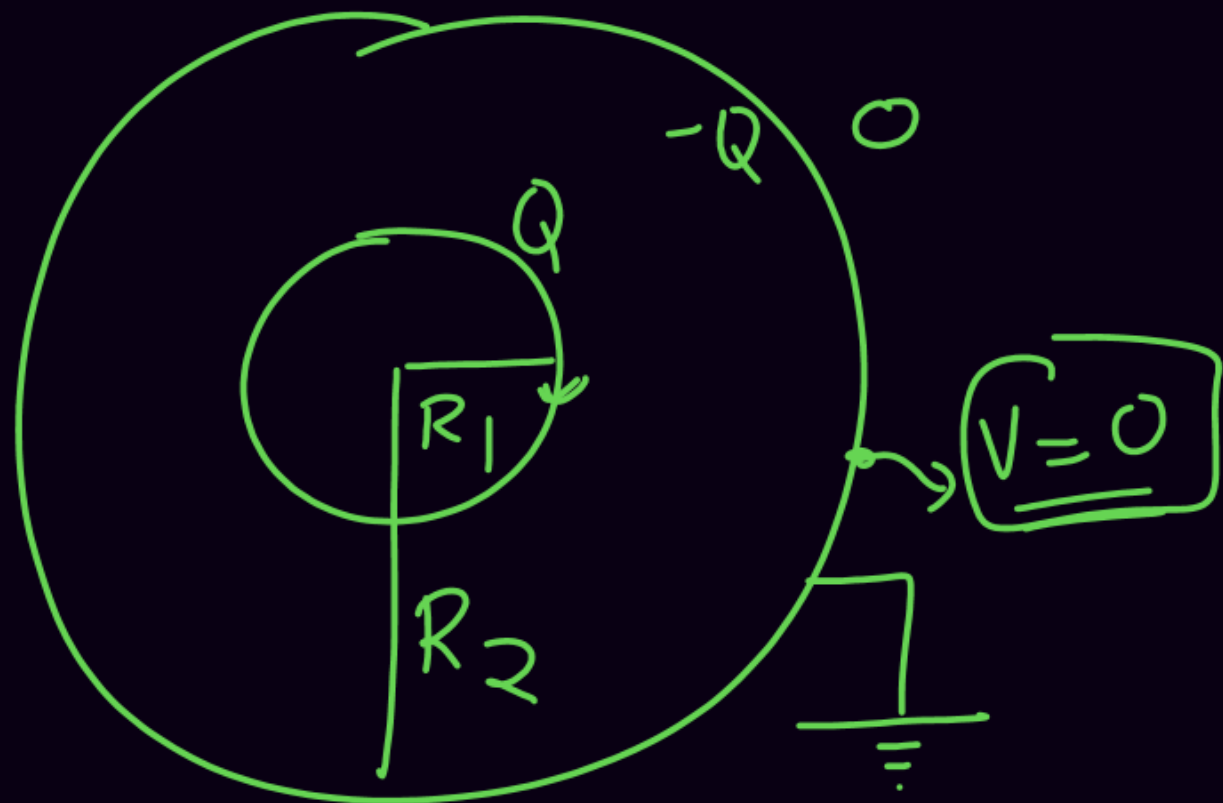
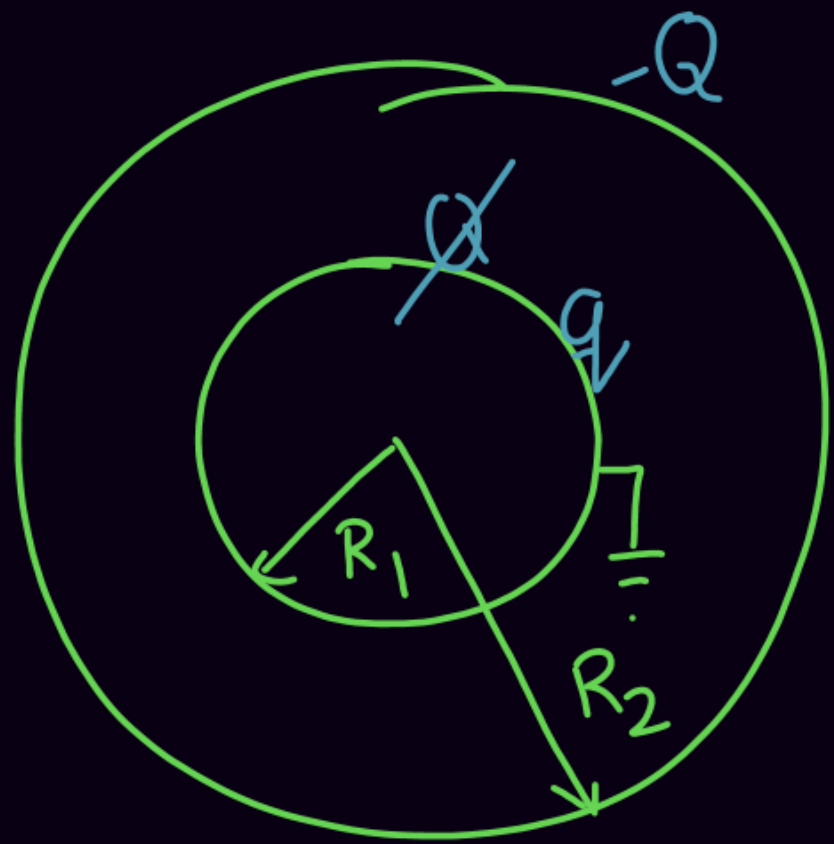
$$V_+ = \frac{kQ}{R_1} - \frac{kQ}{R_2}$$
$$V_- = 0$$



$$C = \frac{Q}{\Delta V} = \frac{C}{V} = \frac{C^2}{J}$$


$$= \frac{It}{\frac{Q}{W}} = \frac{I^2 t^2}{W}$$

$$= \frac{I^2 t^2}{F \cdot d} \Rightarrow [C] = \left[ \frac{A^2 T^2}{MLT^{-2} L} \right]$$

$$[C] = [M^{-1} L^{-2} T^4 A^2]$$

Unit  $\Rightarrow$  Farad.

$$\frac{kg^{-1} m^{-2} s^4 A^2}{}$$

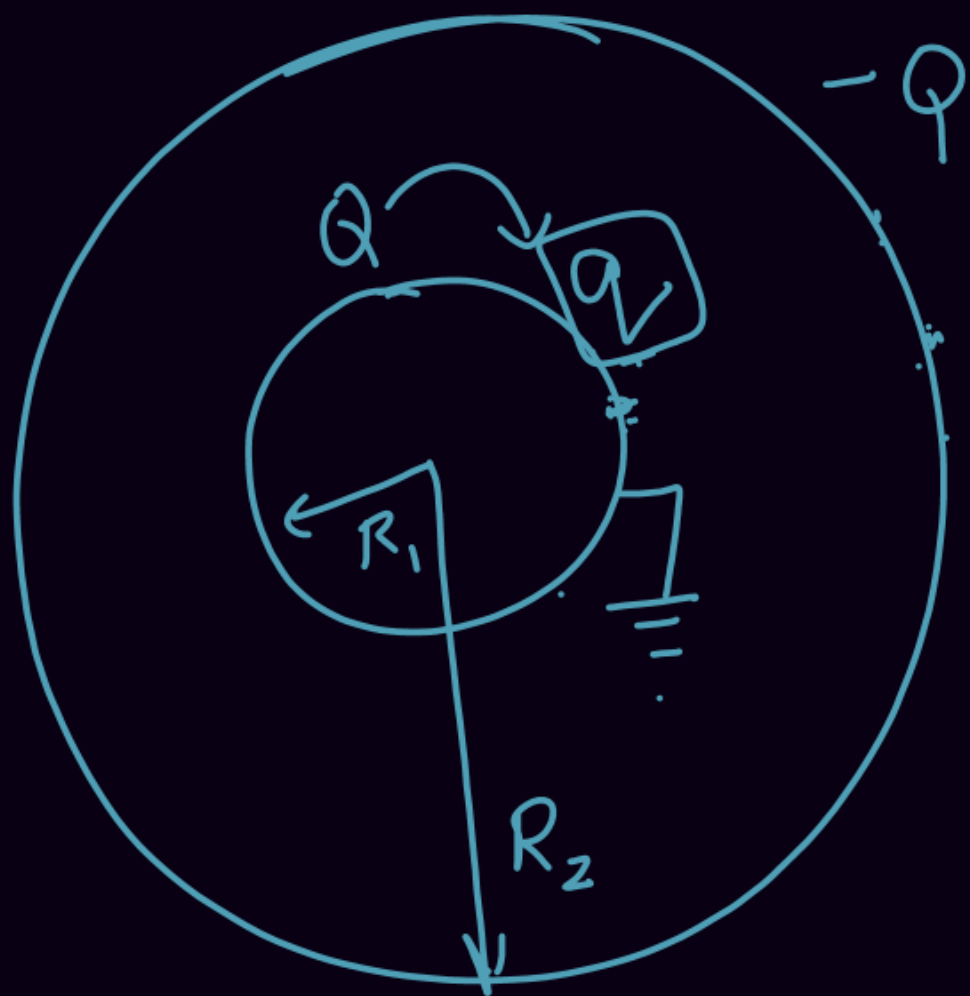

$$V_{R_1} = \frac{kq}{R_1} - \frac{kQ}{R_2} = 0$$

$$Q = \frac{R_1 Q}{R_2} \quad \checkmark \checkmark$$

$$\begin{aligned} \Delta V &= V_{R_1} - V_{R_2} \\ &= 0 - V_2 \\ &= -V_2 \end{aligned}$$

$$\begin{aligned} V_{R_2} &= \frac{kq}{R_2} - \frac{kQ}{R_2} \\ &= \frac{k}{R_2} \left[ \frac{R_1 Q}{R_2} - Q \right] = \frac{kQ}{R_2} \left( \frac{R_1 - R_2}{R_2} \right) \end{aligned}$$

$$C = \frac{Q}{DV}$$


$$= \frac{Q}{-V_2}$$

$$= \frac{\cancel{Q}}{-\left(\frac{K\cancel{Q}(R_1 - R_2)}{R_2^2}\right)}$$

$$C = \frac{4\pi\epsilon_0 R_2^2}{R_2 - R_1}$$



# Isolated sphere

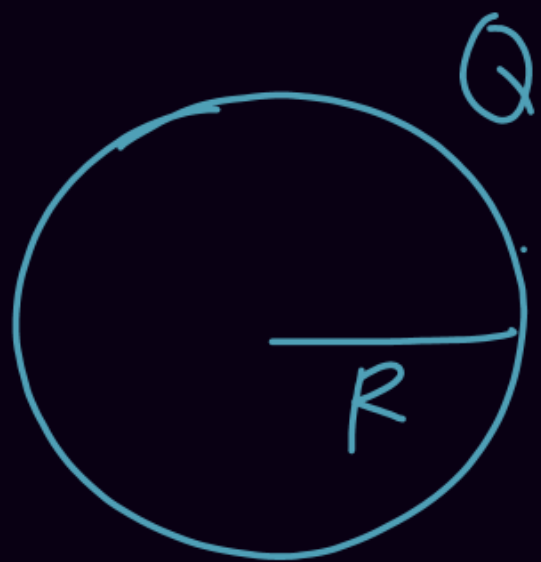

$$V_R = \frac{kQ}{R}$$


$$\Delta V = V_R - V_\infty$$

$$\Delta V = \frac{kQ}{R} - 0$$
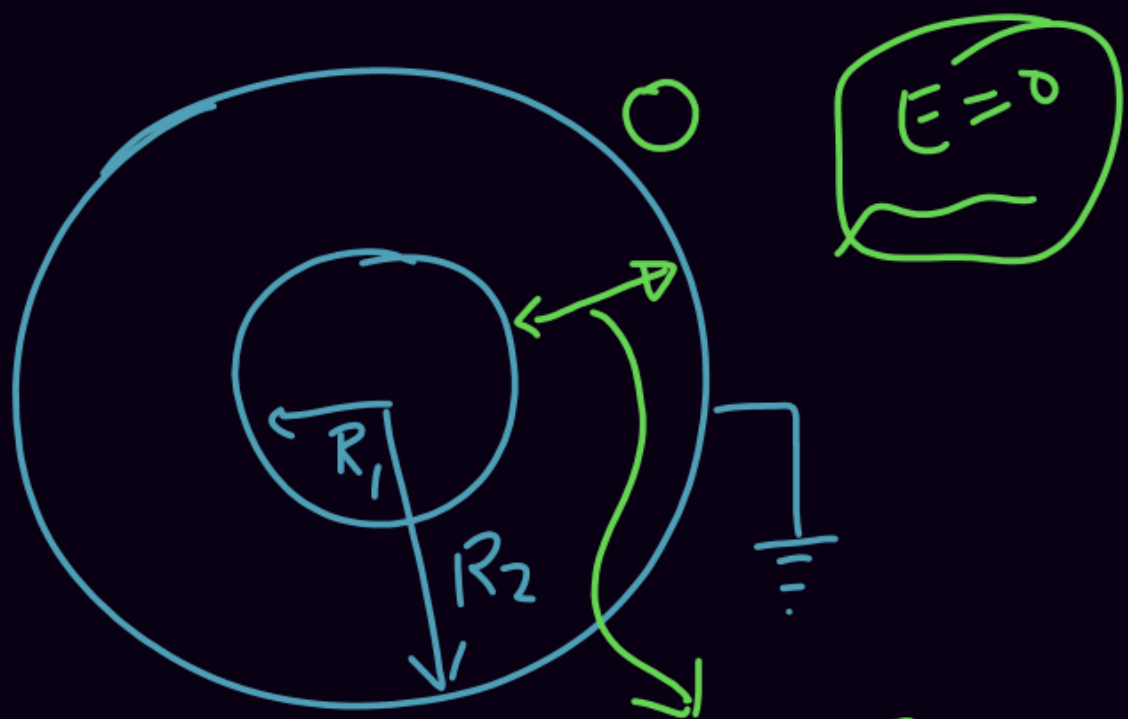
$$C = \frac{Q}{\Delta V} = \frac{Q}{\frac{kQ}{R}} = \frac{R}{k}$$








$$C = \frac{4\pi\epsilon_0 R_1 R_2}{R_2 - R_1} \Rightarrow$$

$$C = \frac{4\pi\epsilon_0 R_1}{1 - \frac{R_1}{R_2}}$$
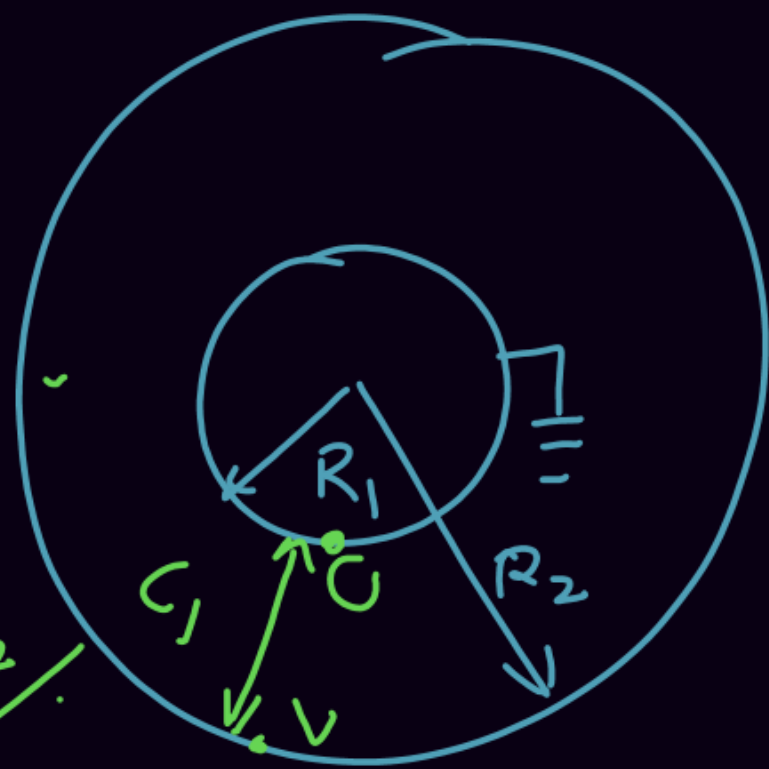
$$C = \frac{4\pi\epsilon_0 R}{1 - \left(\frac{R}{\infty}\right)} = 4\pi\epsilon_0 R$$



$$C = \frac{4\pi\epsilon_0 R_2^2}{R_2 - R_1}$$

Parallel

$$C_{eq} = C_1 + C_2$$


$$C_{eq} = C_1 + C_2$$

$$= \frac{4\pi\epsilon_0 R_1 R_2}{R_2 - R_1} + 4\pi\epsilon_0 R_2$$

$$= 4\pi\epsilon_0 R_2 \left( \frac{R_1}{R_2 - R_1} + 1 \right)$$

$$= 4\pi\epsilon_0 R_2 \left( \frac{\cancel{R_1} + R_2 - \cancel{R_1}}{R_2 - R_1} \right)$$
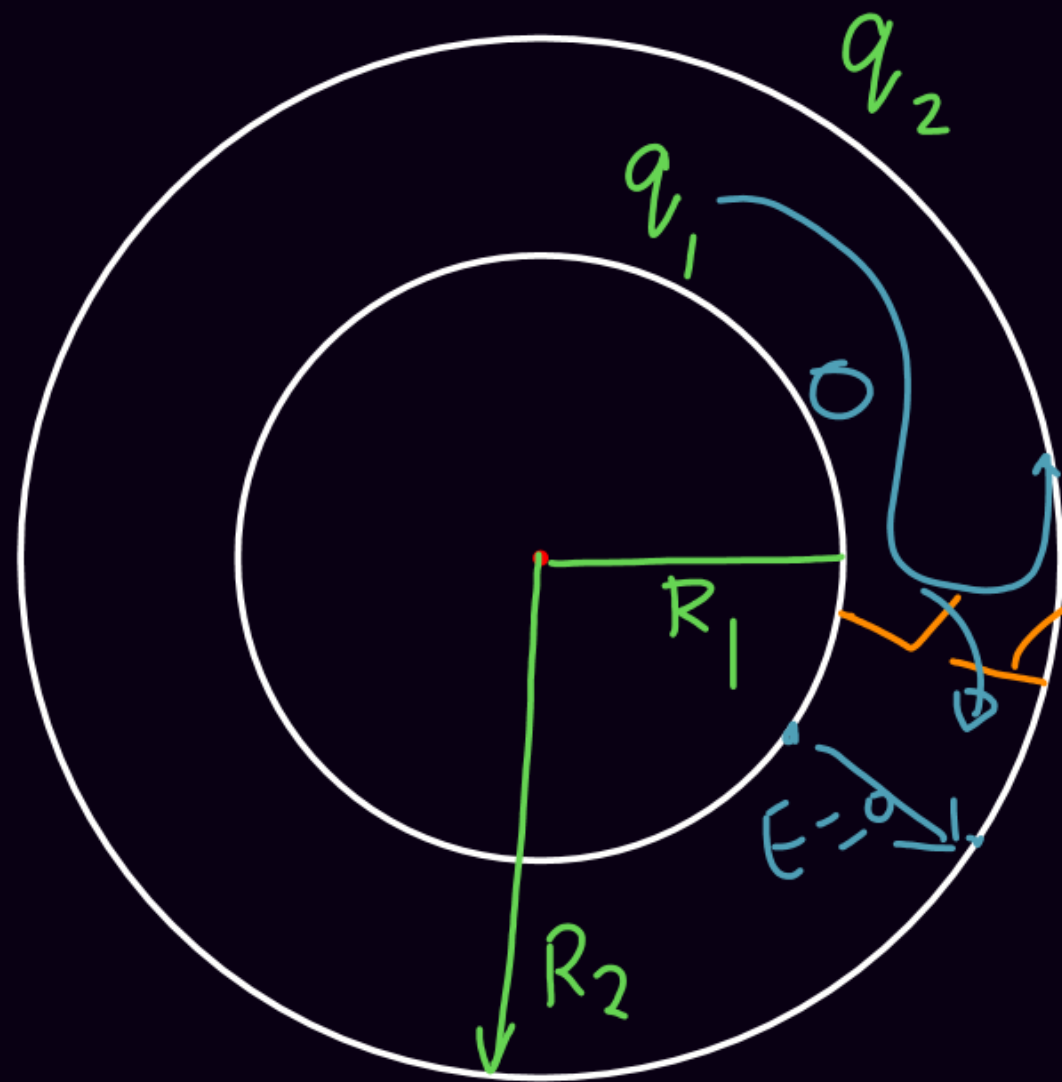
$$C_{eq} = \frac{4\pi\epsilon_0 R_2^2}{R_2 - R_1}$$




Find the charges on  
inner & outer spheres  
after the switch is closed.

conducting  
wire.

In the dir. of field potential decreases.




# Series Combination

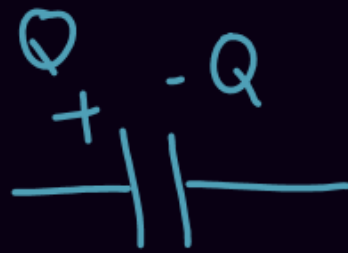

C  
← ΔV →

$$\Delta V = \frac{Q}{C}$$

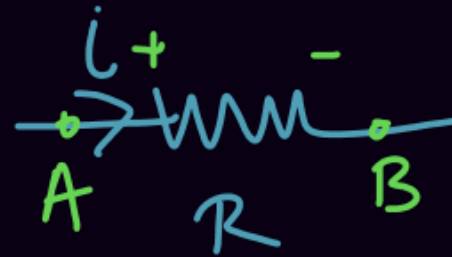


$$V_A > V_B$$

$$V_A - V_B = iR$$

ohm's law

H.W.


Find c

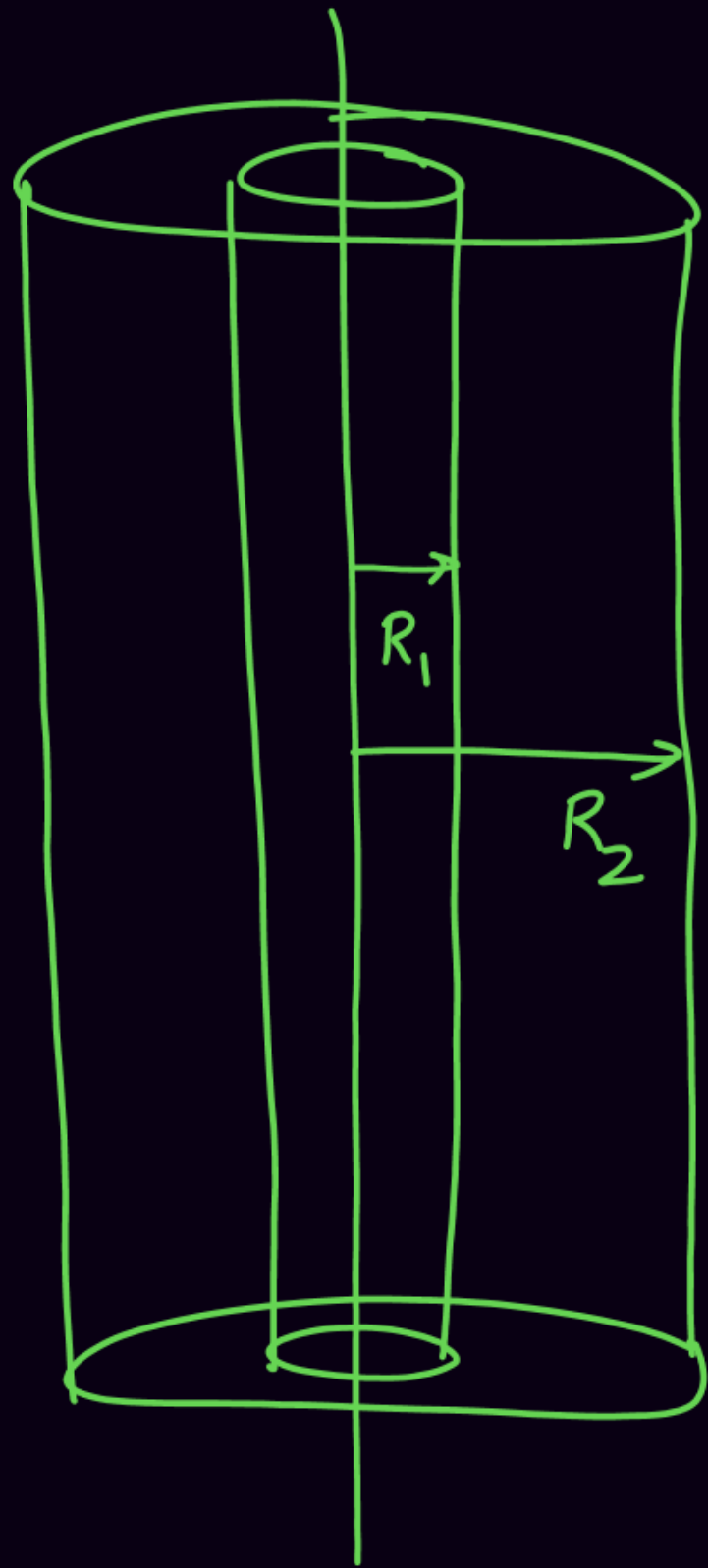

Very long

# Series Combination

Same Current -

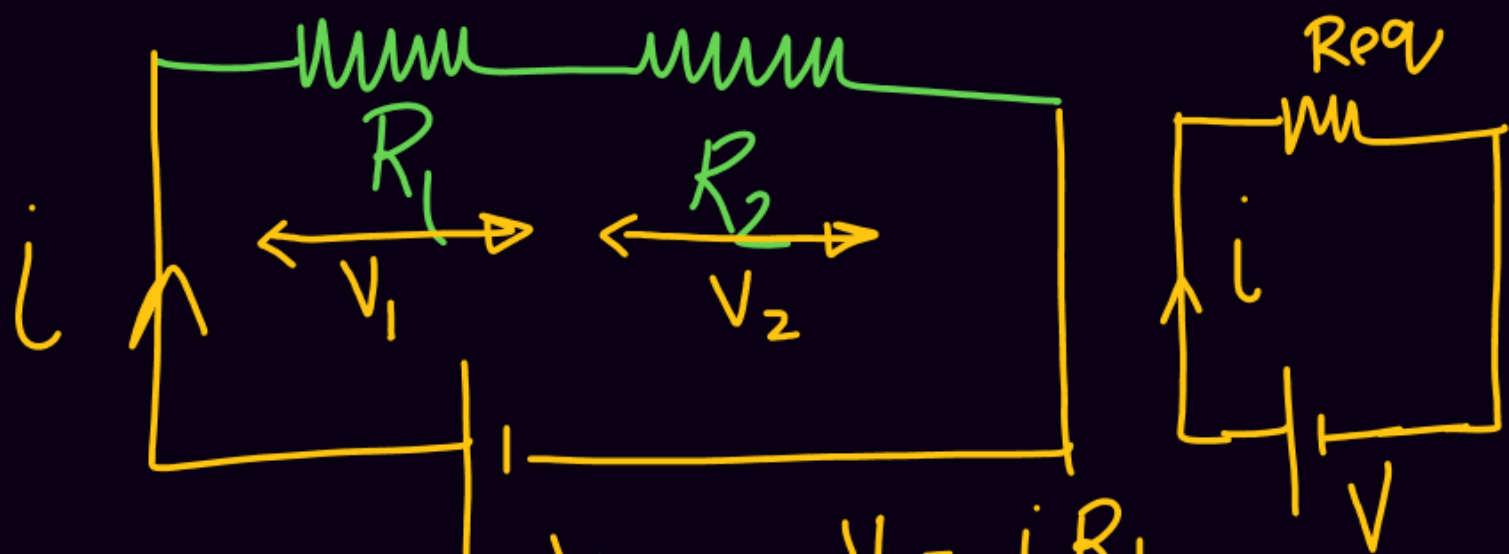

Battery  $V$

$$V_1 = i R_1$$


$$V_2 = i R_2$$

$$V = i R_{eq}$$

$$V_1 + V_2 = i R_{eq}$$

$$i R_1 + i R_2 = i R_{eq} \quad * i$$

$$R_{eq} = R_1 + R_2$$

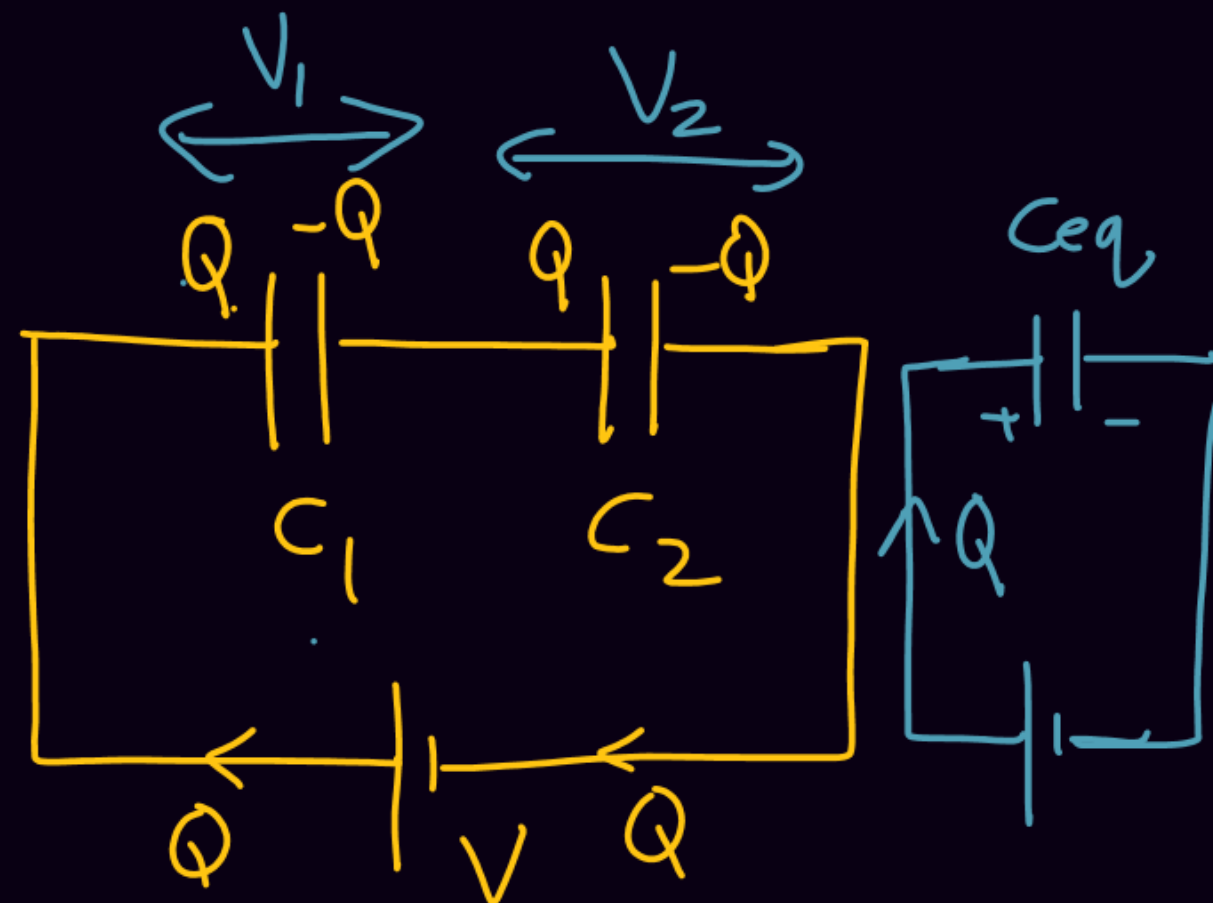

$$V_1 = \frac{Q}{C_1}$$

$$V_2 = \frac{Q}{C_2}$$


$$V = \frac{Q}{C_{eq}}$$

$$V = V_1 + V_2$$

$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$\boxed{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}}$$

Series combination is potential divider

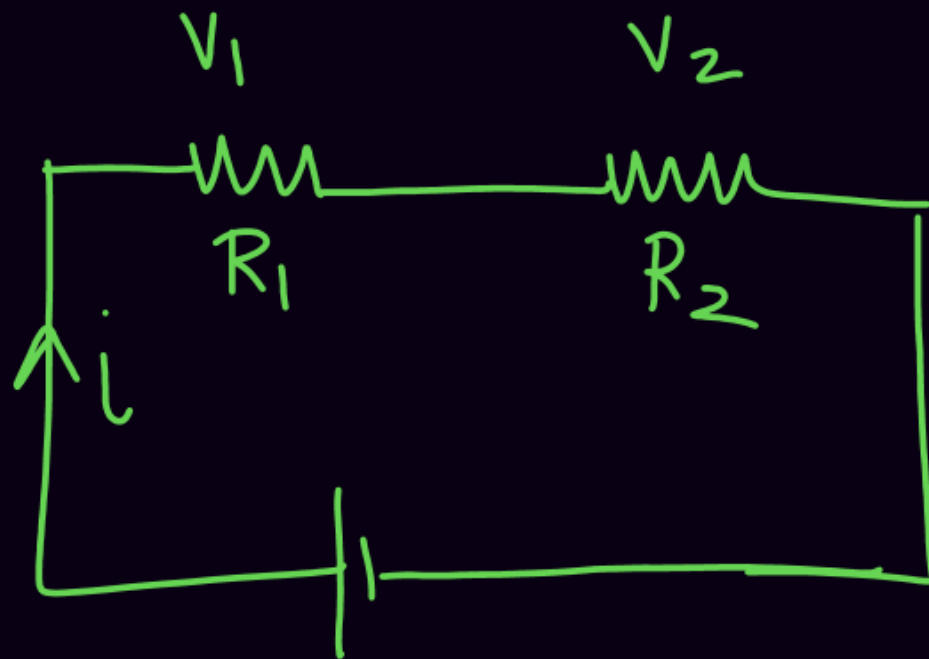

$$V_1 = \frac{R_1 V}{R_1 + R_2} \quad \frac{V_1}{V_2} = \frac{R_1}{R_2}$$
$$V_2 = \frac{R_2 V}{R_1 + R_2}$$

$$V_1 = i R_1$$

$$V_2 = i R_2$$

$$\frac{V_1}{V_2} = \frac{R_1}{R_2} \quad (1)$$

$$V = V_1 + V_2 \quad (2)$$

$$\frac{V_1}{V_2} + 1 = \frac{R_1}{R_2} + 1$$


$$\frac{V_1 + V_2}{V_2} = \frac{R_1 + R_2}{R_2}$$

$$\rightarrow \frac{V}{V_2} = \frac{R_1 + R_2}{R_2}$$

$$V_2 = \frac{R_2 V}{R_1 + R_2}$$

$$V = \frac{R_1 V}{R_1 + R_2}$$



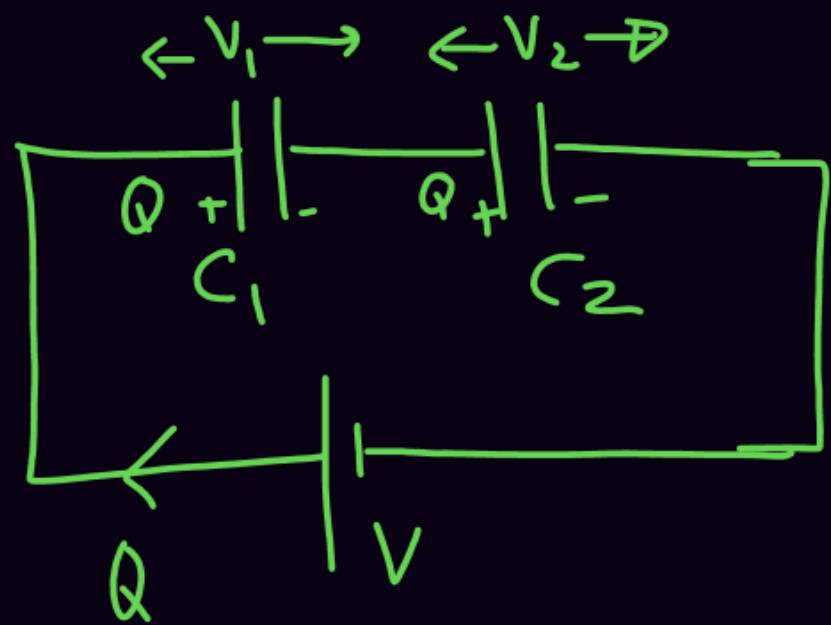

$$V_1 = \frac{Q}{C_1}$$

$$V_2 = \frac{Q}{C_2}$$

$$\frac{V_1}{V_2} = \frac{C_2}{C_1}$$

$$V_1 + V_2 = V$$

$$V_2 \left( \frac{V_1}{V_2} + 1 \right) = V$$



$$V_2 \left( \frac{C_2}{C_1} + 1 \right) = V$$

$$V_2 \left( \frac{C_1 + C_2}{C_1} \right) = V$$

$$V_2 = \frac{C_1 V}{C_1 + C_2}$$




$$V_1 = \frac{C_2 V}{C_1 + C_2}$$
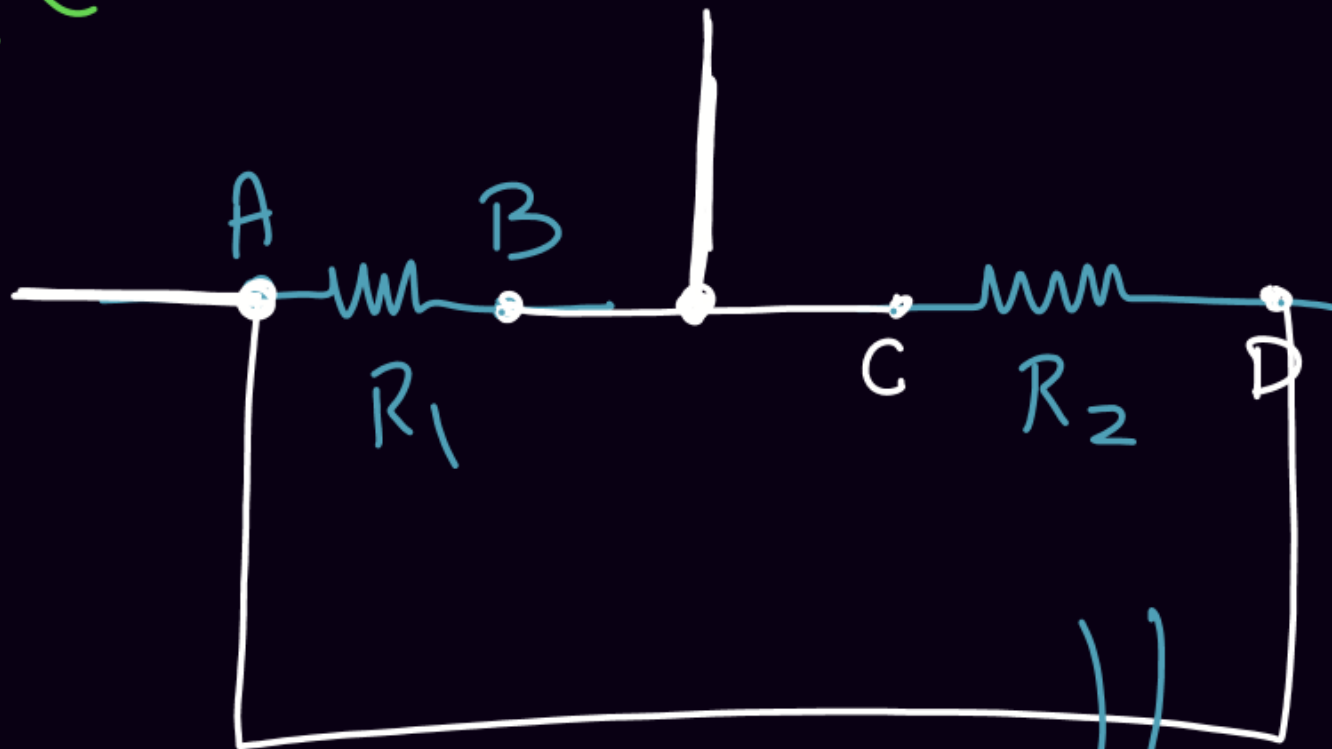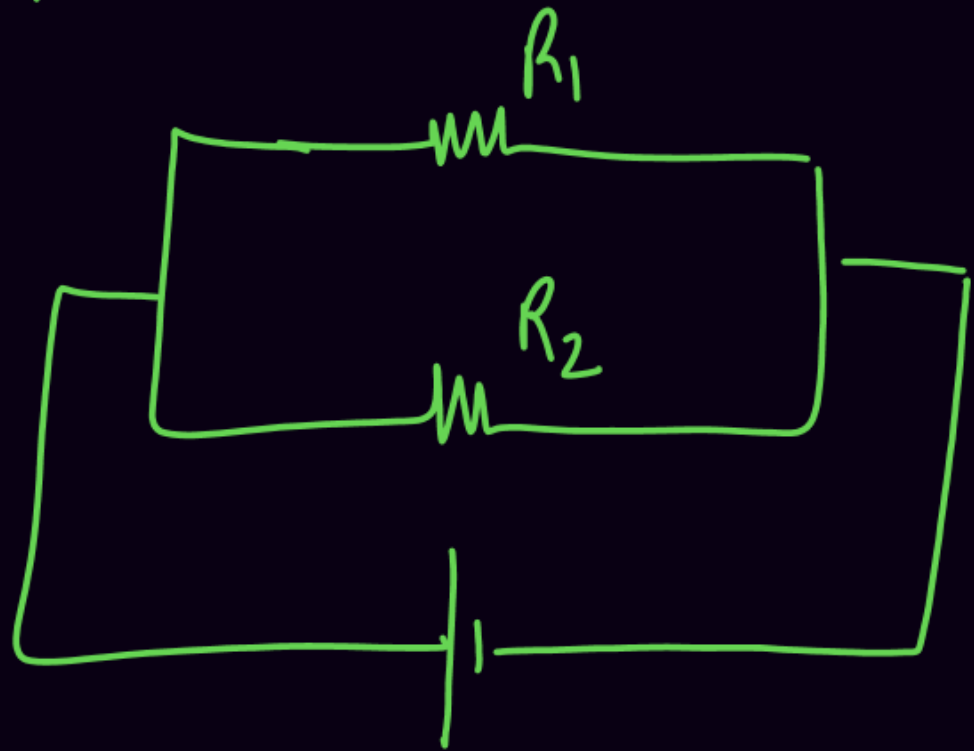
# Parallel combination (Same potential drop).



M.N.

$R_{eq}$

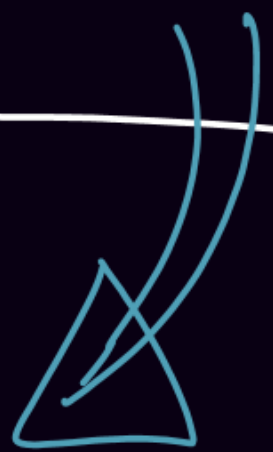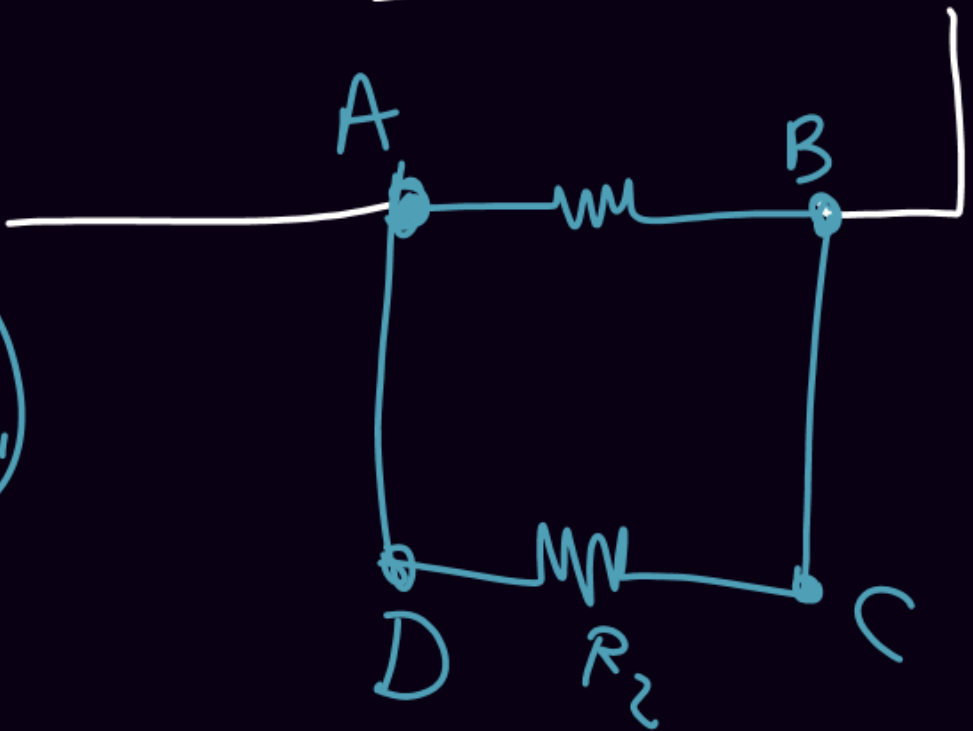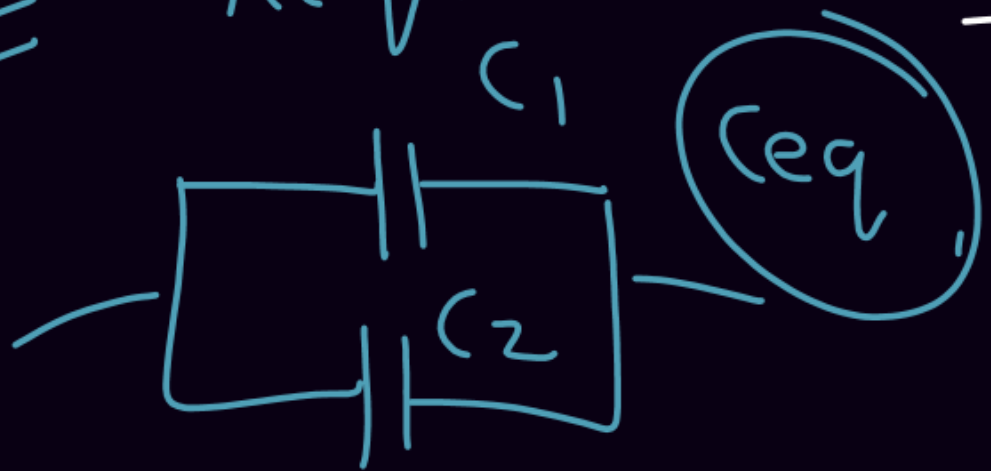



*Thank You Lakshyians*