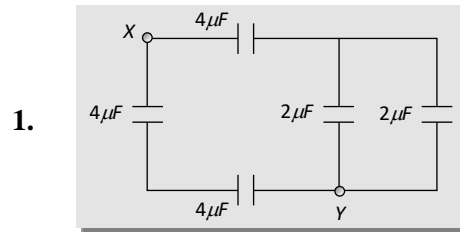


LAKSHYA (JEE)


Electrostatic Potential and Capacitance

DPP-11


Find equivalent capacitance between X and Y in the following circuits.



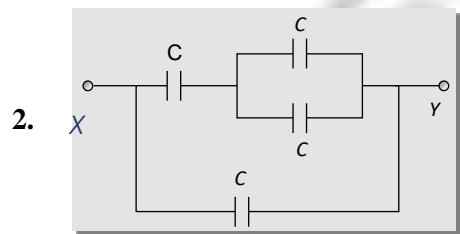
- (A) $3\mu\text{F}$ (B) $2\mu\text{F}$
(C) $4\mu\text{F}$ (D) $8\mu\text{F}$



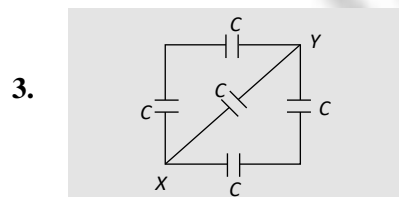
- (A) $\frac{5}{8}C$ (B) $\frac{3}{5}C$
(C) $\frac{5}{3}C$ (D) C




- (A) $2C$ (B) $C/5$
(C) $5C$ (D) $C/2$

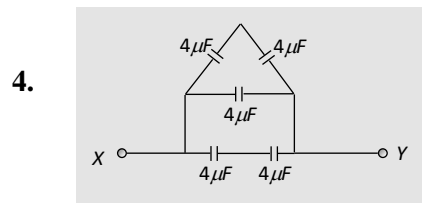

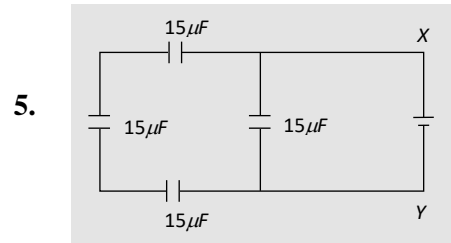
- (A) $8\mu\text{F}$ (B) $6\mu\text{F}$
(C) $268\mu\text{F}$ (D) $10/38\mu\text{F}$



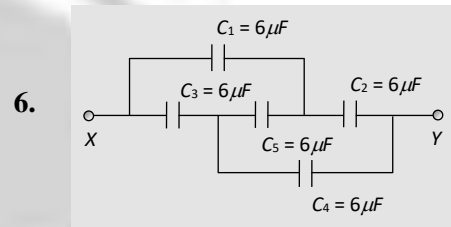
- (A) $15\mu\text{F}$ (B) $20\mu\text{F}$
(C) $25\mu\text{F}$ (D) $30\mu\text{F}$



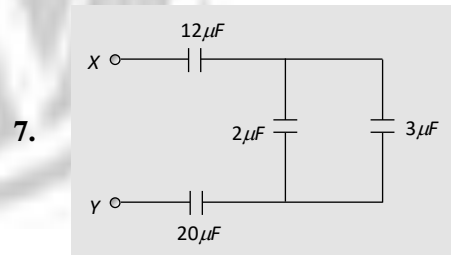- (A) $24\mu\text{F}$ (B) $18\mu\text{F}$
(C) $12\mu\text{F}$ (D) $6\mu\text{F}$




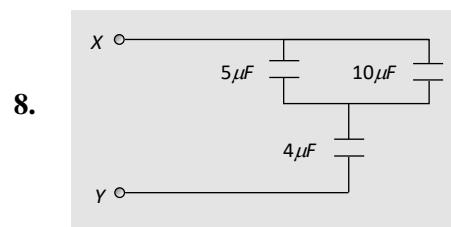- (A) $47\mu\text{F}$ (B) $3\mu\text{F}$
(C) $60\mu\text{F}$ (D) $10\mu\text{F}$




- (A) $2.2\mu\text{F}$ (B) $3.2\mu\text{F}$
(C) $1.2\mu\text{F}$ (D) $4.7\mu\text{F}$

9.

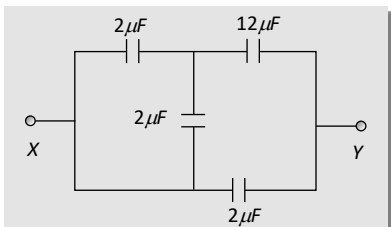


- (A) $28/9 \mu\text{F}$ (B) $4 \mu\text{F}$
 (C) $5 \mu\text{F}$ (D) $18 \mu\text{F}$

10.

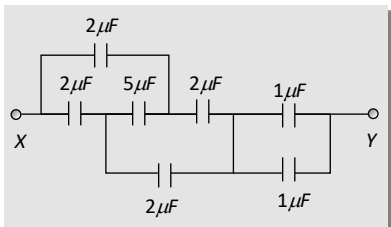


- (A) $1/2 \mu\text{F}$ (B) $1 \mu\text{F}$
 (C) $2 \mu\text{F}$ (D) $1.33 \mu\text{F}$

11.

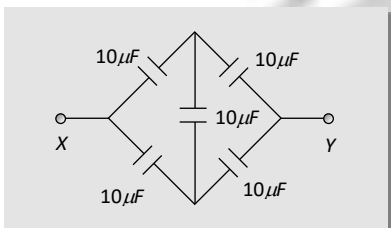


- (A) $40 \mu\text{F}$ (B) $20 \mu\text{F}$
 (C) $30 \mu\text{F}$ (D) $10 \mu\text{F}$

12.

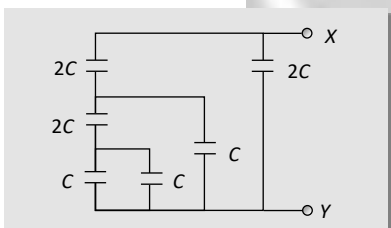


- (A) $3C$ (B) $2C$
 (C) C (D) $C/3$

13.

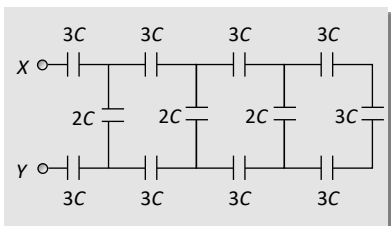


- (A) C (B) $9C$
 (C) $0.86C$ (D) $5.0C$

14.

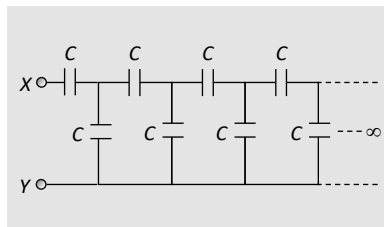


- (A) Zero (B) Infinite
 (C) $0.60C$ (D) $1.62C$

15.

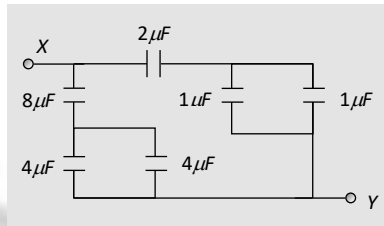

- (A) $10 \mu\text{F}$ (B) $20 \mu\text{F}$
 (C) $5 \mu\text{F}$ (D) $2.5 \mu\text{F}$

16.

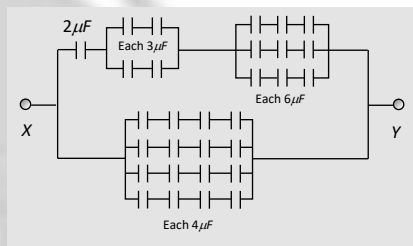

- (A) $3 \mu\text{F}$ (B) $4 \mu\text{F}$
 (C) $5 \mu\text{F}$ (D) $6 \mu\text{F}$



ANSWERS

1. (C)
2. (C)
3. (A)
4. (A)
5. (B)
6. (D)
7. (B)
8. (B)
9. (C)
10. (B)
11. (D)
12. (A)
13. (A)
14. (C)
15. (C)
16. (C)



Note - If you have any query/issue

Mail us at support@physicswallah.org



support@physicswallah.org