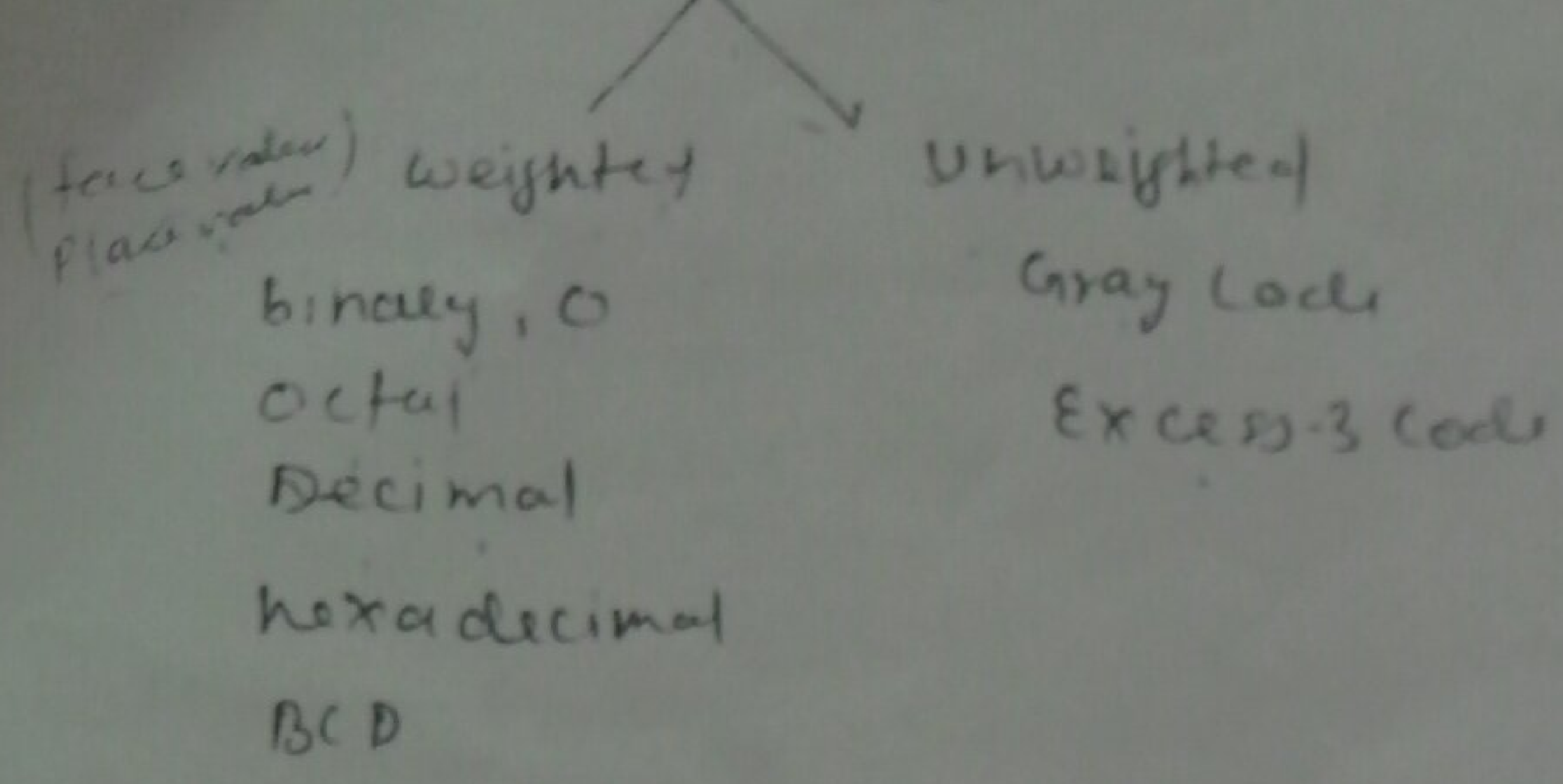


Number System



Any No. Such as $8936 = 8 \text{ thousand} + 900 + 30 + 6$
 $= 8 \times 10^3 + 9 \times 10^2 + 3 \times 10^1 + 6 \times 10^0$

So any No. with decimal can be represented as

$$\dots a_4 a_3 a_2 a_1 a_0 \cdot a_{-1} a_{-2} a_{-3} a_{-4} \dots$$

The coefficient a_j are any of ten digit (0, 1, ..., 9) and subscript j gives place value and hence power of ten by which the coefficient must be multiplied -

$$\dots + a_2 \times 10^2 + a_1 \times 10^1 + a_0 \times 10^0 + a_{-1} \times 10^{-1} + a_{-2} \times 10^{-2} + \dots$$

A decimal system is said to be of base or radix 10, because it uses 10 digits and coefficient are multiplied by power of 10.

In general a number expressed in a base r system has coefficient multiplied by base of r .

$$a_n r^n + \dots + a_3 r^3 + a_2 r^2 + a_1 r^1 + a_0 r^0 + a_{-1} r^{-1} + a_{-2} r^{-2} + \dots + a_{-m} r^{-m}$$

The coefficient a_j ranges \rightarrow 0 to $r-1$

for example. 0 base 5 No. is

$$(4021.2)_5 = 4 \times 5^3 + 0 \times 5^2 + 2 \times 5^1 + 1 \times 5^0 + 2 \times 5^{-1}$$

if we calculate = $(511.4)_{10}$

Coefficient value - 0, 1, 2, 3, 4

3

Number System	base	Digit coefficient
Binary	2	0, 1
Octal	8	0, 1, 2, 3, 4, 5, 6, 7
Decimal	10	0, 1, 2, 3, 4, 5, 6, 7, 8, 9
hexadecimal	16	0, 1, 2, ..., 9, A, B, C, D, E, F

In computer

1K = 2^{10} byte
 1M = 2^{20} byte
 1G = 2^{30} byte

1 byte = 8 bit

4G Hardis = 2^{32} byte

$$(10101)_2 \rightarrow 1 \times 2^4 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$$

$$= 16 + 4 + 1 = (21)_{10}$$



$$(B65F)_{16} \rightarrow 11 \times 16^3 + 6 \times 16^2 + 5 \times 16^1 + 15 \times 16^0 = (46687)_{10}$$

Base conversion

Decimal to others

$$(x_1 x_2 x_3 . y_1 y_2 y_3)_{10} \rightarrow ()_r$$

\downarrow Integer \downarrow fraction

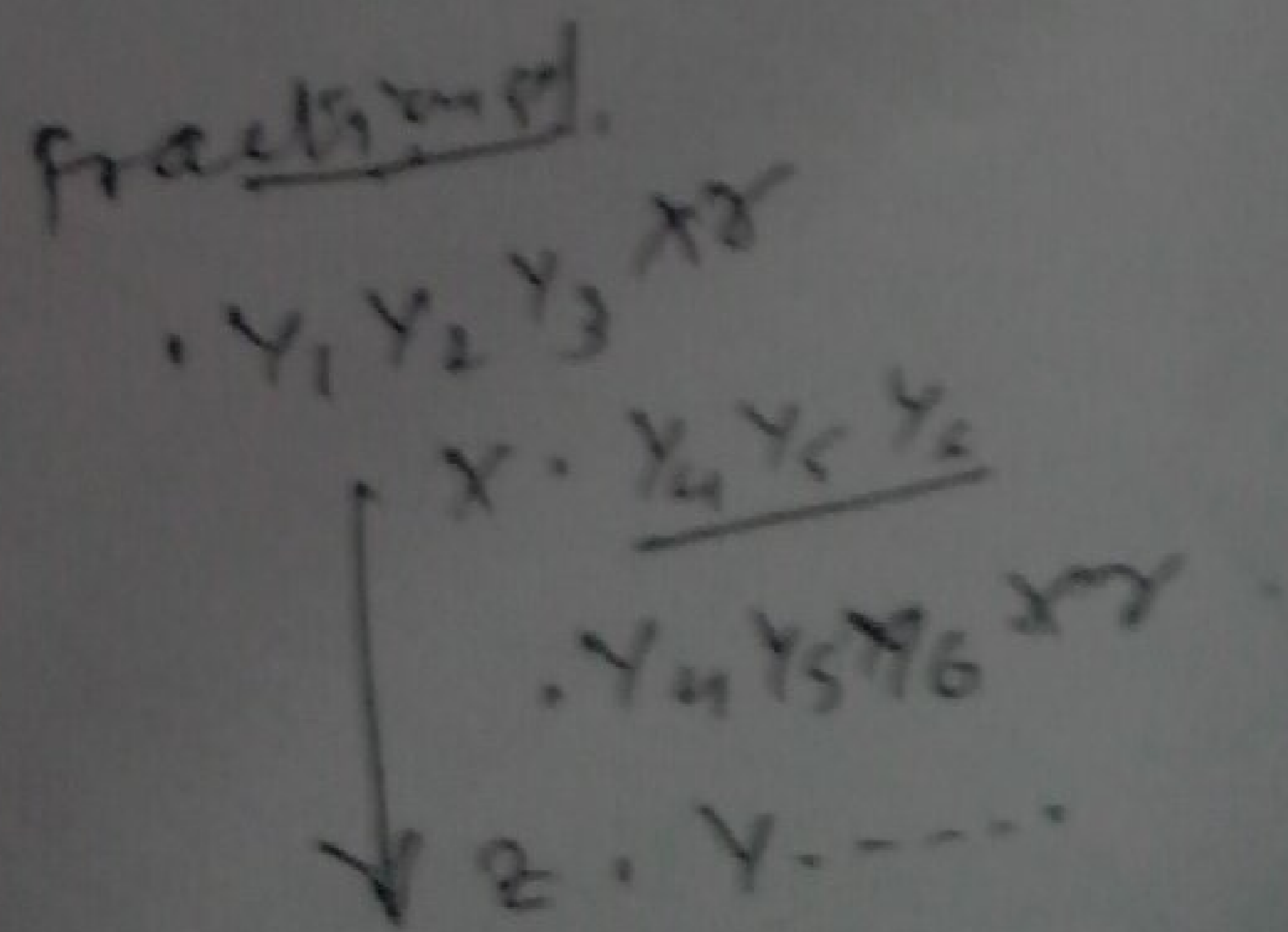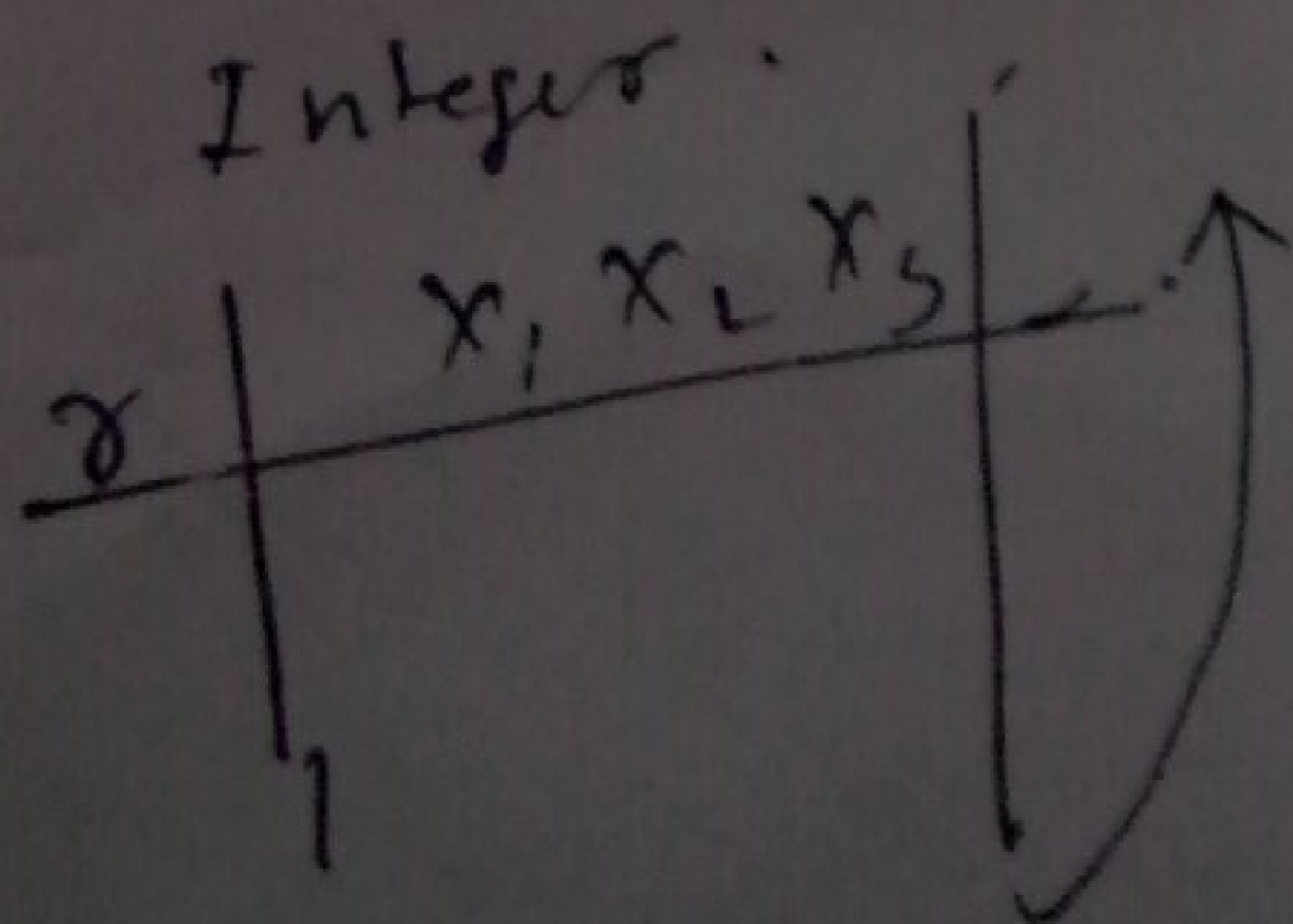

decimal to binary
 $(25.25)_{10} \rightarrow ()_2$

2	25	1
2	12	0
2	6	0
2	3	1
	1	

$(1001.01)_2$
 ,11001.

$0.25 \times 2 = 0.50$
 $0.50 \times 2 = 1.00$

4

decimal to octal

$(25.25)_{10} \rightarrow ()_8$

8	25	1
	3	

$(31.2)_8$

$0.25 \times 8 = 2.00$

$(37.625)_{10} \rightarrow ()_2$

2	37	1
2	18	0
2	9	1
2	4	0
2	2	0
	1	

$(100101.101)_2$

$0.625 \times 2 = 1.250$
 $0.250 \times 2 = 0.500$
 $0.500 \times 2 = 1.000$

decimal to hexadecimal

$(127)_{10} \rightarrow ()_{16}$

$(7F)_{16}$

16	127	15
	7	

Octal to decimal

$$(x_3 x_2 x_1 x_0)_8 \rightarrow ()_{10}$$

$$(x_3 x_2 x_1 x_0)_8 \rightarrow ()_{10}$$

5

Binary to decimal

$$(x_3 x_2 x_1 x_0 \cdot x_{-1} x_{-2} x_{-3})_2 \rightarrow ()_{10}$$

$$\rightarrow (x_3 2^3 + x_2 2^2 + x_1 2^1 + x_0 \cdot 2^0 + x_{-1} 2^{-1} + x_{-2} 2^{-2} + x_{-3} 2^{-3})_{10}$$

Binary to decimal

$$(11010.11)_2 \rightarrow ()_{10}$$

$$(1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 + 1 \times 2^{-1} + 1 \times 2^{-2})_{10}$$
$$(16 + 8 + 2 + .5 + .25)_{10}$$
$$(26.75)_{10}$$

Octal to decimal

$$(137.4)_8 \rightarrow ()_{10}$$

$$(1 \times 8^2 + 3 \times 8^1 + 7 \times 8^0 + 4 \times 8^{-1})_{10}$$

$$(64 + 24 + 7 + .5)_{10}$$

$$(95.5)_{10}$$

Note: the digit 8 and 9 cannot appear in an octal no.

Hexadecimal to decimal

$$(B65F)_{16} \rightarrow ()_{10}$$

$$B \times 16^3 + 6 \times 16^2 + 5 \times 16^1 + F \times 16^0$$


$$11 \times 16^3 + 6 \times 16^2 + 5 \times 16 + 15 \times 16^0 = (46687)_{10}$$

Binary to Octal & Hexadecimal

Binary to Octal:


Since $2^3 = 8$, each octal digit corresponds to three binary digits.

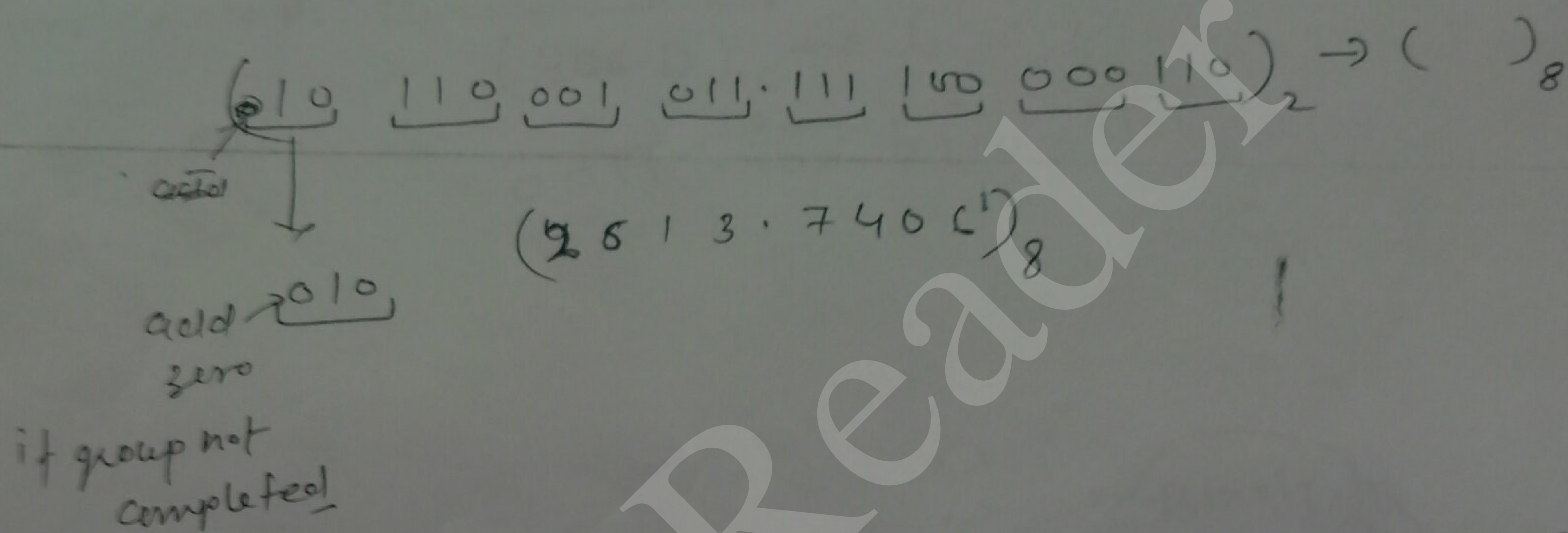So conversion from binary to octal is easily accomplished by partitioning the binary no. into groups of three digit each, starting from binary point and proceeding to the left and to the right.



Binary to Hexadecimal.

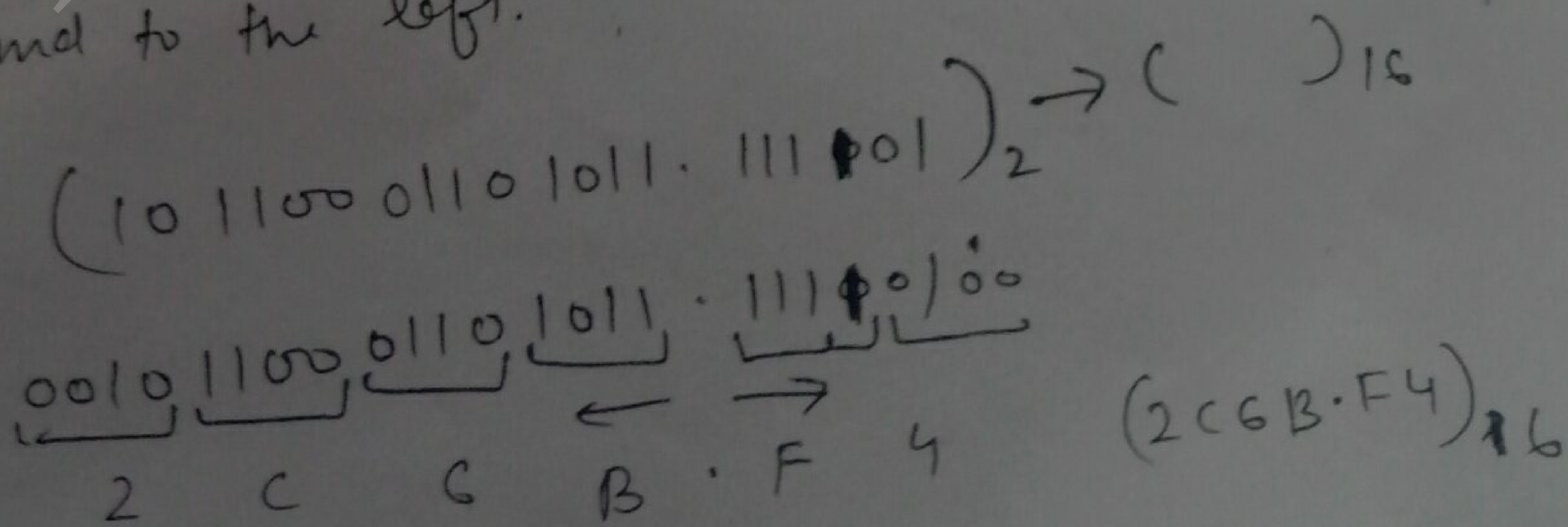Since $2^4 = 16$ each hexadecimal digit corresponds to four binary digits. So by partitioning binary no. into group of four digit each, starting from decimal point and proceeding from the left and to the left.



(Octal & Hexadecimal) to Binary

(By Reversing the preceding procedure.)

Octal to Binary: Each octal digit is converted to its three digit binary equivalent


$$(673.124)_8 \rightarrow (\quad)_2 \quad 7$$

$$\begin{matrix} 6 & 7 & 3 & 1 & 2 & 4 \\ \hline 110 & 111 & 011 & 001 & 010 & 100 \end{matrix}$$

Hexadecimal to Binary: Each hexadecimal digit is converted to its four digit binary equivalent.

$$(306.D)_{16} \rightarrow (\quad)_2$$
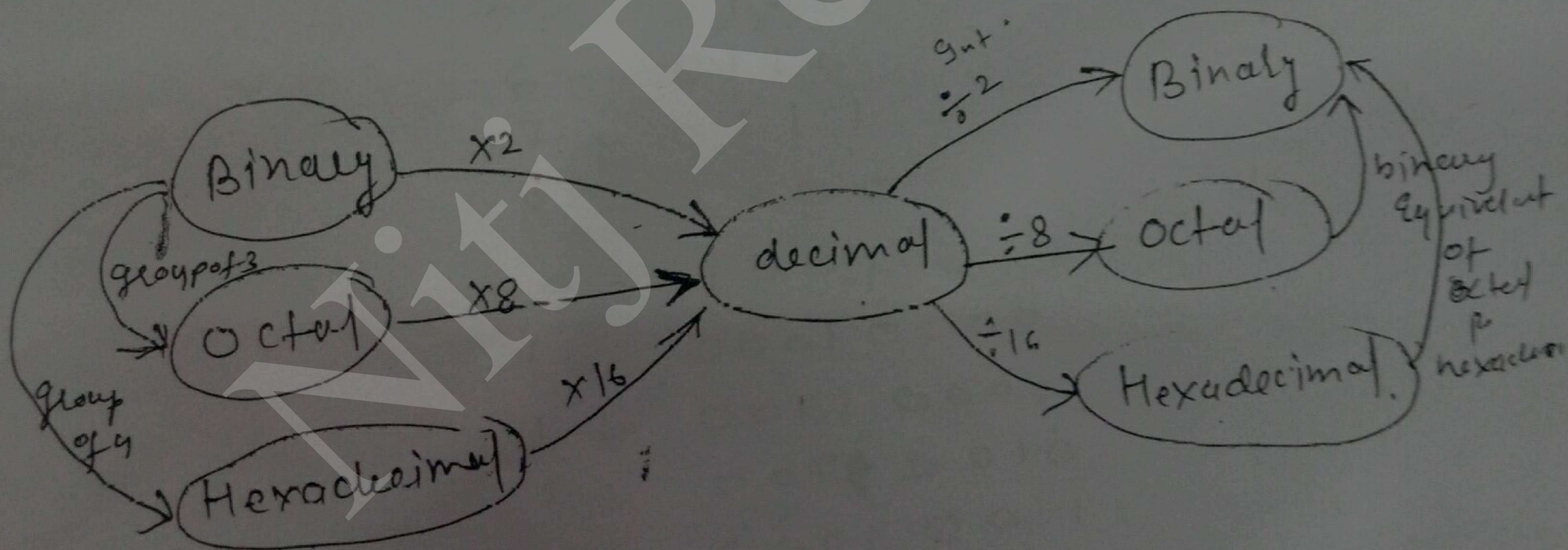
$$\begin{matrix} 3 & 0 & 6 & D \\ \hline 0011 & 0000 & 0110 & 1101 \end{matrix}$$



BCD Code (Binary Coded Decimal)

Each decimal no. is represented with its 4 bit binary equivalent.

such as.

$$(396)_{10} \rightarrow \text{BCD } (\underbrace{0011}_3 \underbrace{1001}_9 \underbrace{0110}_6)_{\text{BCD}}$$

$$(185)_{10} \rightarrow (\quad)_{\text{BCD}}$$

$$(0001 \ 1000 \ 0101)_{\text{BCD}}$$

0 - 0000

1 - 0001

2 - 0010

3 - 0011

4 - 0100

5 - 0101

6 - 0110

7 - 0111

8 - 1000

9 - 1001

10 0001 0000

11 0001 0001

12 0001 0010

13 0001 0011



Note

BCD No. are decimal no. are decimal no. and not binary no., although use bits in their representation.

NAND Gate as universal gate

other gate using universal NAND gate.

① NOT $Y = \bar{A}$

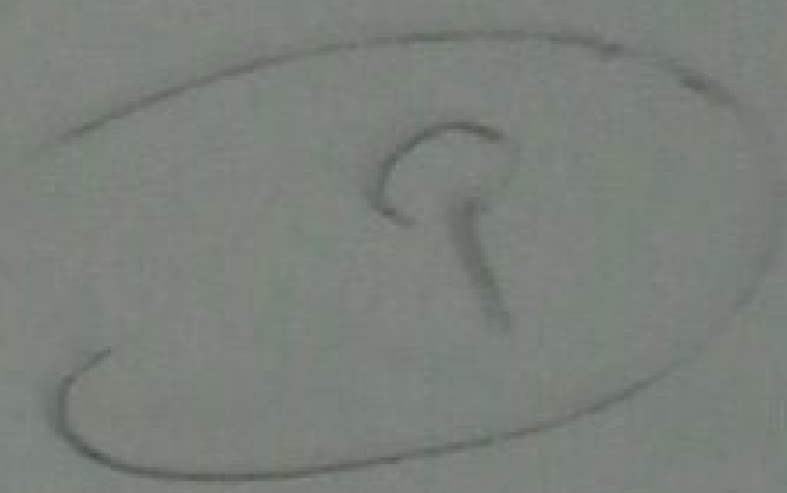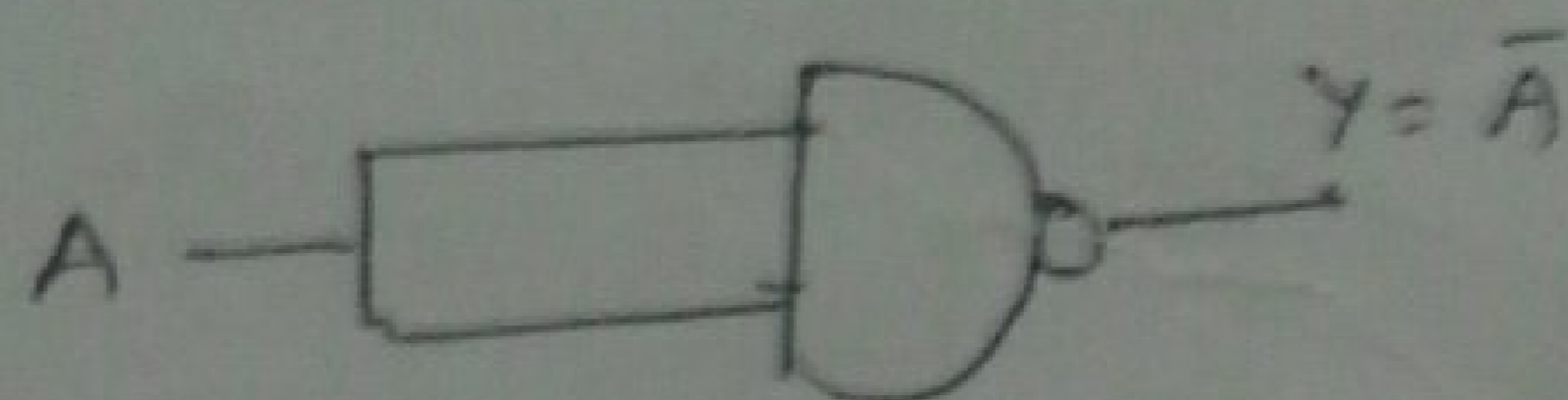


② AND Gate :-

$$Y = AB$$

take bar $\bar{Y} = \overline{AB}$

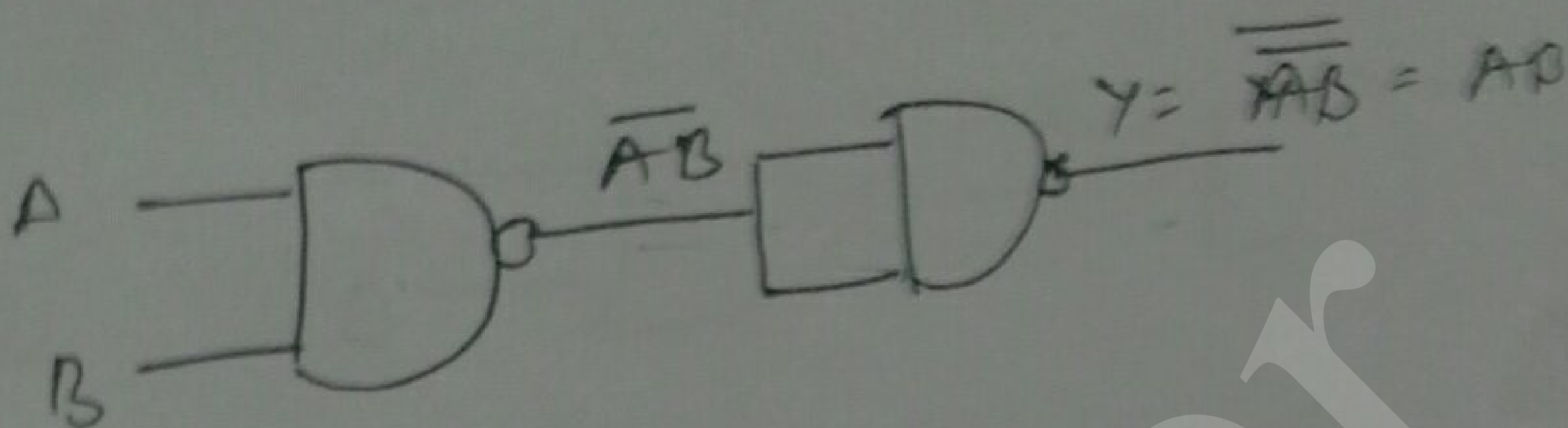take once more bar $\bar{\bar{Y}} = Y = \overline{\overline{AB}}$



807

③ OR Gate

$$Y = A + B$$

$$\bar{Y} = \overline{A + B}$$

$$\bar{Y} = \bar{A} \cdot \bar{B}$$


$$\bar{\bar{Y}} = \overline{\bar{A} \cdot \bar{B}}$$

$$Y = \bar{\bar{A}} + \bar{\bar{B}}$$

$$(Y = A + B)$$


Use demorgan's
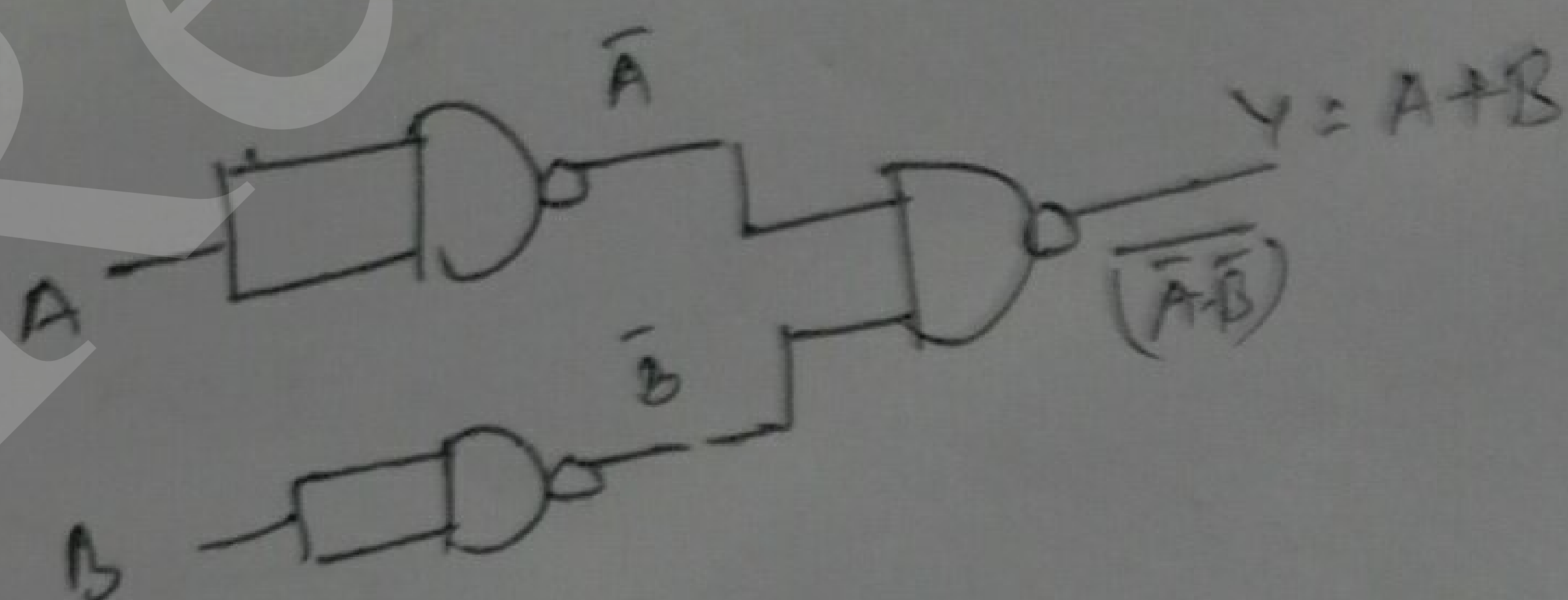
$$\left. \begin{aligned} \overline{A+B} &= \bar{A} \cdot \bar{B} \\ \overline{\bar{A} \cdot \bar{B}} &= A + B \end{aligned} \right\}$$



④ NOR Gate

$$Y = \overline{A + B}$$



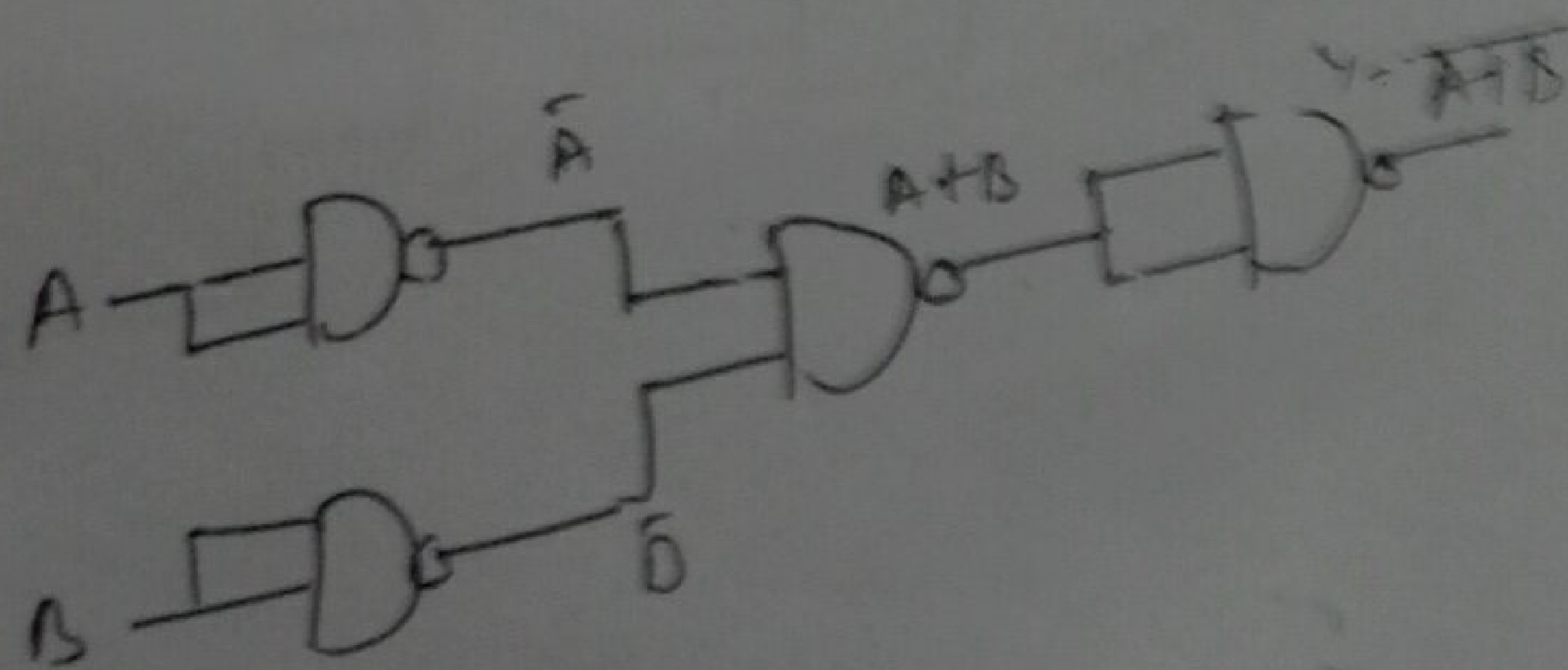


⑤ EX-OR - $Y = A\bar{B} + \bar{A}B$

$$\bar{Y} = \overline{A\bar{B} + \bar{A}B}$$


$$\bar{Y} = \overline{A\bar{B}} \cdot \overline{\bar{A}B}$$
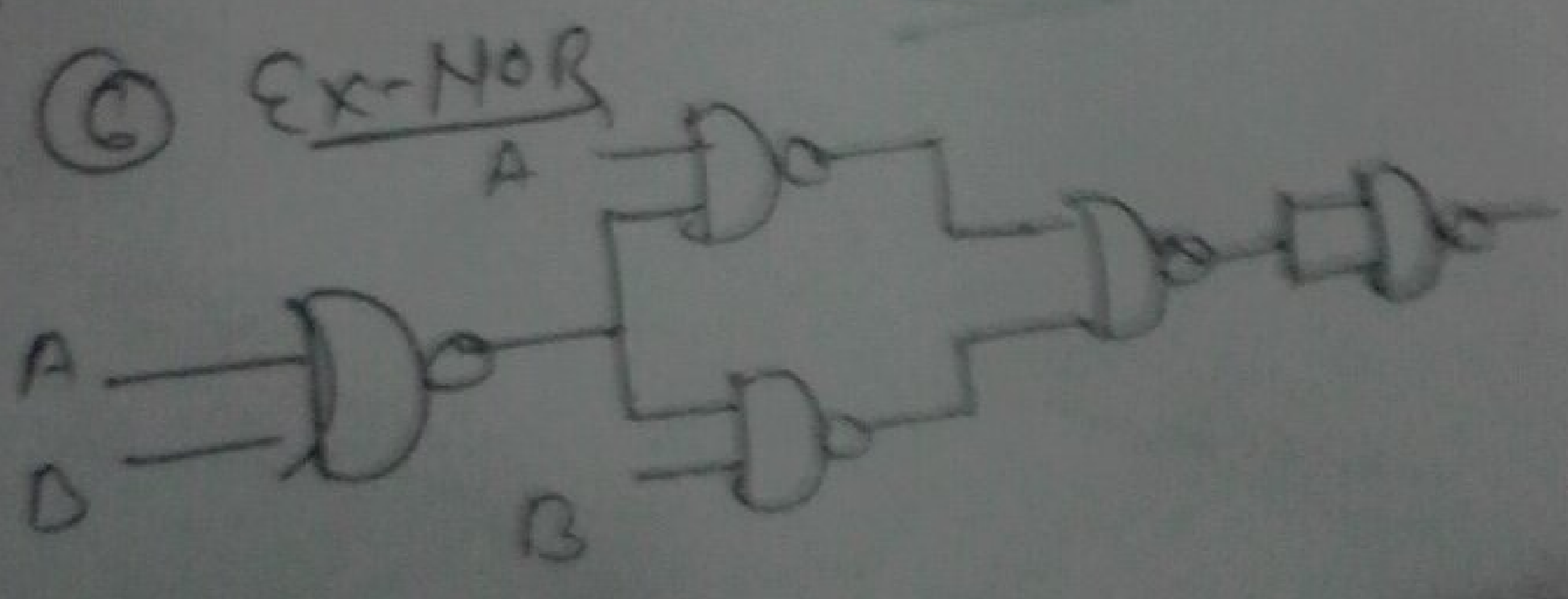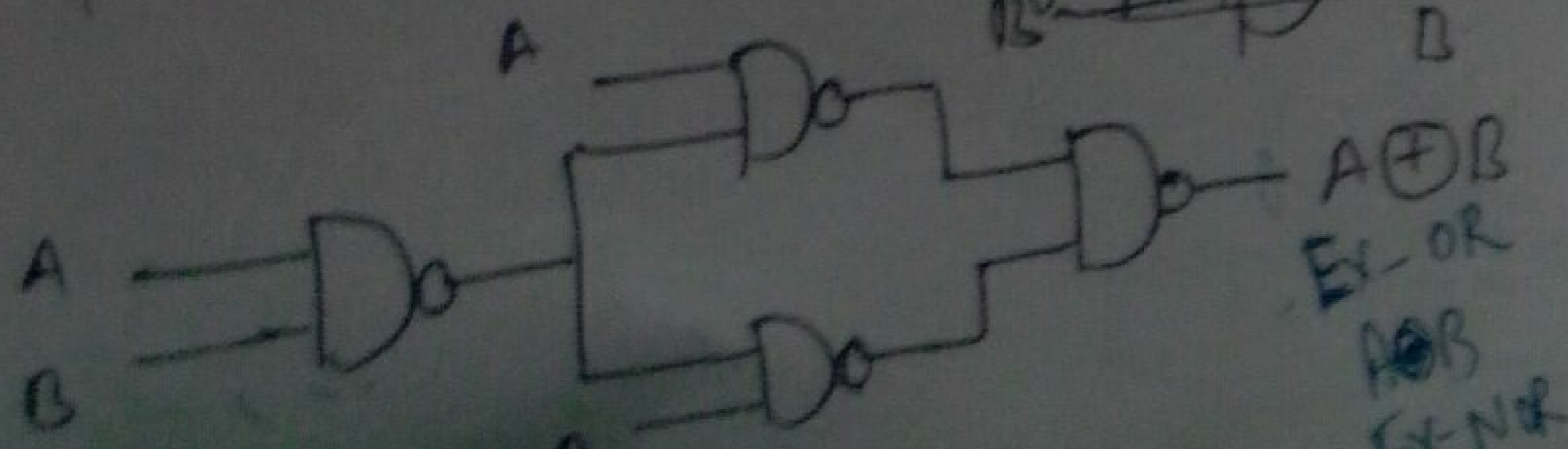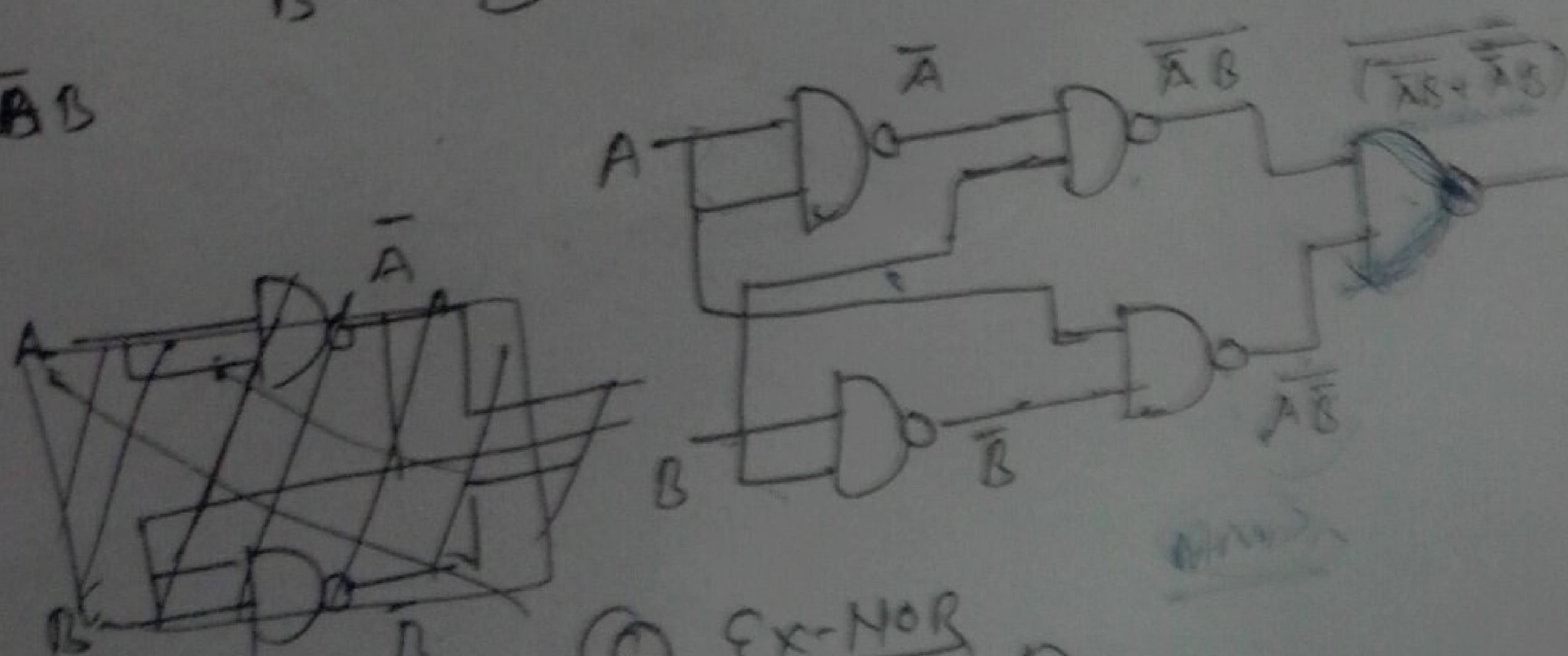
$$\bar{\bar{Y}} = \overline{\overline{A\bar{B}} \cdot \overline{\bar{A}B}}$$



$A \oplus B$
EX-OR
 $A \odot B$
EX-NOR

① NOT

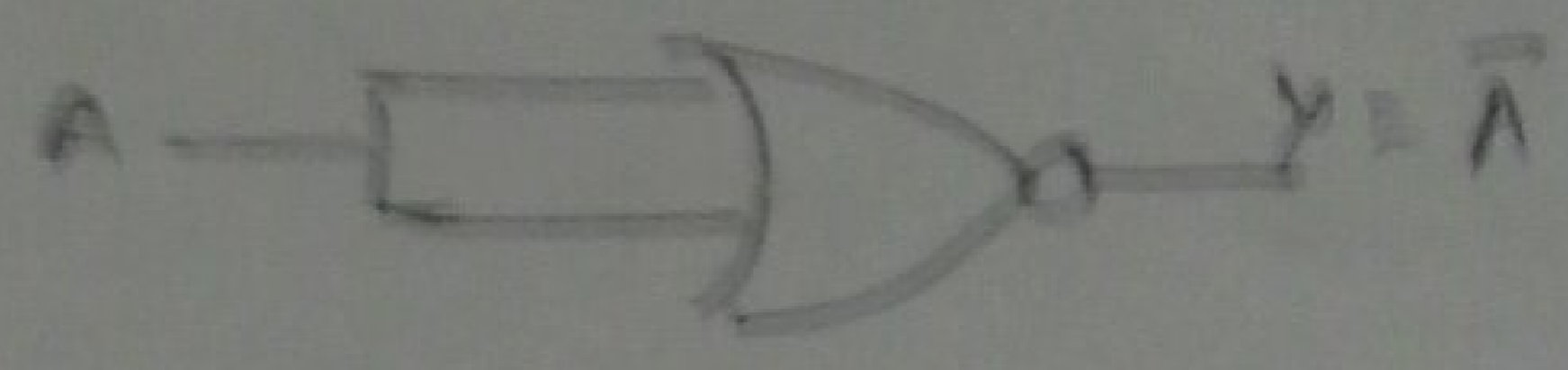

10


② AND

$$Y = AB$$

$$\bar{Y} = \overline{AB} = \bar{A} + \bar{B}$$

$$Y = \overline{\bar{Y}} = \overline{(\bar{A} + \bar{B})}$$

$$Y = AB$$

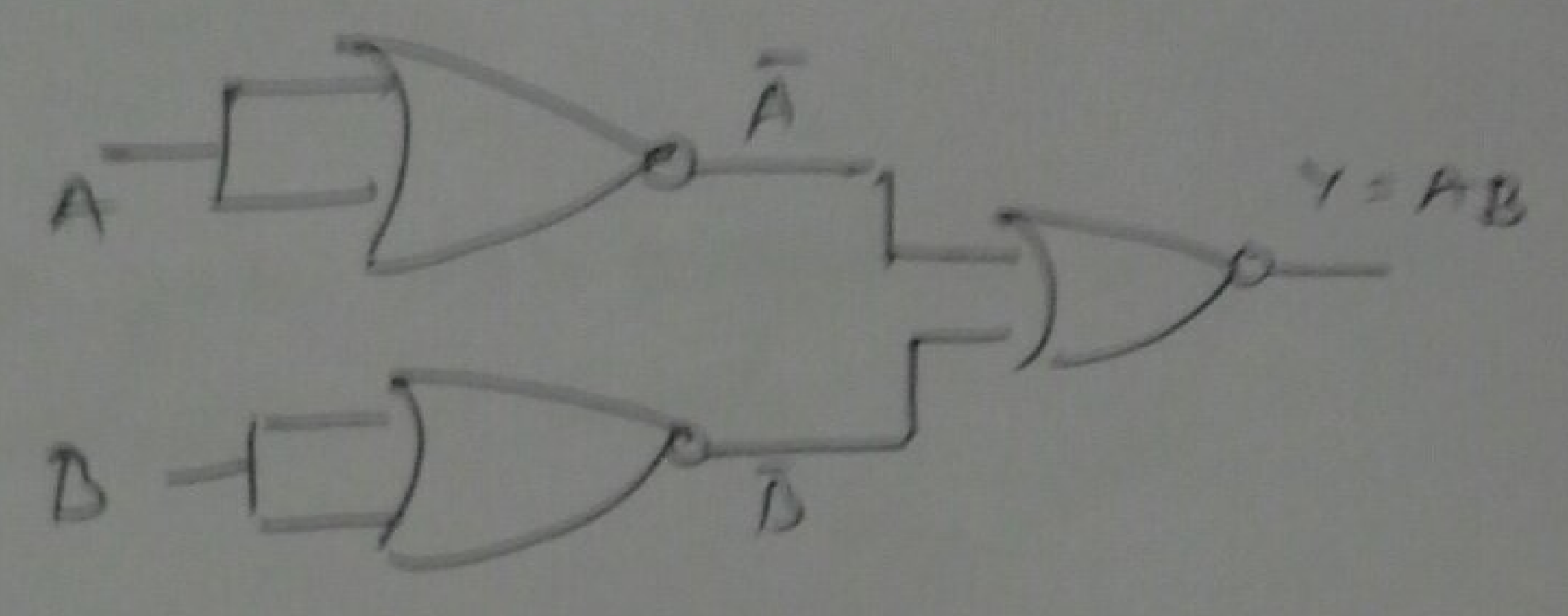


③ OR

$$Y = A + B$$

$$\bar{Y} = \overline{A + B}$$
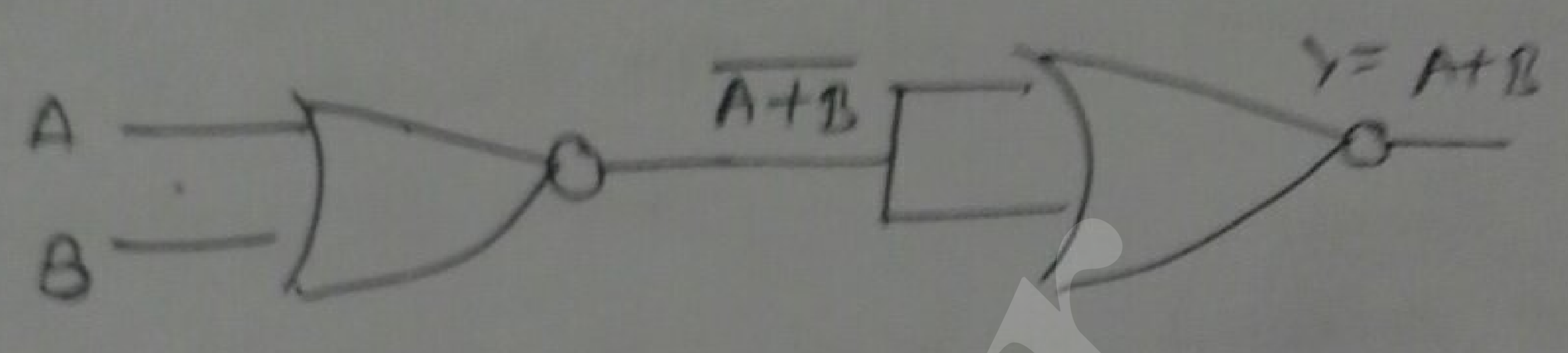
$$Y = \overline{\bar{Y}} = \overline{(\overline{A + B})}$$




④ NAND

$$Y = \overline{AB}$$

$$Y = \overline{AB} = \bar{A} + \bar{B}$$


$$\bar{Y} = \overline{\bar{A} + \bar{B}}$$
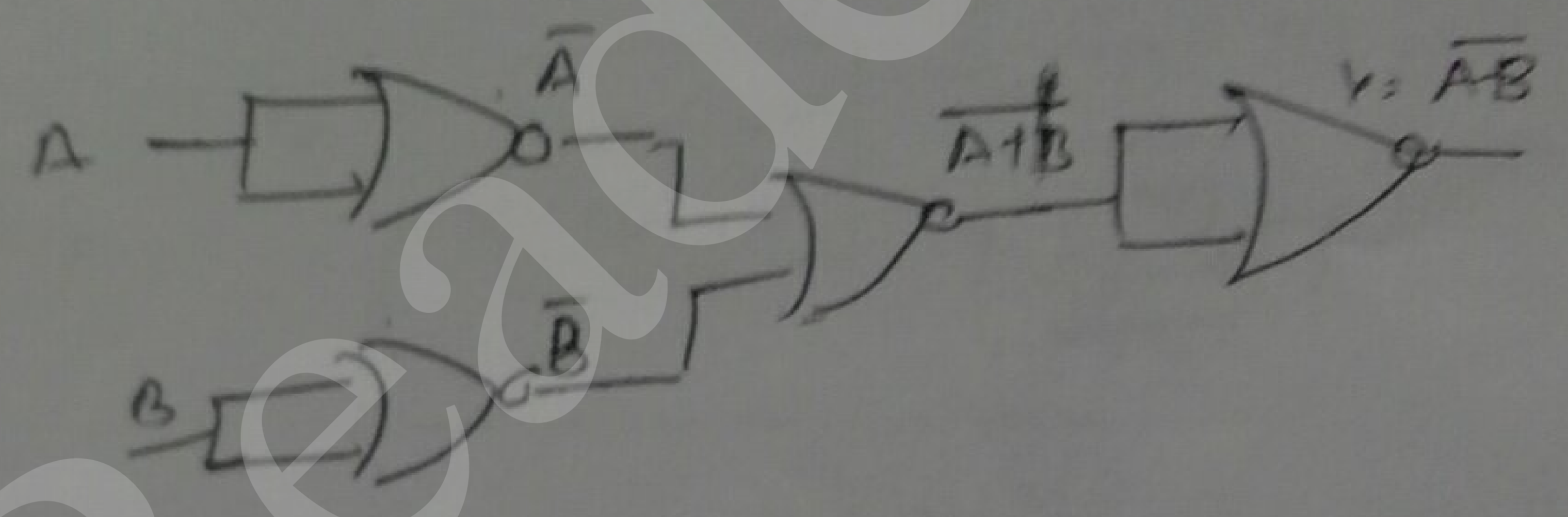
$$Y = \overline{\bar{Y}} = \overline{\overline{\bar{A} + \bar{B}}}$$




⑤ EX-OR

$$Y = A\bar{B} + \bar{A}B = A \oplus B$$

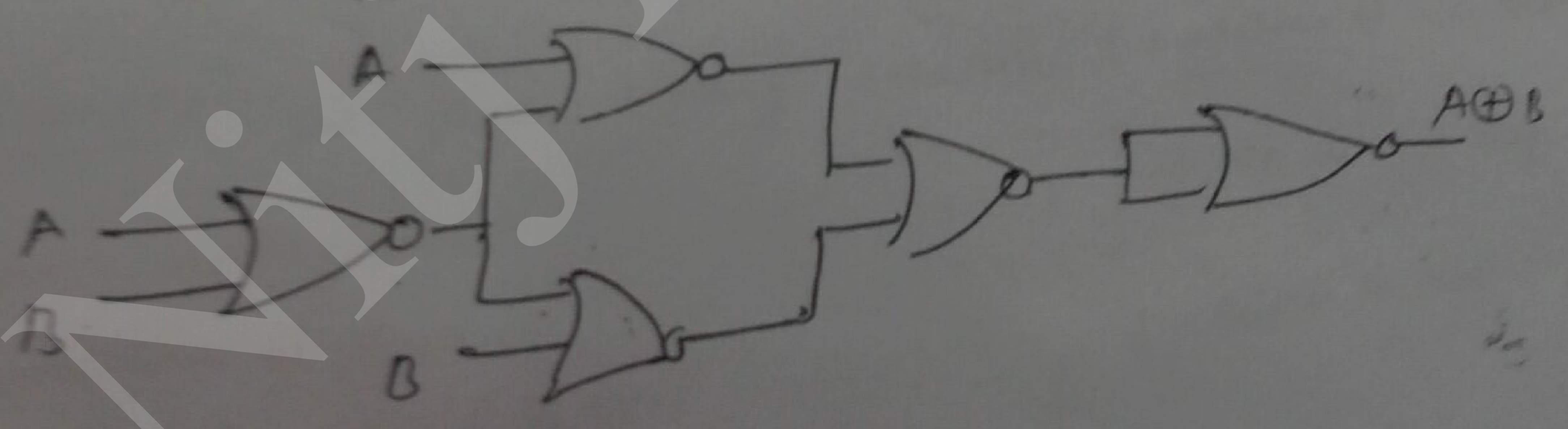

⑥ EX-NOR

$$Y = A \odot B$$

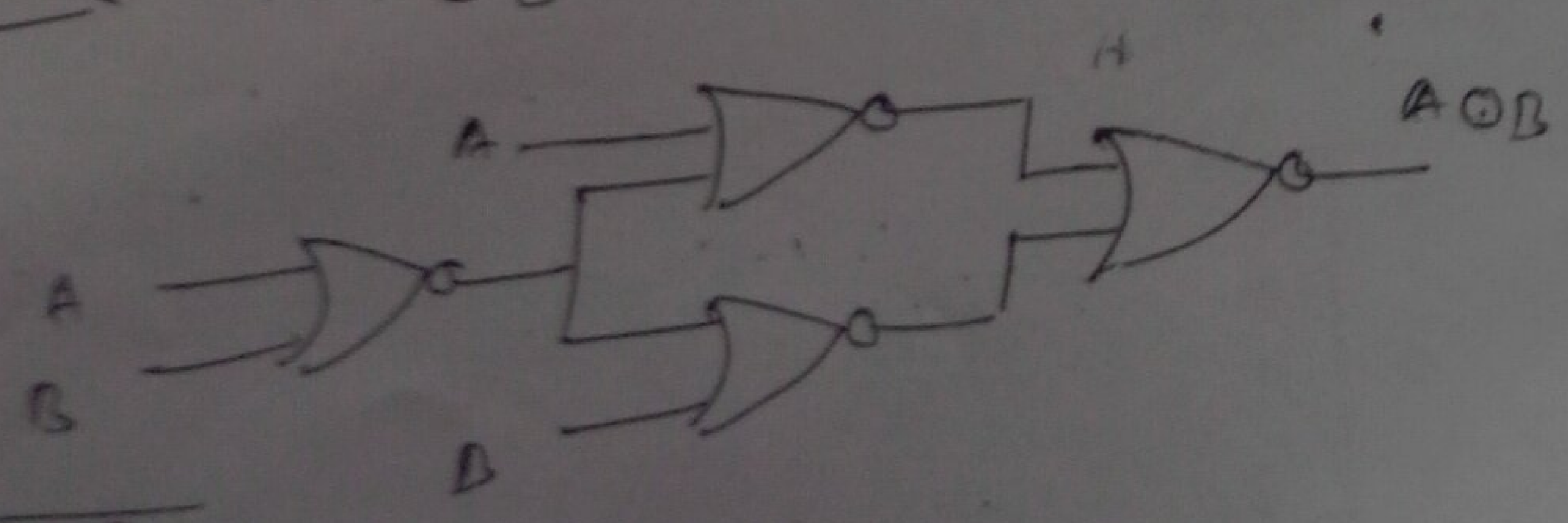


$$Y = \overline{A\bar{B} + \bar{A}B}$$

$$Y = \overline{(\overline{A\bar{B}})(\overline{\bar{A}B})} = \overline{(\bar{A} + B)(\bar{A} + \bar{B})} = \overline{(\bar{A} + B)(A + \bar{B})}$$

$$\bar{Y} = (\bar{A} + B)(A + \bar{B})$$
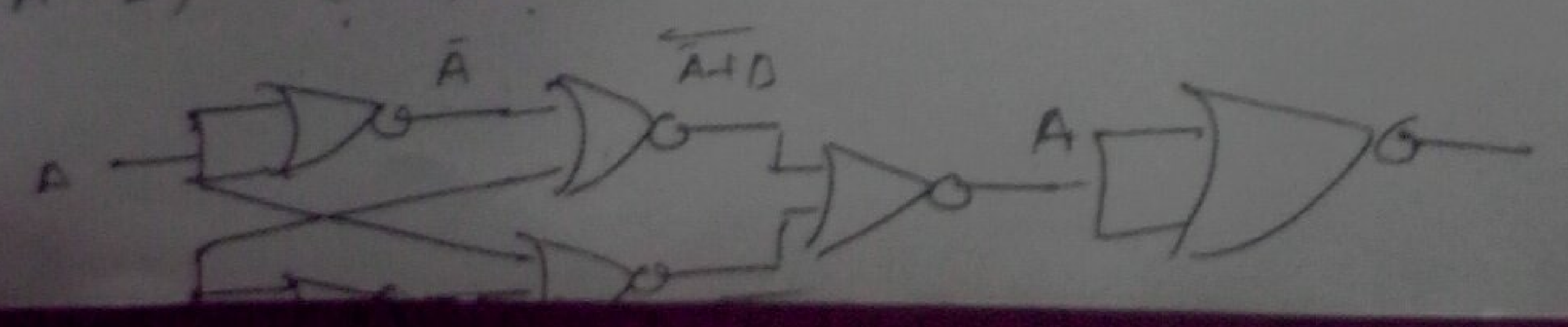
$$Y = \overline{(\bar{A} + B) + (A + \bar{B})}$$




Combinational circuits consist of logic gates whose output at any time are determined from the present combination of inputs

No feedback or memory required.


Sequential circuits - consist of storage element in addition logic gates

The output of sequential circuits depend not only on present values of inputs but also on past values of inputs.

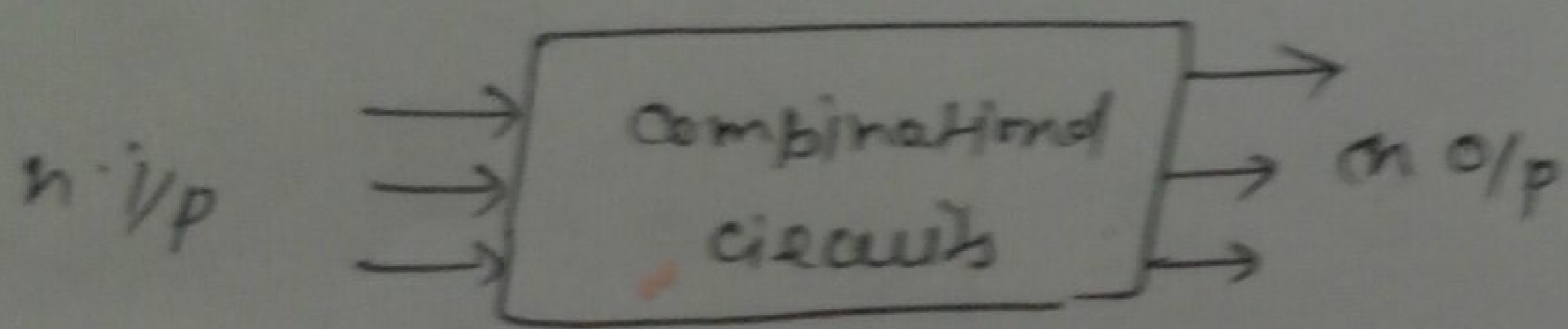The "circuit behaviour" must be specified by time sequence of input & internal states.



Combinational circuit

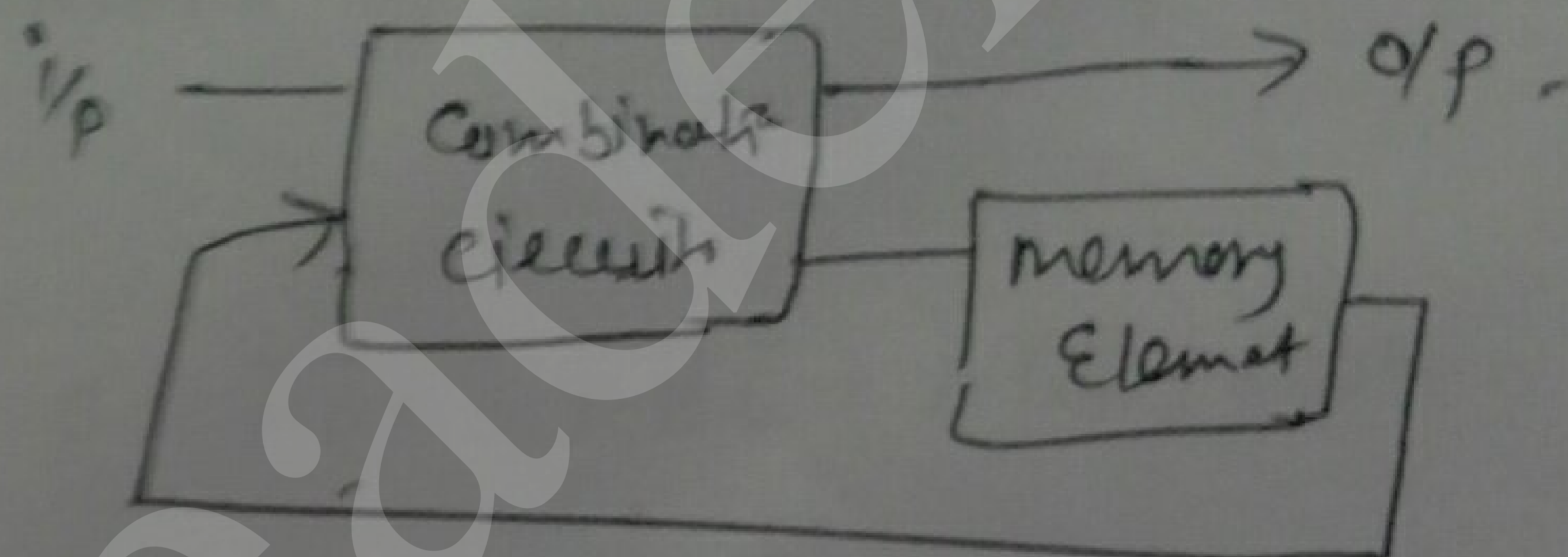

Sequential ckt

① HALF ADDER two binary


combination circuit that perform addition of two bit is called half adder

addition (addition of two binary digit)

$$\left. \begin{array}{l} 0+0=0 \\ 0+1=1 \\ 1+0=1 \end{array} \right\} \rightarrow \text{o/p in one digit}$$

$$1+1=10 \rightarrow \text{o/p - in two digit}$$

↓
Carry

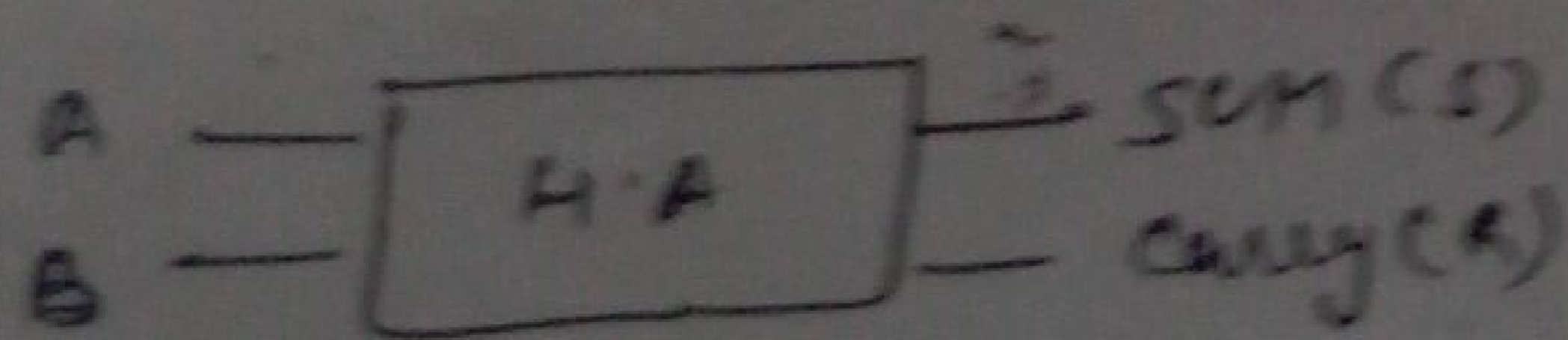

Truth table.

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

simplified Boolean function for two output can be obtained directly from truth table.






$$S = \bar{A}B + A\bar{B}$$

$$C = AB$$

LOGIC DIAGRAM

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = AB$$

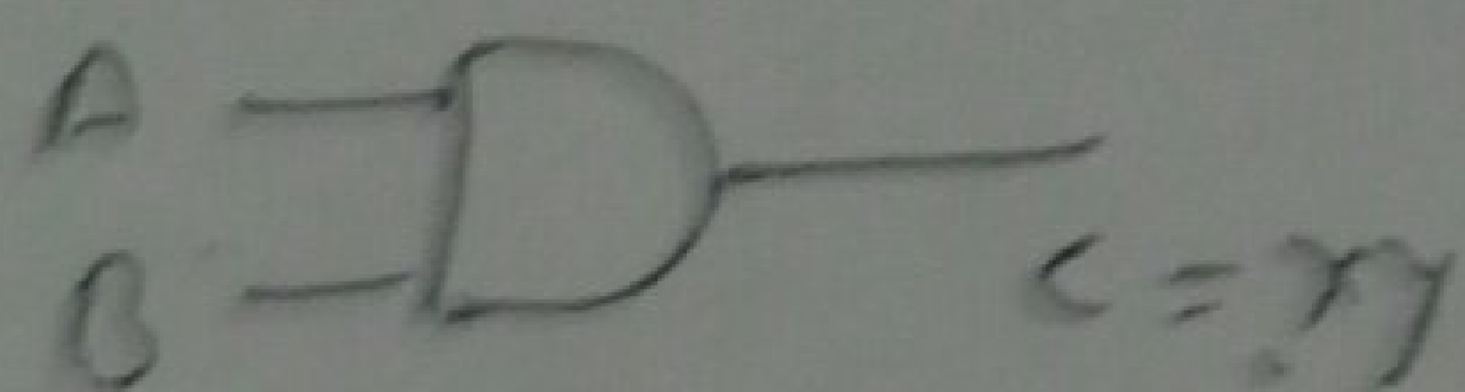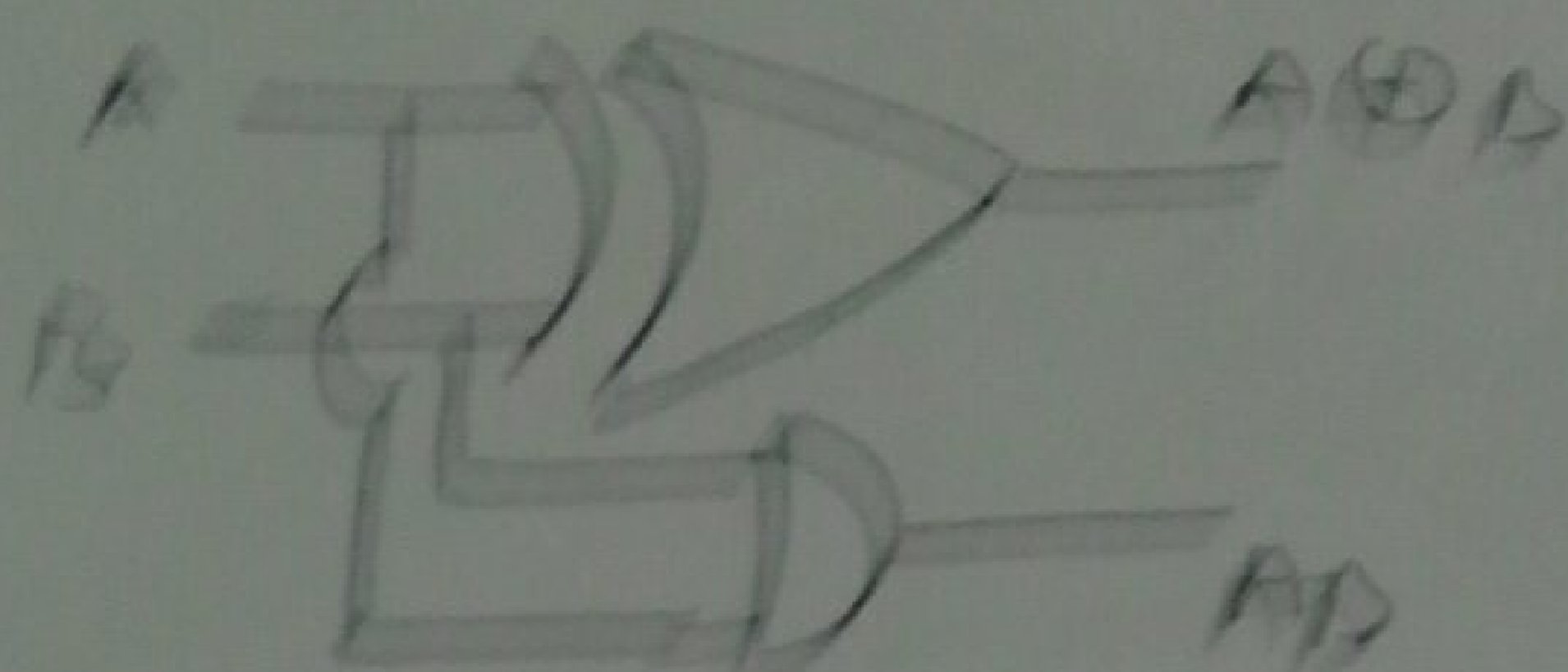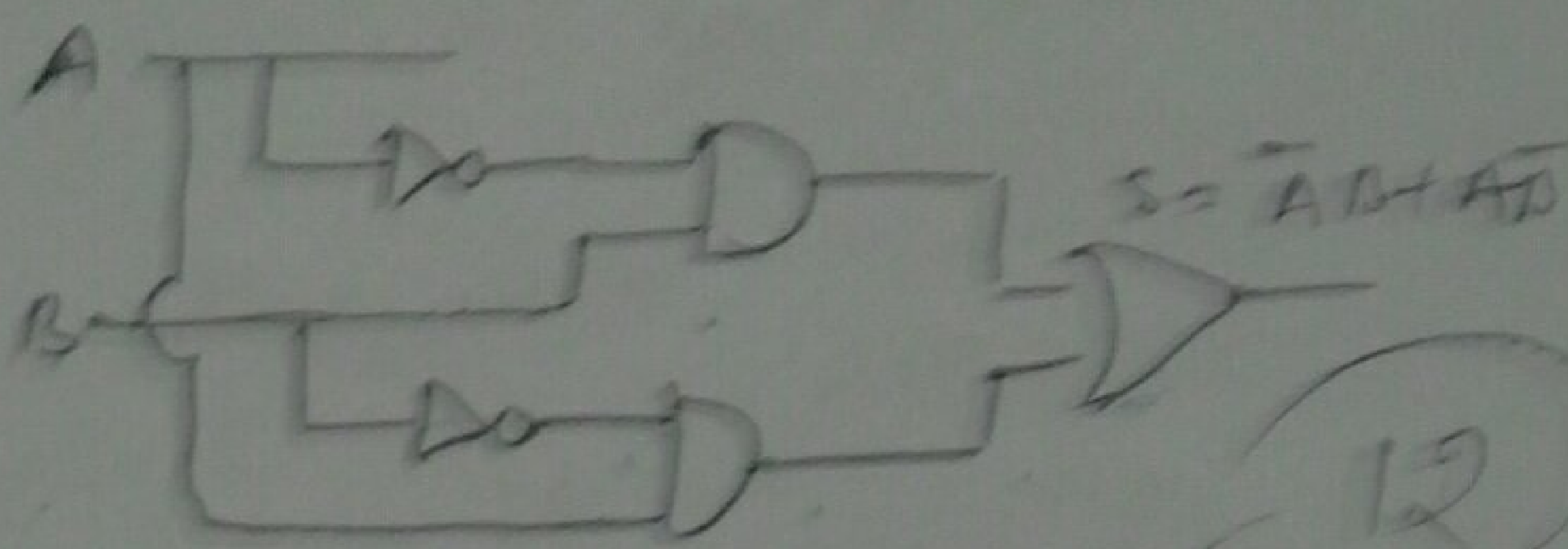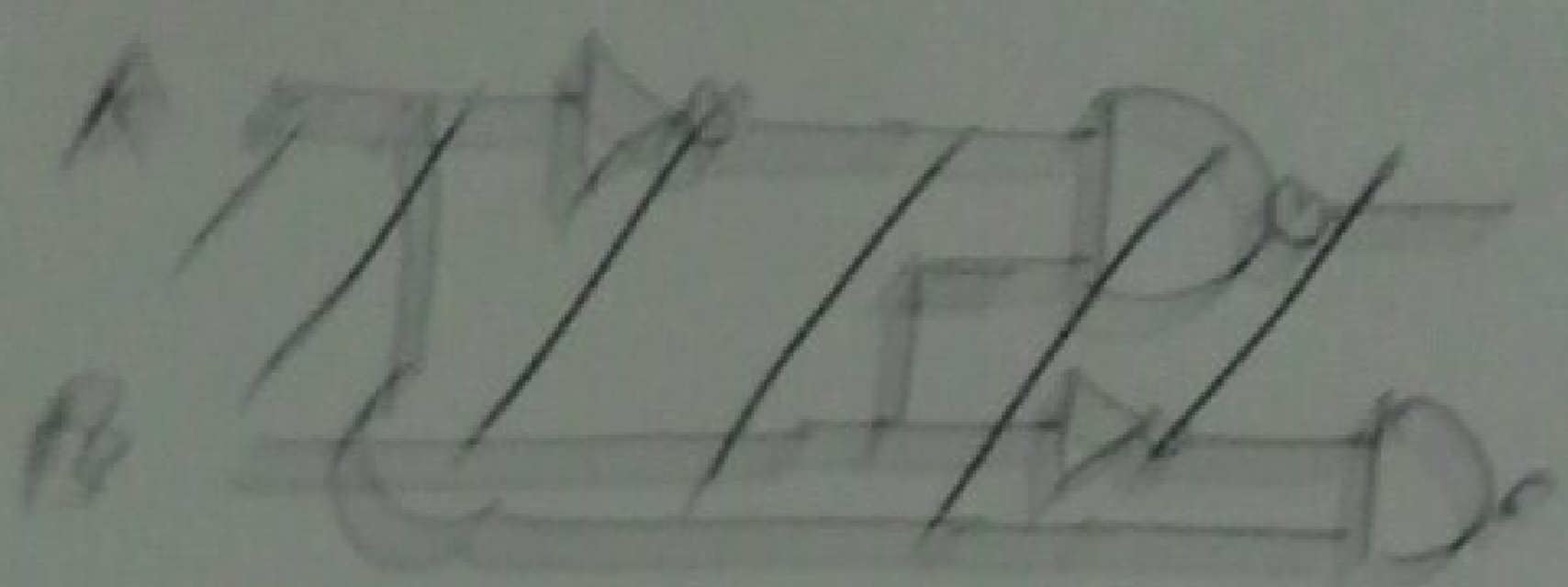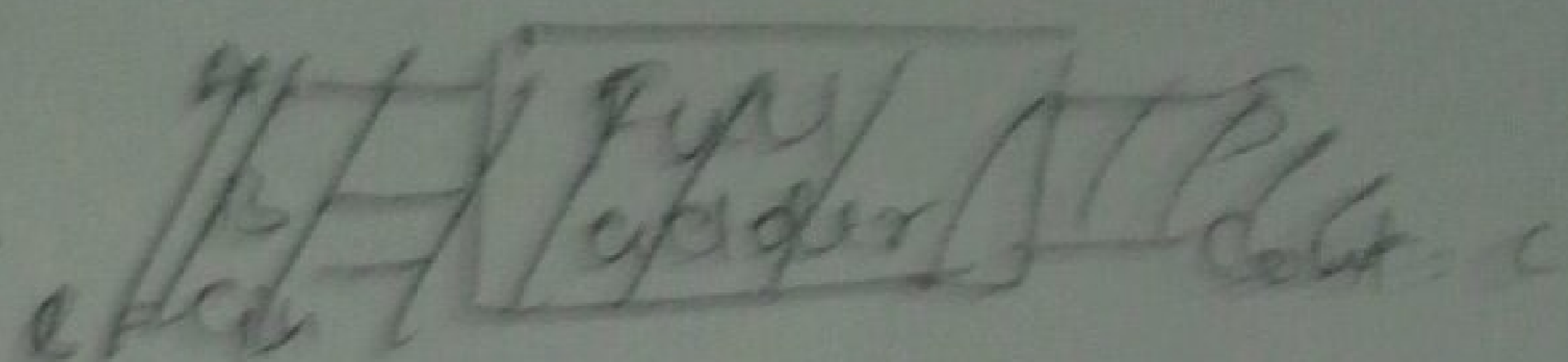


FULL ADDER, (A combinational ckt that perform addition of three bits (two significant bits and a previous carry) is a full adder. It consist of two 1/2 of two o/p)

A	B	C _{in}	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$
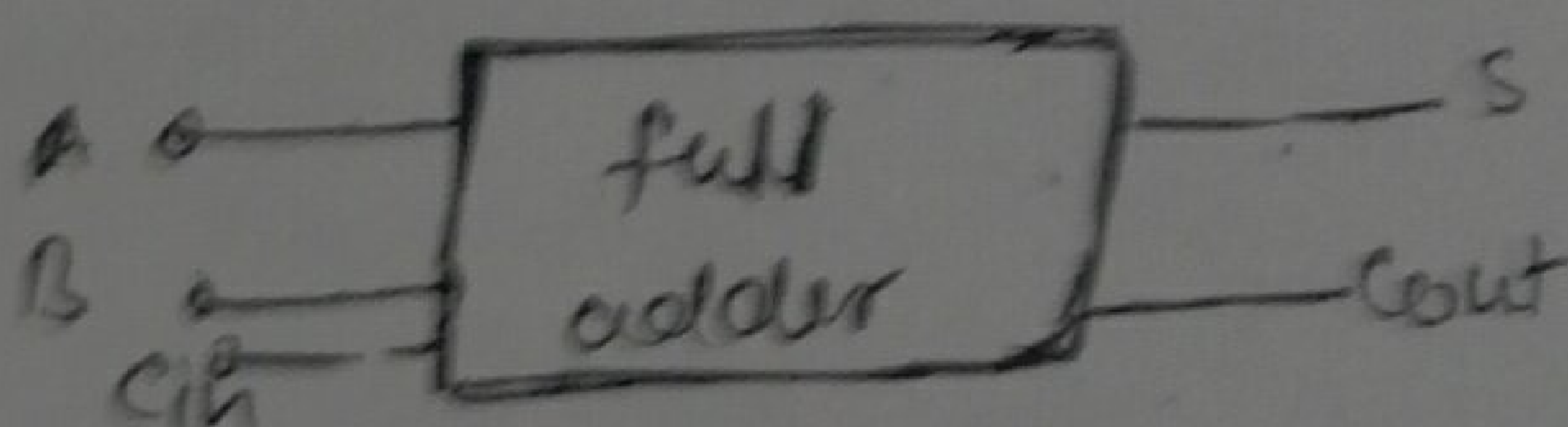
$$C_{out} = \bar{A}BC + A\bar{B}C + ABC + ABC$$



$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$



$$C_{out} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= C(\bar{A} + A) + A(B + B) = C(\bar{A} + A) + A(B + B)$$

$$= C(\bar{A}B + A\bar{B}) + AB(\bar{C} + C)$$

$$= C(A \oplus B) + AB$$


$$C_{out} = AC + BC + AB$$

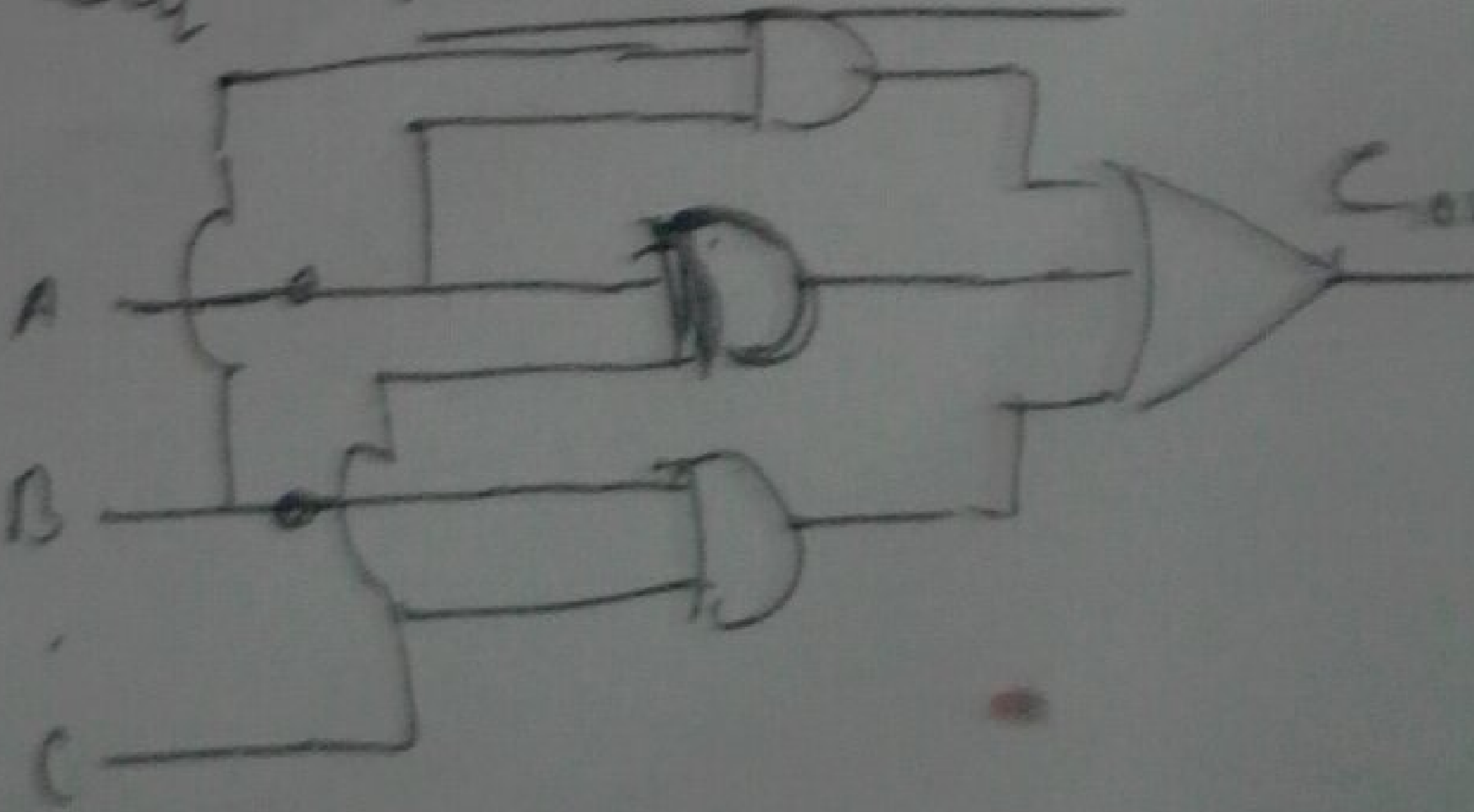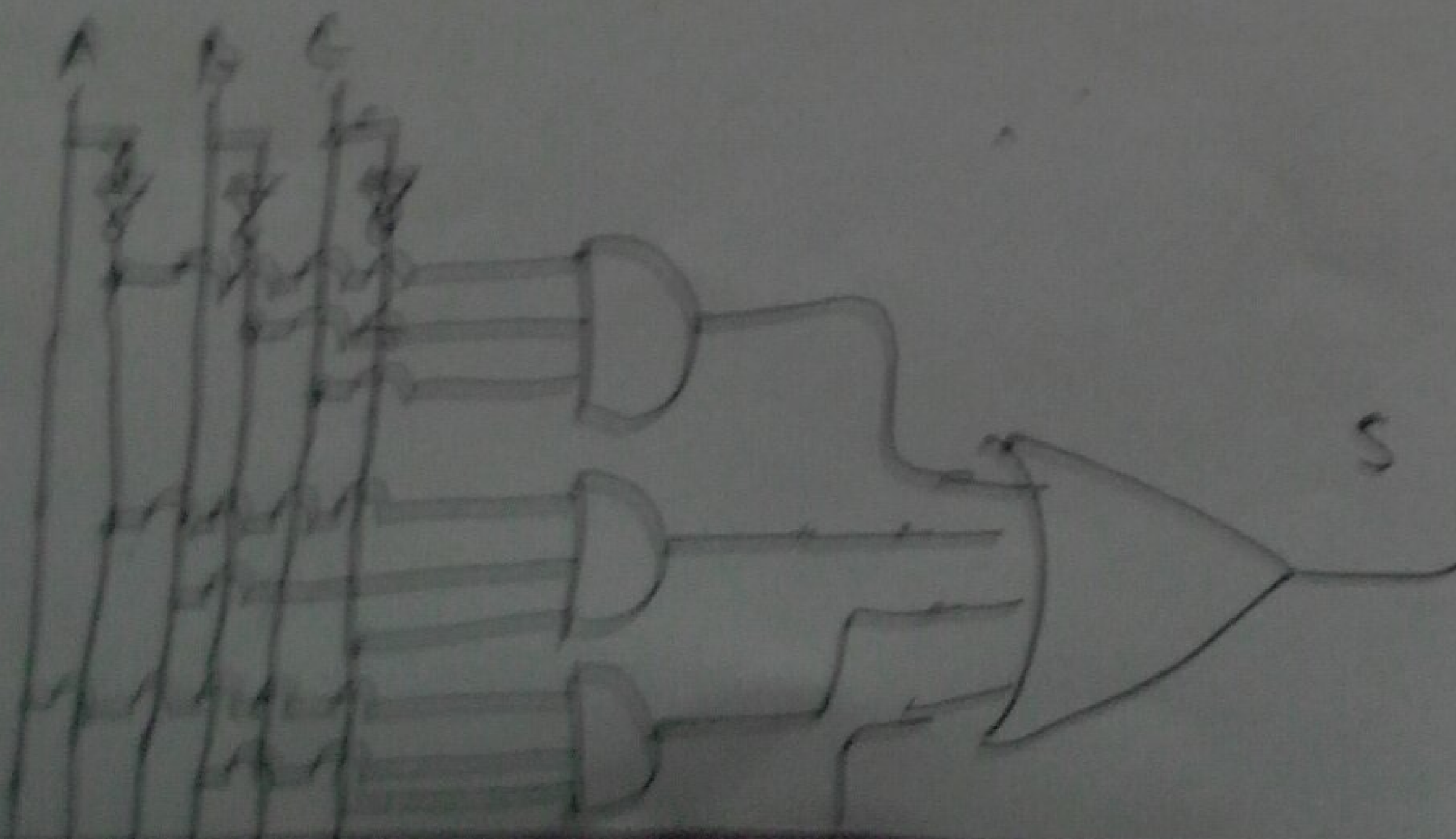

$$\begin{aligned}
 S &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C} \\
 &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + B\bar{C}) \\
 &= \bar{A}(B \oplus C) + A(\overline{B \oplus C}) \\
 S &= \underline{A \oplus B \oplus C}
 \end{aligned}$$

13
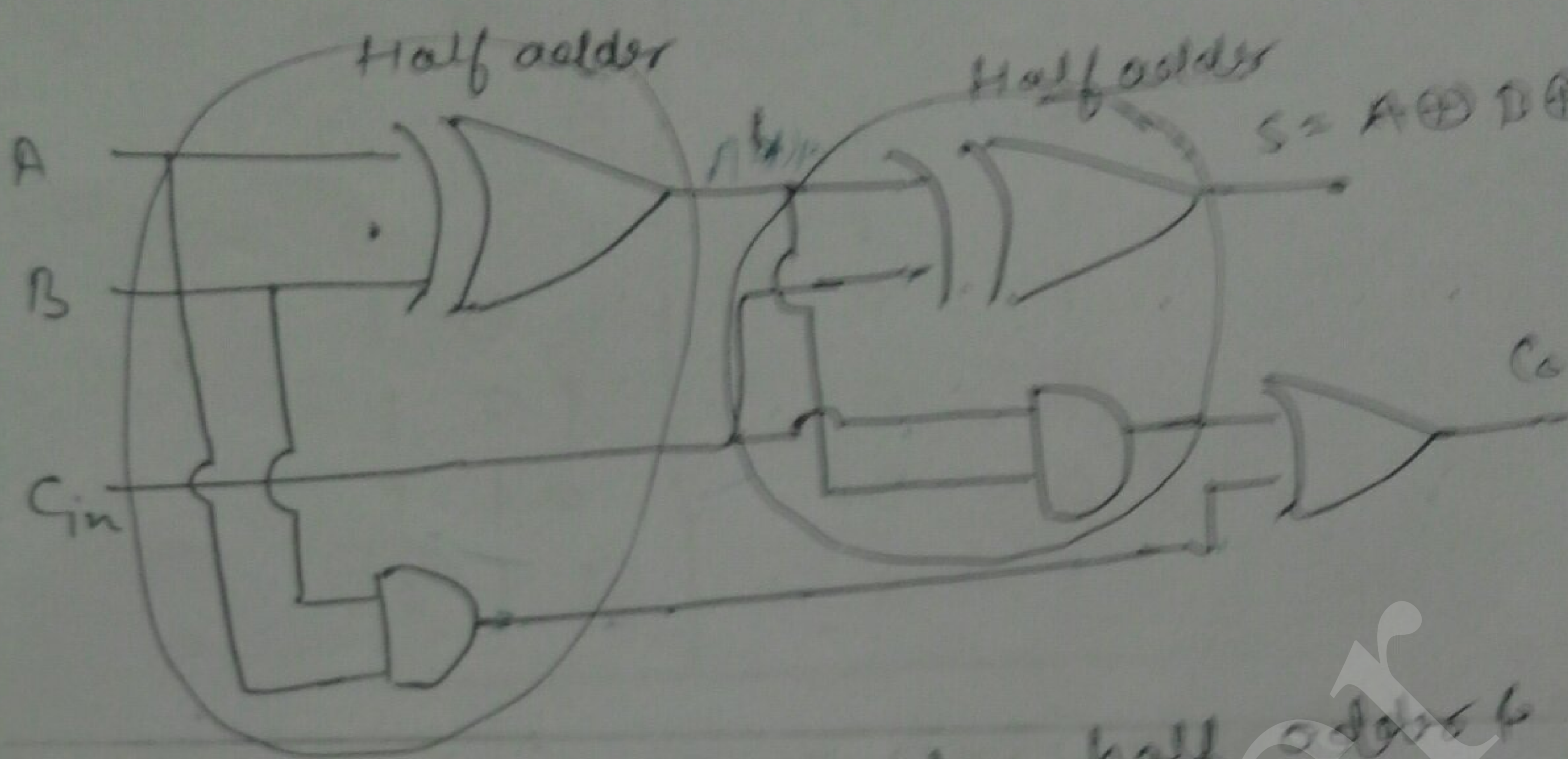
$$\begin{aligned}
 C &= C(A \oplus B) + AB \\
 C &= AC + BC + AB
 \end{aligned}$$




full adder using two half adders & one or gate

The
HALF SUBTRACTORS :-

Combination of ckt that subtract one bit from the other and produces the difference. It also has an output to specify if a 1 has borrowed.


minuend
- Subtrahend

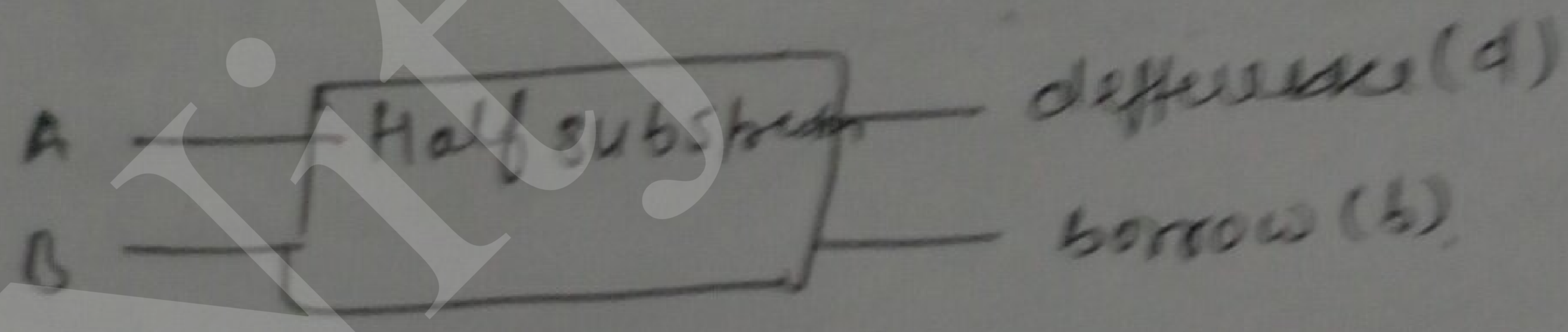

A	B	b	d
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

$$\begin{aligned}
 d &= \bar{A}B + A\bar{B} = A \oplus B \\
 b &= \bar{A}B
 \end{aligned}$$

2-15
10-1

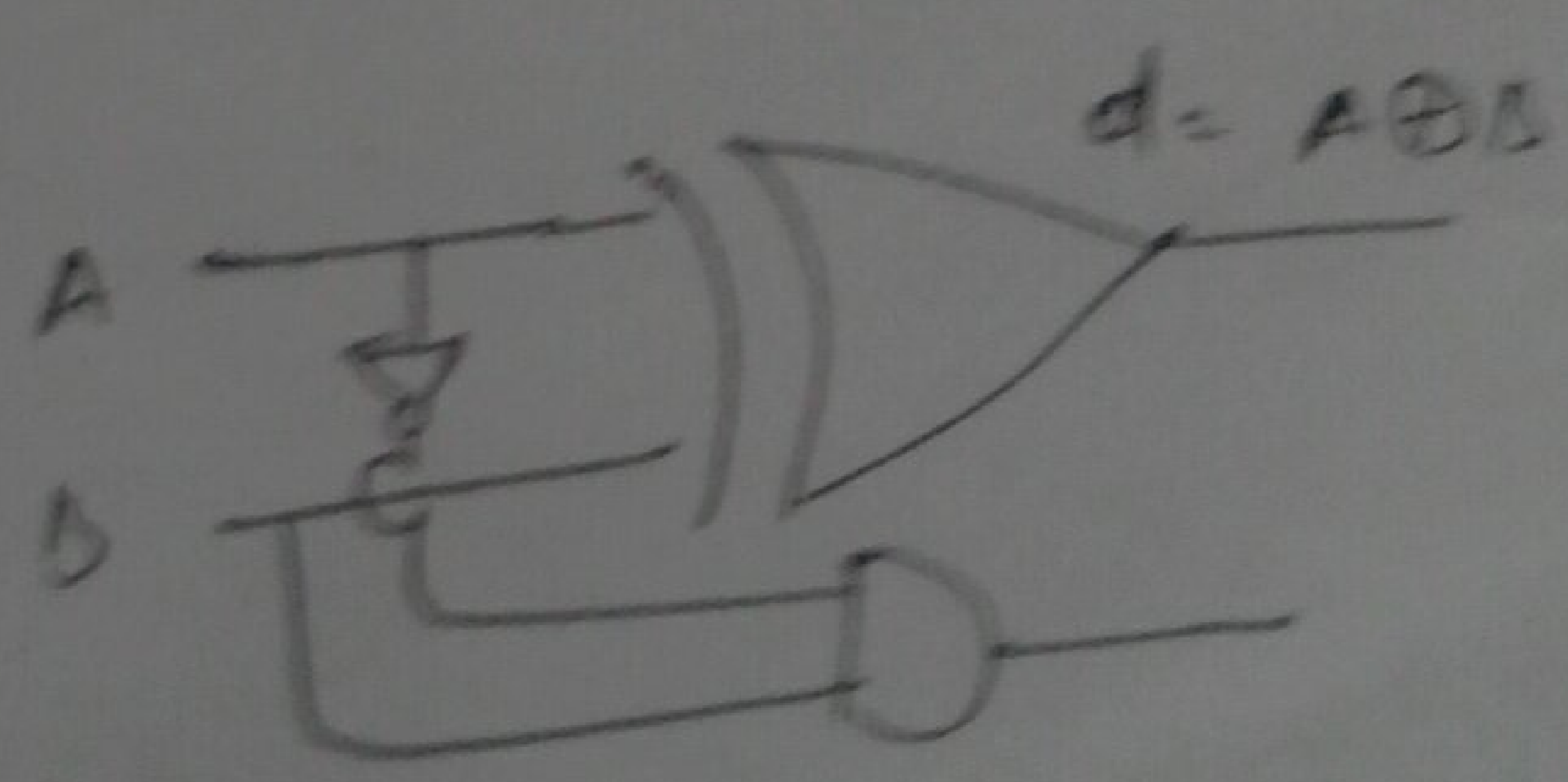

Full subtractor


10-15

14

A	B	C	b	d
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$d = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC = A \oplus B \oplus C$$
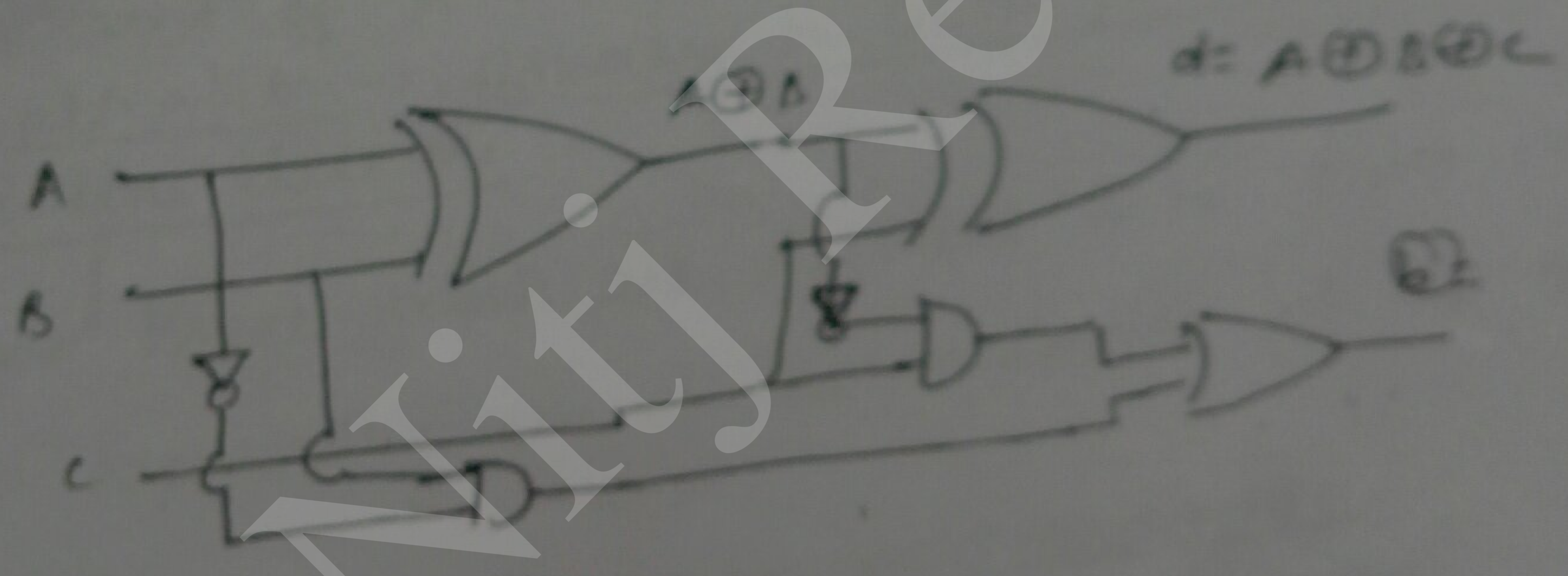
$$b = \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C + ABC = AB + (A \oplus B)C$$



A binary code of n-bits is capable of representing up to 2^n distinct elements of coded information

15

Such as:

$n=2$

$$\begin{matrix} 0 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & 1 \end{matrix} \Rightarrow 2^2 = 4$$

$n=3$

$2^n = 8$

$$\begin{matrix} 0 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \\ 1 & 1 & 1 \end{matrix} = 8$$


A decoder is combinational ckt that convert binary information from n-input lines to a maximum of 2^n output lines

The decoder presented here are called n to m line decoders, where $m \leq 2^n$. Their purpose is to generate the 2^n (or fewer) minterms of n input variables.


Application \rightarrow Binary to Octal Converter
3 to 8 line decoder :-

The three inputs are decoded into eight outputs, each representing one of the minterms of the three input variables.

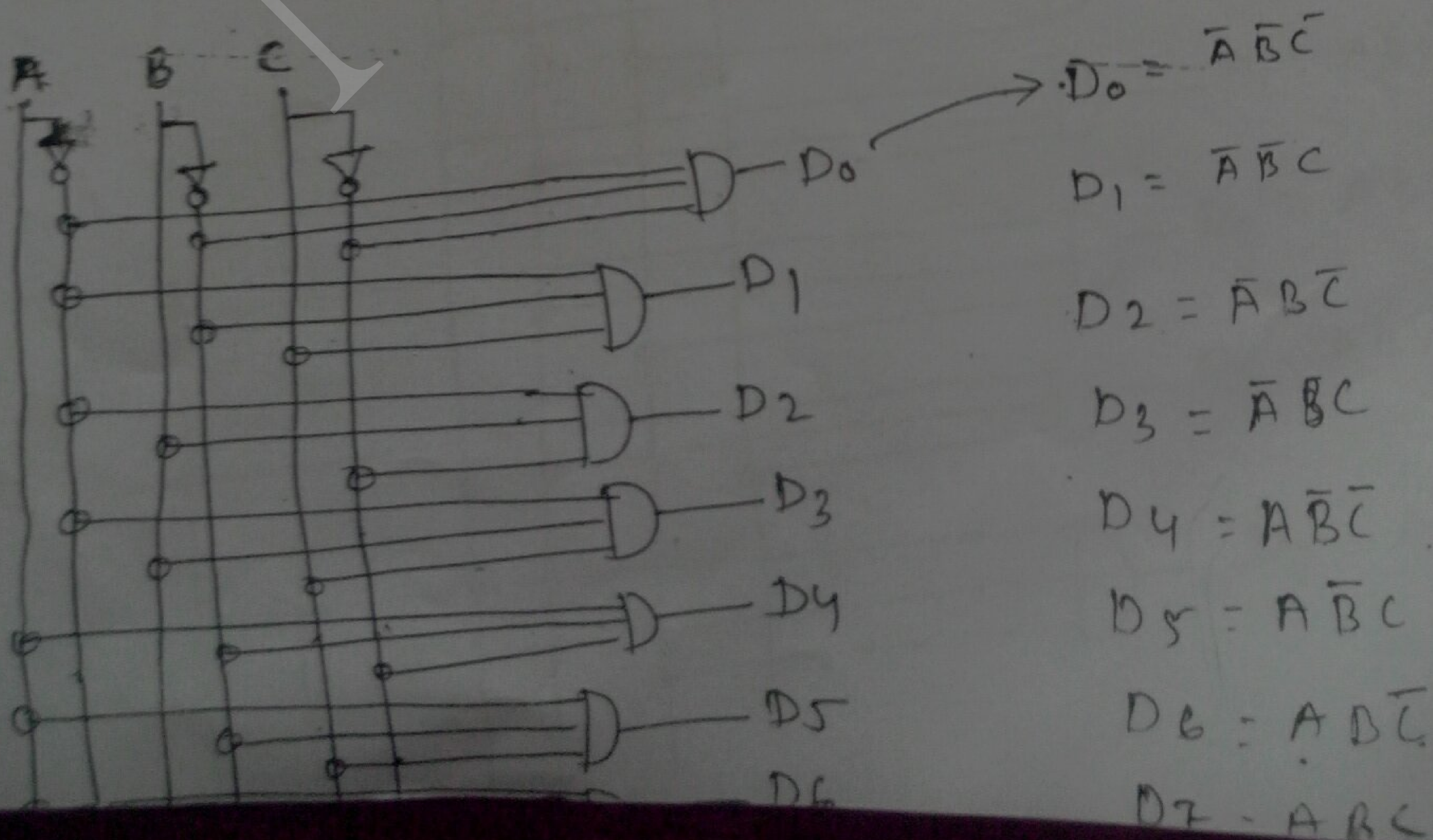Application \rightarrow Binary to Octal Converter



A	B	C	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	0	1	0
1	1	0	0	0	0	0	0	0	0	1
1	1	1	0	0	0	0	0	0	0	0

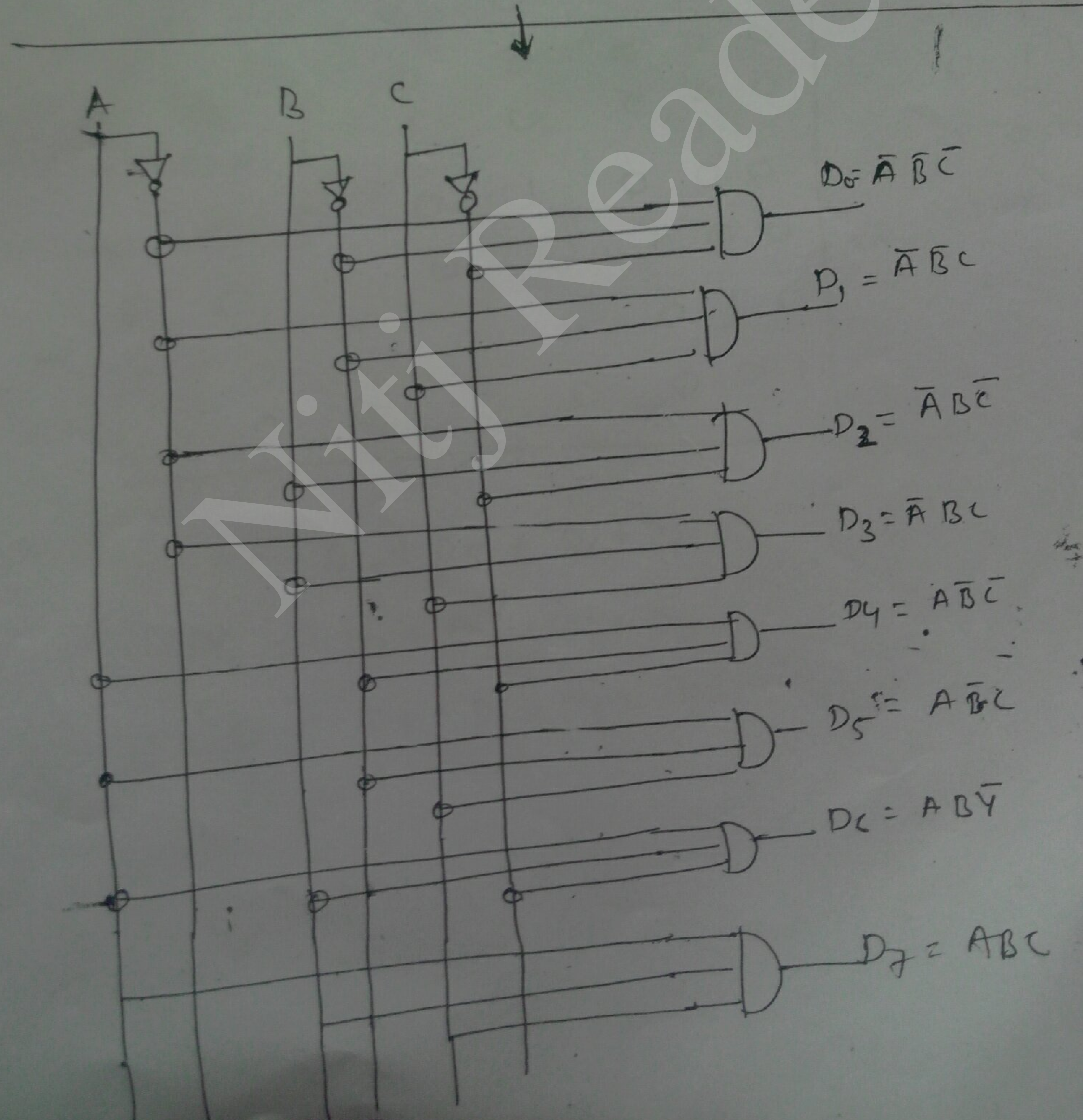

ENCODERS

An Encoder is a digital circuit that performs the inverse operation of decoder. 17

An Encoder has 2^n (or fewer) input lines and output lines.

The Output lines generate the binary code corresponding to the input values. An example of an encoder is octal to binary Encoder. It has eight inputs (one for each of the octal digits) and three outputs that generate the corresponding binary no.

It is assumed that only one input has a value of 1 at a given time.

INPUTS								OUTPUTS		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	A	B	C
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	1
0	1	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	1	0	1
0	0	0	0	0	1	0	0	1	1	0
0	0	0	0	0	0	1	0	0	1	1
0	0	0	0	0	0	0	1	0	1	1

$$A = D_4 + D_5 + D_6 + D_7$$

$$B = D_2 + D_3 + D_6 + D_7$$

$$C = D_1 + D_3 + D_5 + D_7$$

MULTIPLEXERS; (DATA SELECTORS)

A multiplexer is a combinational circuit that selects binary information from one of many inputs lines and directs it to single output line.

Normally there are 2^n inputs lines and n selection lines whose bit combinations determine which input is selected.

2:1 MUX


(18)

if $n=1$
 $2^1 = 2$
 selection lines = $n=1$

This is called 2:1 MUX

Function table

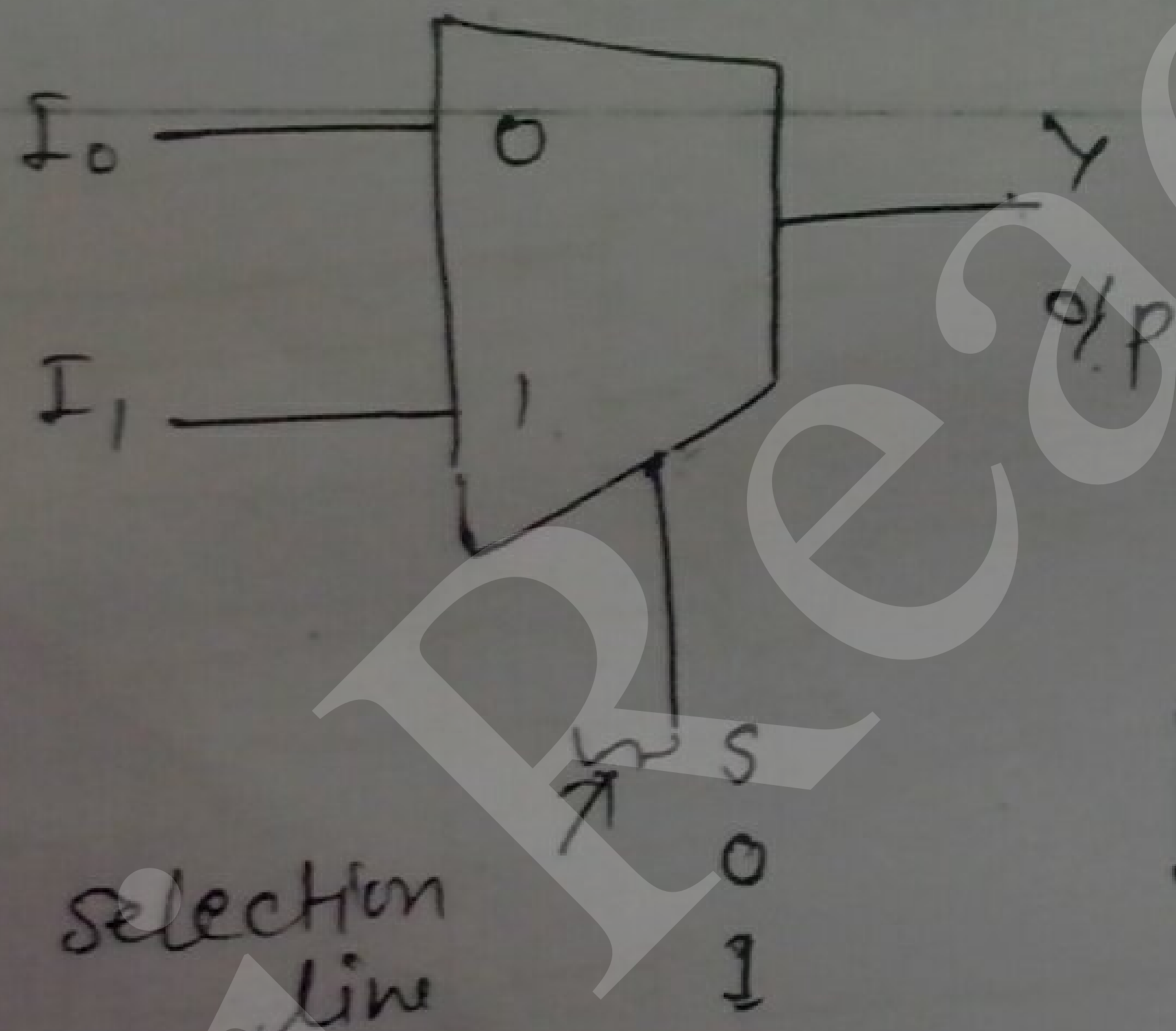~~selection~~
 Data I/p lines
 block diagram.




S	Y
0	I_0
1	I_1

$Y = I_0 \bar{S} + I_1 S$

when $S=0$, I_0 has a path to output
 when $S=1$, I_1 has a path to output.

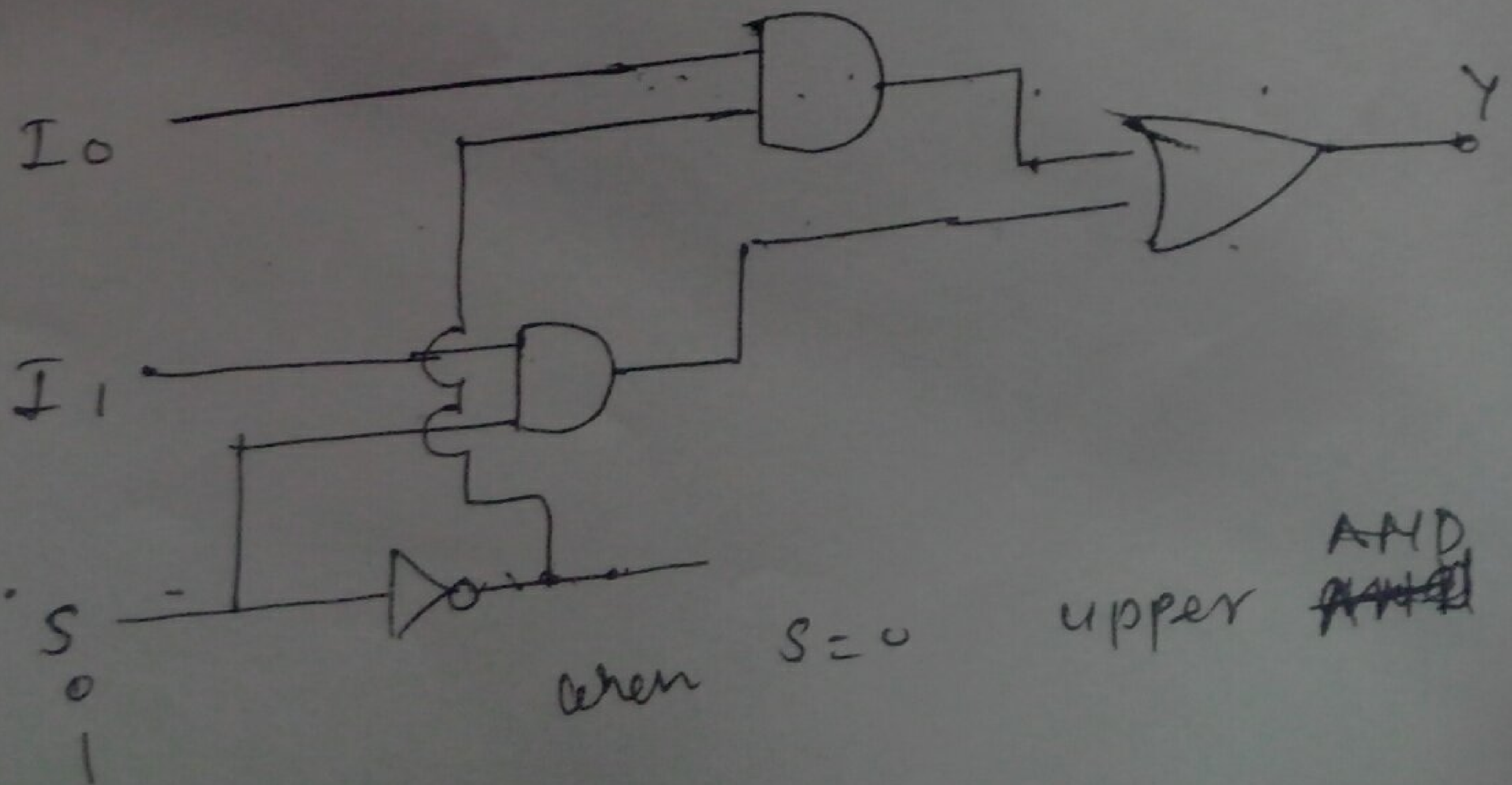The mux acts like an electronic switch that selects one of the two sources.



when $S=0$ upper ~~AND~~ AND gate is on
 when $S=1$ lower AND gate is on

4:1 MUX

n = 2


I/p lines: $2^n = 2^2 = 4$

~~selection~~ selection line: 2 = n


Function table.

S ₁	S ₀	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

data I/p

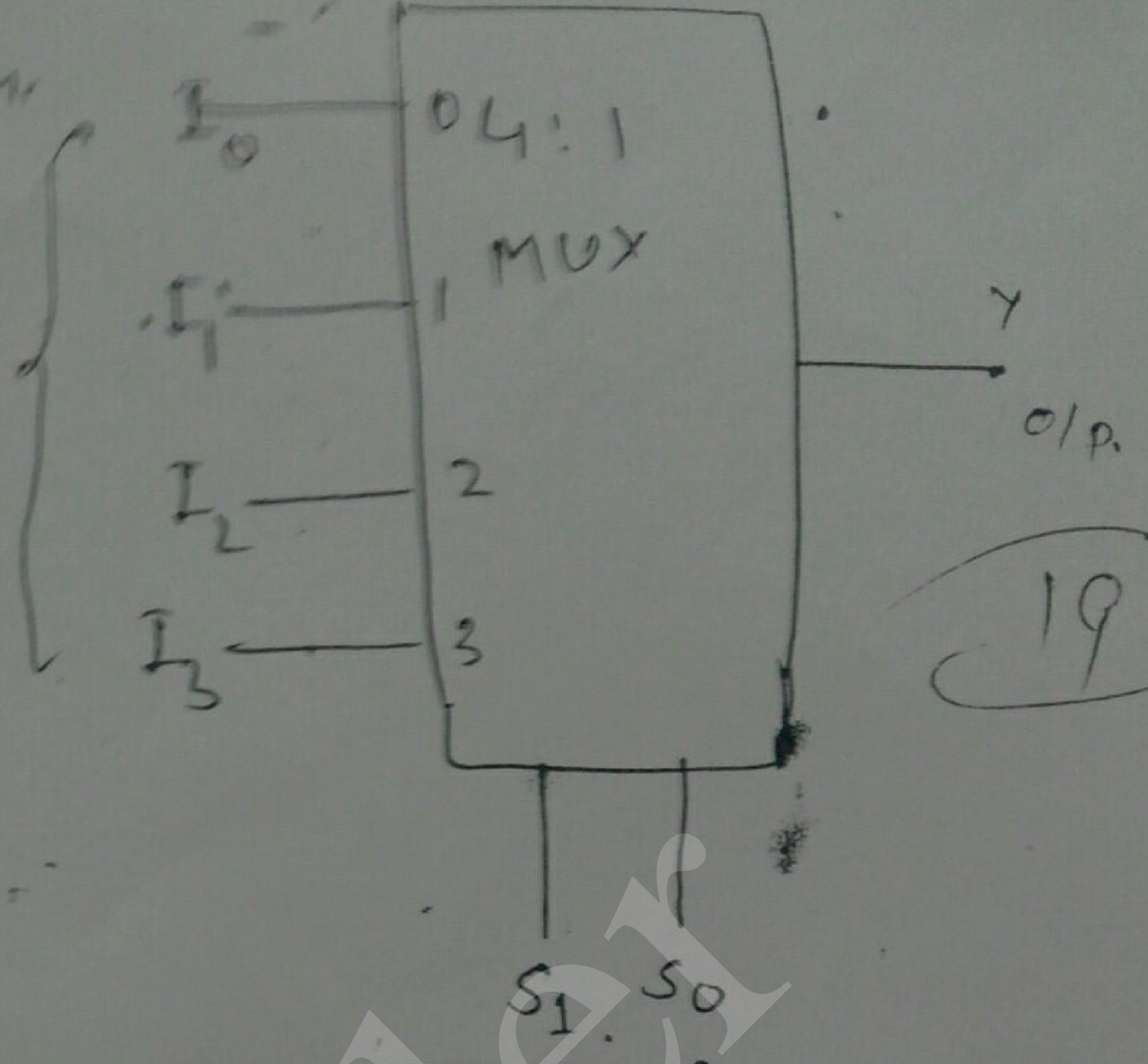

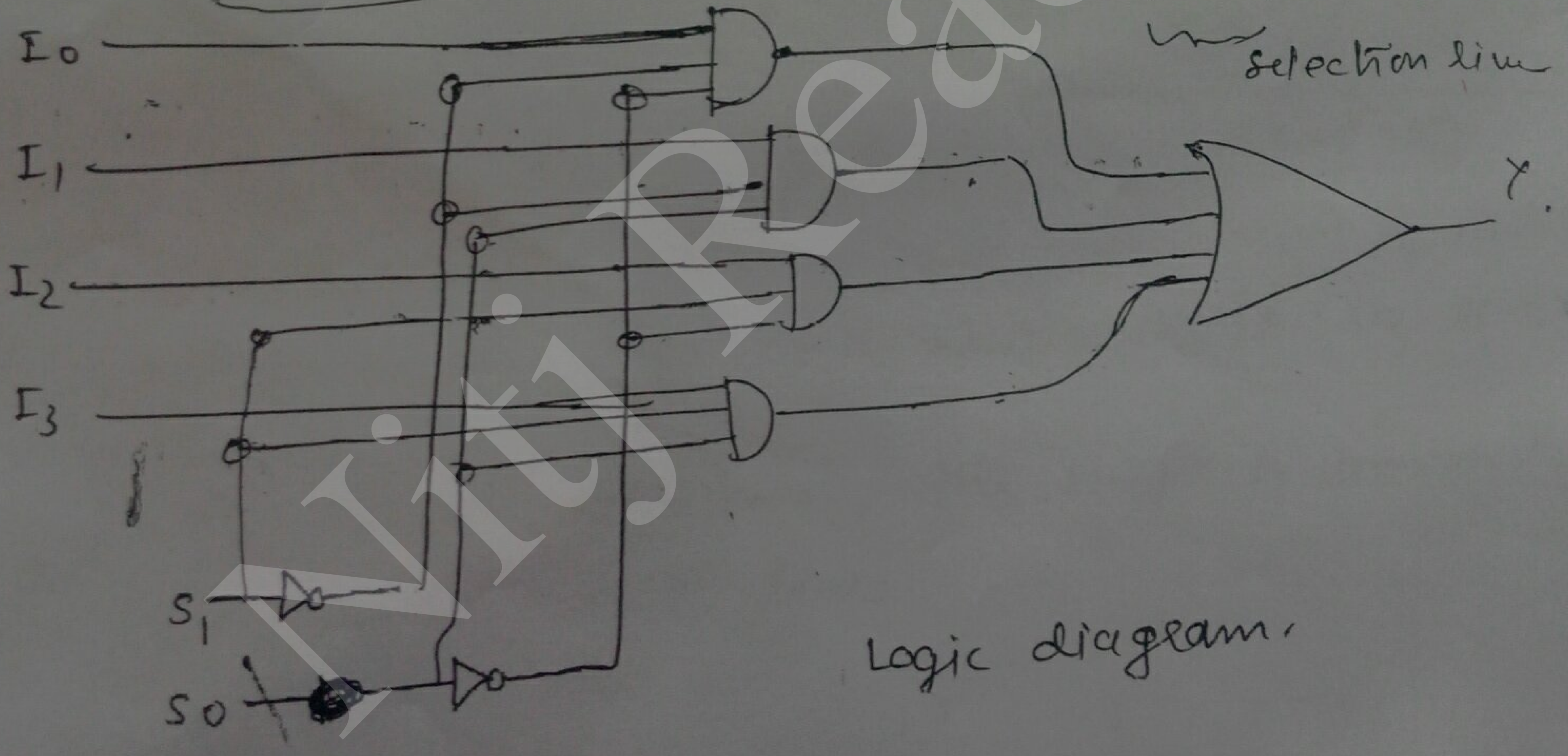
$$Y = I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$



Logic diagram.

s_2	s_1	s_0	y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

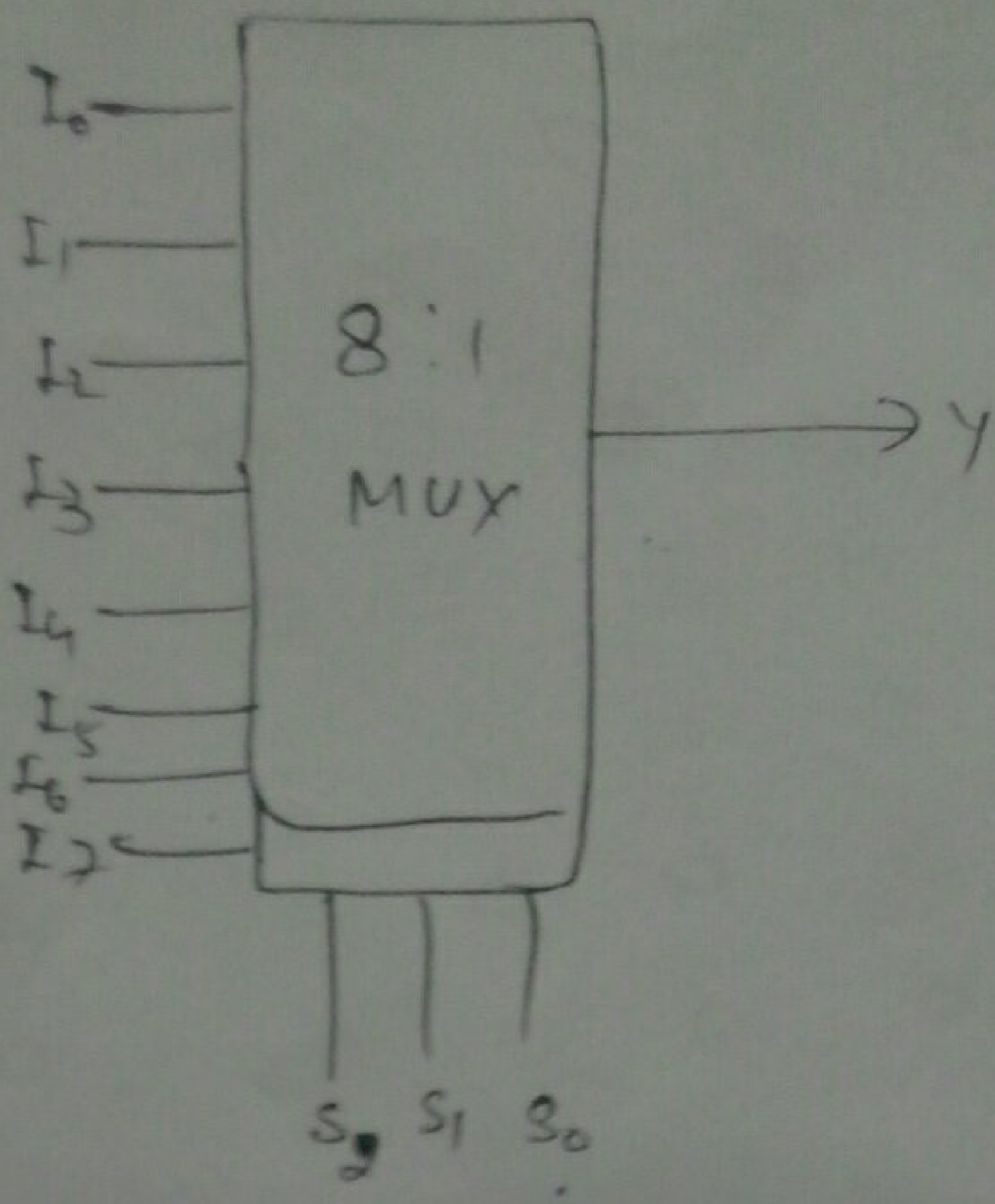

20


$$y = I_0 \bar{s}_2 \bar{s}_1 \bar{s}_0 + I_1 \bar{s}_2 \bar{s}_1 s_0 + I_2 \bar{s}_2 s_1 \bar{s}_0 + I_3 \bar{s}_2 s_1 s_0 + I_4 s_2 \bar{s}_1 \bar{s}_0 + I_5 s_2 \bar{s}_1 s_0 + I_6 s_2 s_1 \bar{s}_0 + I_7 s_2 s_1 s_0$$

DEMULTIPLEXER (DATA DISTRIBUTORS)

A demultiplexer performs the reverse operation of multiplexing. It takes a single input and distributes it to several outputs. The select input determines, the input is transmitted to which of the output lines.

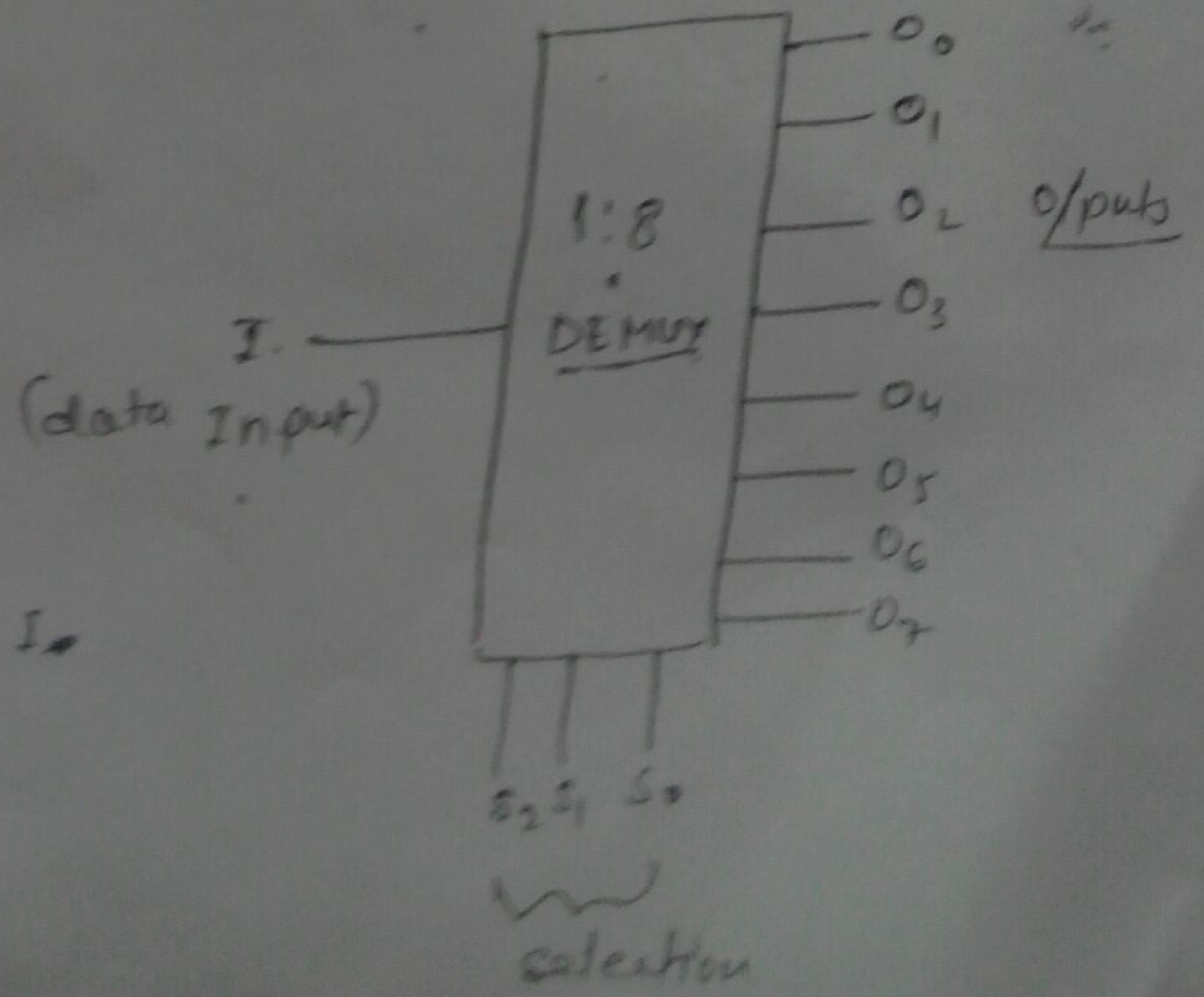
1-8 DEMUX

if $s_2 s_1 s_0 = 000$
the output available at $O_0 = I_0$




S_2	S_1	S_0	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	1	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

21

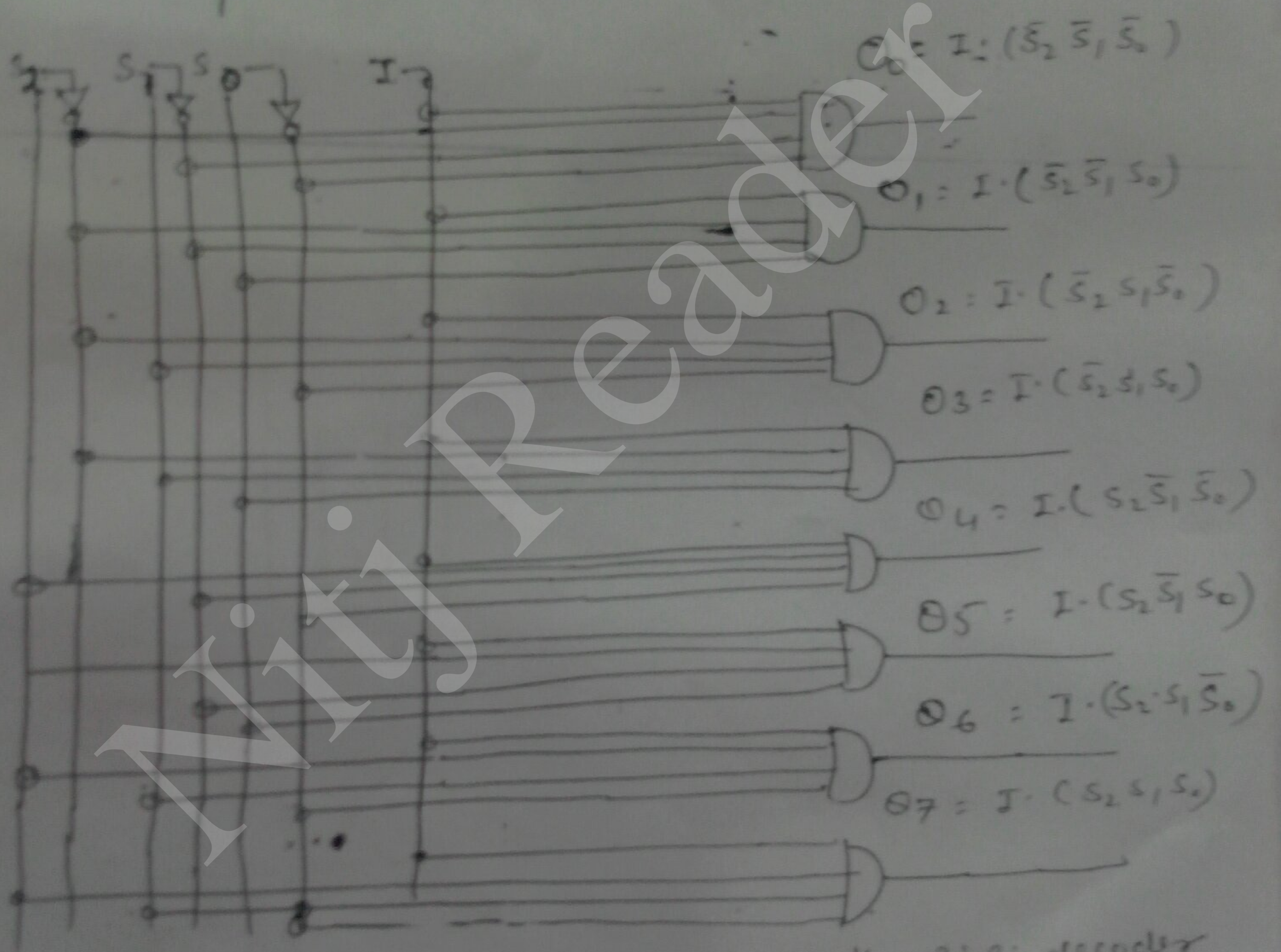


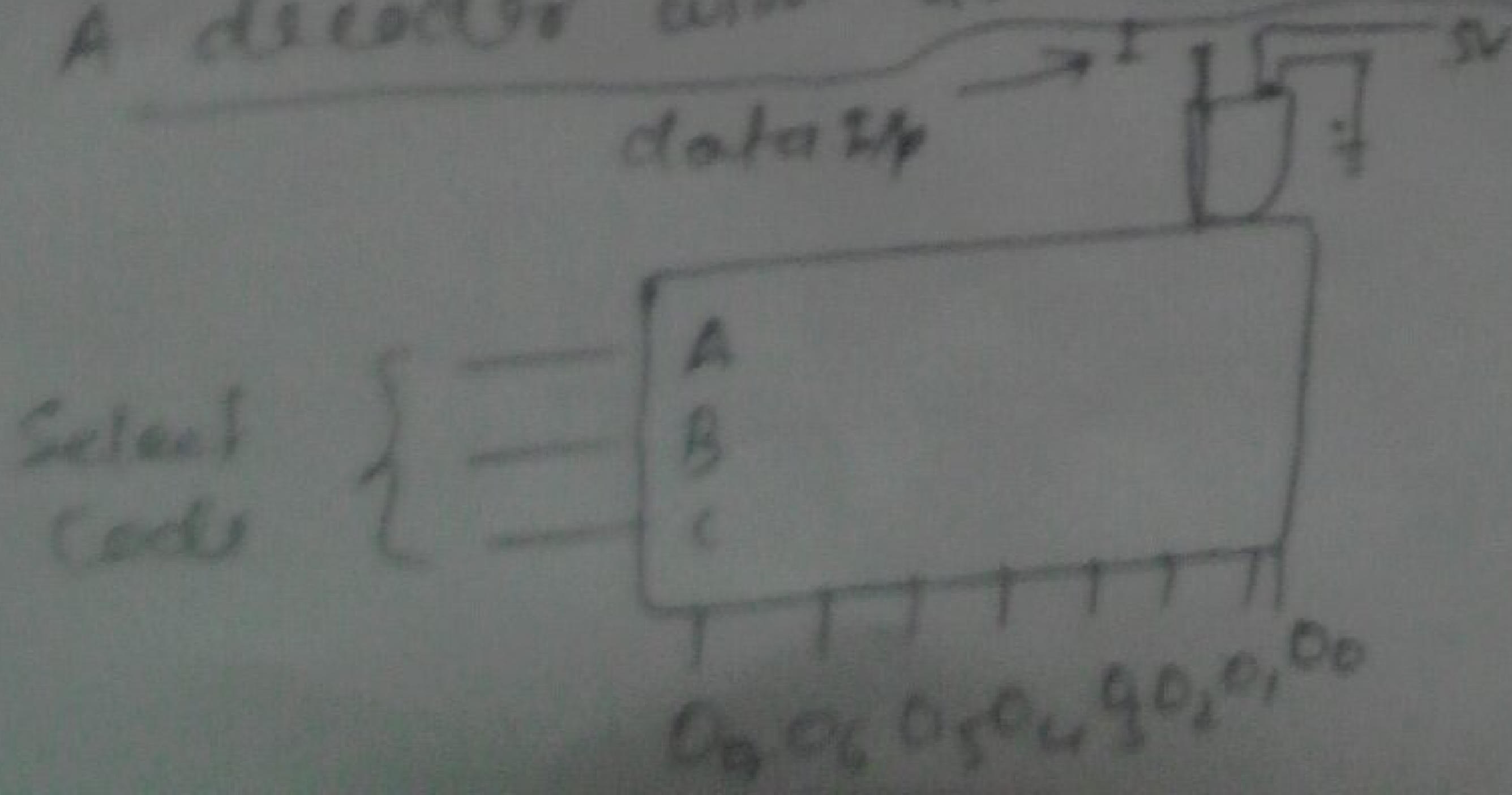The diagram shown above is very similar to the 3:8 decoder except that fourth input I has been added to each gate. i.e. A decoder with an extra (enable) input act as demultiplexer.




1:4 DEMUX

S_1	S_0	O_3	O_2	O_1	O_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

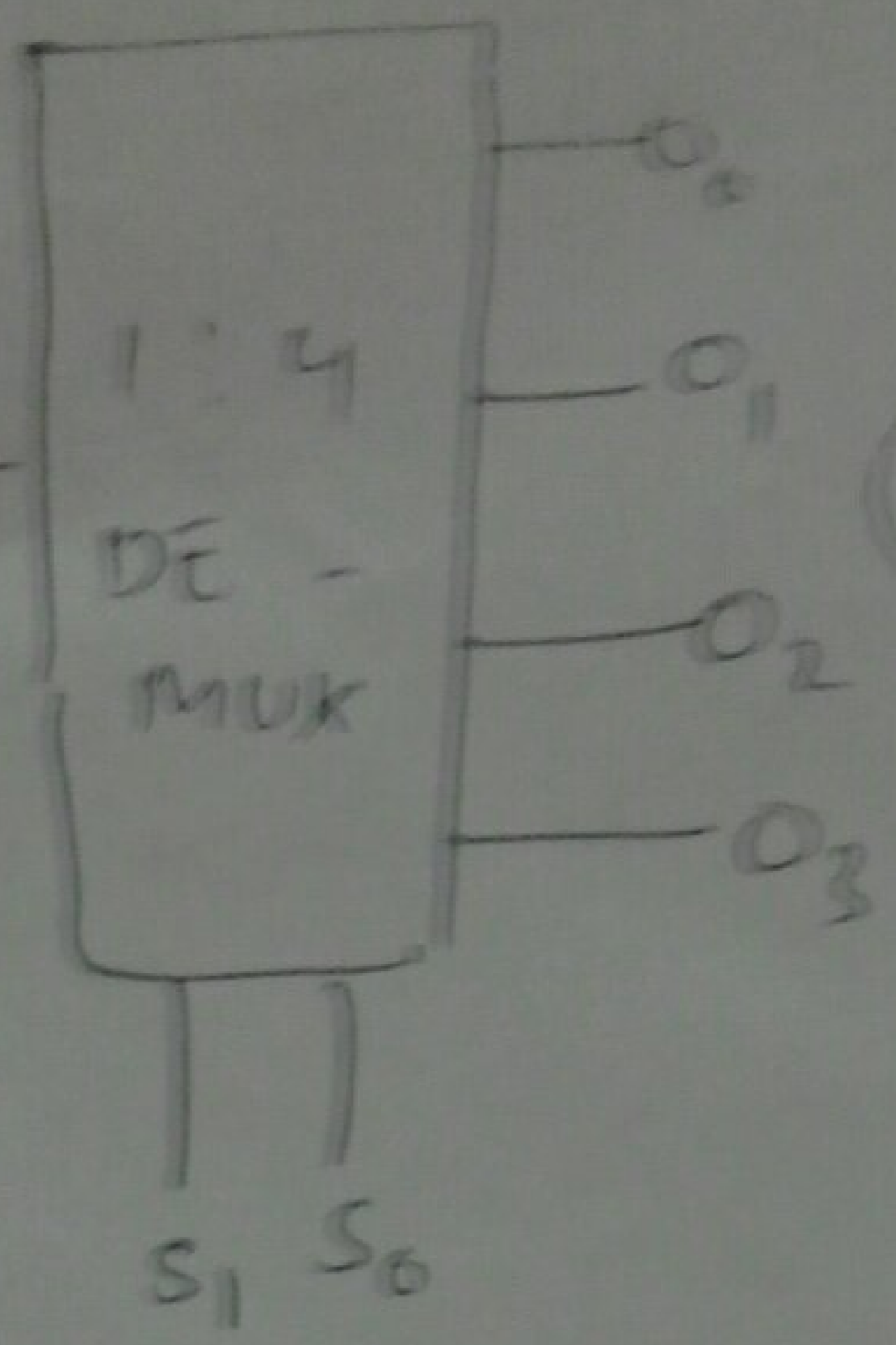



22

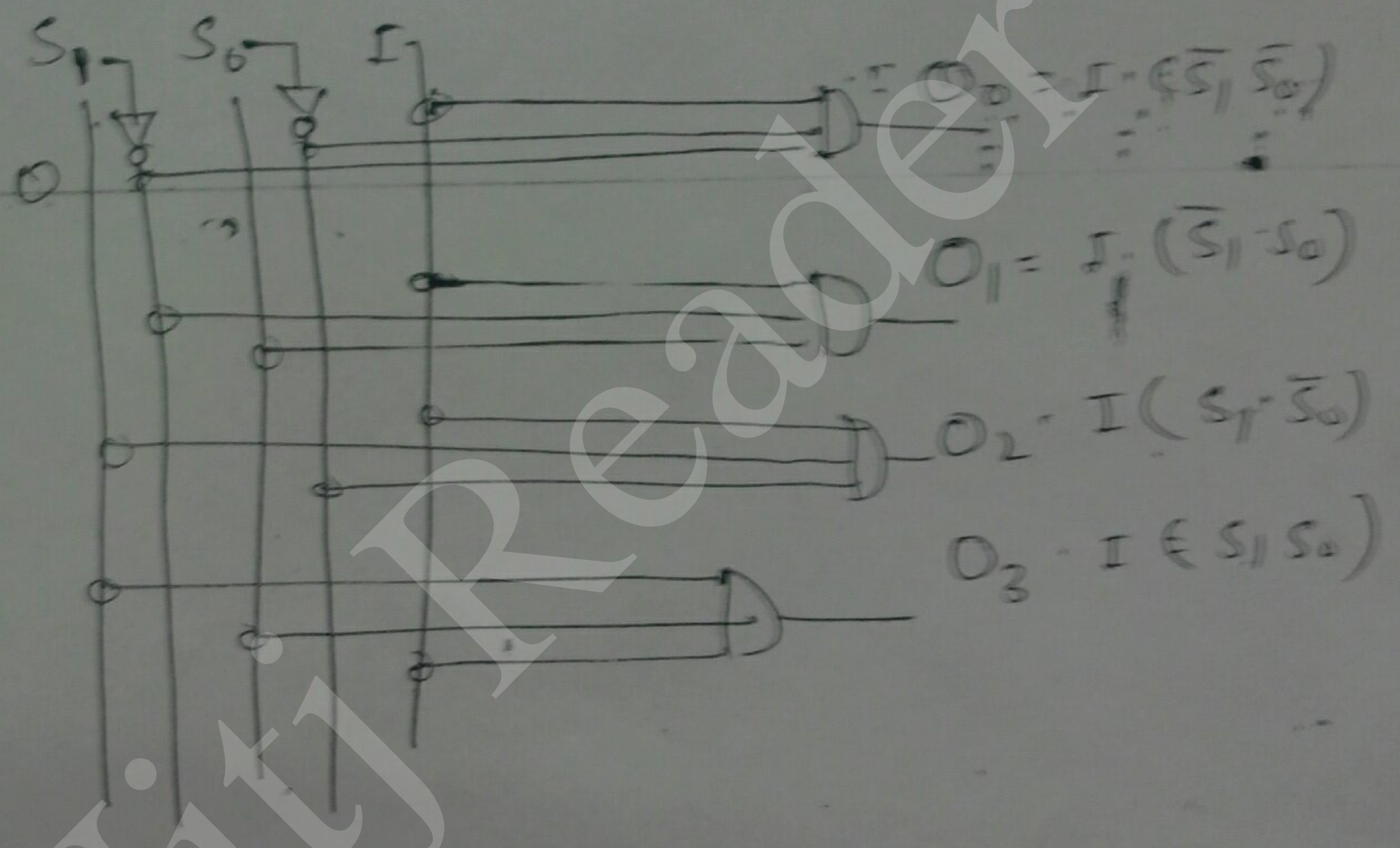

$O_0 = I \cdot (S_1 \cdot S_0)$
 $O_1 = I \cdot (S_1 \cdot \bar{S}_0)$
 $O_2 = I \cdot (\bar{S}_1 \cdot S_0)$
 $O_3 = I \cdot (\bar{S}_1 \cdot \bar{S}_0)$

1:2 DEMUX:

S	O_1	O_0
0	0	I
1	I	0

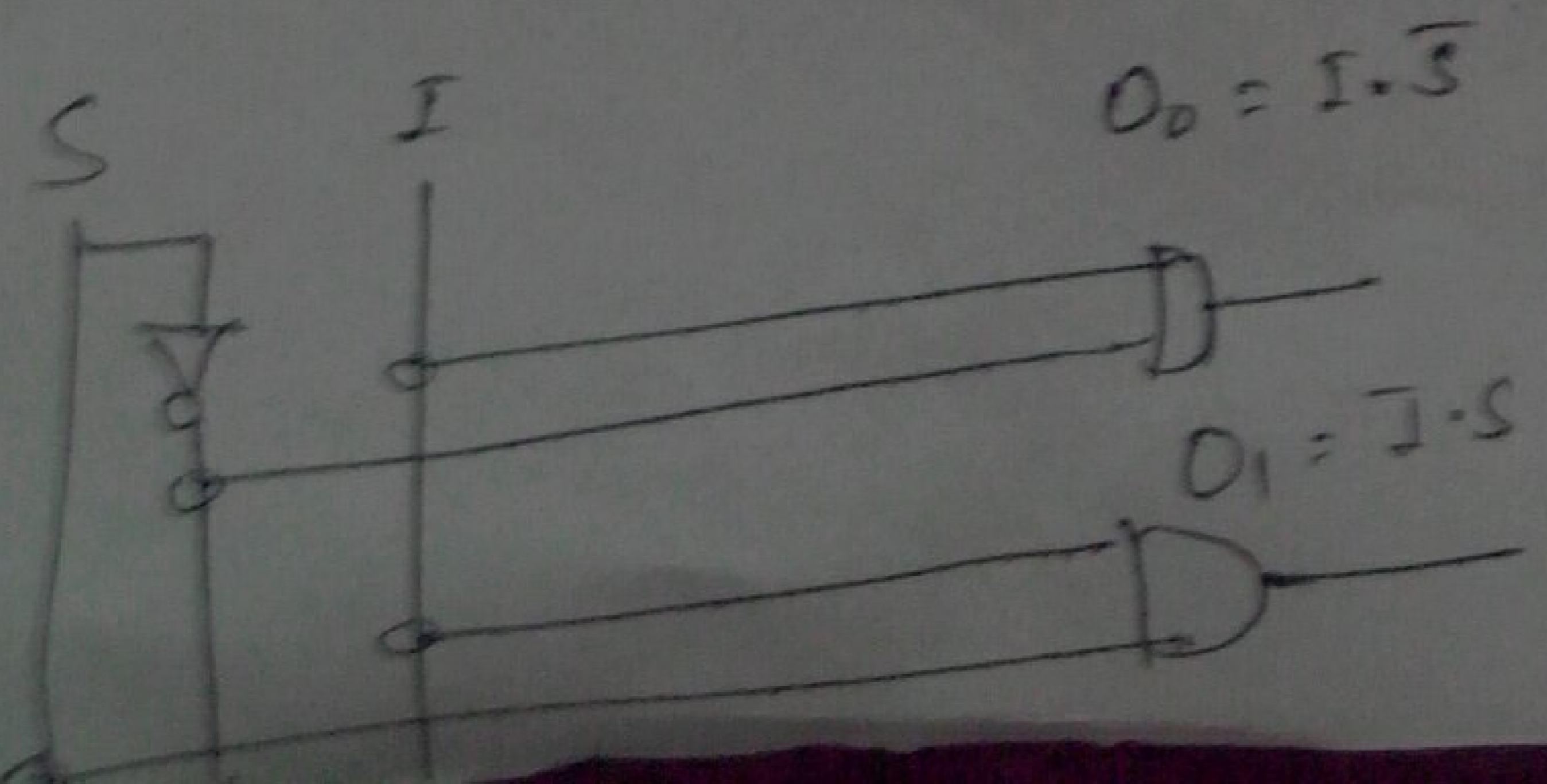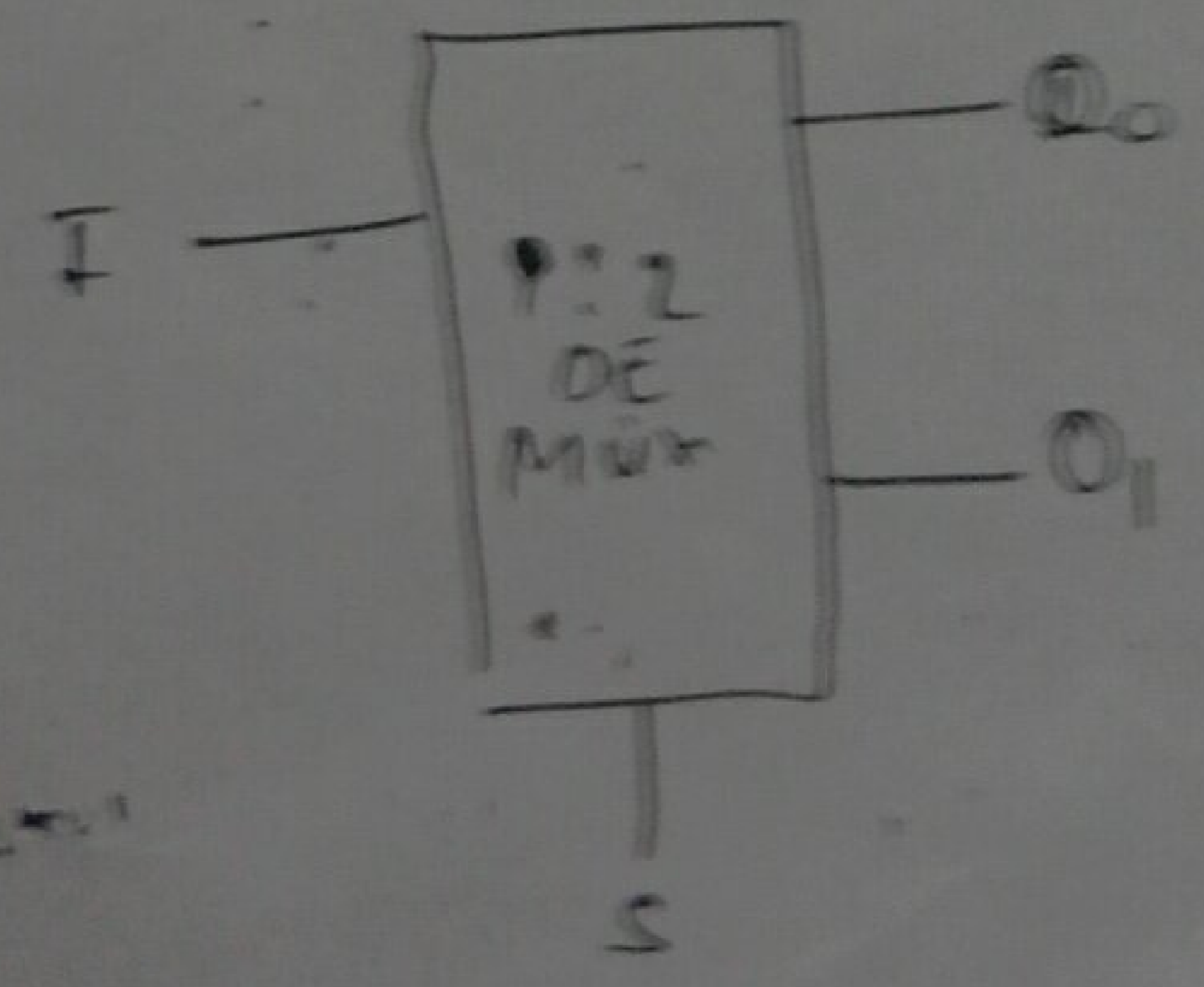

$O_0 = I \cdot \bar{S}$
 $O_1 = I \cdot S$