

LAKSHYA JEE

LAKSHYA KO HAR HAAL ME PAANA HAI



Electric Potential & Capacitance

-Er. Rohit Gupta




Today's GOALS!

Capacitors



Series combination

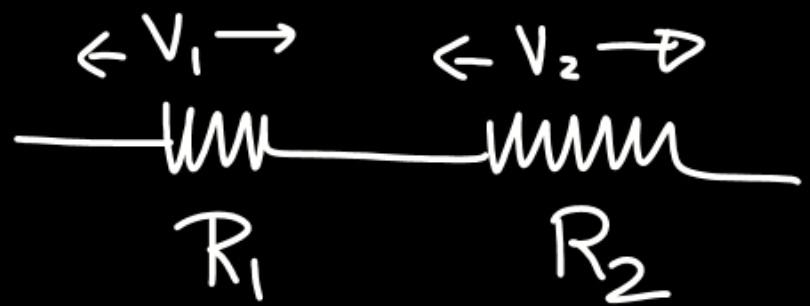


$$R_{eq} = R_1 + R_2$$

$$\frac{V_1}{V_2} = \frac{R_1}{R_2}$$

$$V_1 = \frac{R_1 V}{R_1 + R_2}$$

$$V_2 = \frac{R_2 V}{R_1 + R_2}$$

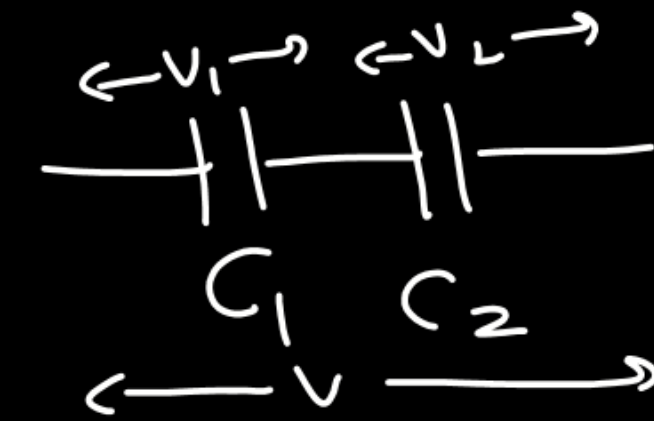

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$V_1 = \frac{C_2 V}{C_1 + C_2}$$

$$V_2 = \frac{C_1 V}{C_1 + C_2}$$


$$V = V_1 + V_2$$

$$\frac{V_1}{V_2} = \frac{C_2}{C_1}$$



Parallel combination

(Same potential drop.
Same terminals.)

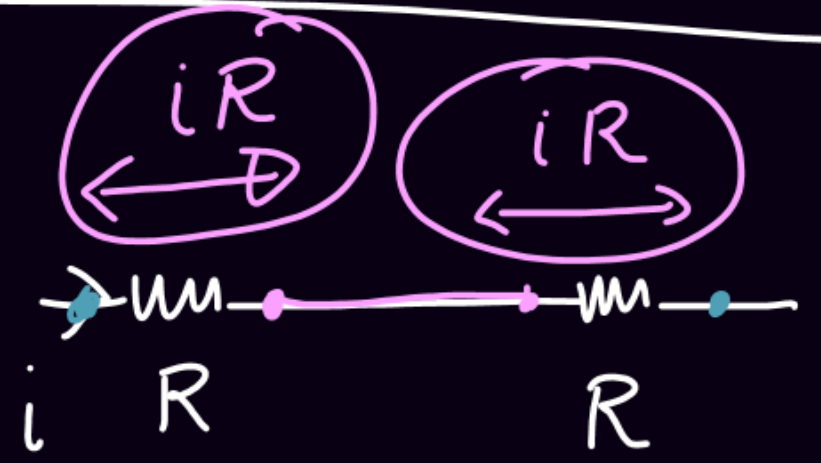

$$V = iR$$



$$i = i_1 + i_2$$

$$i = i_1 + i_2$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$i_1 = \frac{V}{R_1} ; i_2 = \frac{V}{R_2}$$

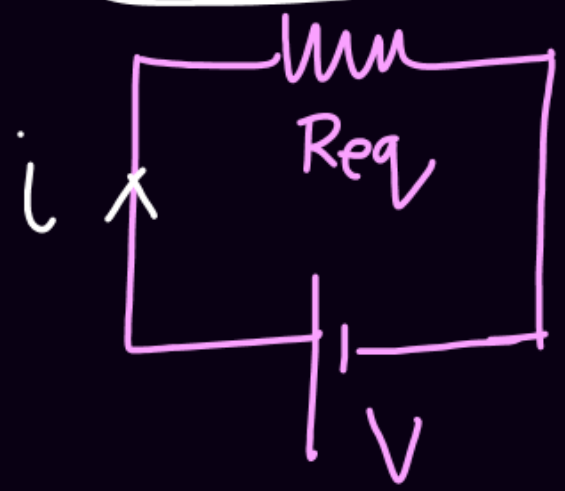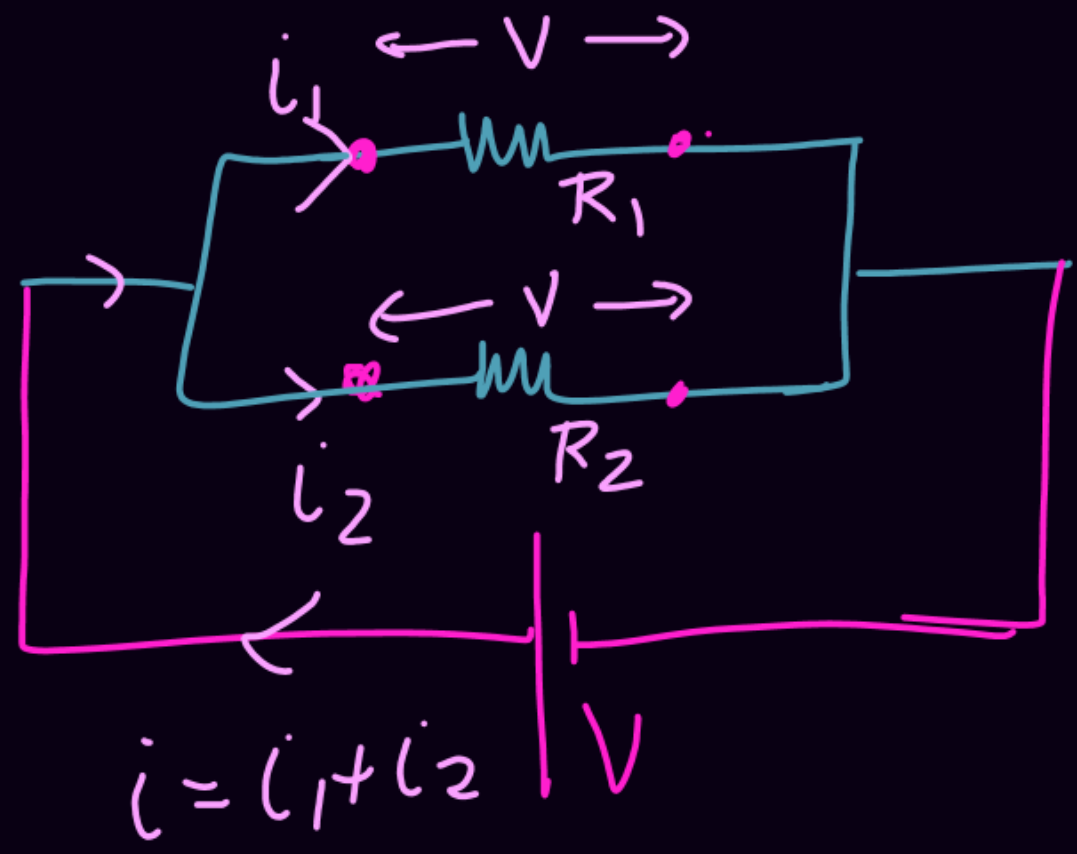
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$i = \frac{V}{R_{eq}}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

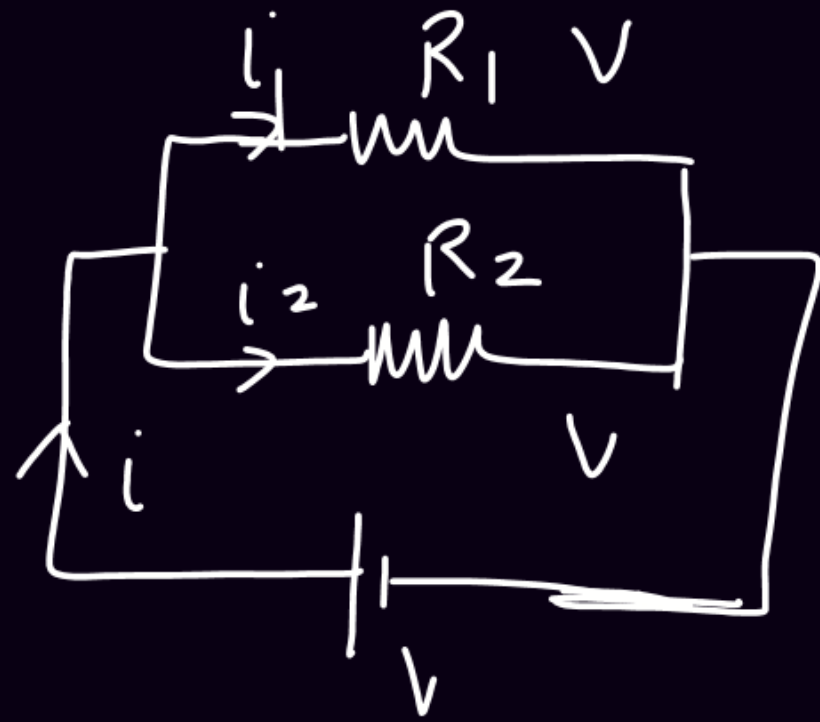Parallel combination divides current/charge



$$i_1 = \frac{V}{R_1}$$

$$i_2 = \frac{V}{R_2}$$

$$\frac{i_1}{i_2} = \frac{R_2}{R_1}$$

$$i \propto \frac{1}{R}$$

$$i = i_1 + i_2$$

$$i = i_2 \left(\frac{i_1}{i_2} + 1 \right)$$


$$i = i_2 \left(\frac{R_2}{R_1} + 1 \right)$$

$$i_2 = \frac{R_1 i}{R_1 + R_2}$$

$$i_1 = \frac{R_2 i}{R_1 + R_2}$$

*


Parallel combination of Capacitors

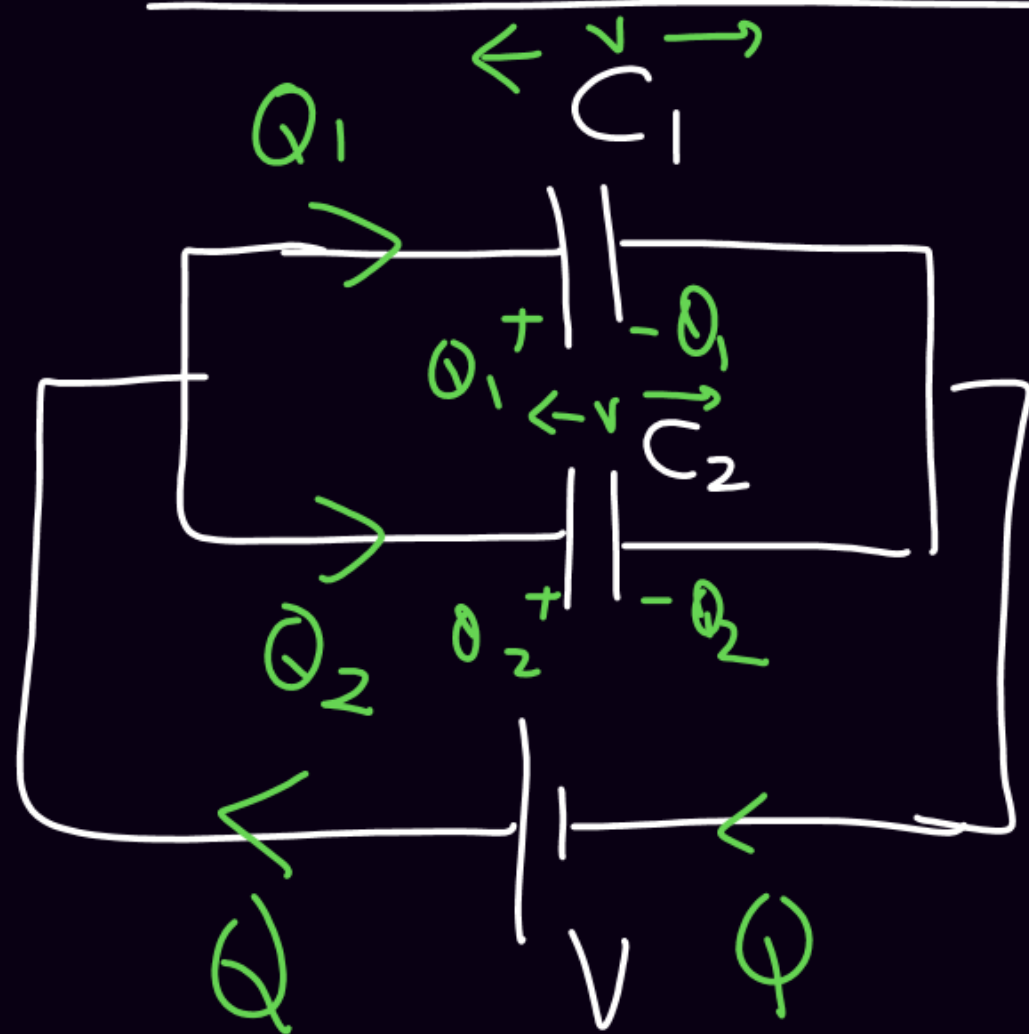

$$Q = CV$$

$$Q_1 = C_1 V$$

$$Q_2 = C_2 V$$

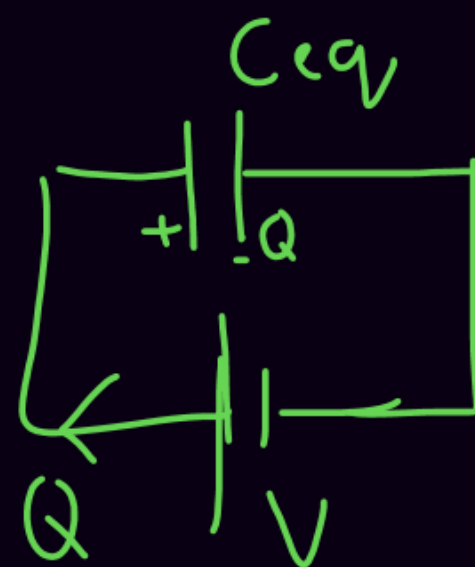


$$Q = C_{eq} V$$

$$Q = Q_1 + Q_2$$
$$C_{eq} V = C_1 V + C_2 V$$

$$C_{eq} = C_1 + C_2$$

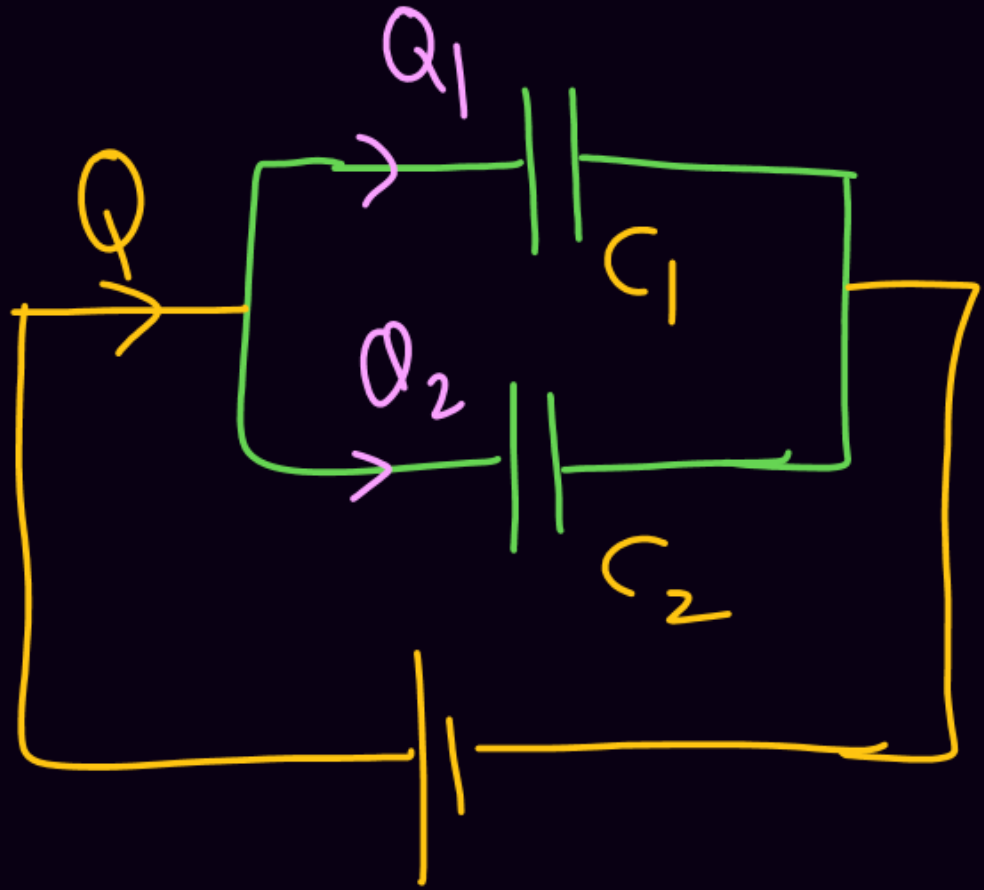Parallel combination of capacitor divides the charge



$$Q_1 = C_1 V$$

$$Q_2 = C_2 V$$

$$\frac{Q_1}{Q_2} = \frac{C_1}{C_2}$$

$$Q = Q_1 + Q_2$$

$$Q = Q_2 \left(\frac{Q_1}{Q_2} + 1 \right)$$

$$\rightarrow Q = Q_2 \left(\frac{C_1}{C_2} + 1 \right)$$


$$Q_2 = \frac{C_2}{C_1 + C_2} Q$$



$$Q_1 = \frac{C_1}{C_1 + C_2} Q$$


Summary

Series

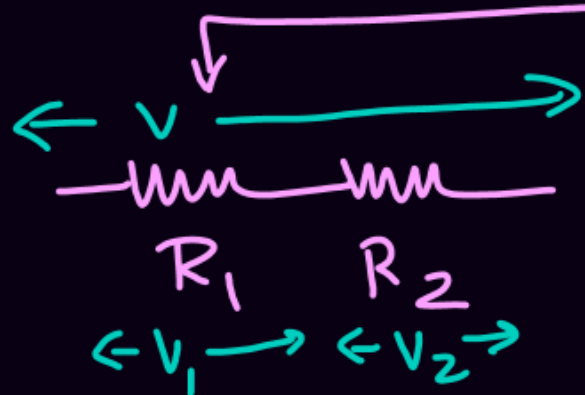

$$R_{eq} = R_1 + R_2$$


$$V_1 = \frac{R_1 V}{R_1 + R_2}$$

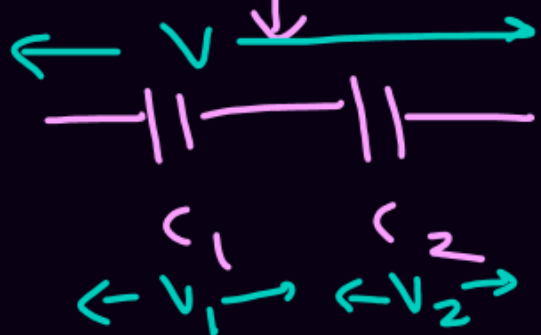

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$


$$V_1 = \frac{C_2 V}{C_1 + C_2}$$

Parallel

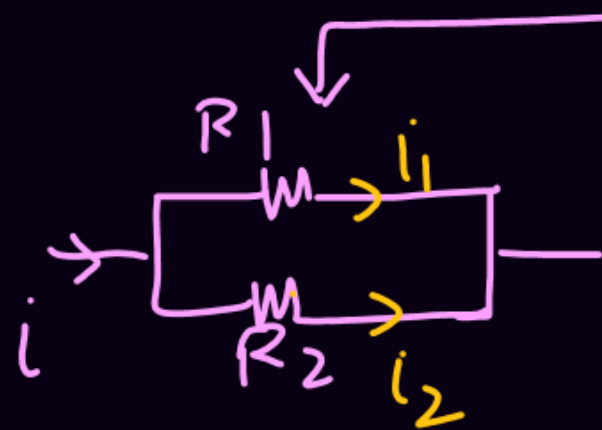

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$i_1 = \frac{R_2 i}{R_1 + R_2}$$

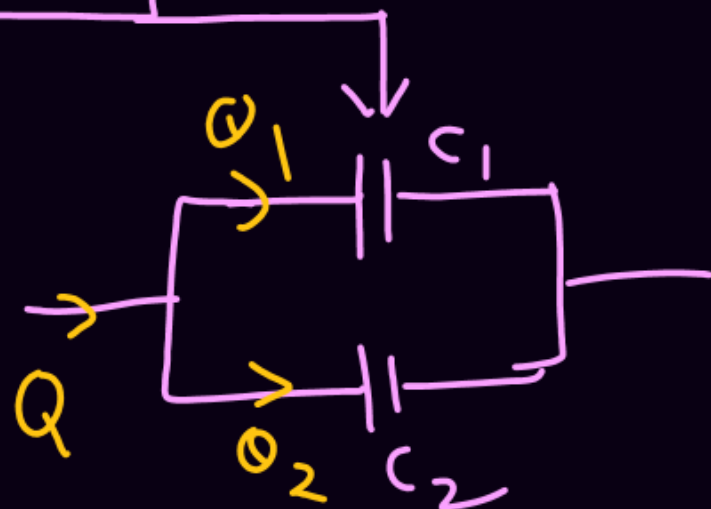

$$C_{eq} = C_1 + C_2$$


$$Q_1 = \frac{C_1 Q}{C_1 + C_2}$$

110

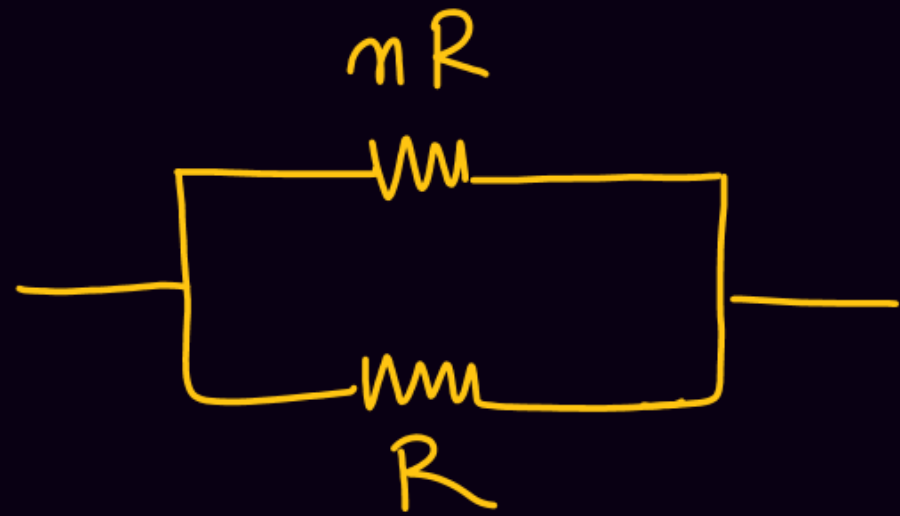


$$\text{Find } R_{eq} = \frac{nR \times R}{nR + R} = \frac{\underline{nR}}{\underline{n+1}} =$$
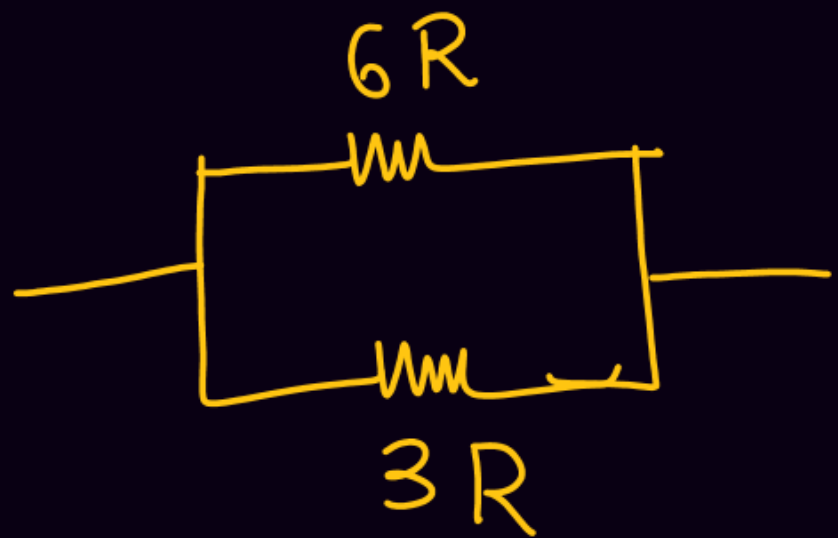
$$\frac{\text{Bade wala resistance}}{n+1}$$



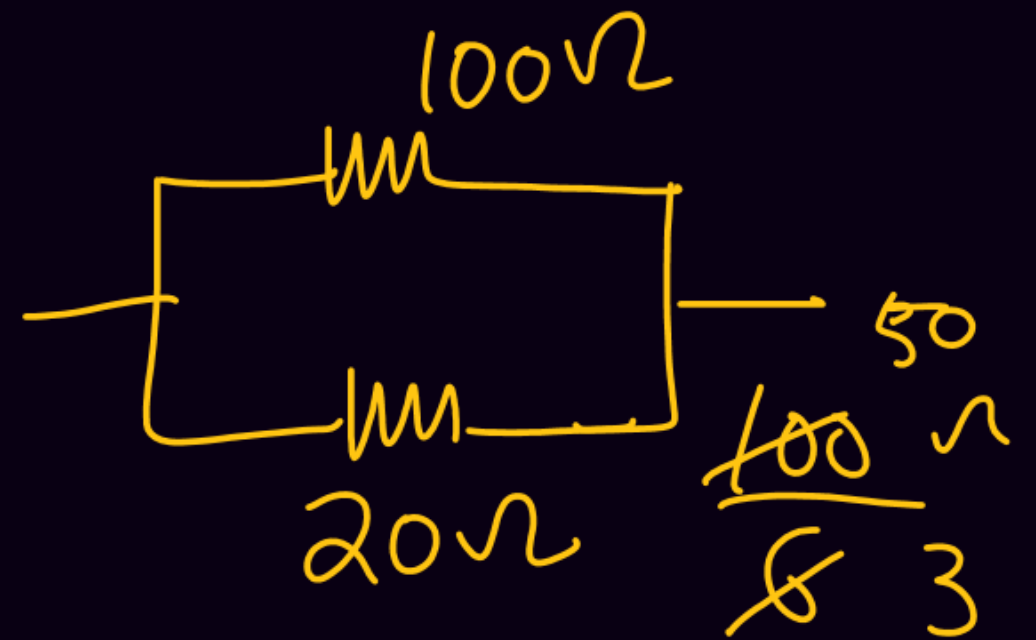
$$R_{eq} = \frac{6R}{3} = \underline{2R}$$






$$C_{eq} = ?$$

$$\frac{12}{3} = 4\ \mu\text{F}$$

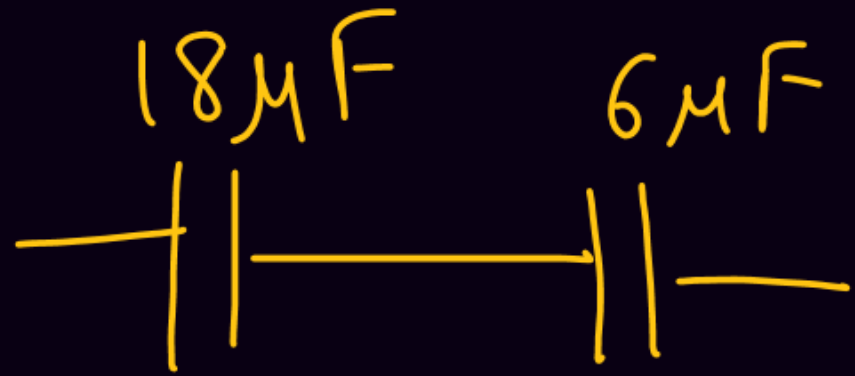

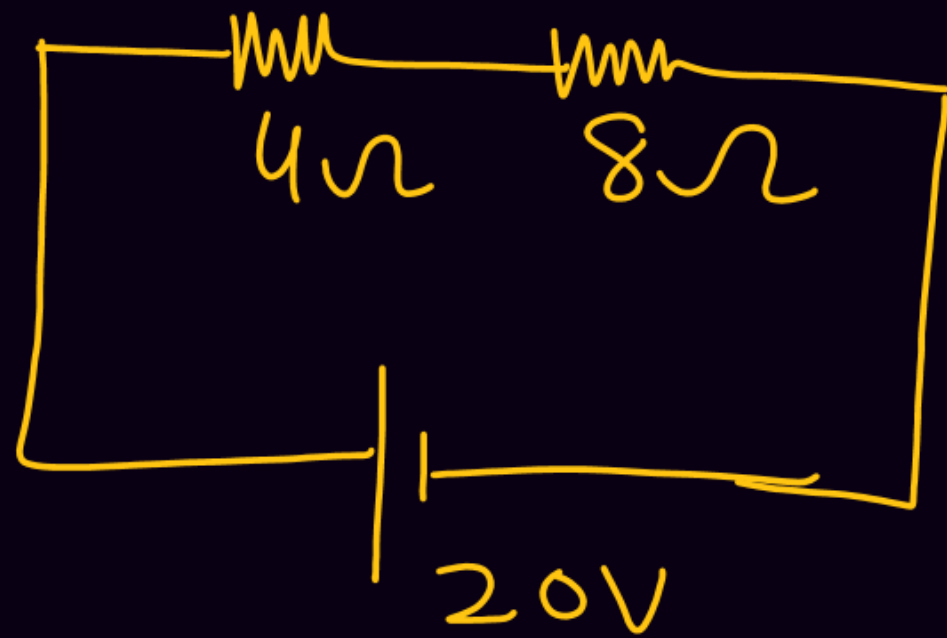
$$C_{eq} = \frac{18}{4} = \frac{9}{2} = 4.5\ \mu\text{F}$$



Find $V_4 = \frac{4 \times 20}{4 + 8} = \frac{4 \times 20}{12} = \frac{20}{3}$

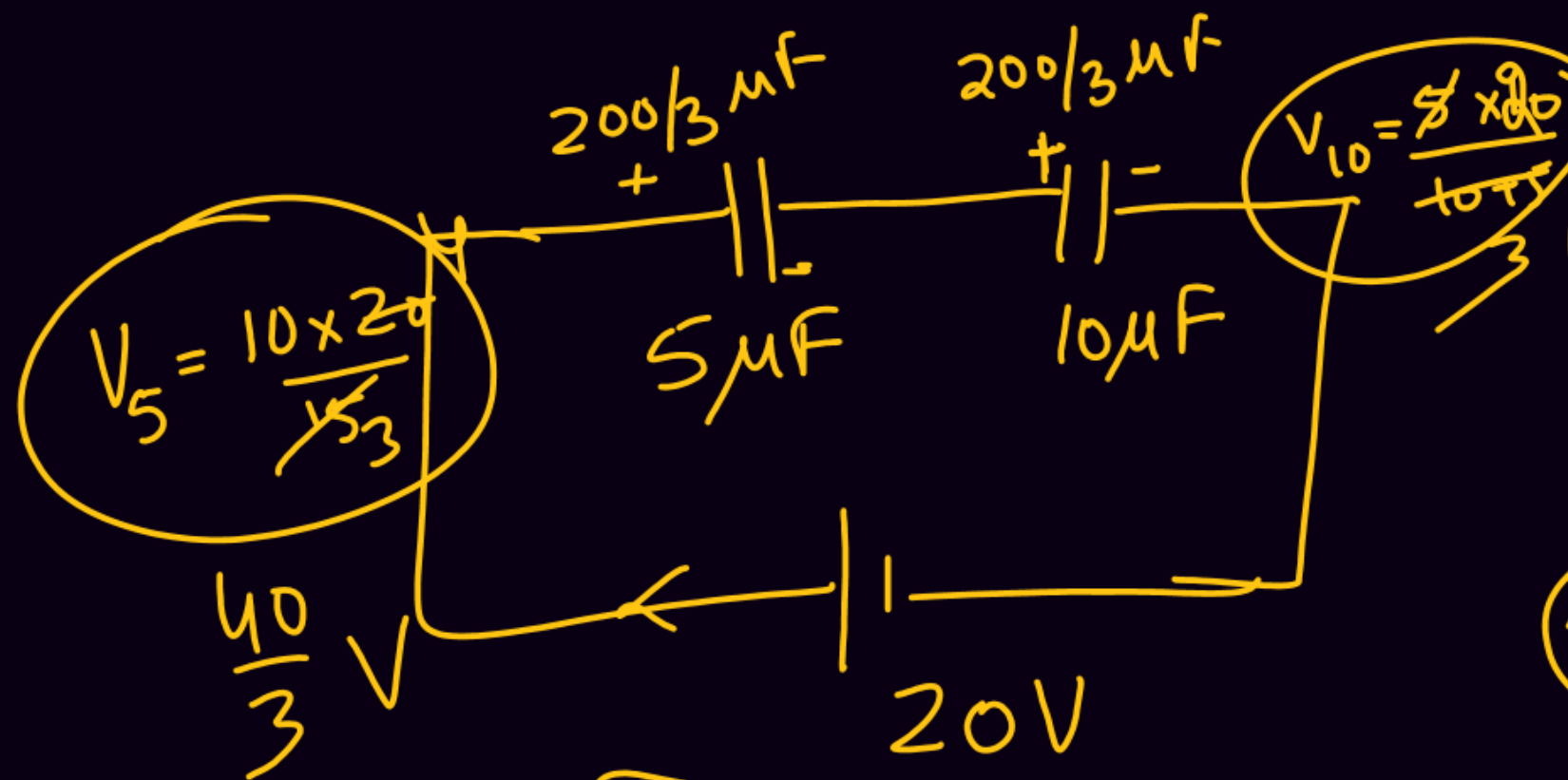$V_8 = \frac{8 \times 20}{4 + 8} = \frac{8 \times 20}{12} = \frac{40}{3}$



- ① Find charge on both the capacitors.
- ② find potential drop on both

$$C_{eq} = \frac{10}{3} \mu F$$

$$Q = C_{eq} V$$

$$= \frac{10}{3} \mu F \times 20V$$


$$= \frac{200}{3} \mu C$$

the capacitors.

For boards

The given $5\mu F$ & $10\mu F$ capacitors are in series.

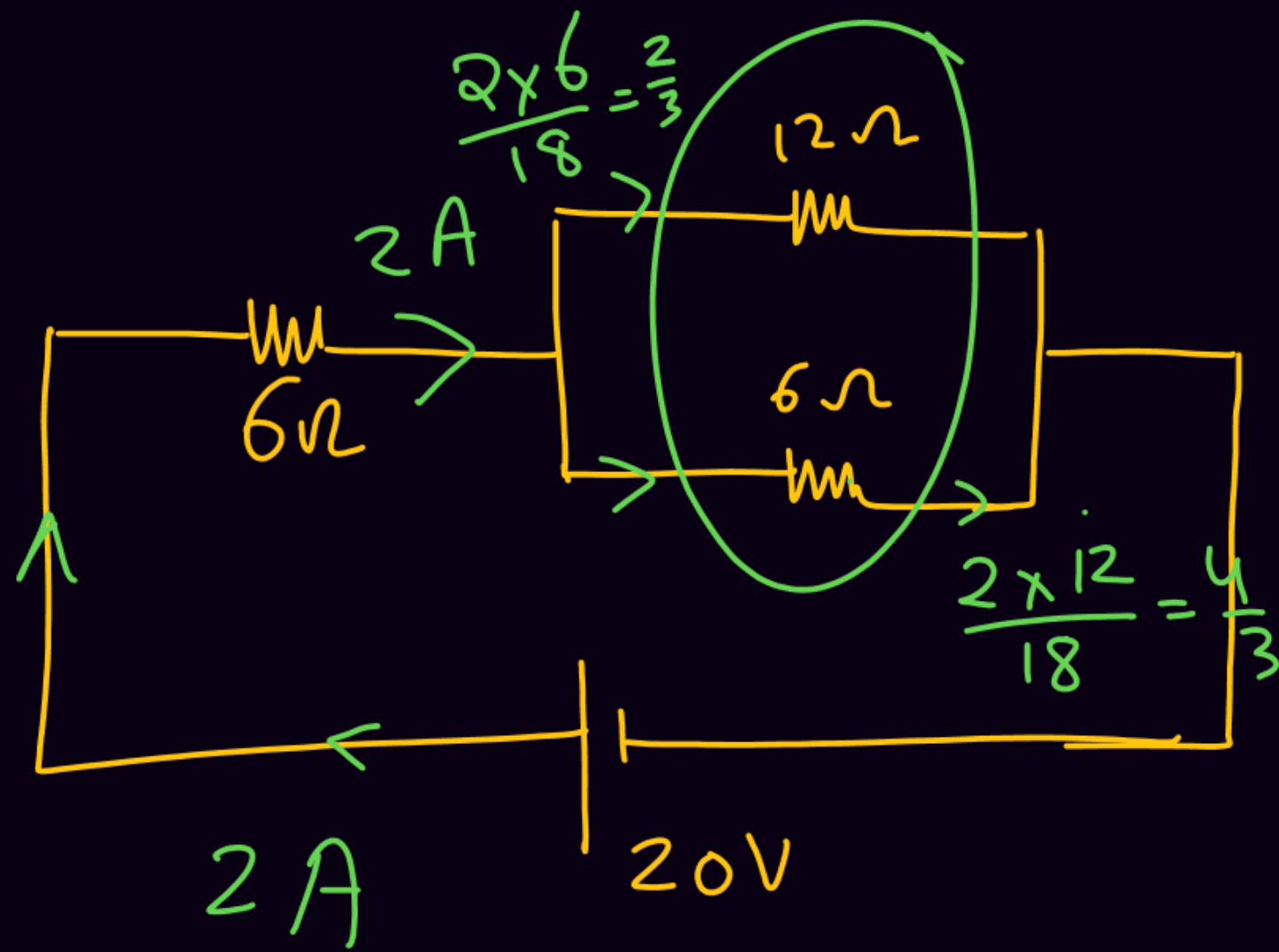We know that for series combination of capacitors $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \frac{1}{C_{eq}} = \frac{1}{5\mu F} + \frac{1}{10\mu F}$



find i in all the branches

$$R_{eq} = 10\Omega$$


$$i = \frac{20}{10} = 2A$$

Dielectrics (Insulators)

Polar



$$P_{net} = 0.$$

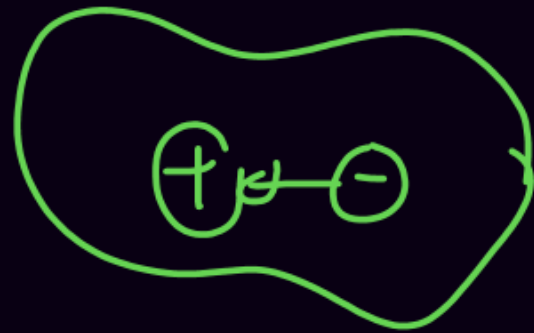


Non Polar





No dipoles

Polar

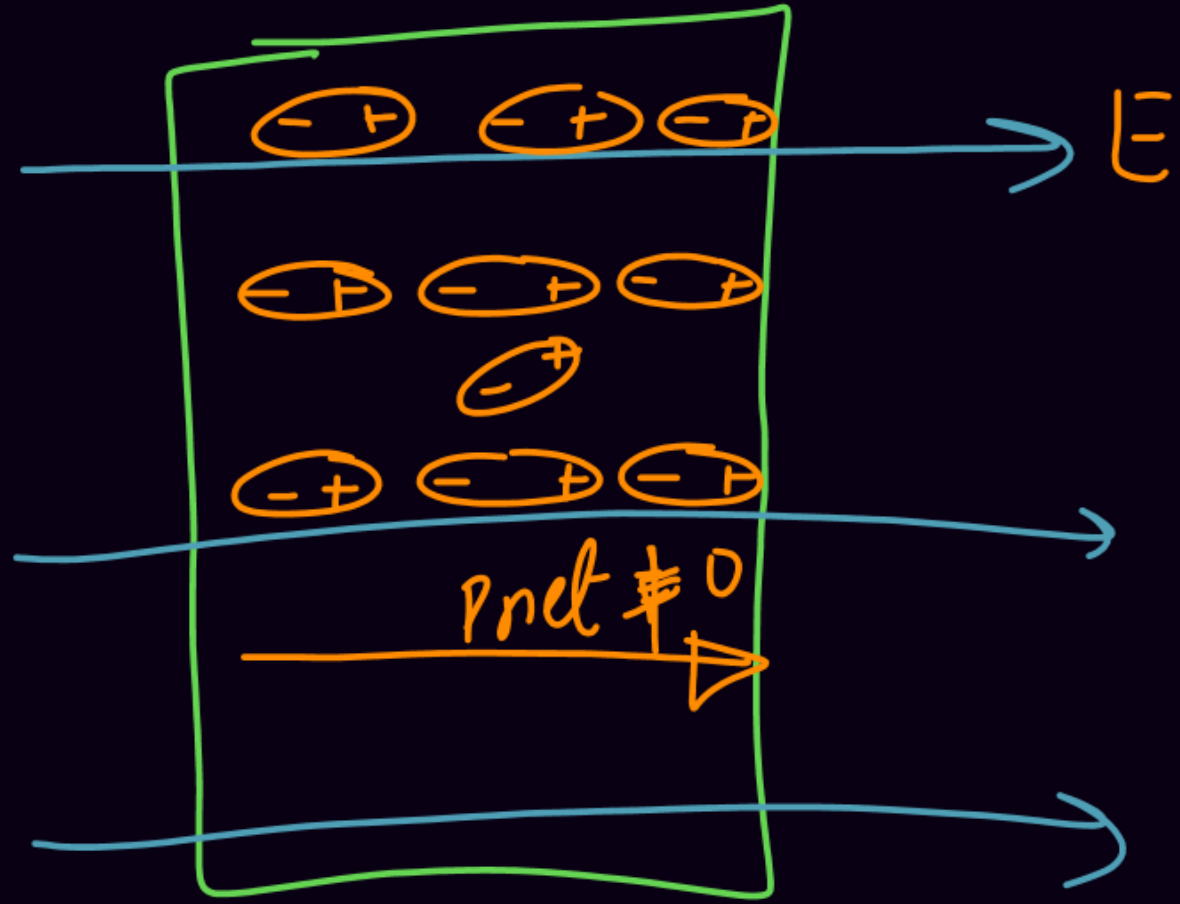


Non Polar

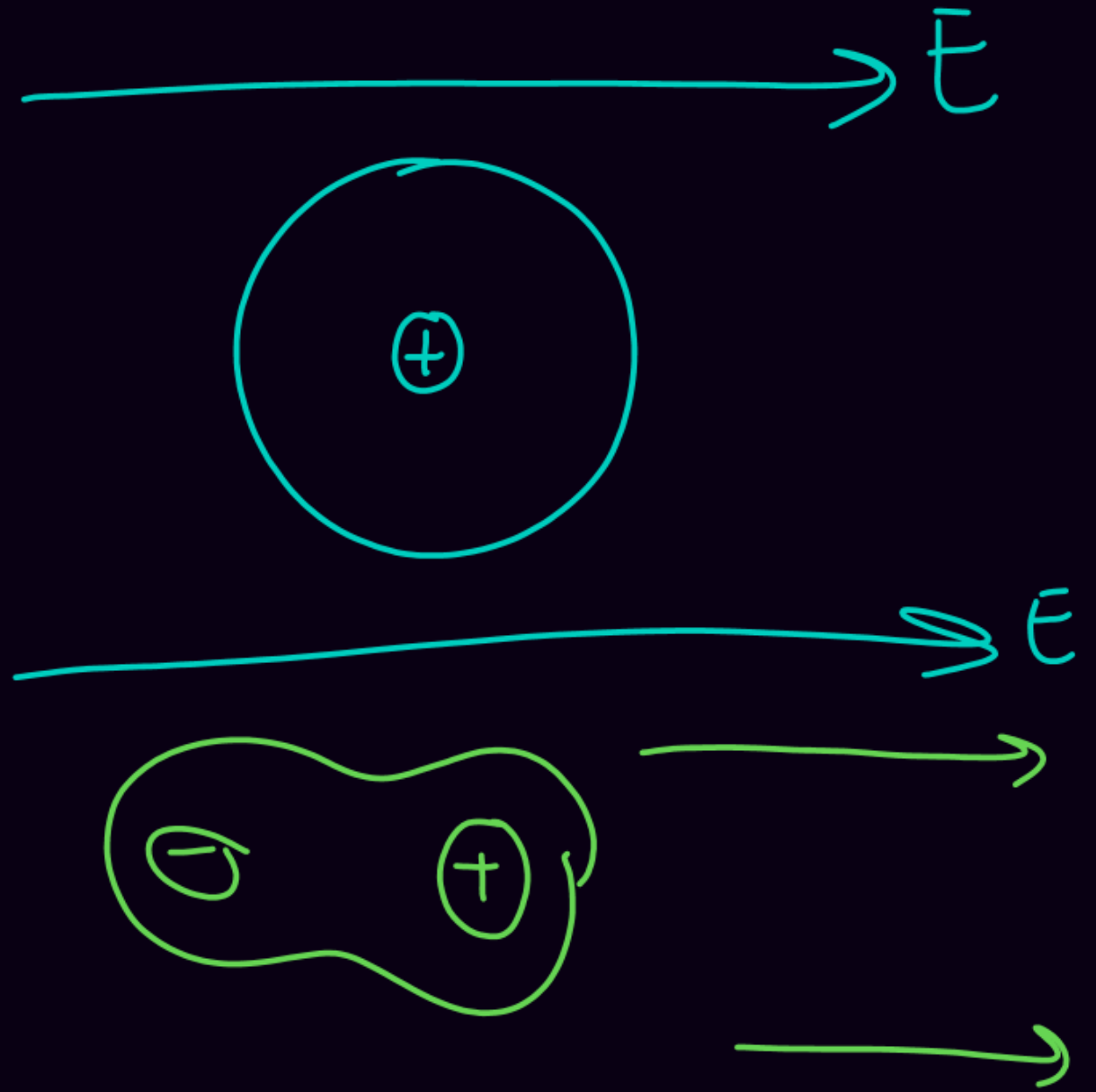

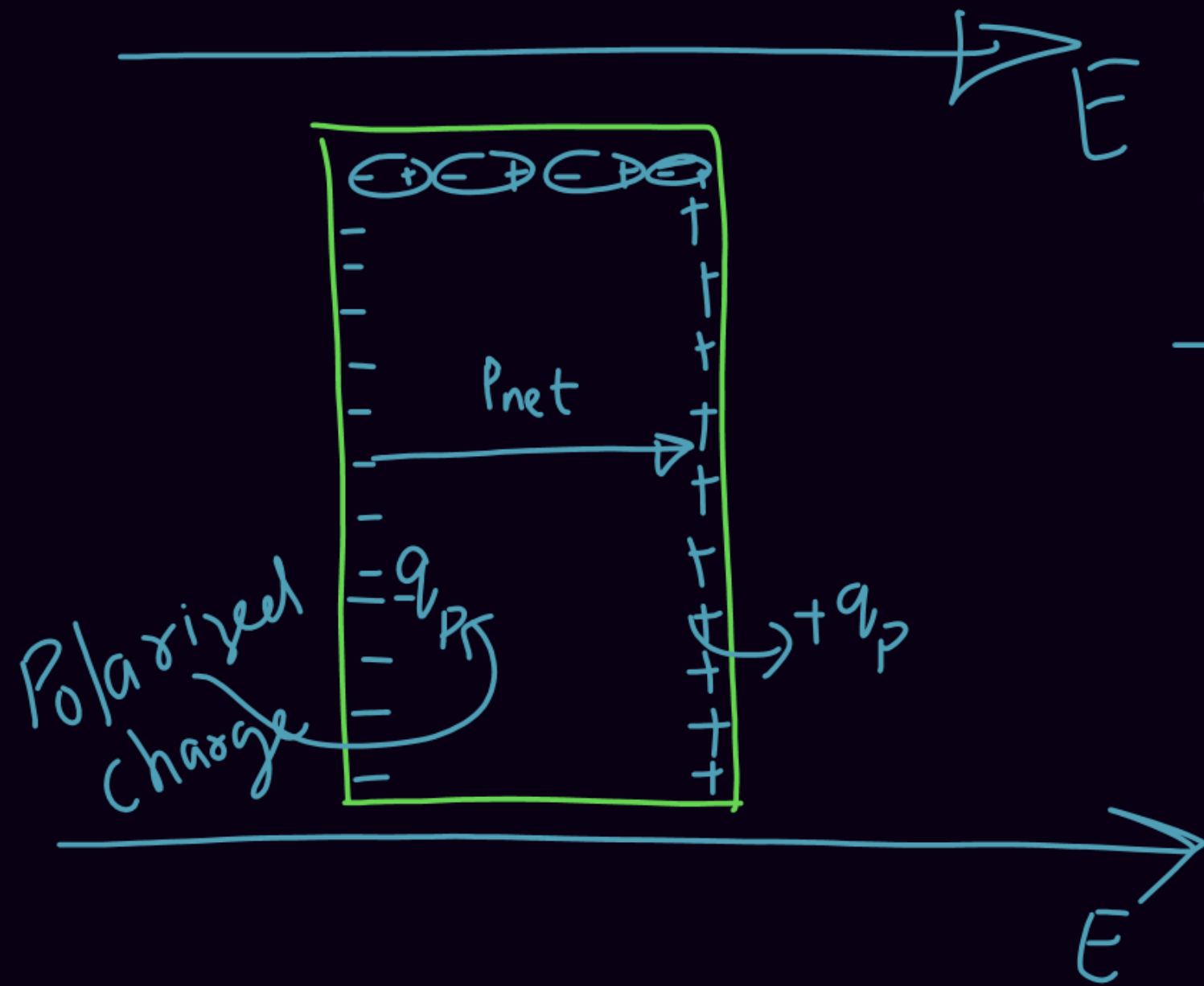

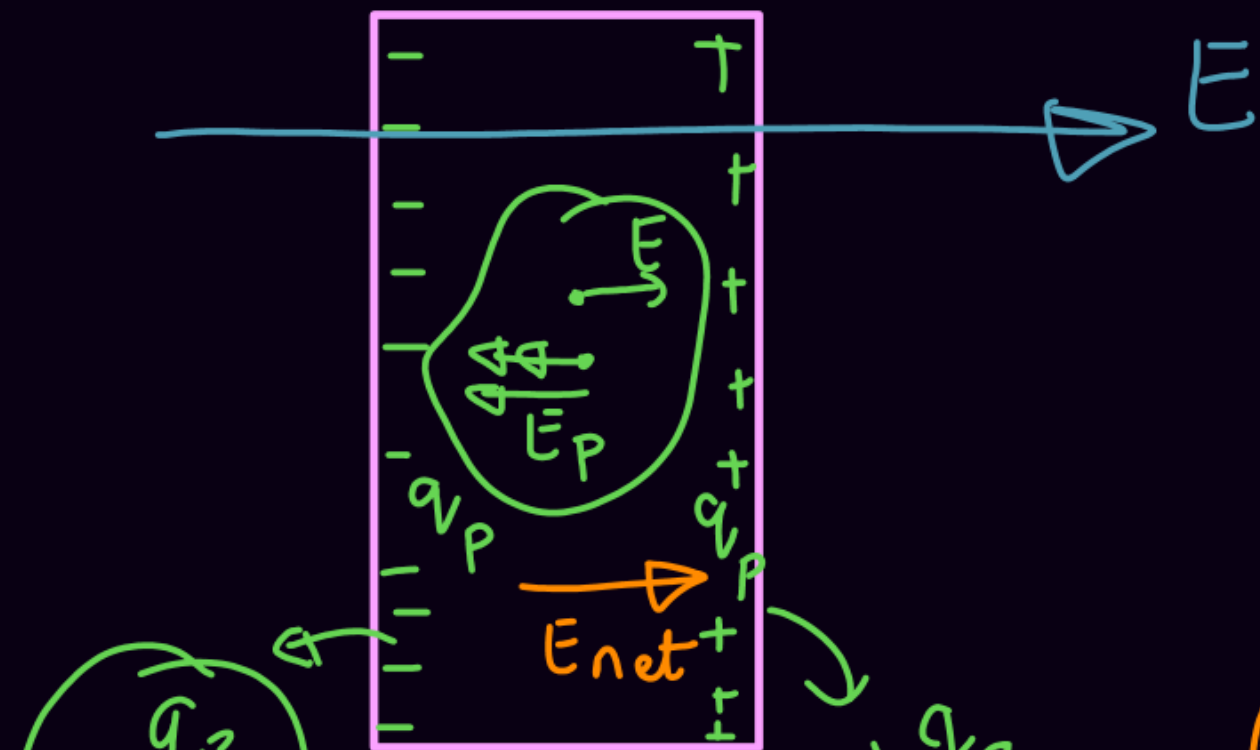Polarization :- Generation of net dipole moment in a dielectric in the presence of external field is called polarization.



dielectric k ander polarization ki wajah se jo electric field aa raha h wo ext. field ka ulta hai.

$$E_{net} = E - E_p.$$


$$E_{net} < E$$

$$E_p = \frac{q \sigma}{\epsilon_0} = \frac{q_p}{A \epsilon_0}$$

Dielectric apne ander field ko \overline{ant} karne ki

koshish kar rha hai.

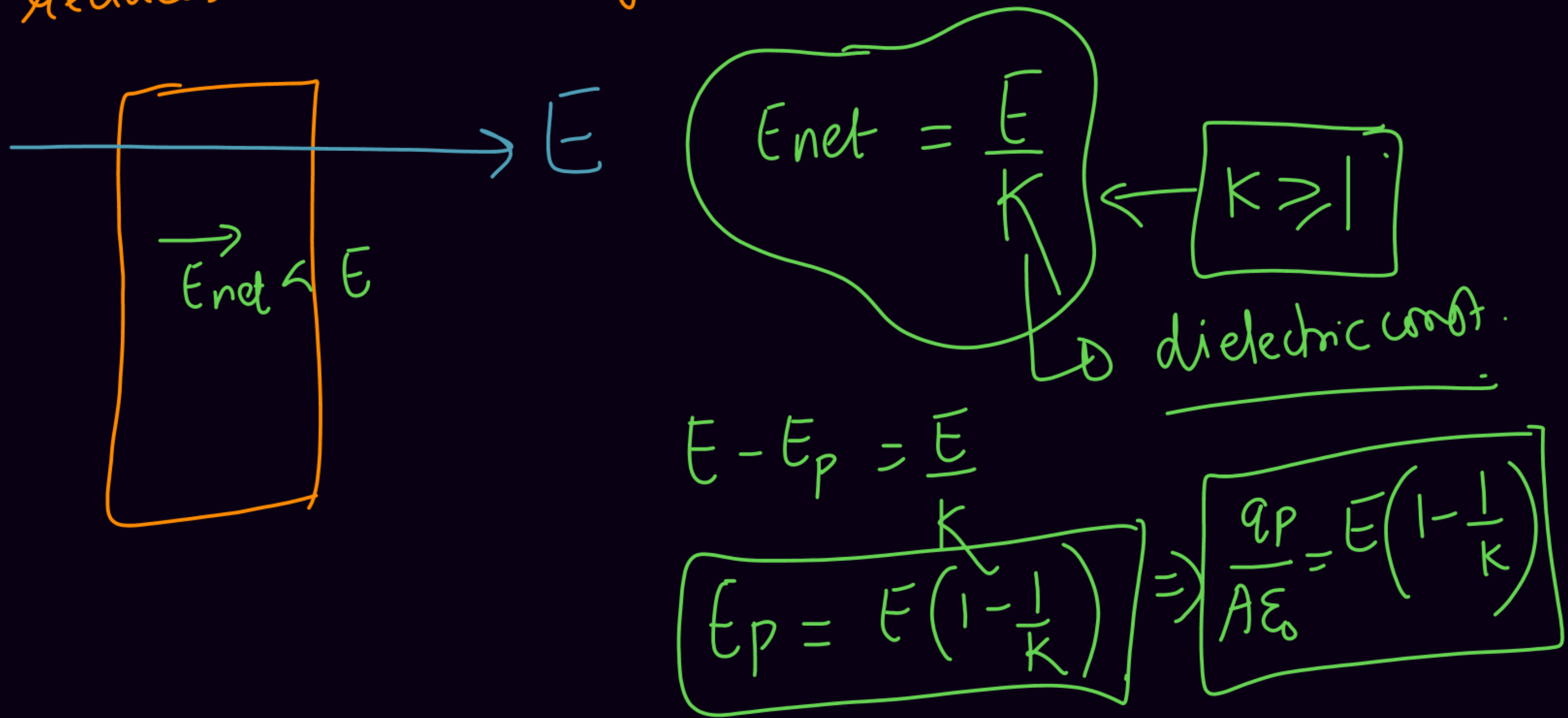Dielectric constant is the factor by which a dielectric reduces the electric field inside it.





Thank You Lakshyians