

LAKSHYA JEE

LAKSHYA KO HAR HAAL ME PAANA HAI



Electric Potential & Capacitance


-Er. Rohit Gupta




Today's GOALS!

Capacitors
&
Dielectrics



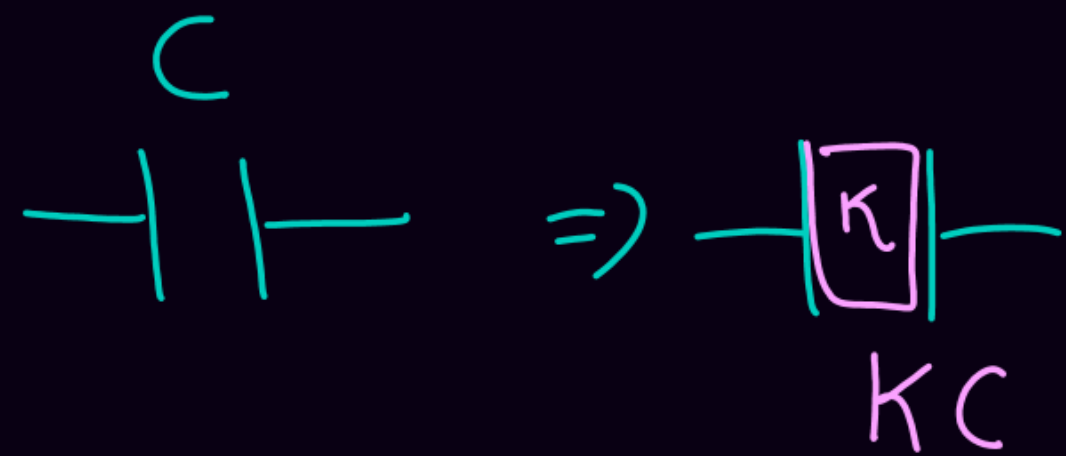

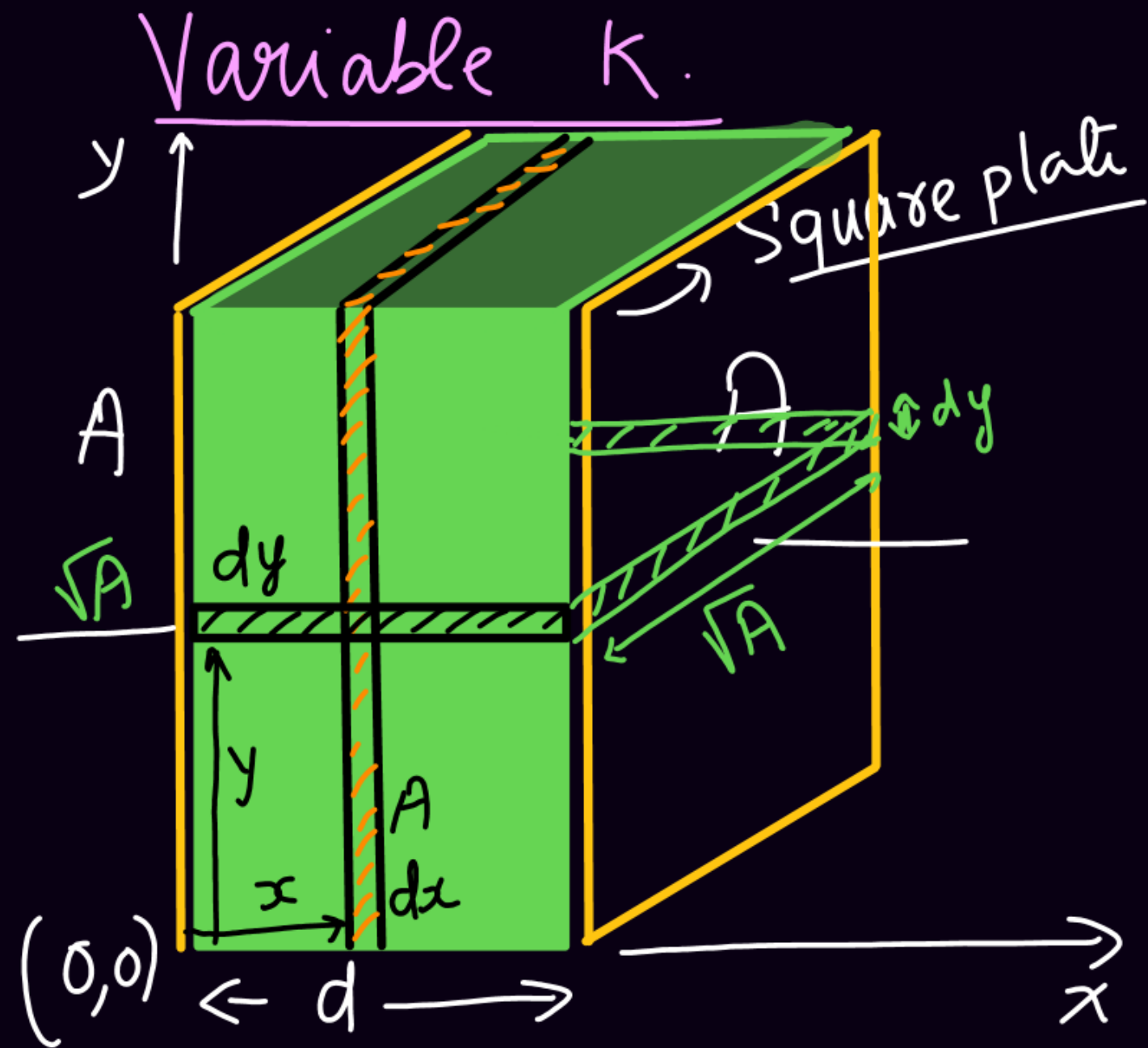

① $K = K_0 + K_1 x$
find C (Series)

② $K = K_0 + K_1 y$
find C . (Parallel)

① $dC = (K_0 + k_1 x) \frac{\epsilon_0 A}{dx}$

$$\frac{1}{C_{eq}} = \frac{1}{dC_1} + \frac{1}{dC_2} + \frac{1}{dC_3} + \dots$$

$$\frac{1}{C_{eq}} = \int \frac{1}{dC} = \int_0^d \frac{dx}{\epsilon_0 A (K_0 + k_1 x)}$$

$$\frac{1}{C_{eq}} = \int \frac{1}{dC} = \int_0^d \frac{dx}{(k_0 + k_1 x) \epsilon_0 A}$$

$$= \frac{1}{\epsilon_0 A} \frac{\ln(k_0 + k_1 x)}{k_1} \Big|_0^d$$

$$= \frac{1}{k_1 \epsilon_0 A} \left[\ln(k_0 + k_1 d) - \ln(k_0 + k_1 \cdot 0) \right]$$


$$\frac{1}{C_{eq}} = \frac{1}{k_1 \epsilon_0 A} \left(\ln \left(\frac{k_0 + k_1 d}{k_0} \right) \right)$$

$$C_{eq} = \frac{k_1 \epsilon_0 A}{\ln \left(\frac{k_0 + k_1 d}{k_0} \right)}$$

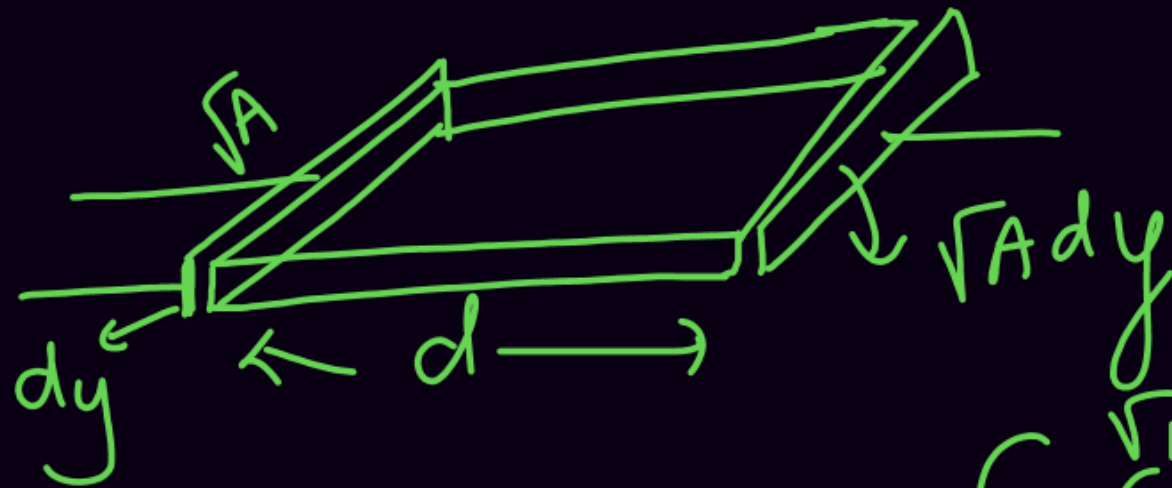(2)

$$dC = (K_0 + K_1 y) \frac{\epsilon_0 (\sqrt{A} dy)}{d}$$

$$\frac{\epsilon_0 A}{d} \left[K_0 + \frac{K_1 \sqrt{A}}{2} \right]$$




$$C_{eq} = \int dC = \int_0^{\sqrt{A}} (K_0 + K_1 y) \left(\frac{\epsilon_0 \sqrt{A}}{d} \right) dy$$

$$= \frac{\epsilon_0 \sqrt{A}}{d} \left[\int_0^{\sqrt{A}} K_0 dy + \int_0^{\sqrt{A}} K_1 y dy \right]$$

$$= \frac{\epsilon_0 \sqrt{A}}{d} \left[K_0 y \Big|_0^{\sqrt{A}} + \frac{K_1 y^2}{2} \Big|_0^{\sqrt{A}} \right]$$

$$= \frac{\epsilon_0 \sqrt{A}}{d} \left[K_0 \sqrt{A} + \frac{K_1 (\sqrt{A})^2}{2} \right]$$

Square plate

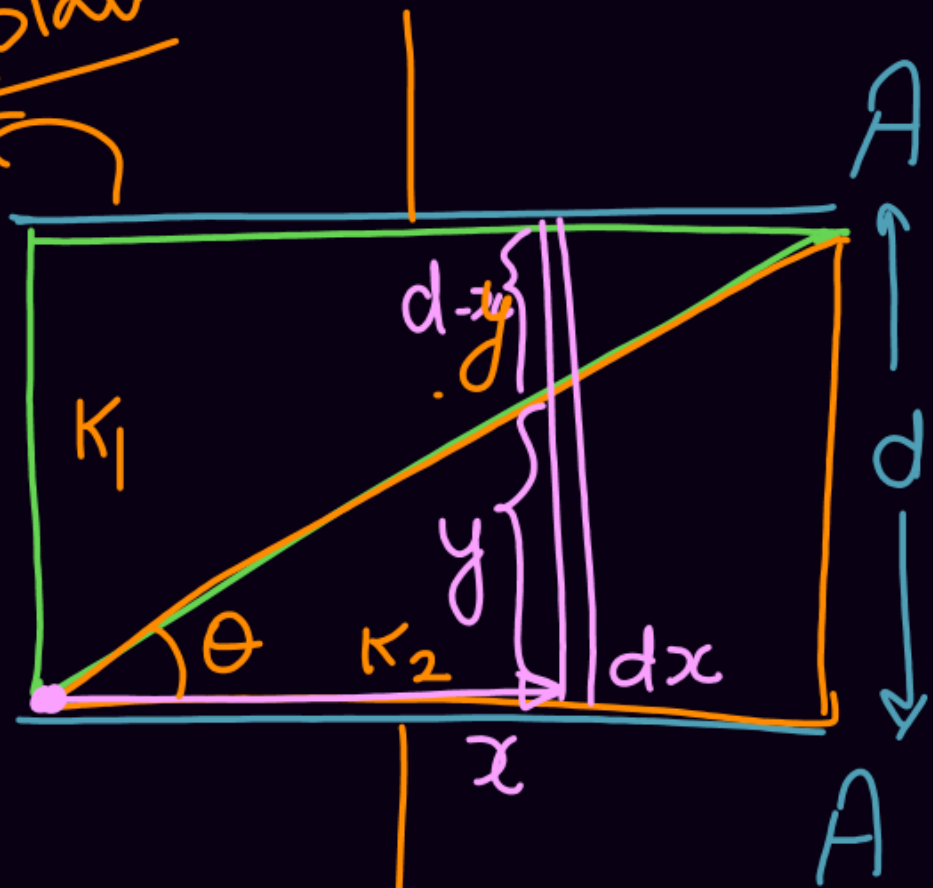


$$\tan \theta = \frac{y}{x} = \frac{d}{\sqrt{A}}$$

$$y = \frac{d}{\sqrt{A}} x$$

Find C?

$$dC_1 = \frac{\kappa_1 \epsilon_0 \sqrt{A} dx}{d-y}$$
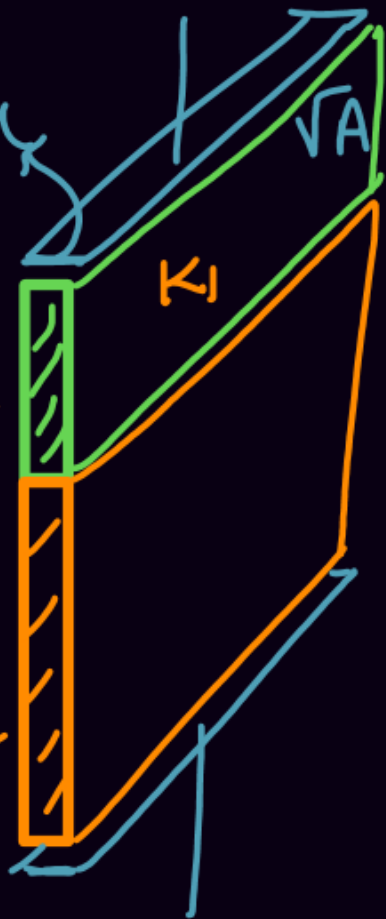
$$dC_2 = \frac{\kappa_2 \epsilon_0 \sqrt{A} dx}{y}$$



$$\frac{1}{dC} = \frac{1}{dC_1} + \frac{1}{dC_2} = \frac{d - \frac{d}{\sqrt{A}} x}{\kappa_1 \epsilon_0 \sqrt{A} dx} + \frac{\frac{d}{\sqrt{A}} x}{\kappa_2 \epsilon_0 \sqrt{A} dx}$$

$$\frac{1}{dC} = \frac{d}{\epsilon_0 \sqrt{A} dx} \left[\frac{\frac{\sqrt{A} - x}{\sqrt{A}}}{\kappa_1} + \frac{\frac{x}{\sqrt{A}}}{\kappa_2} \right]$$

$$\frac{1}{dC} = \frac{d}{\epsilon_0 \sqrt{A} dx \kappa_1 \kappa_2} \left[\kappa_2 \sqrt{A} + (\kappa_1 - \kappa_2) \frac{x}{\sqrt{A}} \right]$$


$$\int dc = \int \frac{\epsilon_0 A k_1 k_2 dx}{d (k_2 \sqrt{A} + (k_1 - k_2) x)}$$

$$= \frac{\epsilon_0 A k_1 k_2}{d} \ln \left(\frac{k_2 \sqrt{A} + (k_1 - k_2) x}{(k_1 - k_2)} \right) \Big|_0^{\sqrt{A}}$$

$$= \frac{\epsilon_0 A k_1 k_2}{d (k_1 - k_2)} \ln \left(\frac{k_2 \sqrt{A} + (k_1 - k_2) \sqrt{A}}{k_2 \sqrt{A}} \right)$$

Battery

$$V_B - V_A = V$$

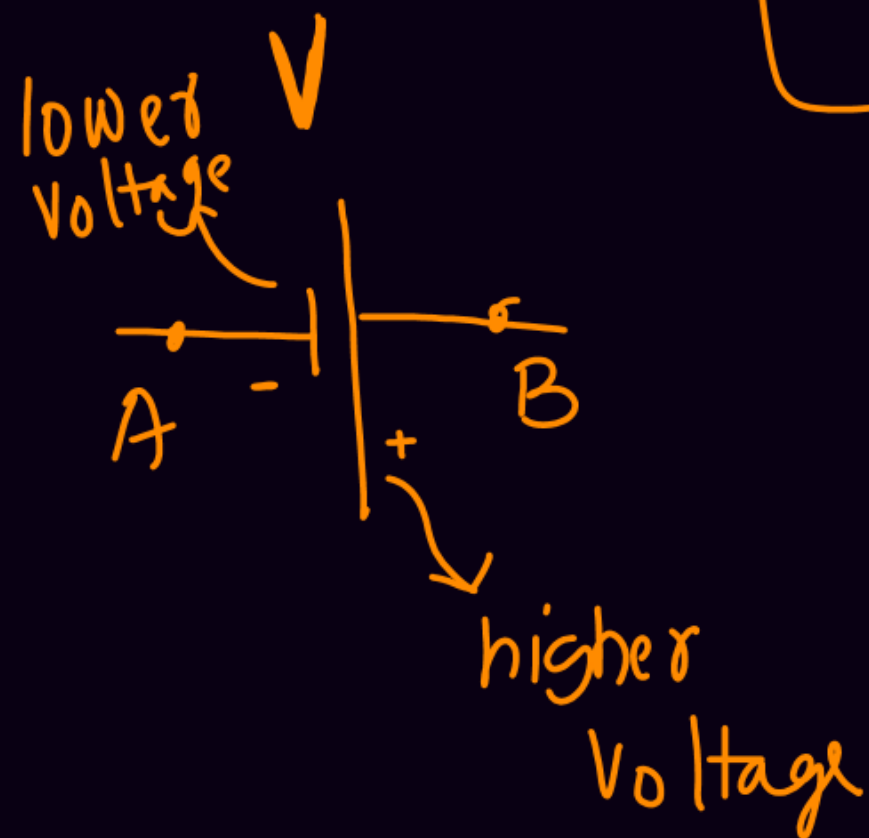

Work done by battery


Discharging
of battery



$$W_{\text{battery}} = qV$$





Charging

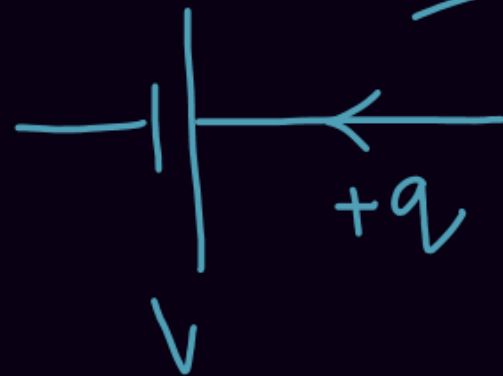

$$W_{\text{battery}} = -qV$$



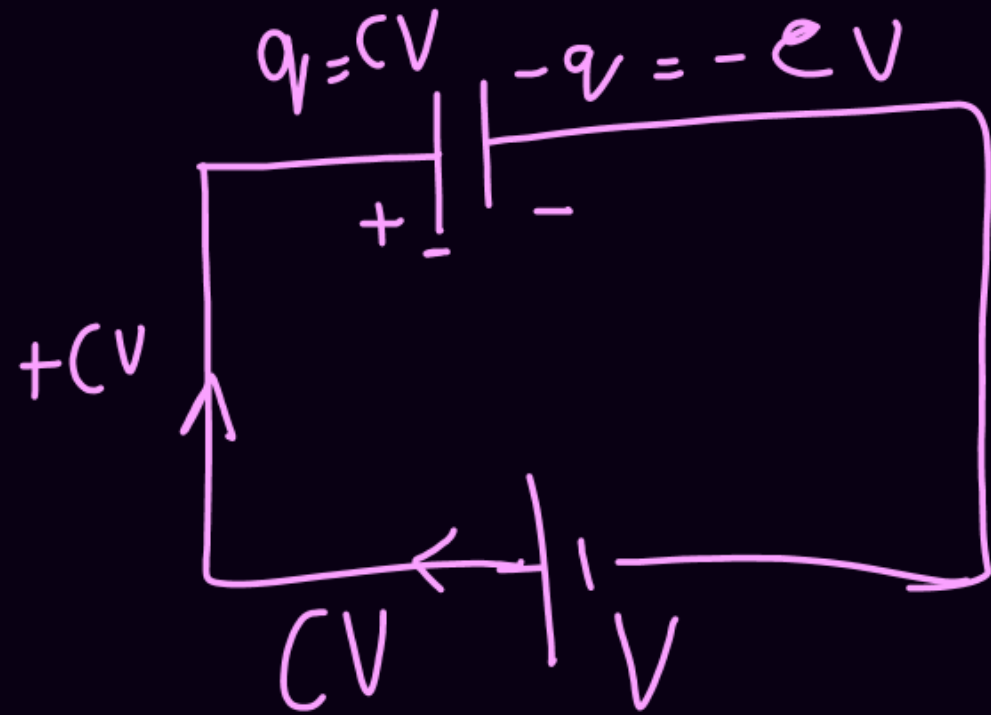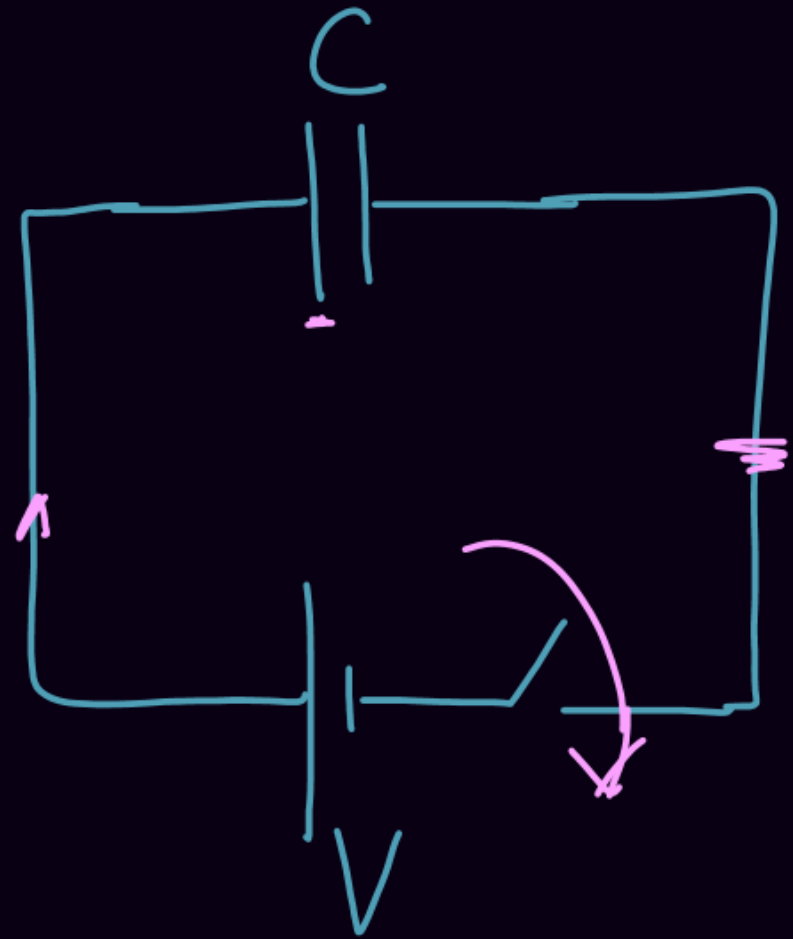

$$\textcircled{1} W_{\text{battery}} = + (CV)V = +CV^2$$

$$\textcircled{2} U_{\text{capacitor}} = \frac{1}{2} CV^2$$

$$U_{\text{cap}} = \frac{1}{2} W_{\text{battery}}$$

Numerical

find W_{battery} when dielectric of dielectric constant k is inserted in the capacitor.


$$W_{\text{battery}} = (k-1)CV^2$$

$$= (k-1)CV^2$$

Find the heat loss?

★ Initial energy + $W_{\text{by battery}}$ = Final energy
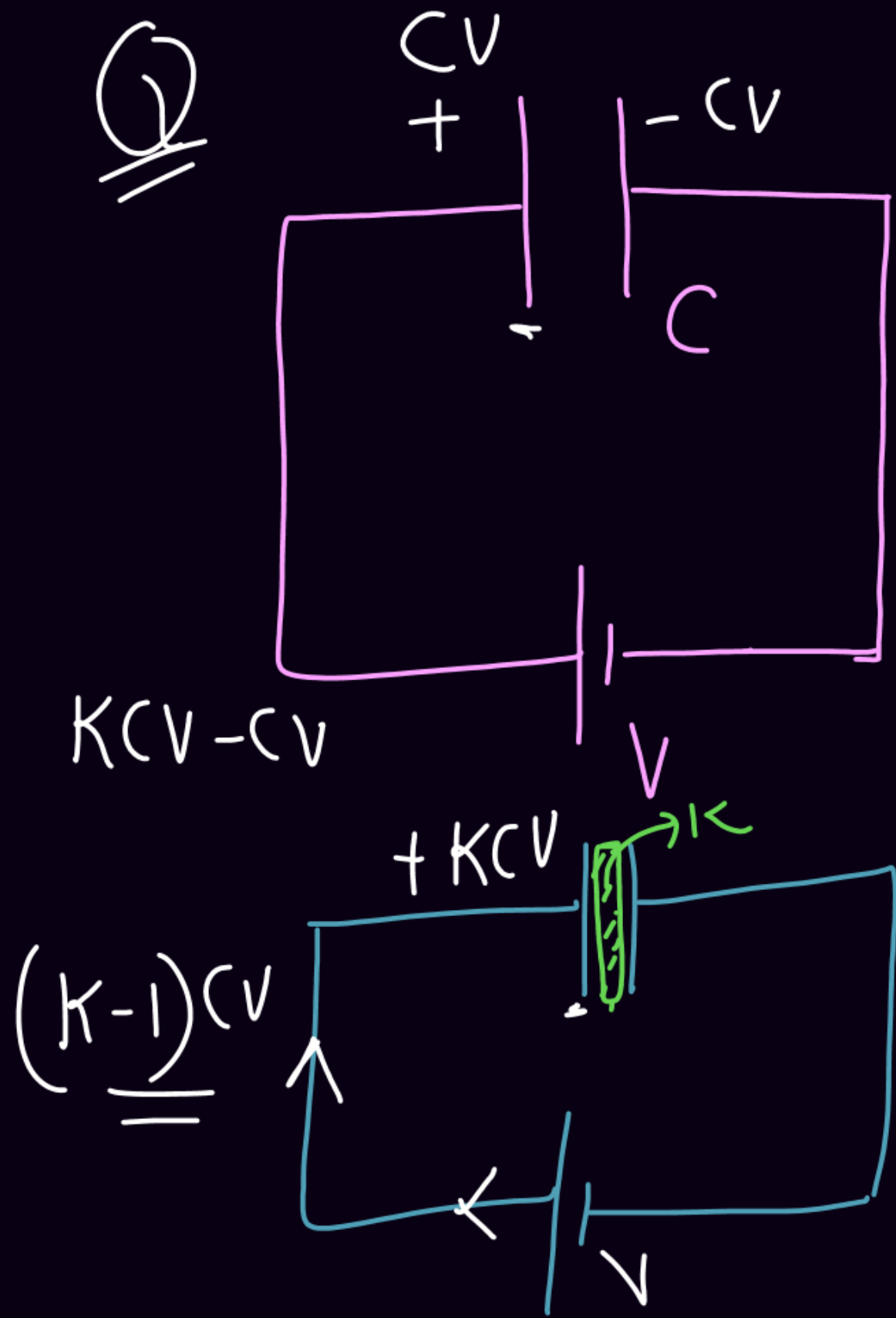
$$\frac{1}{2}CV^2 + (k-1)CV^2 = \frac{1}{2}(kC)V^2 + \Delta H_{\text{Heat loss}}$$



$$\frac{1}{2} c v^2 + (k-1) c v^2 = \frac{1}{2} (k c) v^2 + \Delta H.$$

$$c v^2 \left[\frac{1}{2} + k - 1 - \frac{k}{2} \right] = \Delta H.$$

$$c v^2 \left(\frac{k}{2} - \frac{1}{2} \right)$$

$$\frac{1}{2} (k-1) c v^2 = \Delta H$$

Two condensers of capacities C_1 and C_2 are connected in parallel and charged. Then the ratio of charge on C_1 to charge on C_2 is

- 1) $\frac{C_2}{C_1}$ 2) $\left(\frac{C_2}{C_1}\right)^2$ 3) $\frac{C_1}{C_2}$ 4) $\left(\frac{C_1}{C_2}\right)^2$



Two identical parallel plate capacitors are joined in series to 100 V battery. Now a dielectric constant ($K = 4$) is introduced between the plates of second capacitor. The potential differences on capacitors are

1) 60 V, 40 V

2) 70 V, 30 V

3) 75 V, 25 V

4) 80 V, 20 V

The work done in increasing the potential difference across the plates of a capacitor from 4 V to 6 V is W . The further work done in increasing the potential difference from 6 V to 8 V is

1) W

2) $5W/7$

3) $7W/5$

4) $2W/5$

Three condensers of capacities $3\ \mu\text{F}$, $4\ \mu\text{F}$ and $5\ \mu\text{F}$ are connected in series and a constant potential is applied between the ends of the combination. Their potentials are in the ratio of

1) $5 : 4 : 3$

2) $3 : 4 : 5$

3) $4 : 5 : 3$

4) $20 : 15 : 12$

The radius of the circular plates of a parallel plate condenser is r_1 . Air is there as dielectric. The distance between the plates if its capacitance is equal to that of an isolated sphere of radius r is

1) $r_1^2 / 4r$

2) r^2 / r_1

3) r / r_1

4) $r^2 / 4$

Three condensers each of capacity $6 \mu\text{F}$ are available. The effective capacity that cannot be obtained by combining them all is

1) $18 \mu\text{F}$

2) $9 \mu\text{F}$

3) $4 \mu\text{F}$

4) $8 \mu\text{F}$

The capacity of a parallel plate condenser with air medium is $60 \mu\text{F}$ having distance of separation d . If the space between the plates is filled with two slabs each of thickness $d/2$ and dielectric constants 4 and 8, the effective capacity becomes

1) $160 \mu\text{F}$

2) $320 \mu\text{F}$

3) $640 \mu\text{F}$

4) $360 \mu\text{F}$

Two metal spheres of radii 16 cm and 20 cm having charges 10 nC and 6 nC respectively are connected by a wire. Then the common potential is

1) 400 V

2) 200 V

3) 300 V

4) 100 V



Two condensers of capacities C_1 and C_2 charged to potentials V_1 and V_2 are connected in two ways as shown in the figure. The ratio of loss of energies in the case (i) to case (ii) is

1) $\frac{V_1 - V_2}{V_1 + V_2}$

2) $\frac{(V_1 - V_2)^2}{(V_1 + V_2)^2}$

3) $\frac{V_1^2 - V_2^2}{V_1^2 + V_2^2}$

4) $\frac{(V_1 + V_2)^2}{(V_1 - V_2)^2}$

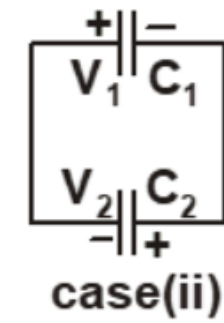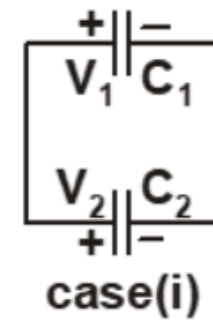

A parallel plate capacitor with air as medium between the plates has a capacitance $10\ \mu\text{F}$. The area of the capacitor is divided into two equal halves and filled with two media having dielectric constants 2 and 4. The capacitance of the system will be

1) $10\ \mu\text{F}$

2) $20\ \mu\text{F}$

3) $30\ \mu\text{F}$

4) $40\ \mu\text{F}$



Thank You Lakshyians