



## CS302- Digital Logic Design

**May 07,2011**

LATEST SOLVED MCQS FROM MIDTERM PAPERS

Latest Mcqs

Bc100400662

[bc100400662asad@gmail.com](mailto:bc100400662asad@gmail.com)

VGJW01

MC100401285

[Moaaz.pk@gmail.com](mailto:Moaaz.pk@gmail.com)      [MC100401285@gmail.com](mailto:MC100401285@gmail.com)

PSMD01

### CS302-MIDTERM SOLVED MCQS WITH REFERENCES



**Virtual University**

Muhammad Moaaz Siddiq – MCS (2nd)

[mc100401285@gmail.com](mailto:mc100401285@gmail.com)

Campus:- Institute of E-Learning & Modern Studies (IEMS)

Muhammad Asad Ali – BCS(3rd)

[bc100400662asad@gmail.com](mailto:bc100400662asad@gmail.com)

Campus : -Virtual University Campus, Gujranwala

Muhammad Moaaz Siddiq – MCS (2nd)

[mc100401285@gmail.com](mailto:mc100401285@gmail.com)

Campus:- Institute of E-Learning & Modern Studies (IEMS)

Muhammad Asad Ali – BCS(3rd)

[bc100400662asad@gmail.com](mailto:bc100400662asad@gmail.com)

Campus : -Virtual University Campus, Gujranwala

**MIDTERM EXAMINATION**  
**Spring 2010**

**Question No: 1 ( Marks: 1 ) - Please choose one**

A SOP expression is equal to 1 \_\_\_\_\_

- ▶ All the variables in domain of expression are present
- ▶ At least one variable in domain of expression is present.
- ▶ When one or more product terms in the expression are equal to 0.
- ▶ [When one or more product terms in the expression are equal to 1. \(Page 86\)](#)

**Question No: 2 ( Marks: 1 ) - Please choose one**

The output  $A < B$  is set to 1 when the input combinations is \_\_\_\_\_

- ▶ A=10, B=01
- ▶ A=11, B=01
- ▶ A=01, B=01
- ▶ [A=01, B=10 \(Page 109\)](#)

**Question No: 3 ( Marks: 1 ) - Please choose one**

Two 2-bit comparator circuits can be connected to form single 4-bit comparator

- ▶ [True \(Page 154\)](#)
- ▶ False

**Question No: 4 ( Marks: 1 ) - Please choose one**

High level Noise Margins ( $V_{NH}$ ) of CMOS 5 volt series circuits is \_\_\_\_\_

- ▶ 0.3 V
- ▶ 0.5 V
- ▶ [0.9 V \(Page 65\)](#)
- ▶ 3.3 V

**Question No: 5 ( Marks: 1 ) - Please choose one**

If we multiply “723” and “34” by representing them in floating point notation i.e. by first, converting them in floating point representation and then multiplying them, the value of mantissa of result will be \_\_\_\_\_

- ▶ [24.582 \(But not sure\)](#)
- ▶ 2.4582
- ▶ 24582

▶ 0.24582

**Question No: 6 ( Marks: 1 ) - Please choose one**

The output of the expression  $F=A+B+C$  will be Logic \_\_\_\_\_ when  $A=0, B=1, C=1$ . the symbol '+' here represents OR Gate.

- ▶ Undefined
- ▶ [One](#)
- ▶ Zero
- ▶ 10 (binary)

**Question No: 7 ( Marks: 1 ) - Please choose one**

If an active-HIGH S-R latch has a 0 on the S input and a 1 on the R input and then the R input goes to 0, the latch will be \_\_\_\_\_.

- ▶ [SET \(page 220\)](#)
- ▶ RESET
- ▶ Clear
- ▶ Invalid

**Question No: 8 ( Marks: 1 ) - Please choose one**

3.3 v CMOS series is characterized by \_\_\_\_\_ and \_\_\_\_\_ as compared to the 5 v CMOS series.

- ▶ Low switching speeds, high power dissipation
- ▶ Fast switching speeds, high power dissipation
- ▶ [Fast switching speeds, very low power dissipation \(page61\)](#)
- ▶ Low switching speeds, very low power dissipation

**Question No: 9 ( Marks: 1 ) - Please choose one**

The binary value "1010110" is equivalent to decimal \_\_\_\_\_

- ▶ [86 \(According to Formula\)](#)
- ▶ 87
- ▶ 88
- ▶ 89

**Question No: 10 ( Marks: 1 ) - Please choose one**

The \_\_\_\_\_ Encoder is used as a keypad encoder.

- ▶ 2-to-8 encoder
- ▶ 4-to-16 encoder
- ▶ BCD-to-Decimal


[▶ Decimal-to-BCD Priority \(Page 166\)](#)

**Question No: 11 ( Marks: 1 ) - Please choose one**

How many data select lines are required for selecting eight inputs?

- ▶ 1
- ▶ 2
- ▶ [3](#) [click here for detail](#)
- ▶ 4

 **Question No: 12 ( Marks: 1 ) - Please choose one**



the diagram above shows the general implementation of \_\_\_\_\_ form

- ▶ boolean
- ▶ arbitrary
- ▶ POS
- ▶ [SOP](#)

**Question No: 13 ( Marks: 1 ) - Please choose one**

The Quad Multiplexer has \_\_\_\_\_ outputs

- ▶ [4 \(Page 217\)](#)
- ▶ 8
- ▶ 12
- ▶ 16

**Question No: 14 ( Marks: 1 ) - Please choose one**

Demultiplexer has

- ▶ Single input and single outputs.
- ▶ Multiple inputs and multiple outputs.
- ▶ [Single input and multiple outputs. \(Page 178\)](#)
- ▶ Multiple inputs and single output.

**Question No: 15 ( Marks: 1 ) - Please choose one**

The expression \_\_\_\_\_ is an example of Commutative Law for Multiplication.

- ▶  $AB+C = A+BC$
- ▶  $A(B+C) = B(A+C)$
- ▶ [AB=BA \(Page 72\)](#)
- ▶  $A+B=B+A$

**Question No: 16 ( Marks: 1 ) - Please choose one**

"Sum-of-Weights" method is used \_\_\_\_\_

- ▶ [to convert from one number system to other \(Page 14\)](#)
- ▶ to encode data
- ▶ to decode data
- ▶ to convert from serial to parralel data

### MIDTERM EXAMINATION Spring 2010

**Question No: 1 ( Marks: 1 ) - Please choose one**

The maximum number that can be represented using unsigned octal system is \_\_\_\_\_

- ▶ 1
- ▶ [7 \(Page 31\)](#)
- ▶ 9
- ▶ 16


**Question No: 2 ( Marks: 1 ) - Please choose one**

If we add "723" and "134" by representing them in floating point notation i.e. by first, converting them in floating point representation and then adding them, the value of exponent of result will be \_\_\_\_\_

- ▶ 0
- ▶ 1
- ▶ [2 \(Page 26\)](#)
- ▶ 3

 **Question No: 3 ( Marks: 1 ) - Please choose one**

The diagram given below represents \_\_\_\_\_



- ▶ Demorgans law



- ▶ Associative law
- ▶ [Product of sum form \(According to rule of theorem\)](#)
- ▶ Sum of product form

**Question No: 4 ( Marks: 1 ) - Please choose one**

The range of Excess-8 code is from \_\_\_\_\_ to \_\_\_\_\_

- ▶ [+7 to -8 \(Page 34\)](#)
- ▶ +8 to -7
- ▶ +9 to -8
- ▶ -9 to +8

**Question No: 5 ( Marks: 1 ) - Please choose one**

A non-standard POS is converted into a standard POS by using the rule \_\_\_\_\_

- ▶  $A + \bar{A} = 1$
- ▶  $A\bar{A} = 0$  [\(Page 85\)](#)
- ▶  $1 + A = 1$
- ▶  $A + B = B + A$

**Question No: 6 ( Marks: 1 ) - Please choose one**

The 3-variable Karnaugh Map (K-Map) has \_\_\_\_\_ cells for min or max terms

- ▶ 4
- ▶ [8 \(Page 89\)](#)
- ▶ 12
- ▶ 16

**Question No: 7 ( Marks: 1 ) - Please choose one**

The binary numbers A = 1100 and B = 1001 are applied to the inputs of a comparator. What are the output levels?

- ▶  $A > B = 1, A < B = 0, A = B = 1$
- ▶  $A > B = 0, A < B = 1, A = B = 0$
- ▶ [A > B = 1, A < B = 0, A = B = 0 \(Page 109\)](#)
- ▶  $A > B = 0, A < B = 1, A = B = 1$

**Question No: 8 ( Marks: 1 ) - Please choose one**

A particular Full Adder has

- ▶ [3 inputs and 2 output \(Page 135\)](#)
- ▶ 3 inputs and 3 output
- ▶ 2 inputs and 3 output
- ▶ 2 inputs and 2 output

**Question No: 9 ( Marks: 1 ) - Please choose one**

The function to be performed by the processor is selected by set of inputs known as \_\_\_\_\_

▶ [Function Select Inputs \(Page 147\)](#)

- ▶ MicroOperation selectors
- ▶ OPCODE Selectors
- ▶ None of given option

**Question No: 10 ( Marks: 1 ) - Please choose one**

For a 3-to-8 decoder how many 2-to-4 decoders will be required?

▶ [2 \(Page 160\)](#)

- ▶ 1
- ▶ 3
- ▶ 4

**Question No: 11 ( Marks: 1 ) - Please choose one**

GAL is an acronym for \_\_\_\_\_.

- ▶ Giant Array Logic

▶ [General Array Logic \(Page 183\)](#)

- ▶ Generic Array Logic
- ▶ Generic Analysis Logic

**Question No: 12 ( Marks: 1 ) - Please choose one**

The Quad Multiplexer has \_\_\_\_\_ outputs

▶ [4 \(Page 216\)](#)

- ▶ 8
- ▶ 12
- ▶ 16

**Question No: 13 ( Marks: 1 ) - Please choose one**

$A.(B.C) = (A.B).C$  is an expression of \_\_\_\_\_

- ▶ Demorgan's Law
- ▶ Distributive Law
- ▶ Commutative Law

▶ [Associative Law \(Page 72\)](#)

**Question No: 14 ( Marks: 1 ) - Please choose one**

2's complement of any binary number can be calculated by

- ▶ adding 1's complement twice

▶ [adding 1 to 1's complement \(Page 144\)](#)

- ▶ subtracting 1 from 1's complement.
- ▶ calculating 1's complement and inverting Most significant bit

**Question No: 15 ( Marks: 1 ) - Please choose one**

The binary value “1010110” is equivalent to decimal \_\_\_\_\_

▶ **86 (According to formula)**

- ▶ 87
- ▶ 88
- ▶ 89

**Question No: 16 ( Marks: 1 ) - Please choose one**

Tri-State Buffer is basically a/an \_\_\_\_\_ gate.

- ▶ AND
- ▶ OR
- ▶ NOT
- ▶ **XOR (Page 186)**

### MIDTERM EXAMINATION 2010

1. The binary value “11011” is equivalent to \_\_\_\_\_

▶ **1B (According to rule)**

- ▶ 1C
- ▶ 1D
- ▶ 1E

2. An important application of AND Gate is its use in counter circuit

▶ **True (Page 281)**

- ▶ False

3. The OR Gate performs a Boolean \_\_\_\_\_ function

▶ **Addition (Page 42)**

- ▶ Subtraction
- ▶ Multiplication
- ▶ Division

4. TTL based devices work with a dc supply of \_\_\_\_ Volts

- ▶ +10
- ▶ **+5 (Page 61)**
- ▶ +3



▶ 3.3

5. A standard POS form has \_\_\_\_\_ terms that have all the variables in the domain of the expression.

▶ [Sum \(Page 85\)](#)

▶ Product

▶ Min

▶ Composite

6. A SOP expression having a domain of 3 variables will have a truth table having \_\_\_\_\_ combinations of inputs and corresponding output values.

▶ 2

▶ 4

▶ [8 \(According to rule\)](#)

▶ 16


7. A BCD to 7-Segment decoder has

▶ 3 inputs and 7 outputs

▶ [4 inputs and 7 outputs \(Page 103\)](#)

▶ 7 inputs and 3 outputs

▶ inputs and 4 outputs

 

8. In the Karnaugh map shown above, which of the loops shown represents a legal grouping?

▶ A

▶

▶ [C click here for detail](#)

▶ D

9. The binary value of 1010 is converted to the product term  $\overline{A}B\overline{C}D$

- ▶ True
- ▶ [False](#)

10. The binary numbers A = 1100 and B = 1001 are applied to the inputs of a comparator. What are the output levels?

- ▶  $A > B = 1, A < B = 0, A = B = 1$
- ▶  $A > B = 0, A < B = 1, A = B = 0$
- ▶ [A > B = 1, A < B = 0, A = B = 0 \(Page 109\)](#)
- ▶  $A > B = 0, A < B = 1, A = B = 1$


11.  $C_{out1} + S_3(S_2 + S_1)$  is boolean expression for

- ▶ Half Adder
- ▶ Full Adder
- ▶ [The Invalid BCD Detector Circuit \(page 142\)](#)
- ▶ Parity Checker

12. 3-to-8 decoder can be used to implement Standard SOP and POS Boolean expressions

- ▶ [True \(Page 160\)](#)
- ▶ False

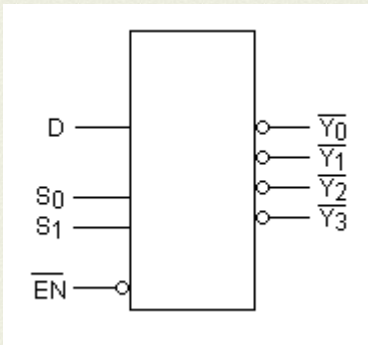13. The device shown here is most likely a \_\_\_\_\_



- ▶ Comparator
- ▶ Multiplexer
- ▶ [Demultiplexer click here for detail](#)
- ▶ Parity generator

14. The GAL22V10 has \_\_\_\_\_ inputs

▶ [22 \(Page 195\)](#)

- ▶ 10
- ▶ 44
- ▶ 20

15. A latch retains the state unless

- ▶ Power is turned off
- ▶ [Input is changed \(page 218\)](#)
- ▶ Output is changed
- ▶ Clock pulse is changed

16. If an active-HIGH S-R latch has a 0 on the S input and a 1 on the R input and then the R input goes to 0, the latch will be \_\_\_\_\_.

▶ [SET \(Page 220\)](#)

- ▶ RESET
- ▶ Clear
- ▶ Invalid

17. Consider a circuit consisting of two consecutive NOT gates, the entire circuit belongs to a CMOS 5 Volt series, if certain voltage is applied on the input, the output voltage of Logic high signal ( $V_{OH}$ ) will be in the range of \_\_\_\_\_ volts.

- ▶ 4 to 4.5
- ▶ [4.5 to 5](#)
- ▶ 0 to 4.5
- ▶ 0 to 3.5

18.  $A.(B.C) = (A.B).C$  is an expression of \_\_\_\_\_

- ▶ Demorgan's Law
- ▶ Distributive Law
- ▶ Commutative Law
- ▶ [Associative Law \(Page 72\)](#)

19. The 4-bit 2's complement representation of "+5" is \_\_\_\_\_

- ▶ 1010
- ▶ 1110
- ▶ [1011](#)
- ▶ 0101

**20. Which of the number is not a representative of hexadecimal system**

- ▶ 1234
- ▶ ABCD
- ▶ 1001
- ▶ **DEHF**      Hexa does not have H as remainder

**MIDTERM EXAMINATION  
Spring 2010**

**Question No: 1 ( Marks: 1 ) - Please choose one**

- ▶ 1
- ▶ 7
- ▶ 9
- ▶ 16


**Question No: 2 ( Marks: 1 ) - Please choose one**

If we add “723” and “134” by representing them in floating point notation i.e. by first, converting them in floating point representation and then adding them, the value of exponent of result will be \_\_\_\_\_

- ▶ 0
- ▶ 1
- ▶ **2**      (Page 26)
- ▶ 3

 **Question No: 3 ( Marks: 1 ) - Please choose one**

The diagram given below represents \_\_\_\_\_



- ▶ Demorgans law
- ▶ Associative law
- ▶ **Product of sum form**      (According to rule)
- ▶ Sum of product form

**Question No: 4 ( Marks: 1 ) - Please choose one**

The range of Excess-8 code is from \_\_\_\_\_ to \_\_\_\_\_

▶ [+7 to -8 \(Page 34\)](#)

- ▶ +8 to -7
- ▶ +9 to -8
- ▶ -9 to +8

**Question No: 5 ( Marks: 1 ) - Please choose one**

A non-standard POS is converted into a standard POS by using the rule \_\_\_\_\_

▶  $A + \overline{A} = 1$

▶  $A\overline{A} = 0$  [\(Page 85\)](#)

▶  $1 + A = 1$

▶  $A + B = B + A$

**Question No: 6 ( Marks: 1 ) - Please choose one**

The 3-variable Karnaugh Map (K-Map) has \_\_\_\_\_ cells for min or max terms

▶ 4

▶ [8 \(Page 89\)](#)

- ▶ 12
- ▶ 16

**Question No: 7 ( Marks: 1 ) - Please choose one**

The binary numbers  $A = 1100$  and  $B = 1001$  are applied to the inputs of a comparator. What are the output levels?

▶  $A > B = 1, A < B = 0, A = B = 1$

▶  $A > B = 0, A < B = 1, A = B = 0$

▶ [A > B = 1, A < B = 0, A = B = 0 \(Page 109\)](#)

▶  $A > B = 0, A < B = 1, A = B = 1$

**Question No: 8 ( Marks: 1 ) - Please choose one**

A particular Full Adder has

▶ [3 inputs and 2 output \(Page 135\)](#)

- ▶ 3 inputs and 3 output
- ▶ 2 inputs and 3 output
- ▶ 2 inputs and 2 output

**Question No: 9 ( Marks: 1 ) - Please choose one**

The function to be performed by the processor is selected by set of inputs known as \_\_\_\_\_

▶ [Function Select Inputs \(Page 147\)](#)



- ▶ MicroOperation selectors
- ▶ OPCODE Selectors
- ▶ None of given option

**Question No: 10 ( Marks: 1 ) - Please choose one**

For a 3-to-8 decoder how many 2-to-4 decoders will be required?

▶ [2 \(Page 160\)](#)

- ▶ 1
- ▶ 3
- ▶ 4

**Question No: 11 ( Marks: 1 ) - Please choose one**

GAL is an acronym for \_\_\_\_\_.

- ▶ Giant Array Logic
- ▶ [General Array Logic \(Page 183\)](#)
- ▶ Generic Array Logic
- ▶ Generic Analysis Logic

**Question No: 12 ( Marks: 1 ) - Please choose one**

The Quad Multiplexer has \_\_\_\_\_ outputs

▶ [4 \(Page 216\)](#)

- ▶ 8
- ▶ 12
- ▶ **16**

**Question No: 13 ( Marks: 1 ) - Please choose one**

$A.(B.C) = (A.B).C$  is an expression of \_\_\_\_\_

- ▶ Demorgan's Law
- ▶ Distributive Law
- ▶ Commutative Law
- ▶ [Associative Law \(Page 72\)](#)

**Question No: 14 ( Marks: 1 ) - Please choose one**

2's complement of any binary number can be calculated by

- ▶ adding 1's complement twice
- ▶ [adding 1 to 1's complement \(Page 144\)](#)
- ▶ subtracting 1 from 1's complement.
- ▶ calculating 1's complement and inverting Most significant bit

**Question No: 15 ( Marks: 1 ) - Please choose one**

Muhammad Moaaz Siddiq – MCS (2nd)  
[mc100401285@Gmail.com](mailto:mc100401285@Gmail.com)  
Campus:- Institute of E-Learning & Modern  
Studies (IEMS)

Muhammad Asad Ali – BCS(3rd)  
[bc100400662asad@gmail.com](mailto:bc100400662asad@gmail.com)  
Campus : -Virtual University Campus,  
Gujranwala

The binary value “1010110” is equivalent to decimal \_\_\_\_\_

▶ [86 \(According to formula\)](#)

▶ 87

▶ 88

▶ 89

**Question No: 16 ( Marks: 1 ) - Please choose one**

Tri-State Buffer is basically a/an \_\_\_\_\_ gate.

▶ AND

▶ OR

▶ [NOT \(page 196\)](#)

▶ **XOR**

### MIDTERM EXAMINATION

Spring 2009

CS302- Digital Logic Design (Session - 1)

**Question No: 1 ( Marks: 1 ) - Please choose one**

\_GAL can be reprogrammed because instead of fuses \_\_\_\_\_ logic is used in it

▶ [E<sup>2</sup>CMOS \(Page 191\)](#)

▶ TTL

▶ CMOS+

▶ None of the given options

**Question No: 2 ( Marks: 1 ) - Please choose one**


The device shown here is most likely a

▶ Comparator

▶ [Multiplexer click here for detail](#)

▶ Demultiplexer

▶ Parity generator

 

**Question No: 3 ( Marks: 1 ) - Please choose one**

If “1110” is applied at the input of BCD-to-Decimal decoder which output pin will be activated:

▶ 2<sup>nd</sup>

▶ 4<sup>th</sup>

Muhammad Moaaz Siddiq – MCS (2nd)  
[mc100401285@gmail.com](mailto:mc100401285@gmail.com)  
Campus:- Institute of E-Learning & Modern  
Studies (IEMS)

Muhammad Asad Ali – BCS(3rd)  
[bc100400662asad@gmail.com](mailto:bc100400662asad@gmail.com)  
Campus : -Virtual University Campus,  
Gujranwala

▶ 14<sup>th</sup>

▶ [No output wire will be activated \(Page 163\)](#)

**Question No: 4 (Marks: 1) - Please choose one**

Half-Adder Logic circuit contains 2 XOR Gates

▶ True

▶ [False \(Page 135\)](#)

**Question No: 5 (Marks: 1) - Please choose one**

A particular Full Adder has

▶ [3 inputs and 2 output \(Page 135\)](#)

▶ 3 inputs and 3 output

▶ 2 inputs and 3 output

▶ 2 inputs and 2 output

**Question No: 6 (Marks: 1) - Please choose one**

Sum =  $A \oplus B \oplus C$

CarryOut =  $C(A \oplus B) + AB$

are the Sum and CarryOut expression of

▶ Half Adder

▶ [Full Adder \(Page 135\)](#)

▶ 3-bit parallel adder

▶ MSI adder circuit

**Question No: 7 (Marks: 1) - Please choose one**

A Karnaugh map is similar to a truth table because it presents all the possible values of input variables and the resulting output of each value.

▶ [True click here for detail](#)

▶ False

**Question No: 8 (Marks: 1) - Please choose one**

The output  $A < B$  is set to 1 when the input combinations is \_\_\_\_\_

▶ A=10, B=01

▶ A=11, B=01

▶ A=01, B=01

▶ [A=01, B=10 \(Page 109\)](#)

**Question No: 9 (Marks: 1) - Please choose one**

The 4-variable Karnaugh Map (K-Map) has \_\_\_\_\_ cells for min or max terms

▶ 4

▶ 8

▶ 12

[▶ 16 \(Page 90\)](#)

**Question No: 10 (Marks: 1) - Please choose one**

Generally, the Power dissipation of \_\_\_\_\_ devices remains constant throughout their operation.

[▶ TTL \(Page 65\)](#)

- ▶ CMOS 3.5 series
- ▶ CMOS 5 Series
- ▶ **Power dissipation of all circuits increases with time.**

**Question No: 11 (Marks: 1) - Please choose one**

The decimal "8" is represented as \_\_\_\_\_ using Gray-Code.

▶ 0011

[▶ 1100 \(page 36\)](#)

- ▶ 1000
- ▶ 1010

**Question No: 12 (Marks: 1) - Please choose one**

$(A+B).(A+C) = \underline{\hspace{2cm}}$

▶ B+C

[▶ A+BC \(According to rule\)](#)

- ▶ AB+C
- ▶ AC+B

**Question No: 13 (Marks: 1) - Please choose one**

$A.(B+C) = A.B + A.C$  is the expression of \_\_\_\_\_

- ▶ Demorgan's Law
- ▶ Commutative Law

[▶ Distributive Law \(Page 73\)](#)

- ▶ Associative Law

**Question No: 14 (Marks: 1) - Please choose one**

NOR Gate can be used to perform the operation of AND, OR and NOT Gate

▶ FALSE

[▶ TRUE \(Page 50\)](#)

**Question No: 15 (Marks: 1) - Please choose one**

In ANSI/IEEE Standard 754 "Mantissa" is represented by \_\_\_\_\_ 32-bits \_\_\_\_\_ bits

- ▶ 8-bits
- ▶ 16-bits

[▶ 32-bits \(Page 24\)](#)

▶ 64-bits

---

**Question No: 16 ( Marks: 1 ) - Please choose one**  
Caveman number system is Base 5 number system

- ▶ 2
- ▶ [5 \(Page 11\)](#)
- ▶ 10
- ▶ 16

**MIDTERM EXAMINATION**  
**Fall 2009**

**Question No: 1 ( Marks: 1 ) - Please choose one**  
According to Demorgan's theorem:

$\overline{A + B + C} =$  \_\_\_\_\_

- ▶ A.B.C
- ▶  $A + \overline{B.C}$
- ▶  $\overline{A.B.C}$  [\(Page 74\)](#)
- ▶  $\overline{A.B} + C$

**Question No: 2 ( Marks: 1 ) - Please choose one**

The Extended ASCII Code (American Standard Code for Information Interchange) is a \_\_\_\_\_ code

- ▶ 2-bit
- ▶ 7-bit
- ▶ [8-bit \(Page 38\)](#)
- ▶ 16-bit

**Question No: 3 ( Marks: 1 ) - Please choose one**

The AND Gate performs a logical \_\_\_\_\_ function

- ▶ Addition
- ▶ Subtraction
- ▶ [Multiplication \(Page 40\)](#)
- ▶ Division

**Question No: 4 ( Marks: 1 ) - Please choose one**

NOR gate is formed by connecting \_\_\_\_\_

- ▶ [OR Gate and then NOT Gate \(Page 47\)](#)
- ▶ NOT Gate and then OR Gate
- ▶ AND Gate and then OR Gate



- ▶ OR Gate and then AND Gate

**Question No: 5 ( Marks: 1 ) - Please choose one**

Generally, the Power dissipation of \_\_\_\_\_ devices remains constant throughout their operation.

▶ [TTL \(Page 65\)](#)

- ▶ CMOS 3.5 series
- ▶ CMOS 5 Series
- ▶ Power dissipation of all circuits increases with time.

**Question No: 6 ( Marks: 1 ) - Please choose one**

Two 2-bit comparator circuits can be connected to form single 4-bit comparator

▶ [True \(Page 154\)](#)

- ▶ False

**Question No: 7 ( Marks: 1 ) - Please choose one**

When the control line in tri-state buffer is high the buffer operates like a \_\_\_\_\_ gate

- ▶ AND
- ▶ OR
- ▶ [NOT \(Page196\)](#)
- ▶ XOR

**Question No: 8 ( Marks: 1 ) - Please choose one**

The GAL22V10 has \_\_\_\_\_ inputs

▶ [22 \(Page 195\)](#)

- ▶ 10
- ▶ 44
- ▶ 20

**Question No: 9 ( Marks: 1 ) - Please choose one**

The ABEL symbol for “OR” operation is

- ▶ !
- ▶ &
- ▶ [# \(Page 201\)](#)
- ▶ \$

**Question No: 10 ( Marks: 1 ) - Please choose one**

The OLMC of the GAL16V8 is \_\_\_\_\_ to the OLMC of the GAL22V10

- ▶ Similar
- ▶ Different
- ▶ [Similar with some enhancements \(Page 207\)](#)
- ▶ Depends on the type of PALs input size

**Question No: 11 ( Marks: 1 ) - Please choose one**

All the ABEL equations must end with \_\_\_\_\_

- ▶ “. “ (a dot)
- ▶ “ \$ “ (a dollar symbol)
- ▶ [“ ; “ \(a semicolon\) \(Page 201\)](#)
- ▶ “ endl “ (keyword “endl”)

**Question No: 12 ( Marks: 1 ) - Please choose one**

The Quad Multiplexer has \_\_\_\_\_ outputs

- ▶ [4 \(Page 216\) rep](#)
- ▶ 8
- ▶ 12
- ▶ 16

**Question No: 13 ( Marks: 1 ) - Please choose one**

"Sum-of-Weights" method is used \_\_\_\_\_

- ▶ [to convert from one number system to other \(Page 14\)](#)
- ▶ to encode data
- ▶ to decode data
- ▶ to convert from serial to parralel data

**Question No: 14 ( Marks: 1 ) - Please choose one**

Circuits having a bubble at their outputs are considered to have an active-low output.

- ▶ [True \(Page 128\)](#)
- ▶ False

**Question No: 15 ( Marks: 1 ) - Please choose one**

$(A + B)(A + \overline{B} + C)(\overline{A} + C)$  is an example of \_\_\_\_\_

- ▶ [Product of sum form \(According to rule\)](#)
- ▶ Sum of product form
- ▶ Demorgans law
- ▶ Associative law

**Question No: 16 ( Marks: 1 ) - Please choose one**

Which one is true:

Muhammad Moaaz Siddiq – MCS (2nd)  
[mc100401285@gmail.com](mailto:mc100401285@gmail.com)  
 Campus:- Institute of E-Learning & Modern  
 Studies (IEMS)

Muhammad Asad Ali – BCS(3rd)  
[bc100400662asad@gmail.com](mailto:bc100400662asad@gmail.com)  
 Campus : -Virtual University Campus,  
 Gujranwala

▶ [Power consumption of TTL is higher than of CMOS \(Page 61\)](#)

- ▶ Power consumption of CMOS is higher than of TTL
- ▶ Both TTL and CMOS have same power consumption
- ▶ Power consumption of both CMOS and TTL depends on no. of gates in the circuit.

**MIDTERM EXAMINATION**  
**Spring 2009**

**Question No: 1 ( Marks: 1 ) - Please choose one**

In the binary number "10011" the weight of the most significant digit is \_\_\_\_\_

▶ [2<sup>4</sup> \(2 raise to power 4\) \(Page 13\)](#)

- ▶ 2<sup>3</sup> (2 raise to power 3)
- ▶ 2<sup>0</sup> (2 raise to power 0)
- ▶ 2<sup>1</sup> (2 raise to power 1)

**Question No: 2 ( Marks: 1 ) - Please choose one**

An S-R latch can be implemented by using \_\_\_\_\_ gates

- ▶ AND, OR
- ▶ [NAND, NOR \(Page 218-220\)](#)
- ▶ NAND, XOR
- ▶ NOT, XOR

**Question No: 3 ( Marks: 1 ) - Please choose one**

A latch has \_\_\_\_\_ stable states

- ▶ One
- ▶ [Two \(Page 218\)](#)
- ▶ Three
- ▶ Four

**Question No: 4 ( Marks: 1 ) - Please choose one**

Sequential circuits have storage elements

- ▶ [True \(Page 8\)](#)
- ▶ False

**Question No: 5 ( Marks: 1 ) - Please choose one**

The ABEL symbol for "XOR" operation is

- ▶ [\\$ \(Page 210\)](#)
- ▶ #
- ▶ !

▶ &

**Question No: 6 ( Marks: 1 ) - Please choose one**

A Demultiplexer is not available commercially.

▶ [True \(Page 178\)](#)

▶ False

**Question No: 7 ( Marks: 1 ) - Please choose one**

Using multiplexer as parallel to serial converter requires \_\_\_\_\_ connected to the multiplexer

▶ [A parallel to serial converter circuit \(Page 244\)](#)


▶ A counter circuit

▶ A BCD to Decimal decoder

▶ A 2-to-8 bit decoder

**Question No: 8 ( Marks: 1 ) - Please choose one**

The device shown here is most likely a

 

▶ Comparator

▶ [Multiplexer click here for detail](#)

▶ Demultiplexer

▶ Parity generator

**Question No: 9 ( Marks: 1 ) - Please choose one**

The main use of the Multiplexer is to

▶ [Select data from multiple sources and to route it to a single Destination \(Page 167\)](#)

▶ Select data from Single source and to route it to a multiple Destinations

▶ Select data from Single source and to route to single destination

▶ Select data from multiple sources and to route to multiple destinations

**Question No: 10 ( Marks: 1 ) - Please choose one**

A logic circuit with an output  $X = \bar{A}BC + A\bar{B}$  consists of \_\_\_\_\_.

Muhammad Moaaz Siddiq – MCS (2nd)

[mc100401285@gmail.com](mailto:mc100401285@gmail.com)

Campus:- Institute of E-Learning & Modern  
Studies (IEMS)

Muhammad Asad Ali – BCS(3rd)

[bc100400662asad@gmail.com](mailto:bc100400662asad@gmail.com)

Campus : -Virtual University Campus,  
Gujranwala

- ▶ two AND gates, two OR gates, two inverters
- ▶ three AND gates, two OR gates, one inverter
- ▶ two AND gates, one OR gate, two inverters
- ▶ two AND gates, one OR gate

**Question No: 11 ( Marks: 1 ) - Please choose one**

The binary value of 1010 is converted to the product term  $\overline{A}B\overline{C}D$

- ▶ True
- ▶ False

**Question No: 12 ( Marks: 1 ) - Please choose one**

The 3-variable Karnaugh Map (K-Map) has \_\_\_\_\_ cells for min or max terms

- ▶ 4
- ▶ 8 (Page 89)
- ▶ 12
- ▶ 16

**Question No: 13 ( Marks: 1 ) - Please choose one**

Following is standard POS expression

$$(A + \overline{B} + C + \overline{D})(A + \overline{B} + C + D)(A + B + \overline{C} + \overline{D})(A + B + C + \overline{D})(A + \overline{B} + \overline{C} + D)$$

- ▶ True (According to logic)
- ▶ False

**Question No: 14 ( Marks: 1 ) - Please choose one**

The output of the expression  $F=A+B+C$  will be Logic \_\_\_\_\_ when  $A=0, B=1, C=1$ . the symbol '+' here represents OR Gate.

- ▶ Undefined
- ▶ One
- ▶ Zero
- ▶ 10 (binary)

**Question No: 15 ( Marks: 1 ) - Please choose one**

The Extended ASCII Code (American Standard Code for Information Interchange) is a \_\_\_\_\_ code

- ▶ 2-bit
- ▶ 7-bit




▶ [8-bit \(Page 38\)](#)

- ▶ 16-bit

 **Question No: 16 ( Marks: 1 ) - Please choose one**

The diagram given below represents \_\_\_\_\_



- ▶ Demorgans law
- ▶ Associative law
- ▶ [Product of sum form \(According to rule\)](#)
- ▶ Sum of product form

**MIDTERM EXAMINATION  
Fall 2009**

**Question No: 1 ( Marks: 1 ) - Please choose one**

Which of the number is not a representative of hexadecimal system

- ▶ 1234
- ▶ ABCD
- ▶ 1001
- ▶ [DEFH](#) **Hexa does not have H as remainder**

**Question No: 2 ( Marks: 1 ) - Please choose one**

The Unsigned Binary representation can only represent positive binary numbers

- ▶ [True \(Page 21\)](#)
- ▶ False

**Question No: 3 ( Marks: 1 ) - Please choose one**

The values that exceed the specified range can not be correctly represented and are considered as \_\_\_\_\_

► [Overflow \(Page 23\)](#)

- Carry
- Parity
- Sign value

**Question No: 4 ( Marks: 1 ) - Please choose one**

The 4-bit 2's complement representation of "-7" is \_\_\_\_\_

- 0111
- 1111
- [1001 \(Page 21\)](#)
- 0110


**Question No: 5 ( Marks: 1 ) - Please choose one**

$\overline{A}B + \overline{A}BC + AC$  is an example of \_\_\_\_\_

- Product of sum form
- [Sum of product form \(Page 77\)](#)
- Demorgans law
- Associative law

 **Question No: 6 ( Marks: 1 ) - Please choose one**

The diagram given below represents \_\_\_\_\_



- Demorgans law
- Associative law
- Product of sum form
- [Sum of product form](#)

**Question No: 7 ( Marks: 1 ) - Please choose one**

The output of an AND gate is one when \_\_\_\_\_

▶ [All of the inputs are one](#)

- ▶ Any of the input is one
- ▶ Any of the input is zero
- ▶ All the inputs are zero

**Question No: 8 ( Marks: 1 ) - Please choose one**

The 4-variable Karnaugh Map (K-Map) has \_\_\_\_\_ cells for min or max terms

- ▶ 4
- ▶ 8
- ▶ 12

▶ [16 \(Page 90\)](#)

**Question No: 9 ( Marks: 1 ) - Please choose one**

A BCD to 7-Segment decoder has

- ▶ 3 inputs and 7 outputs
- ▶ [4 inputs and 7 outputs \(Page 103\)](#)
- ▶ 7 inputs and 3 outputs
- ▶ 7 inputs and 4 outputs

**Question No: 10 ( Marks: 1 ) - Please choose one**

Two 2-input, 4-bit multiplexers 74X157 can be connected to implement a \_\_\_\_ multiplexer.

- ▶ 4-input, 8-bit
- ▶ 4-input, 16-bit
- ▶ 2-input, 8-bit
- ▶ [2-input, 4-bit \(Page 169\)](#)

**Question No: 11 ( Marks: 1 ) - Please choose one**

The PROM

consists of a fixed non-programmable \_\_\_\_\_ Gate array configured as a decoder.

▶ [AND \(Page 182\)](#)

- ▶ OR
- ▶ NOT
- ▶ XOR

**Question No: 12 ( Marks: 1 ) - Please choose one**

In ABEL the variable 'A' is treated separately from variable 'a'

▶ [True \(Page 201\)](#)

▶ False

**Question No: 13 ( Marks: 1 ) - Please choose one**

The ABEL notation equivalent to Boolean expression  $A+B$  is:

▶ A & B

▶ A ! B

▶ [A # B \(Page 201\)](#)

▶ A \$ B

L-21

**Question No: 14 ( Marks: 1 ) - Please choose one**

If an active-HIGH S-R latch has a 0 on the S input and a 1 on the R input and then the R input goes to 0, the latch will be \_\_\_\_\_.

▶ [SET \(Page 220\)](#)

▶ RESET

▶ Clear

▶ Invalid

**Question No: 15 ( Marks: 1 ) - Please choose one**

Demultiplexer has

▶ Single input and single outputs.

▶ Multiple inputs and multiple outputs.

▶ [Single input and multiple outputs. \(Page 178\)](#)

▶ Multiple inputs and single output.

**Question No: 16 ( Marks: 1 ) - Please choose one**

Which one is true:

▶ [Power consumption of TTL is higher than of CMOS \(Page 61\)](#)

▶ Power consumption of CMOS is higher than of TTL

▶ Both TTL and CMOS have same power consumption

▶ Power consumption of both CMOS and TTL depends on no. of gates in the circuit.

## MIDTERM EXAMINATION Fall 2009

**Question No: 1 ( Marks: 1 ) - Please choose one**

The first Least Significant digit in decimal number system has

[position 0 and weight equal to 1](#)

position 1 and weight equal to 0

Muhammad Moaaz Siddiq – MCS (2nd)  
[mc100401285@Gmail.com](mailto:mc100401285@Gmail.com)  
Campus:- Institute of E-Learning & Modern  
Studies (IEMS)

Muhammad Asad Ali – BCS(3rd)  
[bc100400662asad@gmail.com](mailto:bc100400662asad@gmail.com)  
Campus : -Virtual University Campus,  
Gujranwala

position 1 and weight equal to 10  
position 0 and weight equal to 10

**Question No: 2 ( Marks: 1 ) - Please choose one**  
**The decimal equivalent of the binary number “10011” is**

[19 \(According to rule\)](#)

99

29

None of given options

**Question No: 3 ( Marks: 1 ) - Please choose one**

In ANSI/IEEE Standard 754 “Mantissa” is represented by \_\_\_\_32-bits \_\_\_\_ bits

▶ 8-bits

▶ 16-bits

▶ [32-bits \(Page 24\)](#)

▶ 64-bits

**Question No: 4 ( Marks: 1 ) - Please choose one**

**The binary value “11011” is equivalent to**

[1B \(According to rule\)](#)


1C

1D

1E

**Question No: 6 ( Marks: 1 ) - Please choose one**

**The diagram given below represents**

 

Demorgans law

Associative law

[Product of sum form \(According to rule\)](#)

Sum of product form

**Question No: 7 ( Marks: 1 ) - Please choose one**

**NOR gate is formed by connecting**

[OR Gate and then NOT Gate \(Page 47\)](#)

NOT Gate and then OR Gate



AND Gate and then OR Gate  
OR Gate and then AND Gate

**Question No: 8** ( Marks: 1 ) - Please choose one  
**“74ALS” stands for**

Advanced Low-frequency Schottky TTL  
Advanced Low-dissipation Schottky TTL  
[Advanced Low-Power Schottky TTL \(Page 61\)](#)  
Advanced Low-propagation Schottky TTL

**Question No: 9** ( Marks: 1 ) - Please choose one  
**An adder circuit can be used to perform subtraction operation**

[True \(Page 146\)](#)

False

**Question No: 10** ( Marks: 1 ) - Please choose one  
**For a 3-to-8 decoder how many 2-to-4 decoders will be required?**

[2 \(Page 160\)](#)

3  
4  
1

**Question No: 11** ( Marks: 1 ) - Please choose one  
**3-to-8 decoder can be used to implement Standard SOP and POS Boolean expressions**

[True Page 161](#)

False

**Question No: 12** ( Marks: 1 ) - Please choose one  
**Two 2-input, 4-bit multiplexers 74X157 can be connected to implement a multiplexer.**

2-input, 4-bit  
4-input, 8-bit  
4-input, 16-bit

[2-input, 8-bit \(Page 171\)](#)

**Question No: 13** ( Marks: 1 ) - Please choose one  
**The four outputs of two 4-input multiplexers, connected to form a 16-input multiplexer, are connected together through a 4-input gate**

AND

[OR \(Page 171-172\)](#)

NAND

XOR



**Question No: 14** ( Marks: 1 ) - Please choose one  
**The Programmable Array Logic (PAL) has AND array and a OR array**

Fixed, programmable

[Programmable, fixed \(Page 182\)](#)

Fixed, fixed

Programmable, programmable

**Question No: 15** ( Marks: 1 ) - Please choose one  
**Sequential circuits have storage elements**

[True \(Page 218\)](#)

False

**Question No: 16** ( Marks: 1 ) - Please choose one  
**Demultiplexer has**

Single input and single outputs.

Multiple inputs and multiple outputs.

[Single input and multiple outputs. \(Page 178\)](#)

Multiple inputs and single output.