

BE 03-11-14 A/c (1)
(OP-AMP) (Operational Amplifier) (2)

→ Designed to perform Mathematical operations hence the name operational amplifiers. (1)

→ OP-amp is an Integrated circuit or a semiconductor chip fabricated under very large integration method by using planer technology.

→ A voltage controlled device.

{ FET, OP-Amp, vacuum tube → voltage controlled
} BJT - current controlled device.

→ Linear analog IC, (Linear → we can apply superposition principle)

→ Low power device.

→ Negligible Internal power consumption.

→ The 1st Internal stage in the Op-amp is emitter coupled diff. amplifier.

The last stage is BUFFER.

→ Input signal can be dc. signal, sine wave or any types of Ac. signals.


→ Popularly used Op-amp is IC-741

IC-741
FET


- for IC-741 max^m. supply is $\pm 15V$

- operated with dual supply

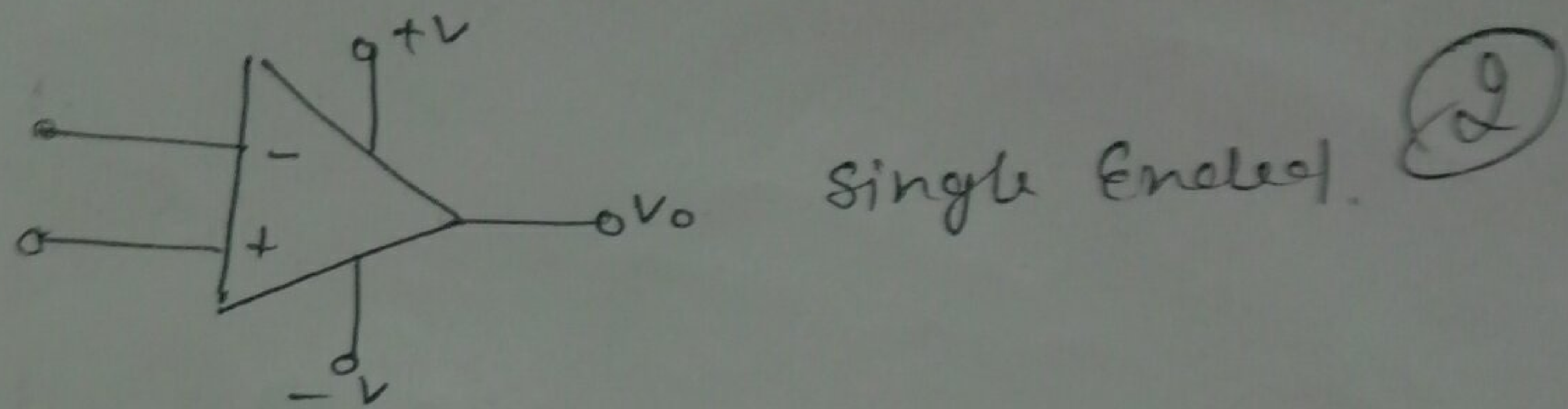- In single ended op-amp no. of output terminal is one. (2)



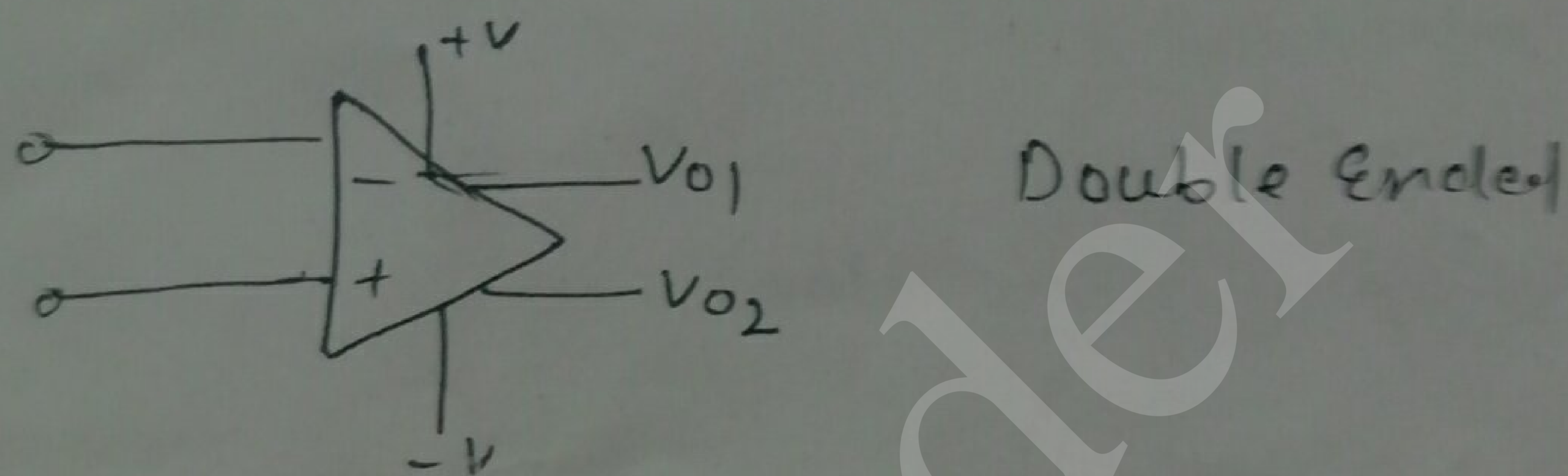- In double op-amp no. of output terminals 2, provide complementary output.




Disadvantage

- (1) very sensitive to humidity
- (2) sensitive to voltage fluctuation, it can be overcome by using Regulated supply.
- (3) sensitive to high temperature.


OPERATING MODE:

- (i) Inverting mode :-

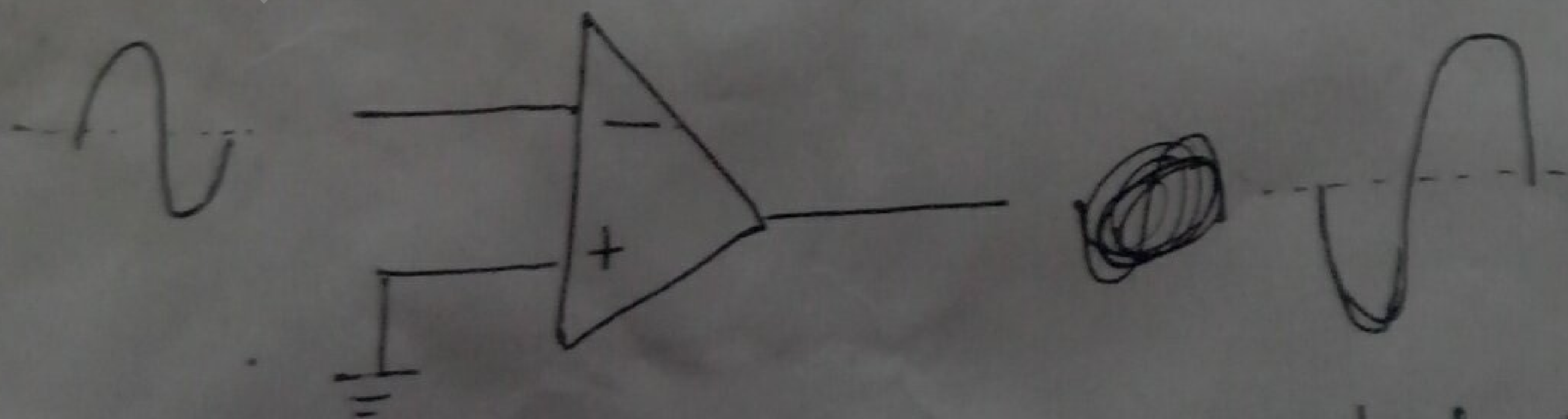


Here output signal will be 180° out of phase with input & hence may have high amplitude due to gain of output op-amp.

(2). Non Inverting mode :-

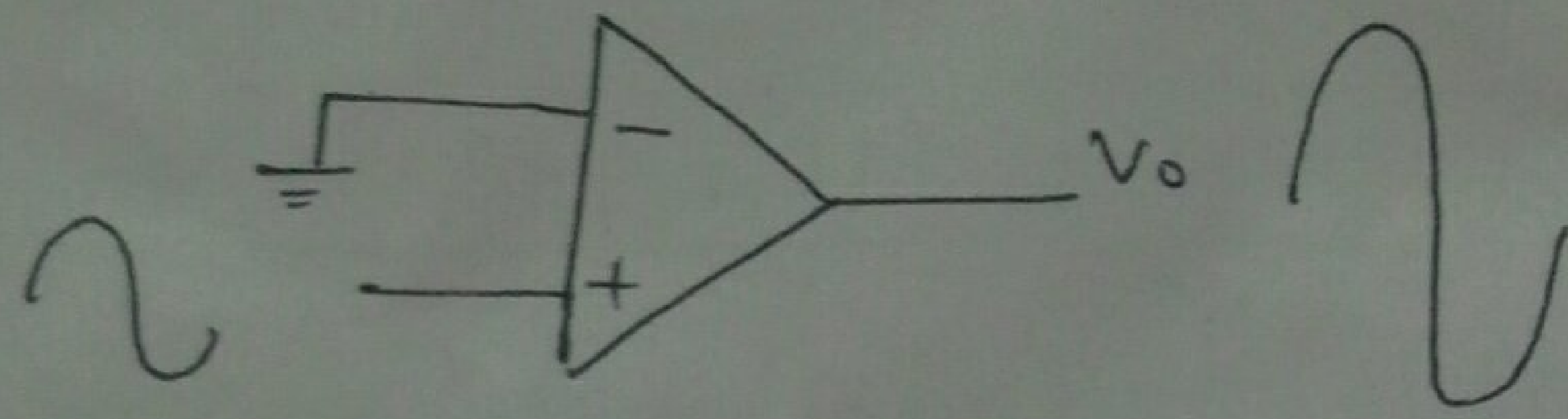

(3)

(3). Differential mode :-

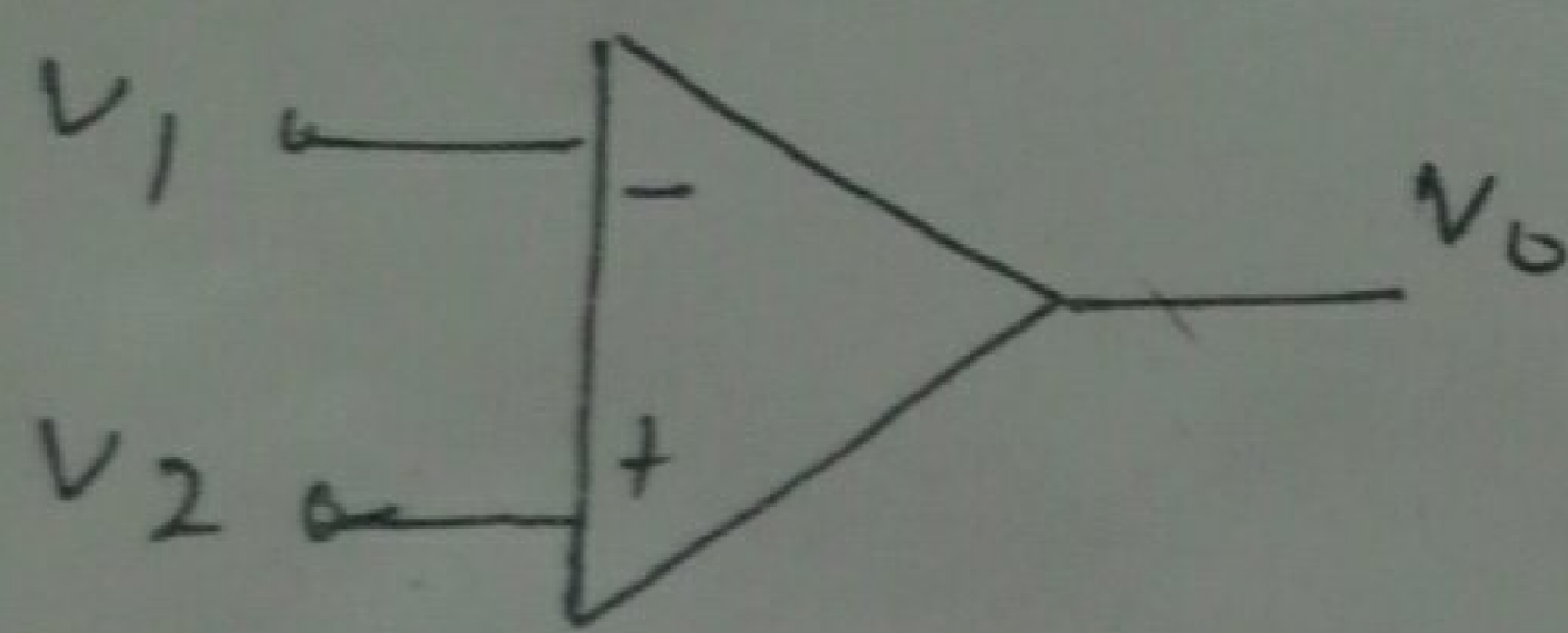

[Used in designing
of Diffⁿ. ampl^r. &
Subtractor ckts.]

Op-Amp are generally available in any one of ^{the} three following packages.

1. DIP - dual in line package.
2. TO-05 case
3. Flat - package.

Properties

Ideal op-Amp.

Practical opAmp.

Prop.

(1)	R_i	∞	10^6 or $1M\Omega$
(2)	R_o	0	10 to 100Ω
(3)	gain $A = \frac{V_o}{V_i}$	$-\infty$	-10^6 ; $ A = 10^6$ -ve sign shows 180° phase shift
(4)	B.W.	∞	10^6 Hz or $1MHz$ (Max)
(5)	CMRR	∞	10^6 or 120 dB
(6)	slew Rate	∞	80V/ μ sec.
(7)	Offset voltage	0	negligible
(8)	off-set current	0	negligible

Input Resistance in ascending order


BJT \rightarrow OP-Amp - JFET - MOSFET

(4)

- \rightarrow In practical op-amp, Gain bandwidth product is constant
- \rightarrow Max^m. bandwidth occurs when gain is minimum that is $gain = 1$
- \rightarrow The Unity Gain Bandwidth product of the op-amp is 10^6
- \rightarrow The open loop gain of the op-amp is very large & therefore stability is less and to compensate this i.e. gain is reduced by applying small amount of (-)ve feedback.
- \rightarrow closed loop gain is always less than open loop gain.
- Op-amps are generally operated in closed loop (with (-)ve feedback)
- \rightarrow Under open loop condition op-amp can be used as Comparator

COMPARATOR CKT

①

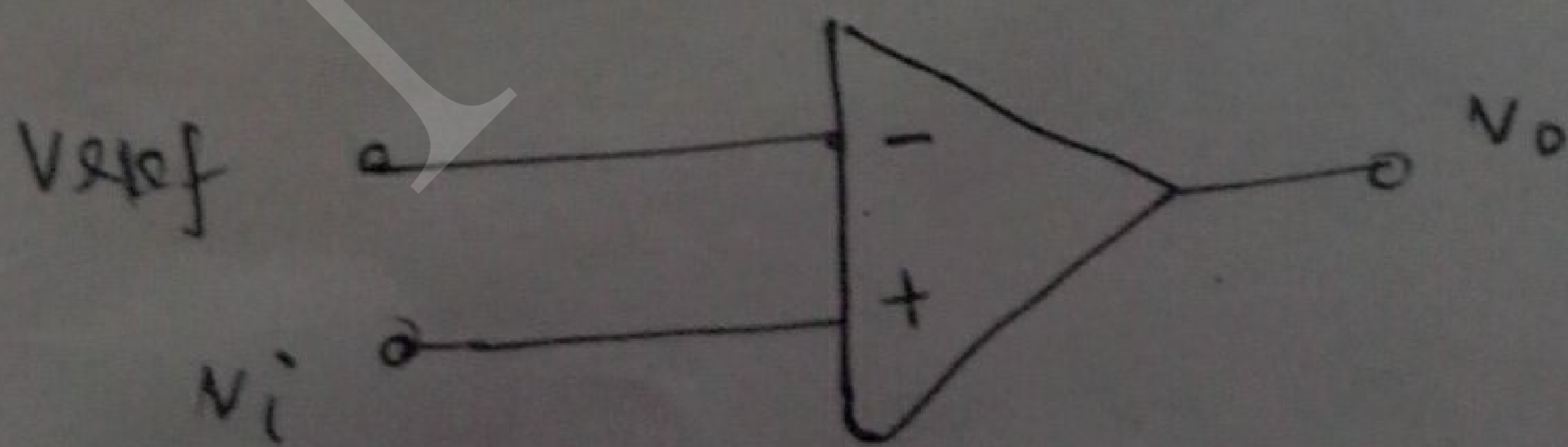


$V_o = 1$ when $V_i > V_{ref}$
 $V_o = 0$ when $V_i \leq V_{ref}$

When I/p signal is applied to the non inverting terminal, the output of comparator is logically 1 only when $V_i > V_{ref}$.

②.


$V_0 = 1$ when $V_i < V_{ref}$

$V_0 = 0$ when $V_i > V_{ref}$.

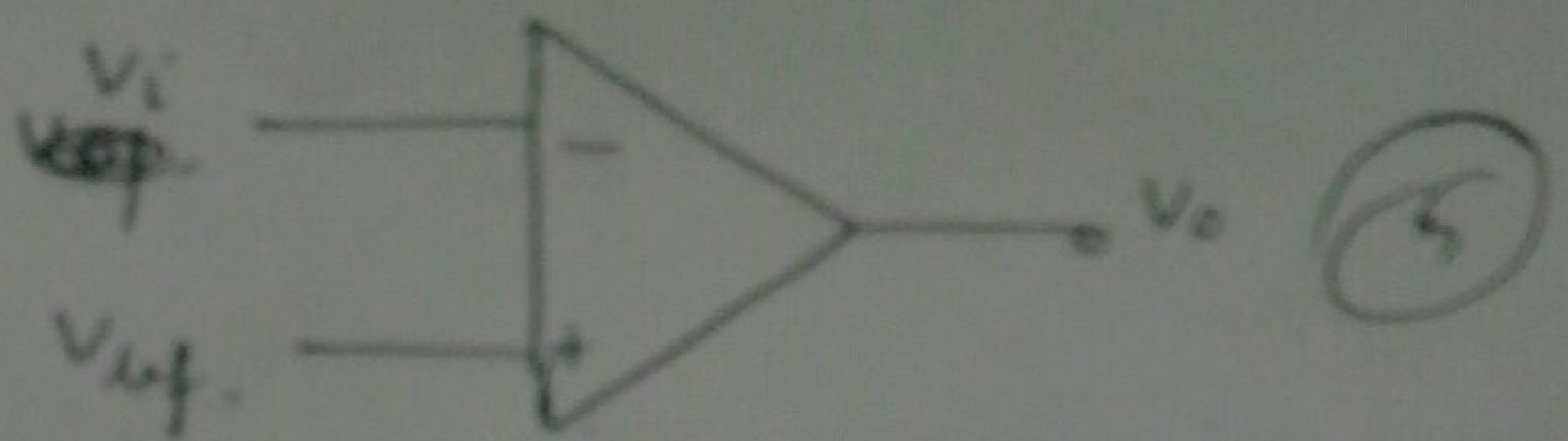

When inverting signal is applied to inverting terminal, the output of the comparator is high only when $V_i < V_{ref}$.

Des.

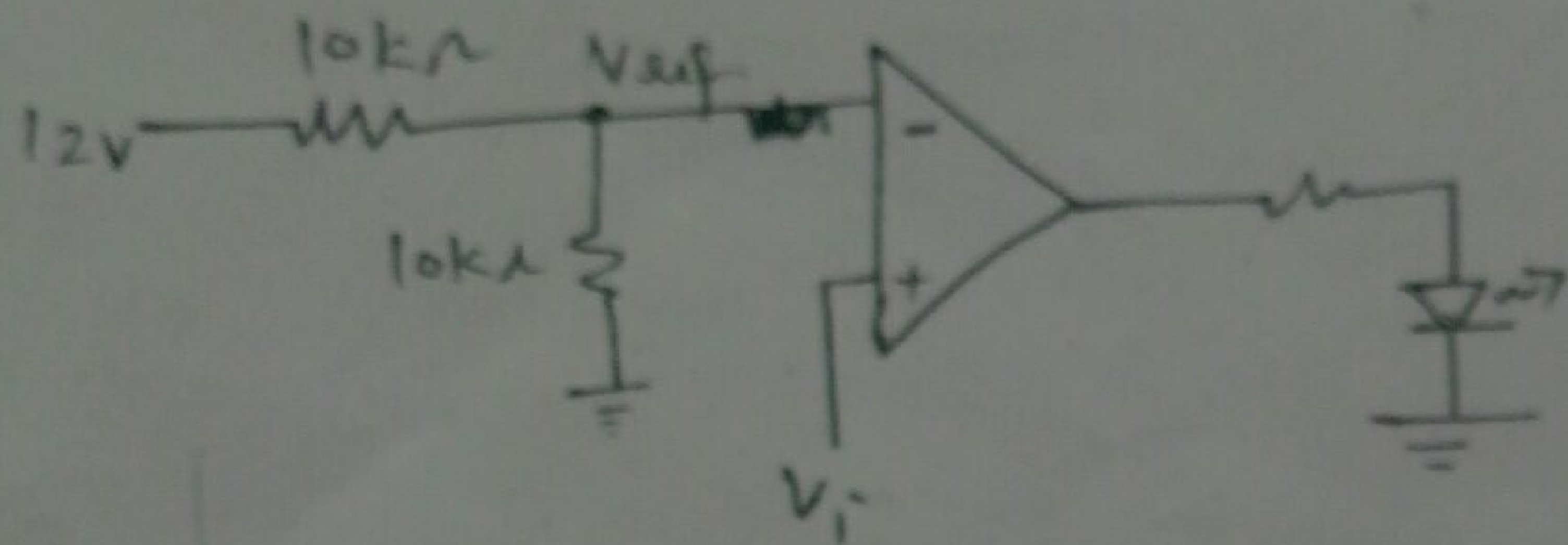


The LED will ON only when $V_i < ?$

$$V_{ref} = \frac{10k \times 12}{20k} = 6V$$

$V_i > 6V$

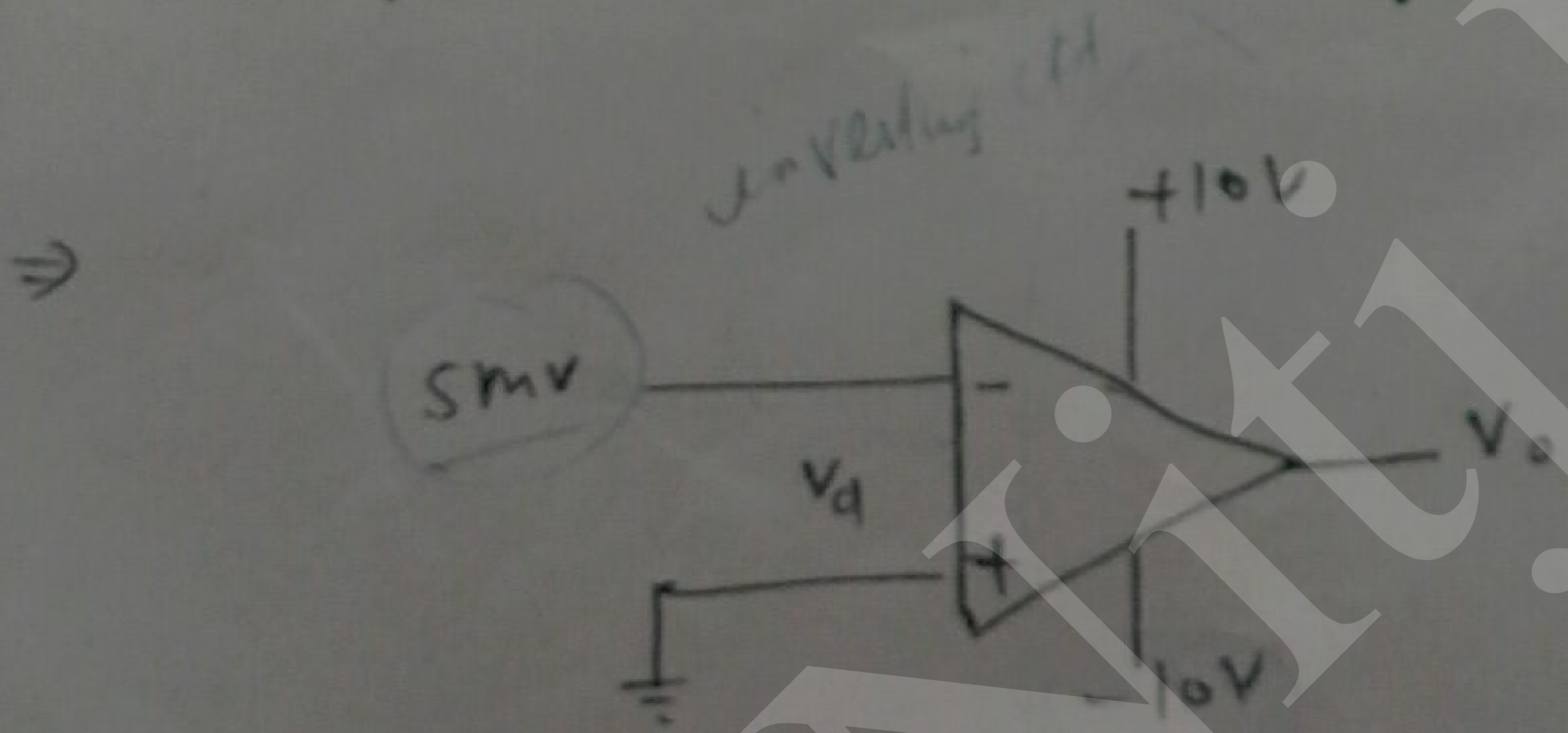
Note! - o/p voltage of a practical OP-Amp can not be exceed its bias voltage.



$|A_{ol}| = 10^6$

$$V_0 = A_{ol}(V^+ - V^-) = 10^6(0 - 5 \times 10^{-3}) = -500000V$$

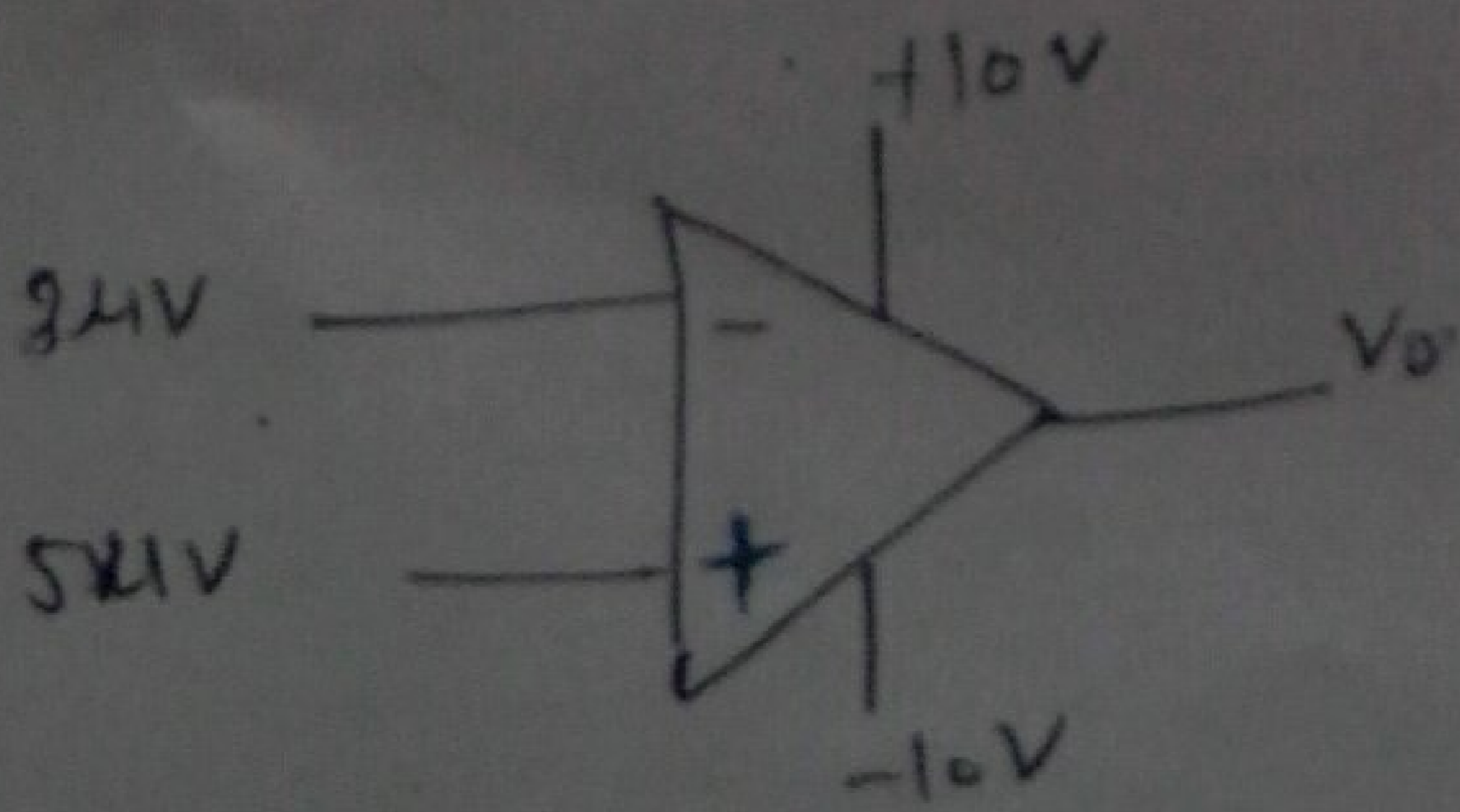but V_0 can not exceed -10
hence $V_0 = -10V$




$|A_{ol}| = 10^6$

$$V_0 = 10^6(V^+ - V^-) = 10^6(5\mu V - 2\mu V) = 10^6 \times 3 \times 10^{-6}V$$

$V_0 = 3V$

Equivalent circuit of Practical op-Amp.

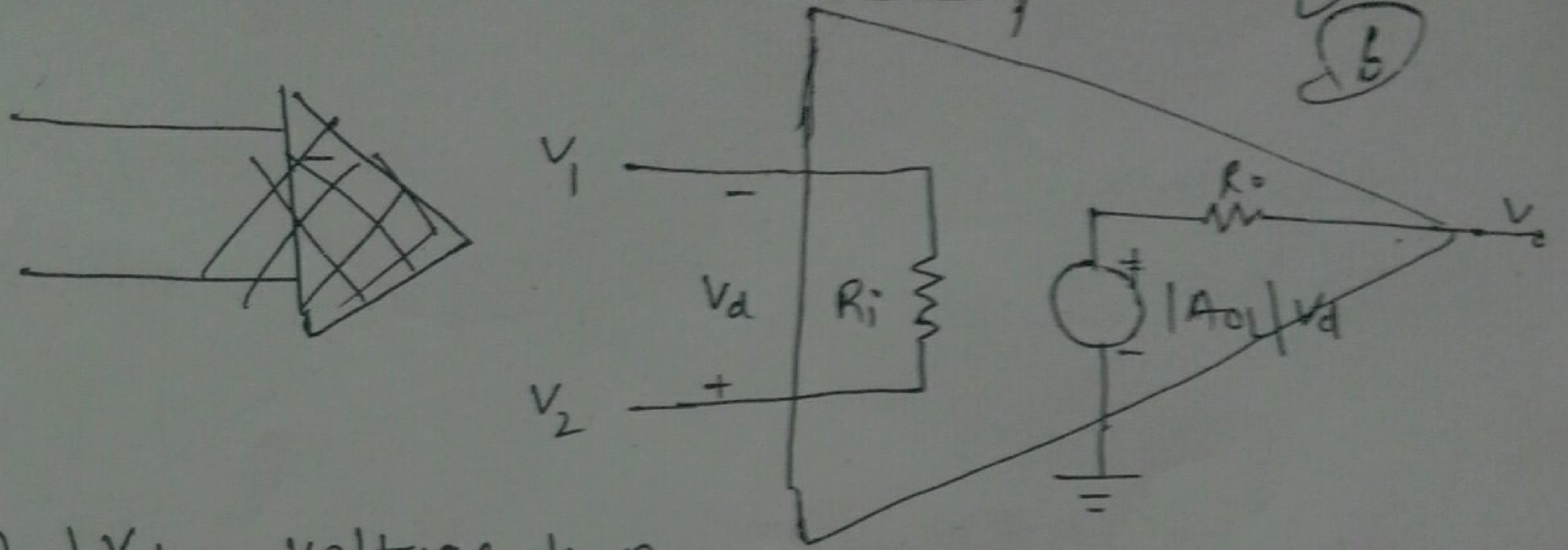


$V_0 = |A_{OL}| V_d$ - voltage drop across R_o

But R_o is very less in practical op-Amp (negligible voltage drop across R_o)


$V_0 = |A_{OL}| V_d$

Equivalent circuit of Ideal OP-Amp.

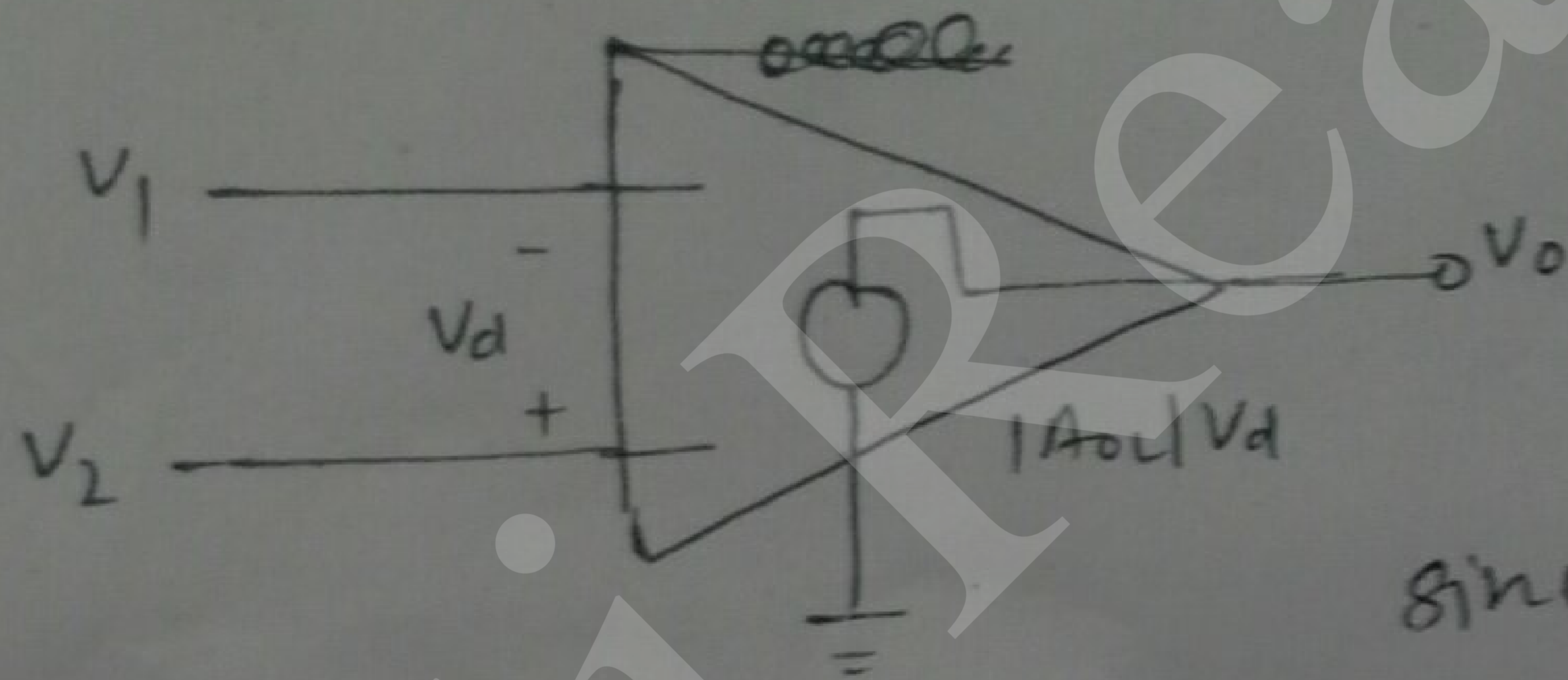

since $R_i = \infty$
 $R_o = 0$

Frequency Response of Practical OP-Amp.

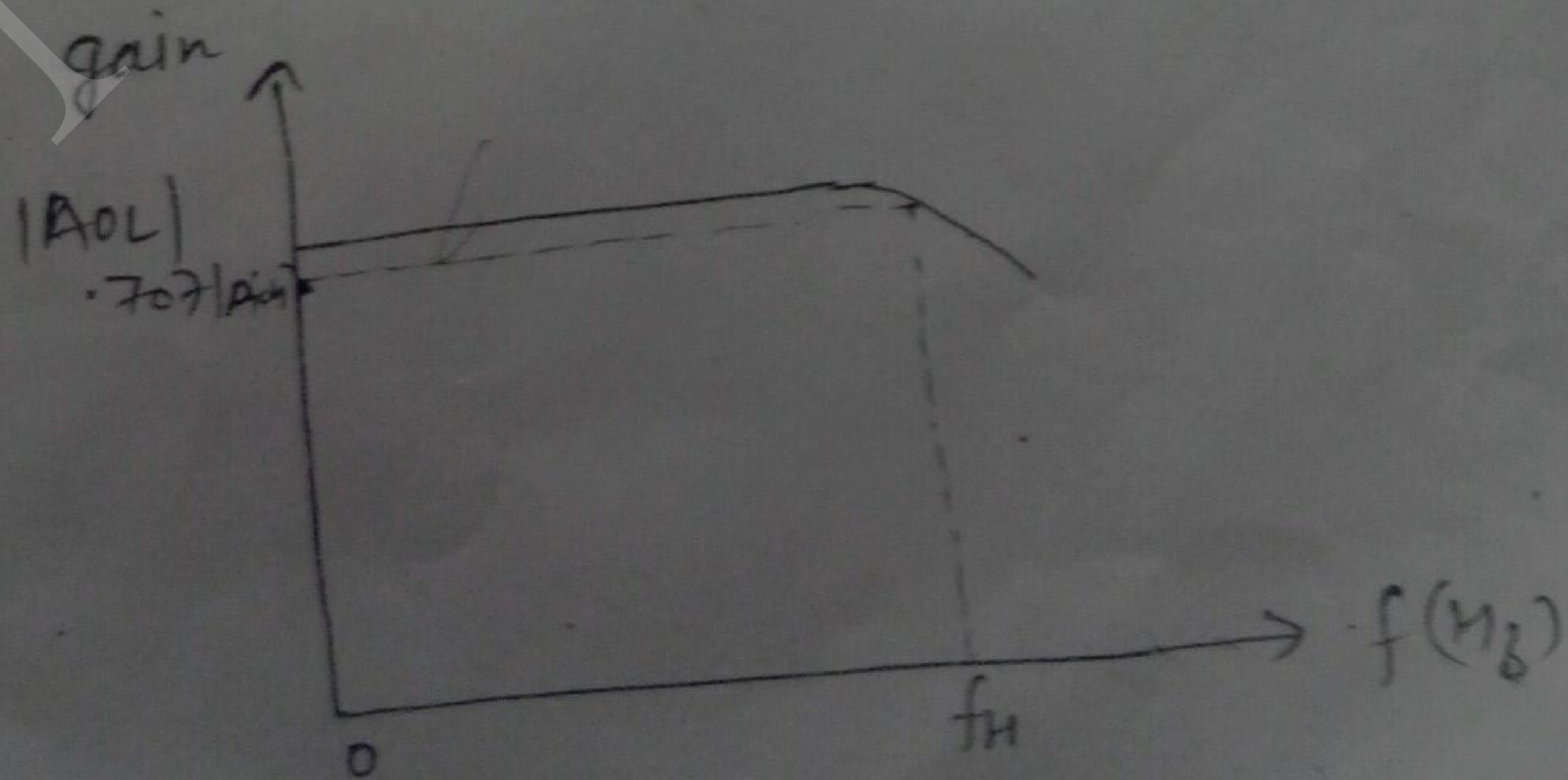

This means


It can also process D.C. signal

since $f_L = 0$ so $B.W = f_H - 0$

$B.W = f_H$

Virtual Short or virtual ground:

1st Method.

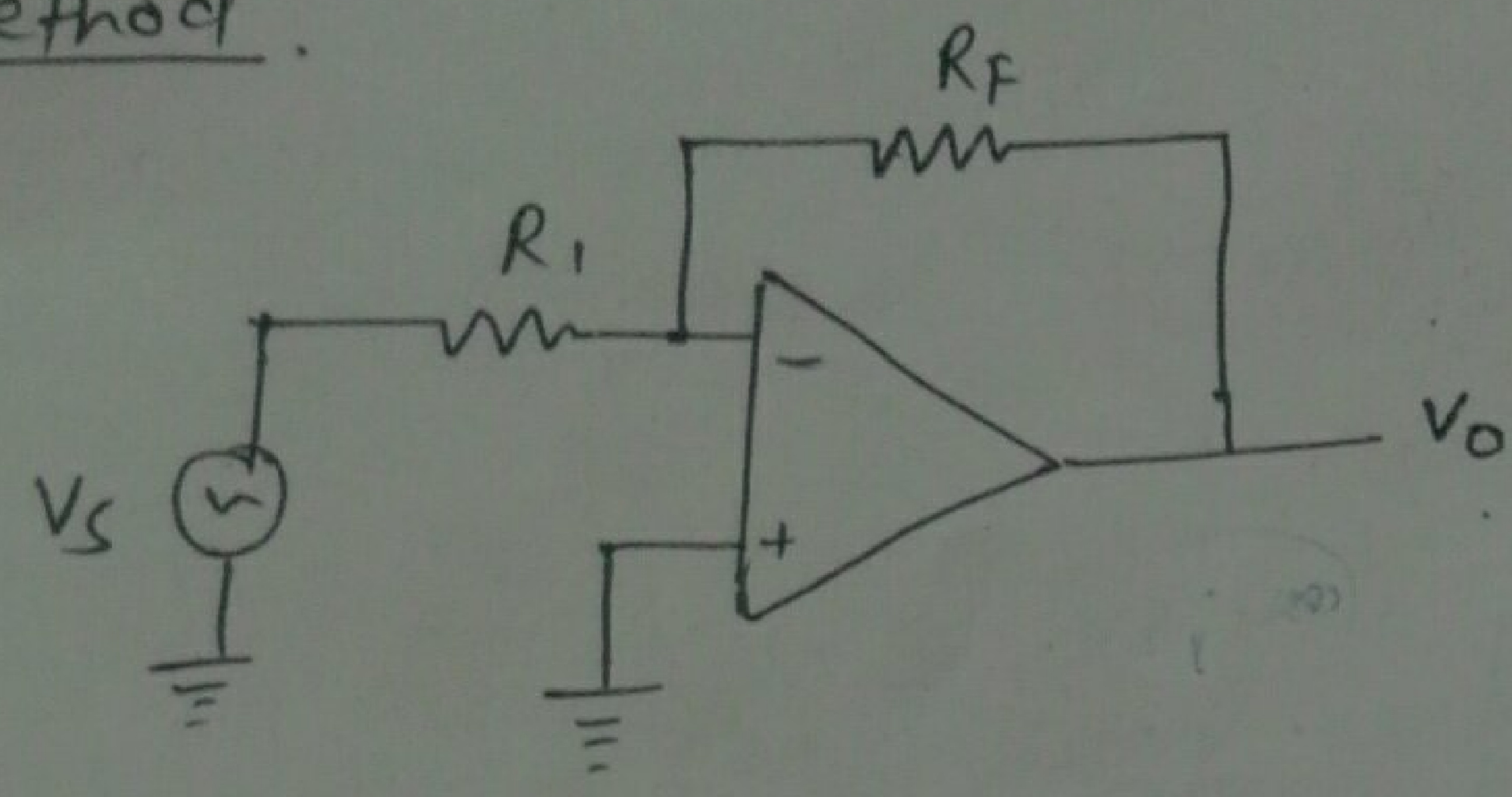


virtual short exist only in ideal op-amp.

$$\frac{V_o}{V_d} = A$$

if $A \rightarrow \infty$ (for ideal)
 $V_d \rightarrow 0$

2nd Method.

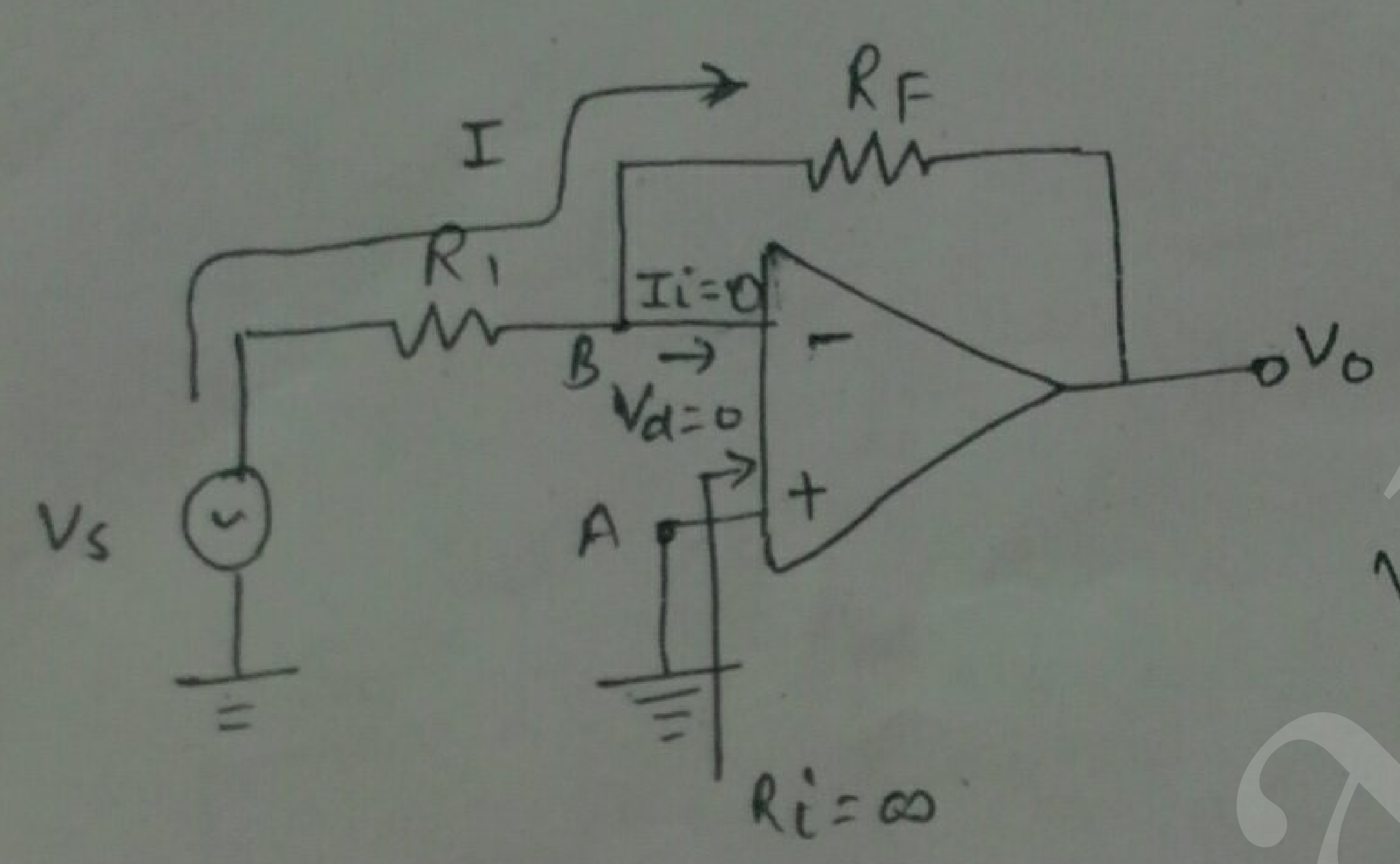

$$I = \frac{V_s - V_B}{R_1}$$

$$V_d = V^+ - V^-$$


$$0 = V^+ - V^-$$

$$V^+ = V^-$$

$$V_A = V_B$$

Node A & B are equipotential. No current passing at the inp terminal of op-amp.

INVERTING AMPLIFIER:

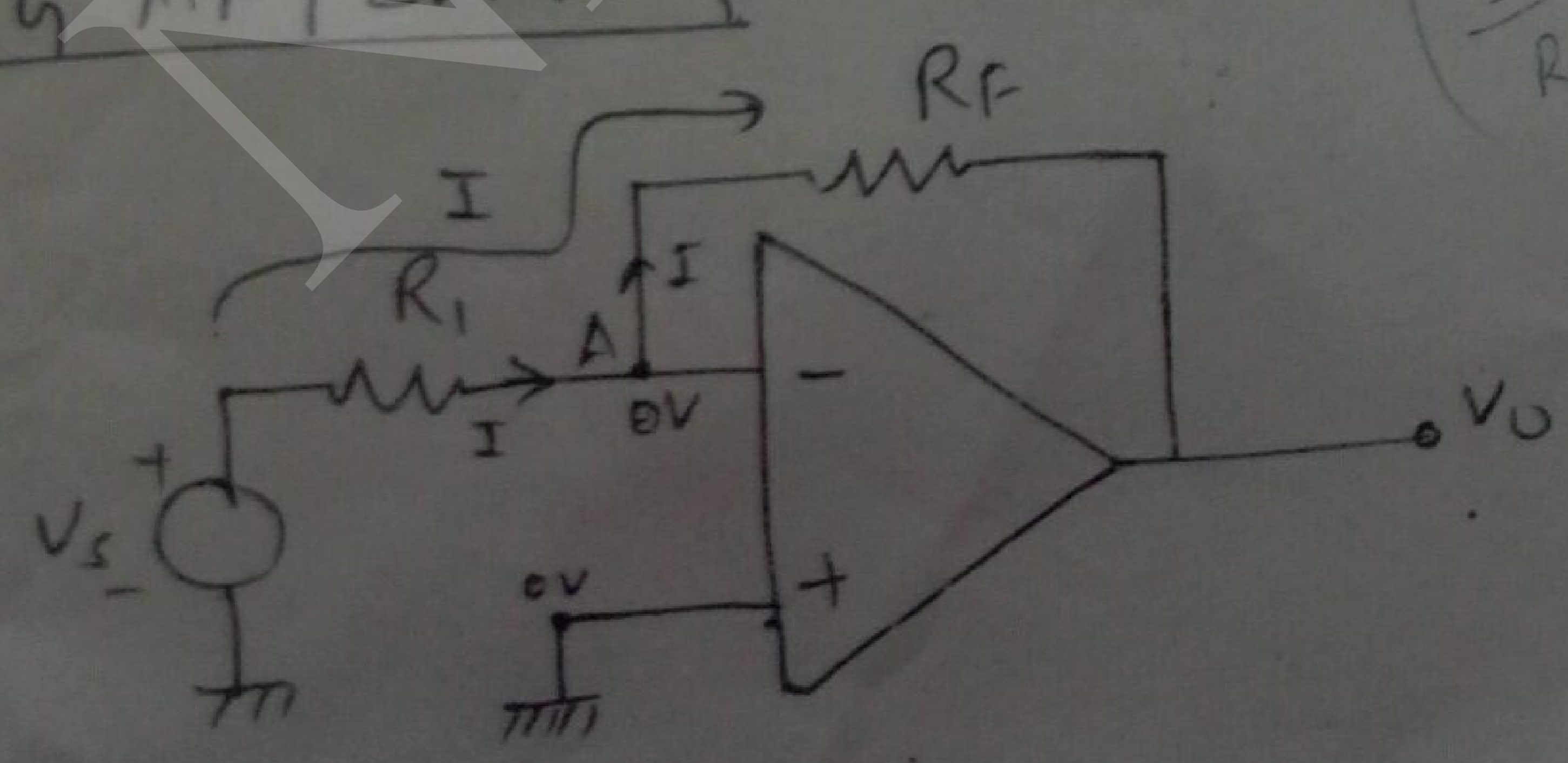

KCL at node A

$$\frac{V_s - 0}{R_1} = \frac{0 - V_o}{R_f}$$

$$\frac{V_o}{V_s} = -\frac{R_f}{R_1}$$

$$\left(\frac{V_s - 0}{R_1}\right) - \left(\frac{V_o - 0}{R_f}\right)$$

$$I - I = 0$$

$$\frac{V_s - 0}{R_1} = \frac{0 - V_o}{R_f}$$


$$\frac{V_o}{V_s} = -\frac{R_f}{R_1}$$

{ since $\frac{V_o}{V_s} = \text{gain (A)}$ }

-ve sign shows 180° phase shift

$$A = -\frac{R_f}{R_1}$$

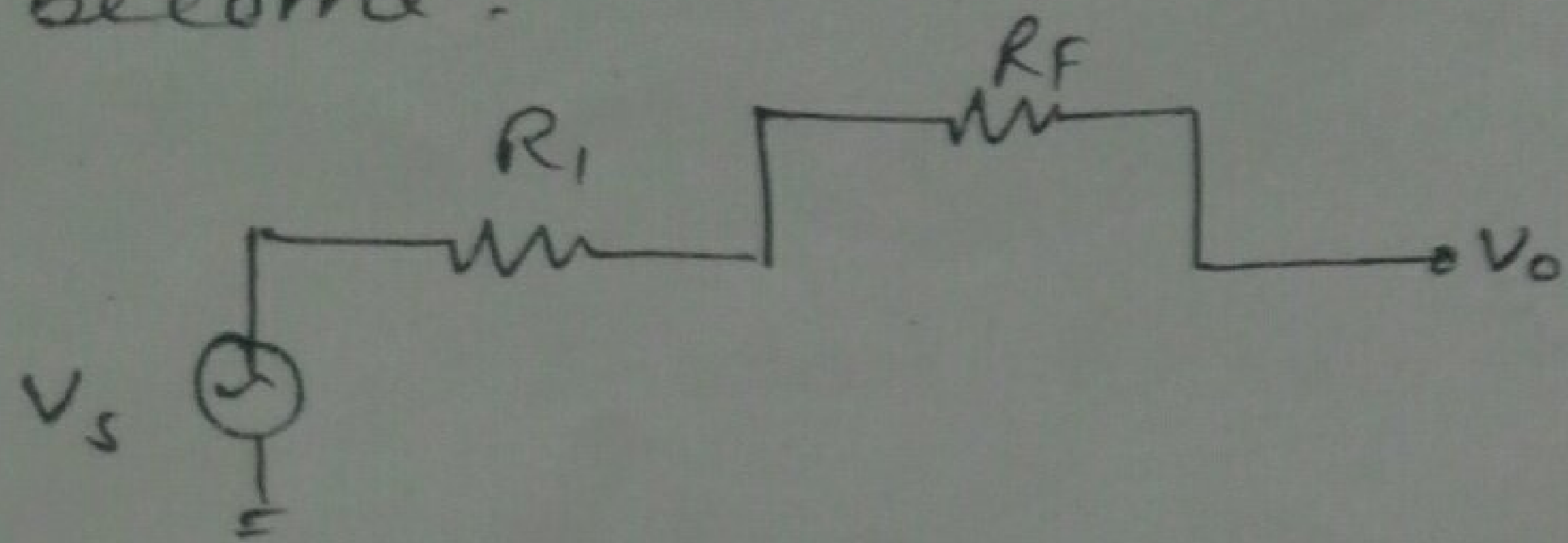
According to Eqⁿ. of gain, gain is independent of op-amp parameter, but if we remove op-amp then ckt become.



Resistive ckt can never provide gain. So it means op-amp is indirectly responding.

Inverter ckt (OR) phase shifter.

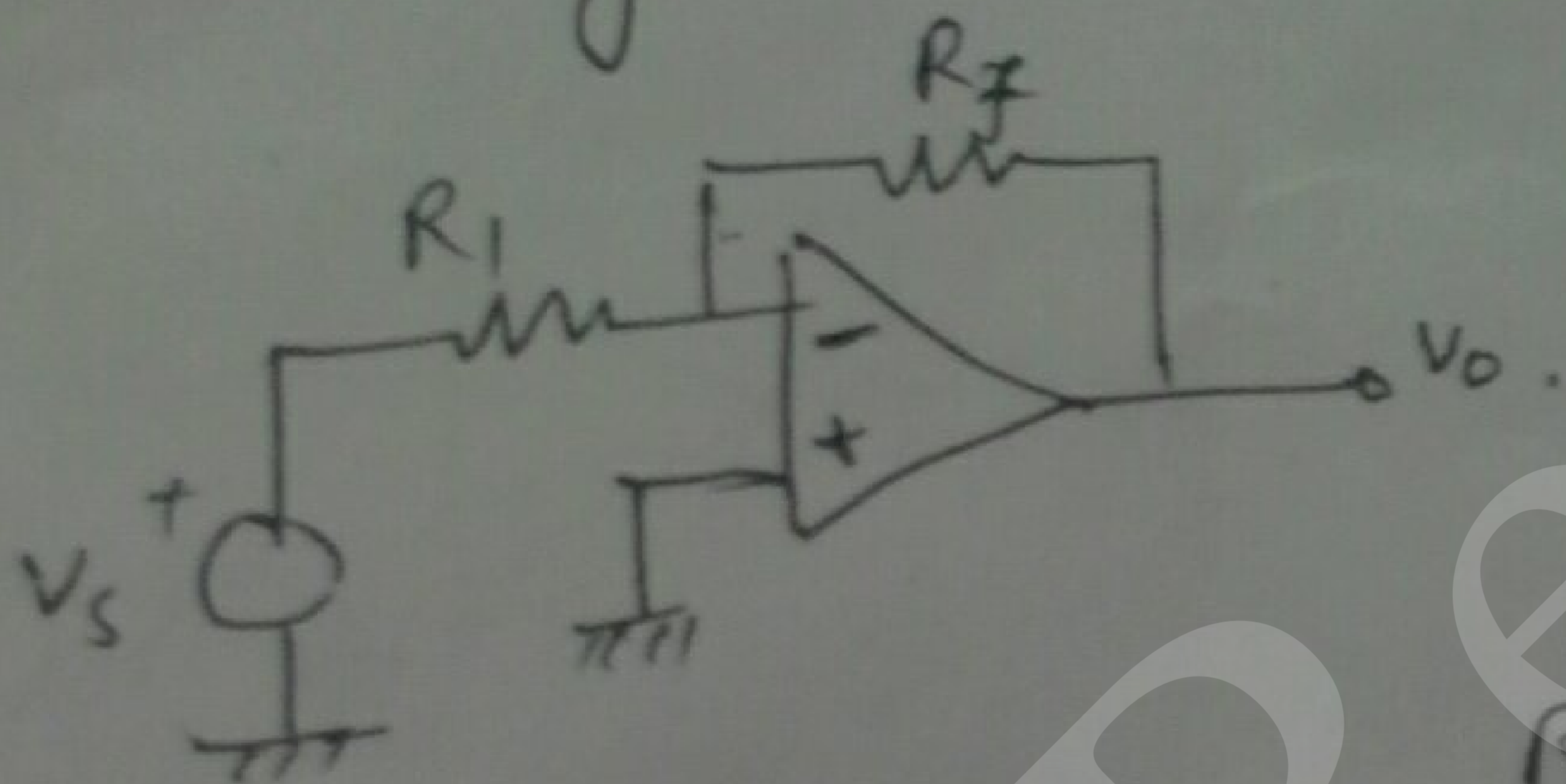It is Inverting Amplifier with unity gain.



$$A = -\frac{R_F}{R_1}$$


for unity gain

$$\frac{R_F}{R_1} = 1 \text{ OR } R_F = R_1$$

$$\frac{V_o}{V_s} = -1$$

$$V_o = -V_s$$

NON-Inverting Amplifier

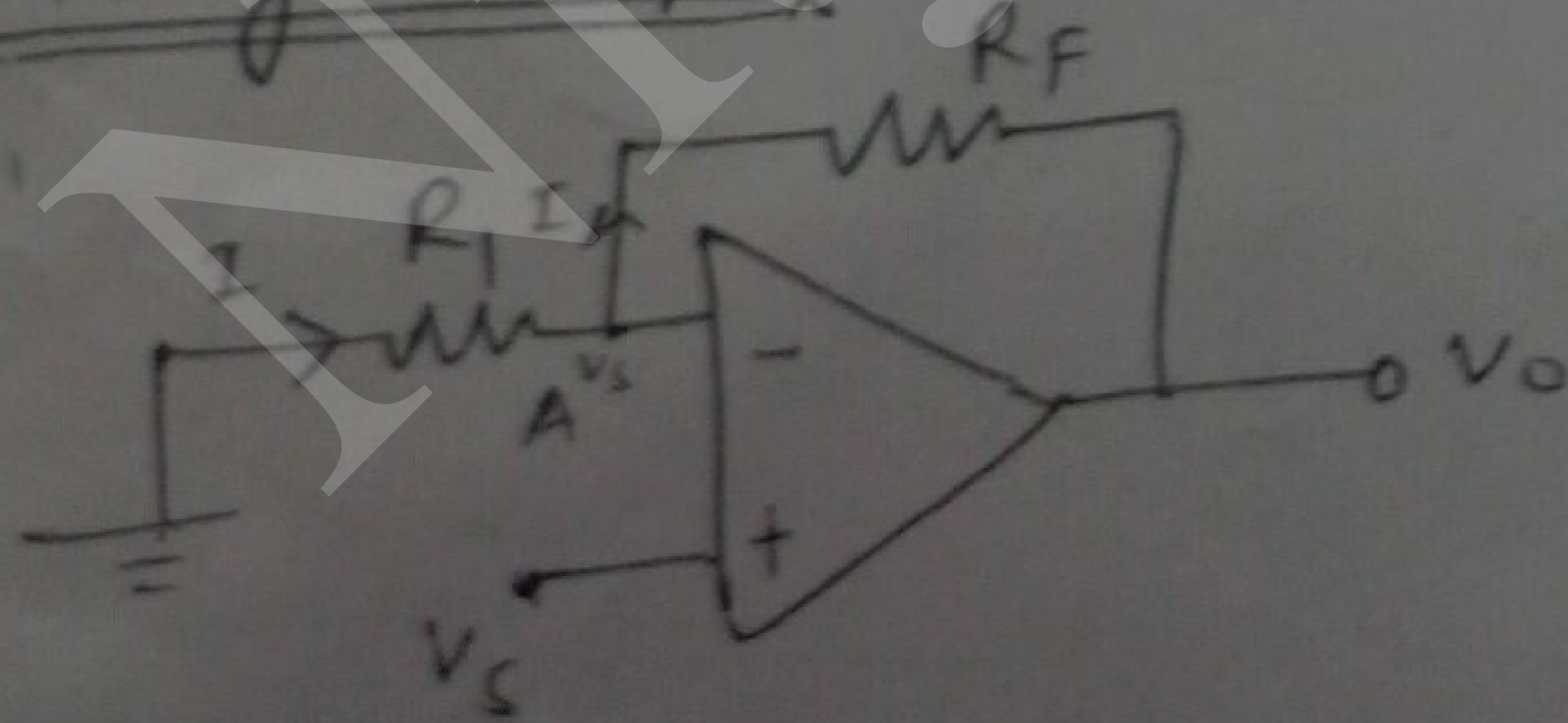

$$V_o - V_s = \frac{V_s - V_o}{R_F}$$

$$-V_s = \frac{V_s - V_o}{R_F}$$

$$V_s \left(\frac{1}{R_1} + \frac{1}{R_F} \right) = \frac{V_o}{R_F}$$

KCL at node (A)

$$\frac{0 - V_s}{R_1} = \frac{V_s - V_o}{R_F}$$

$$-\frac{V_s}{R_1} = \frac{V_s - V_o}{R_F}$$

$$\frac{V_o}{R_F} = \frac{V_s}{R_F} + \frac{V_s}{R_1}$$

$$\frac{V_o}{V_s} = R_F \left(\frac{1}{R_F} + \frac{1}{R_1} \right)$$

$$\frac{V_o}{V_s} = 1 + \frac{R_F}{R_1}$$


$$A = 1 + \frac{R_F}{R_1}$$

Voltage Follower

It is Non-inverting Amplifier with unity gain & 0 phase shift.

$$A = 1 + \frac{R_F}{R_1} = 1 \Rightarrow R_F = 0$$

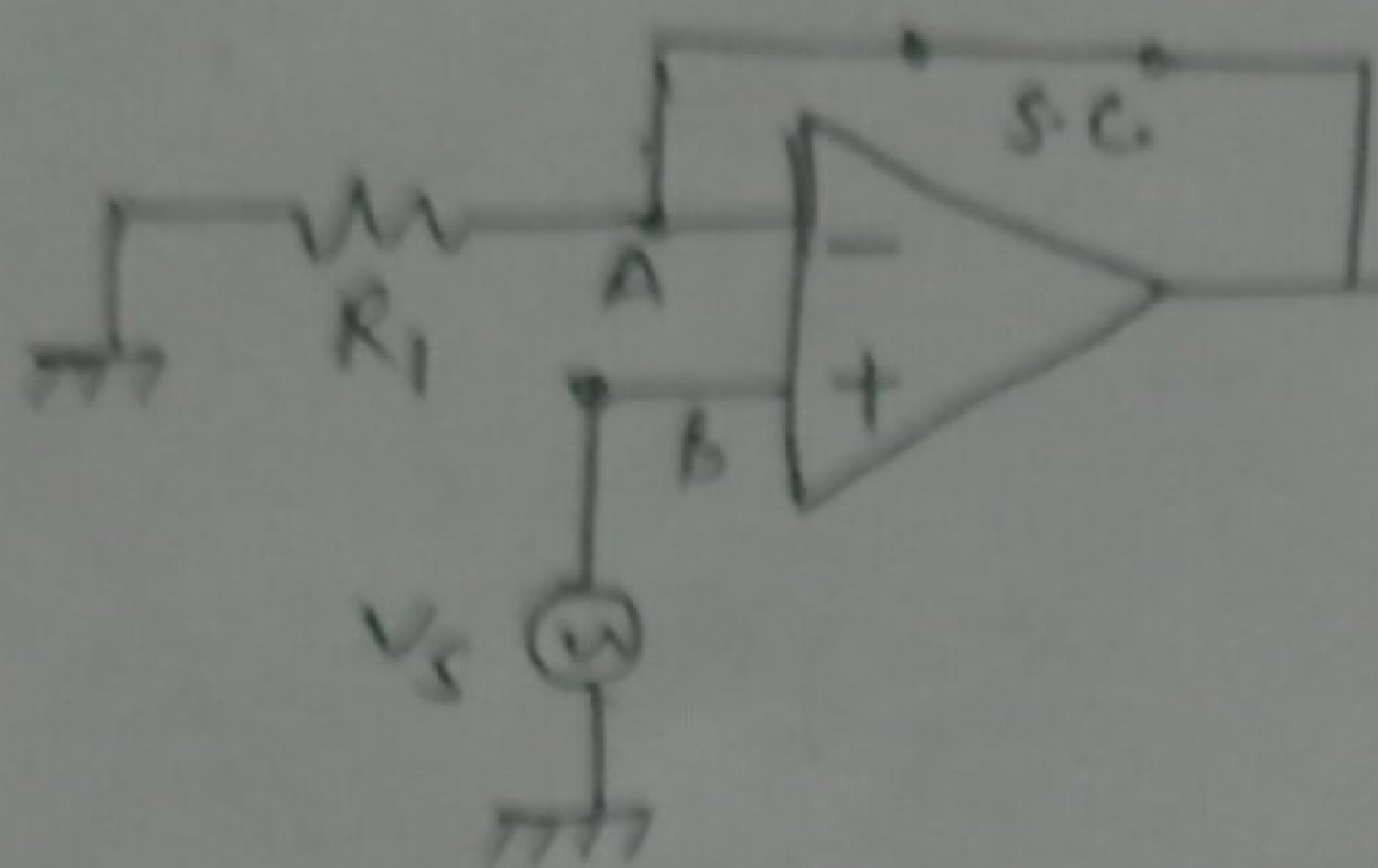If ~~asked~~ $R_F = 0$ then $1 + \frac{0}{R_1} = 1$




$$V_o = \left(1 + \frac{R_F}{R_1}\right) V_A$$

$$V_o = V_A$$


Since $V_A = V_B = V_s$

$$V_o = V_s$$

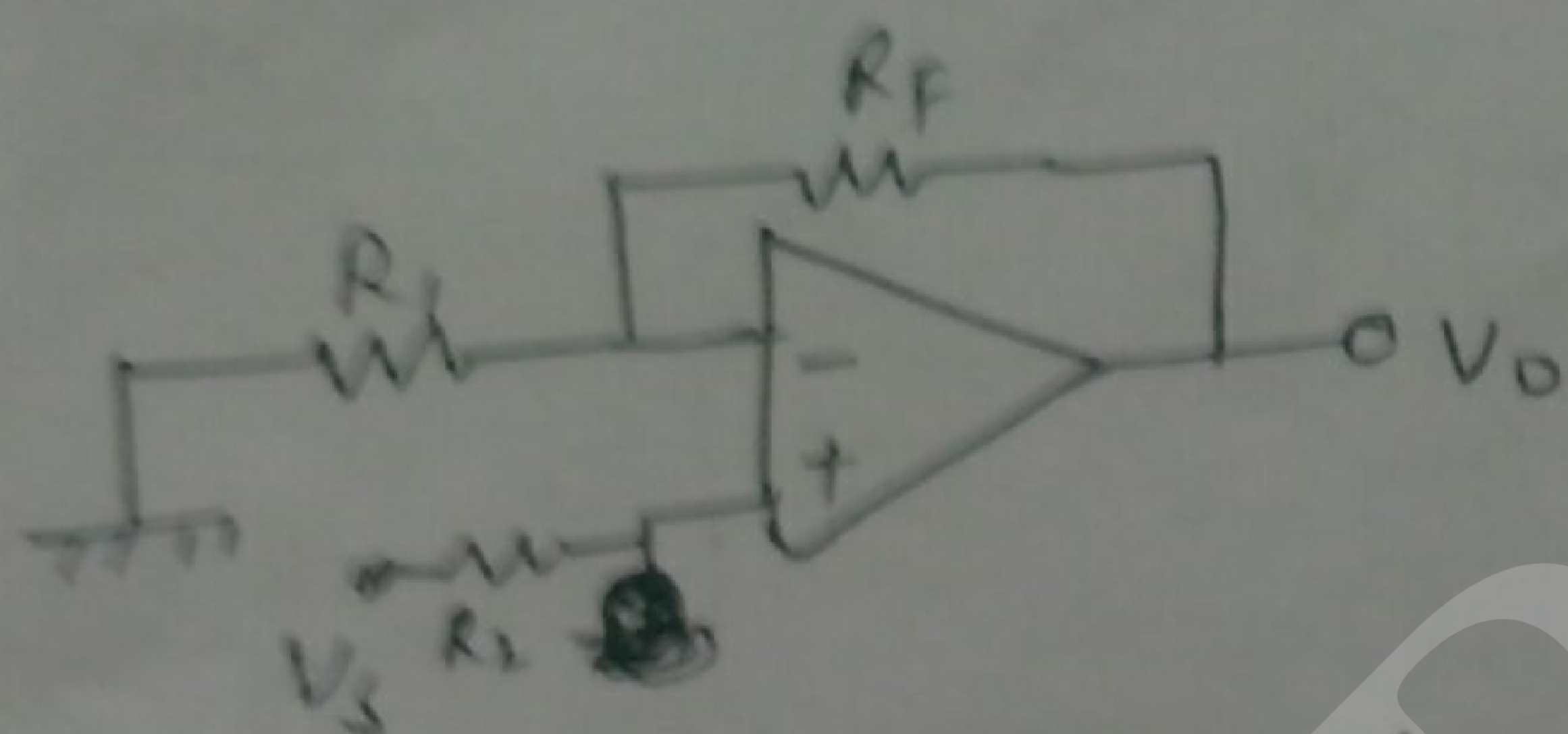O/p. voltage is reflection of i/p voltage.



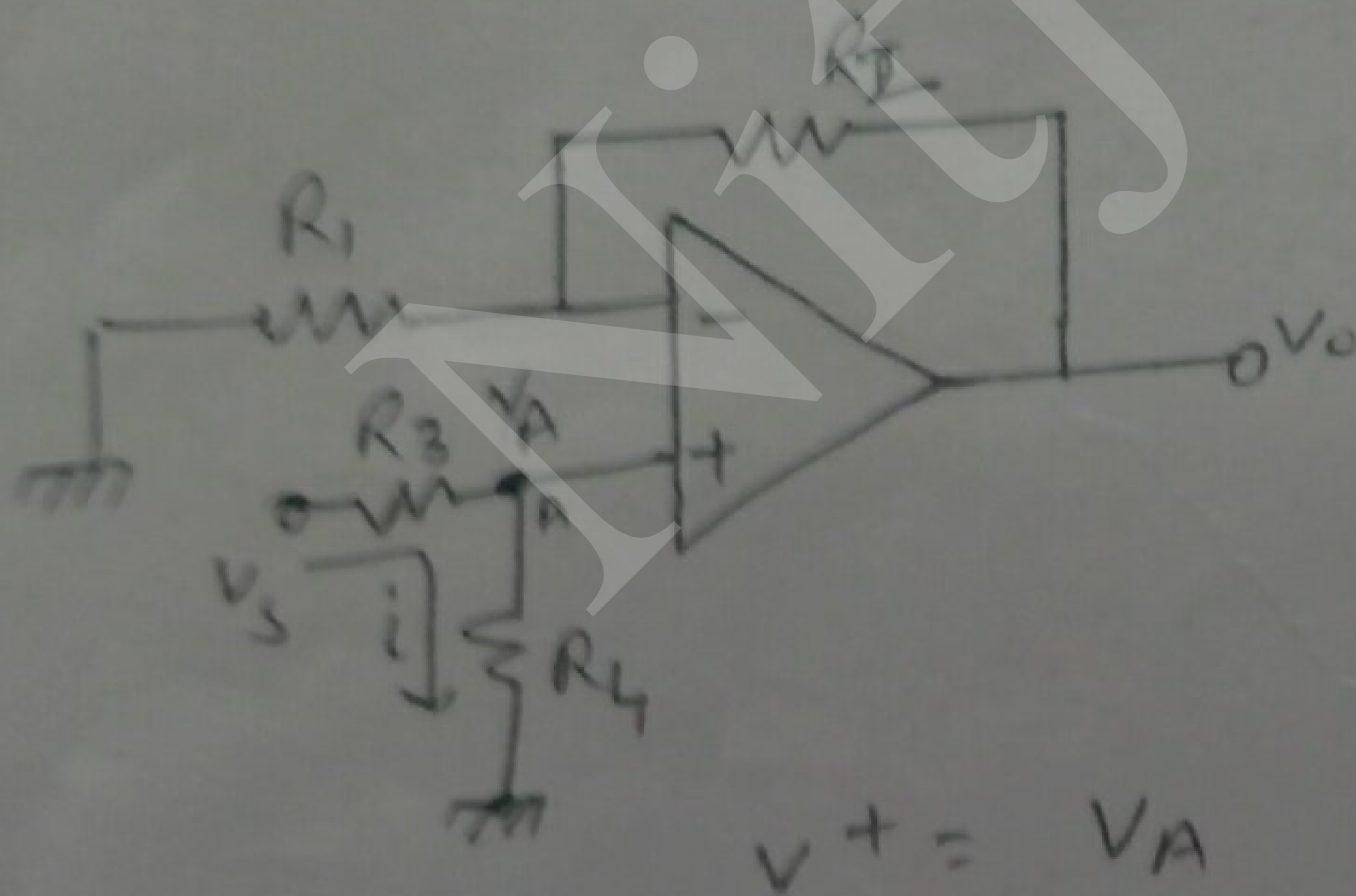Here $V^- = V_s$ (since no current flow through R_2).




$$V^+ = V_A$$

$$V_A = \left(\frac{R_4}{R_3 + R_4}\right) V_s$$

(since current flow through R_3, R_4 and to ground)

Differential Amplifier

(10)

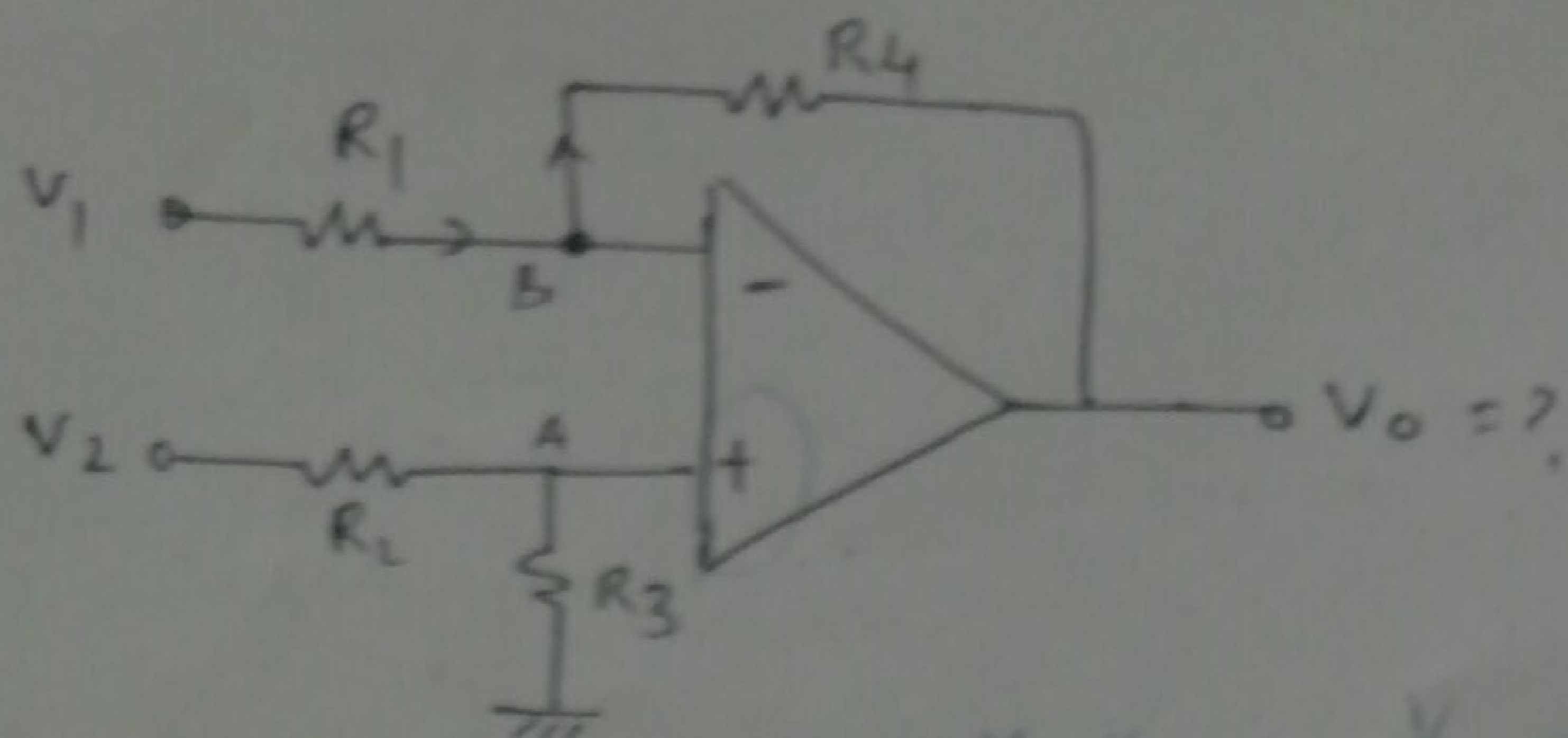

$$V_A = \left(\frac{R_3}{R_2 + R_3} \right) V_2 = V_B$$

$$\frac{V_1 - V_B}{R_1} = \frac{V_B - V_0}{R_4}$$

$$V_A = V_2 - \left(\frac{R_3}{R_2 + R_3} \right) V_2$$

KCL at B.

$$\frac{V_1 - V_B}{R_1} = \frac{V_B - V_0}{R_4}$$

$$\frac{R_4}{R_1} (V_1 - V_B) = V_B - V_0$$

$$V_0 = V_B - \frac{R_4}{R_1} V_1 + \frac{R_4}{R_1} V_B$$

$$V_0 = V_B \left(1 + \frac{R_4}{R_1} \right) - \frac{R_4}{R_1} V_1$$

gain of Non inverting i/p V2

$$V_0 = \frac{R_3}{R_2 + R_3} V_2 \left(1 + \frac{R_4}{R_1} \right) - \frac{R_4}{R_1} V_1$$

gain of Inverting i/p (V1)

$$V_0 = \frac{R_3}{R_1} \left[\frac{R_1 + R_4}{R_2 + R_3} \right] V_2 - \frac{R_4}{R_1} V_1$$

Approximated method apply lineal or superposition law.

$$V_0(-) = - \frac{R_4}{R_1} V_1$$

$$V_0(+)$$

$$\text{while } V_A = \left(\frac{R_3}{R_2 + R_3} \right) V_2$$

$$V_0(+)$$

$$V_0 = V_0(-) + V_0(+)$$

$$V_0 = - \frac{R_4}{R_1} V_1 + \left(1 + \frac{R_4}{R_1} \right) \left(\frac{R_3}{R_2 + R_3} \right) V_2$$


Note: if $R_1 = R_2 = R_3 = R_4$ (In the above ckt)

$$V_0 = -V_1 + V_2 \Rightarrow \boxed{V_2 - V_1 = V_0}$$

Then the circuit is called SUBTRACTOR

(11)

SUBTRACTOR

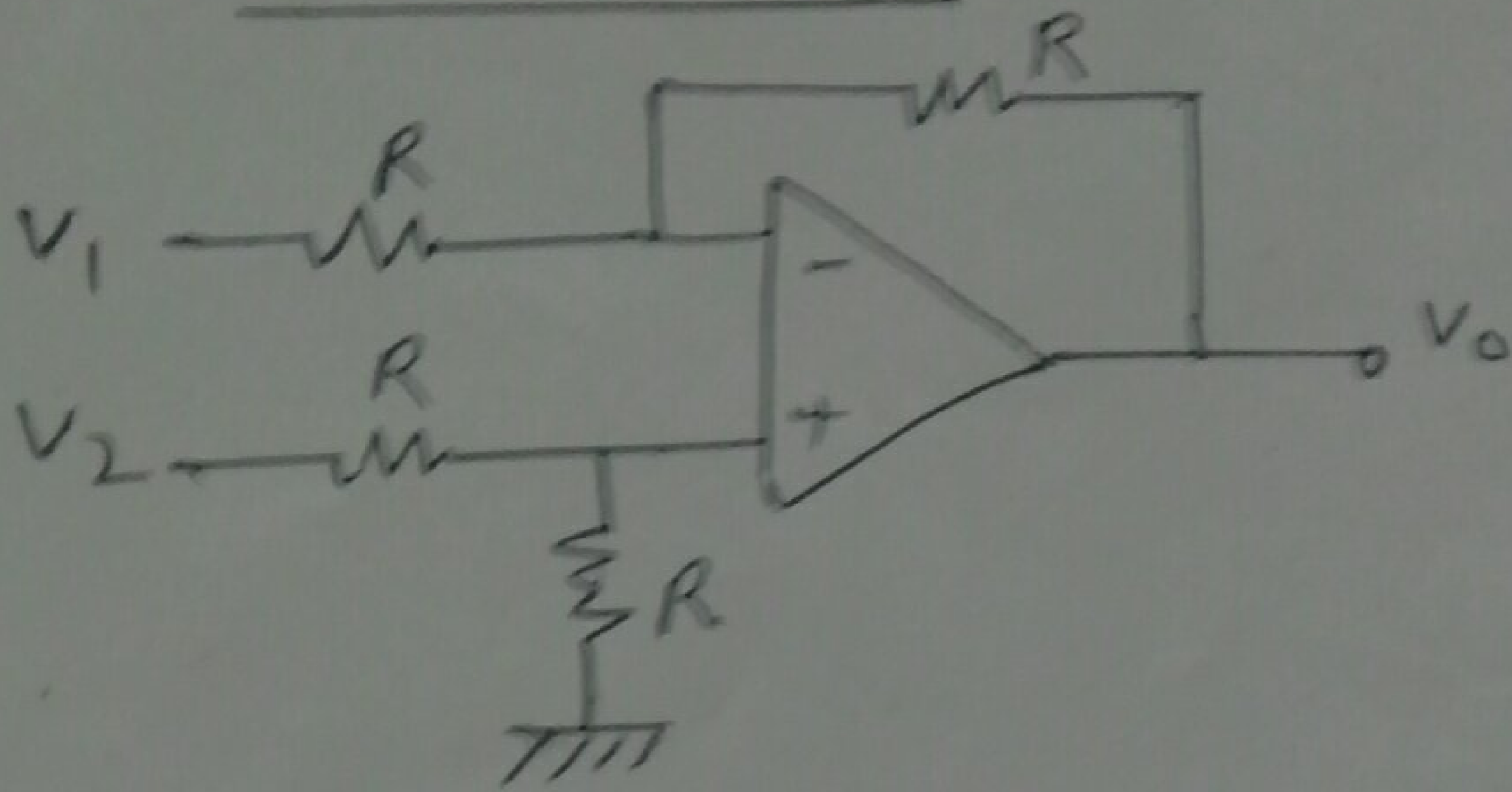

(11)


Subtractor is modification of differential Amplifier with identical Resistor.

Nij Reader

Ques

find v_o for given ckt.

12

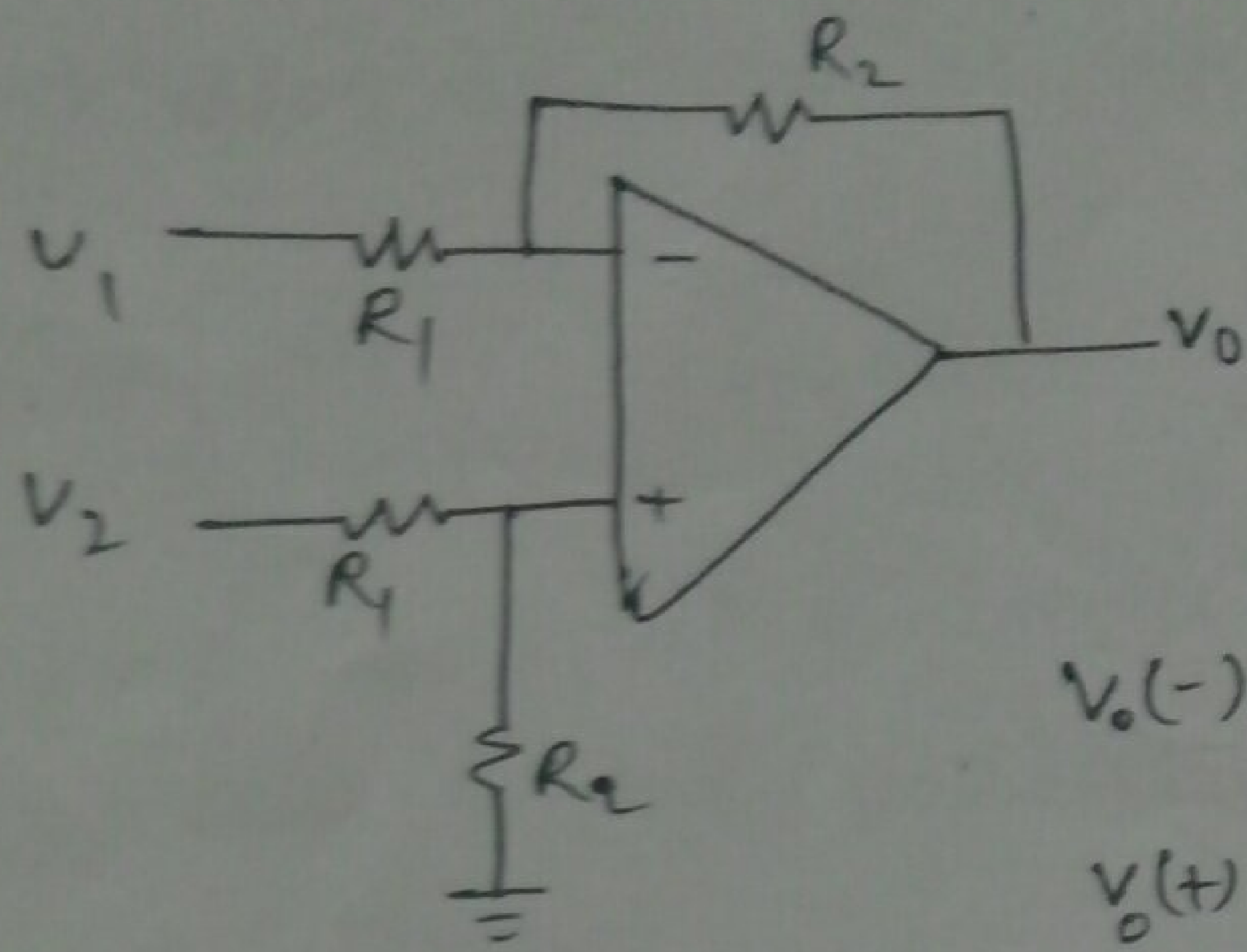

$$V_o(-) = -R_2/R_1 V_1$$


$$V_o(+) = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_2$$

$$V_o(t) = \frac{(R_1 + R_2)}{R_1} \times \frac{R_2}{(R_1 + R_2)} V_2 = \frac{R_2 V_2}{R_1}$$

$$V_o = \frac{R_2 V_2}{R_1} - \frac{R_2 V_1}{R_1}$$


$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

Ques

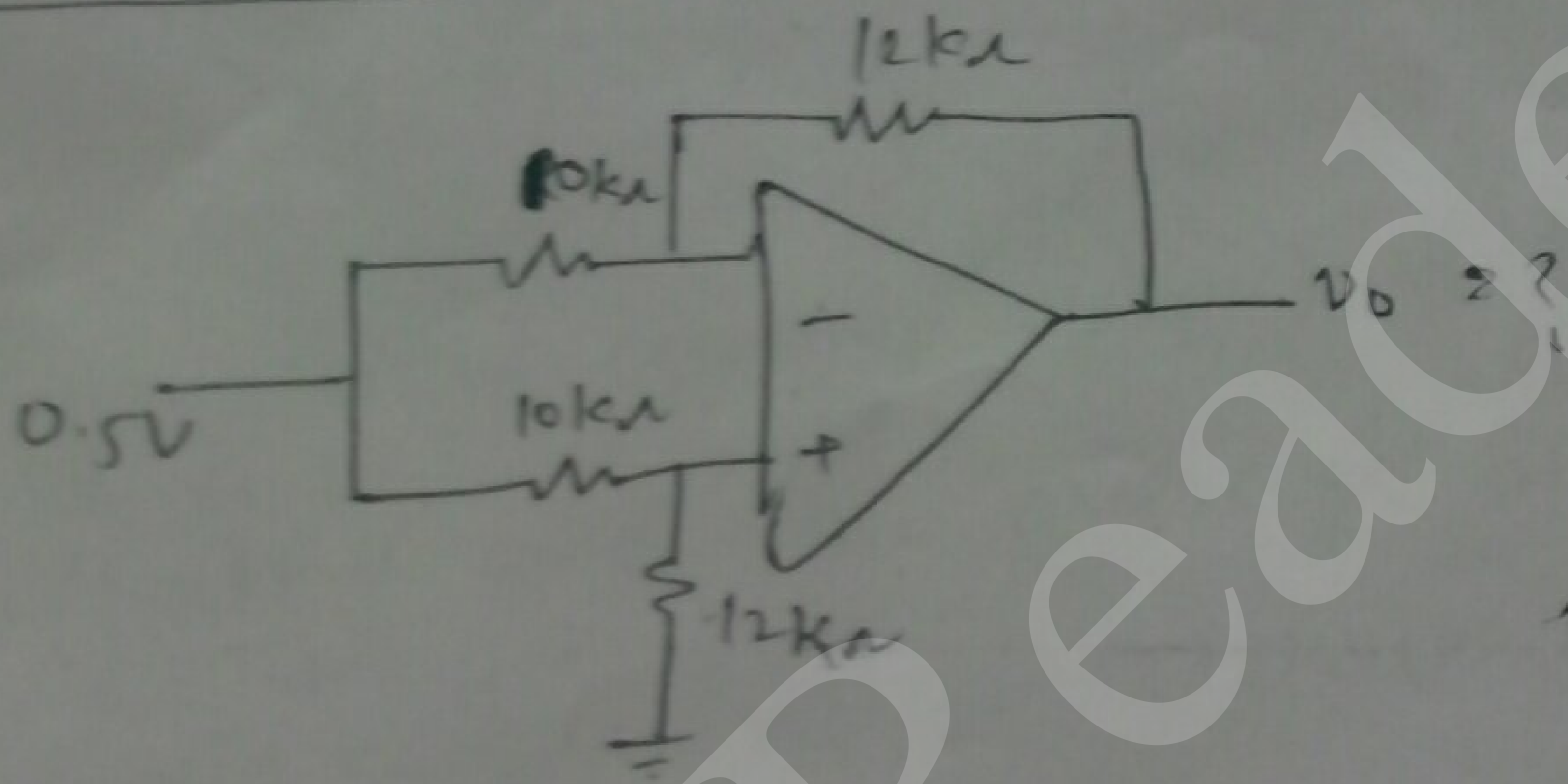

$$V_o = 0$$

Ques

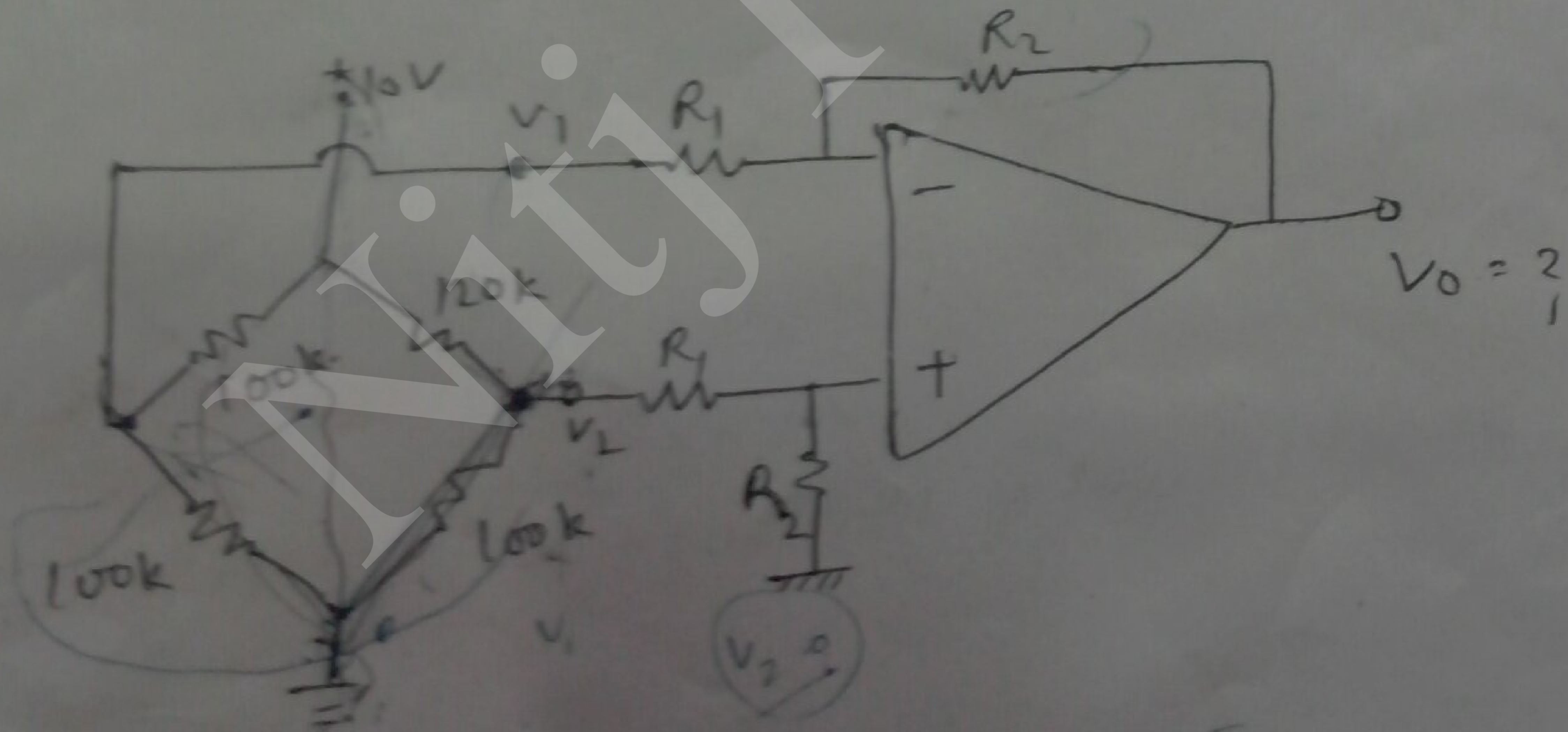

$$V_1 = \left(\frac{100k}{200k}\right) \times 10$$


$$V_2 = \left(\frac{100k}{220k}\right) \times 10$$

$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

$$V_o = \frac{R_2}{R_1} \left(\frac{100k}{220k} - \frac{100k}{200k}\right) 10$$

CMMR (Common mode Rejection Ratio)

Consider block diagram of an op-amp.

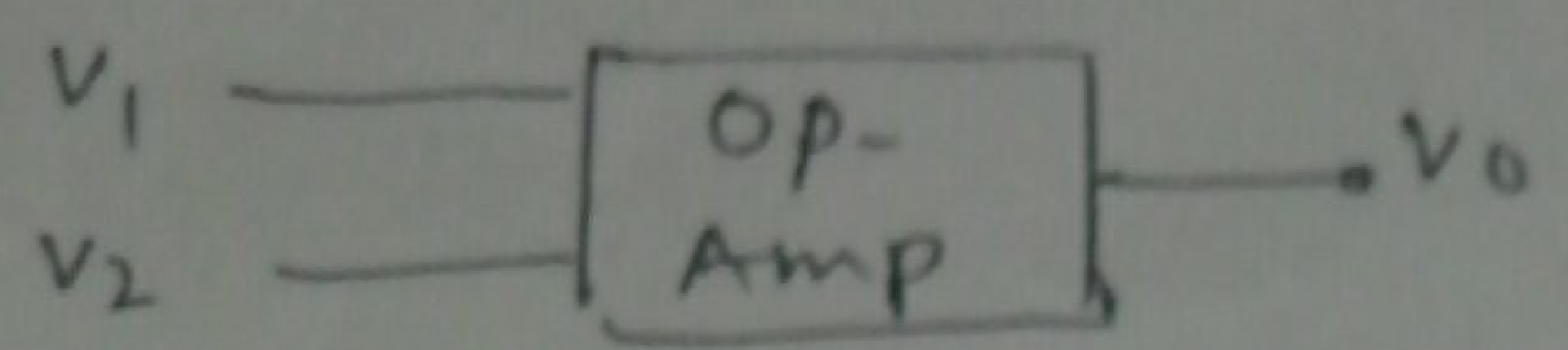

13

In Ideal op-amp output voltage depends only on the difference of the input voltages. If $v_1 = v_2$, then v_0 reduce to zero.

Ideal opAmp.

v_0 is function of $(v_1 - v_2)$

if $v_1 = v_2$ $v_0 = 0$

In a practical op-amp output voltage is a function of the difference and the average of the two voltage hence if $v_1 = v_2$, v_0 never reduce to zero.


In practical op-amp.

v_0 is function of $(v_1 - v_2) + \frac{v_1 + v_2}{2}$

if $v_1 = v_2$ $v_0 \neq 0$

By applying superposition principle to the practical

op-amp.

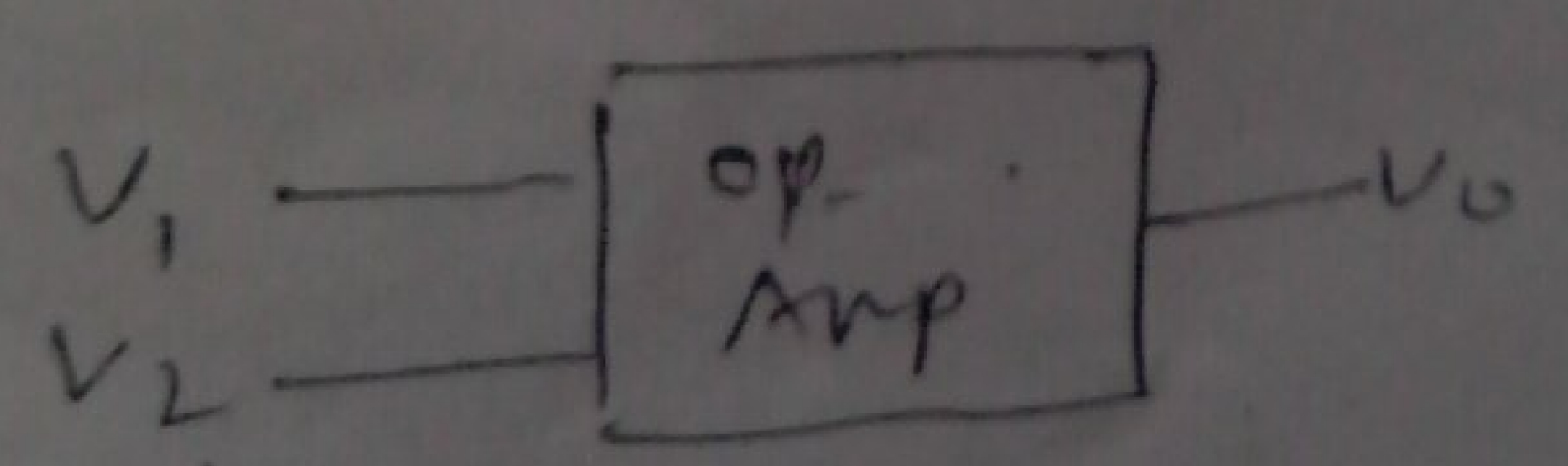

$$v_0 = A_1 v_1 + A_2 v_2 \quad \text{--- (1)}$$

A_1 - gain for I/p v_1 , when $v_2 = 0$

A_2 = gain for I/p v_2 , when $v_1 = 0$

48

Diffⁿ I/p signal $v_d = v_1 - v_2$ — (2)

Common mode signal voltage

$$v_c = \frac{v_1 + v_2}{2} \quad \text{--- (3)}$$

Solving eqⁿ. (2) & (3)

$$v_1 = v_c + \frac{v_d}{2}$$

$$v_2 = v_c - \frac{v_d}{2}$$

Substituting v_1 & v_2 in eqⁿ No. (1)

$$v_o = A_1 \left(v_c + \frac{v_d}{2} \right) + A_2 \left(v_c - \frac{v_d}{2} \right)$$

$$= A_1 v_c + A_1 \frac{v_d}{2} + A_2 v_c - A_2 \frac{v_d}{2}$$

$$v_o = v_c [A_1 + A_2] + \frac{v_d}{2} [A_1 - A_2]$$

$$v_o = |A_c| \cdot v_c + |A_d| \cdot v_d$$

$$\begin{cases} A_d = \frac{1}{2}(A_1 - A_2) \\ A_c = A_1 + A_2 \end{cases}$$

Eqⁿ. for output voltage of practical op-amp.

$$A_c = A_1 + A_2 \rightarrow \text{Common mode gain}$$

$$A_d = \frac{A_1 - A_2}{2} \rightarrow \text{Differential mode gain}$$

CMRR is denoted by ρ & is defined as the Ratio of differential mode gain to the common mode gain taken in magnitude.

$$CMRR = \rho = \left| \frac{A_d}{A_c} \right|$$

For Ideal op-amp. Common mode gain $A_c = 0$ so for

Ideal op-amp. $CMRR = \infty$

For better performance CMRR must be larger. For OP-Amp CMRR is called the Figure of merit (FOM) for ideal op-Amp

$$\boxed{FOM = \infty}$$

(15)

CMRR can be expressed in dB. as

$$\beta = 20 \log \left| \frac{A_d}{A_c} \right| = 20 \log A_d - 20 \log A_c$$

CMRR can also be defined as the ability of the op-Amp to reject the common mode signal.

For practical op-Amp CMRR is 106 or 120 dB.

Ques: Practical op-Amp $A_c = 10 \text{ dB}$, $A_d = 60 \text{ dB}$, CMRR = ?

$$\text{CMRR} = 60 - 10 = 50 \text{ dB}$$

Ques: A practical op-Amp having $A_d = 100$, $A_c = -0.1$ is operated with IP voltages $1050 \mu\text{V}$ & $950 \mu\text{V}$

Calculate CMRR, & V_o ?

$$\text{CMRR} = 60 \text{ dB}$$


$$V_d = V_1 - V_2 = 1050 - 950 = 100 \mu\text{V}$$

$$V_c = \frac{V_1 + V_2}{2} = \frac{1050 + 950}{2} = 1000 \mu\text{V}$$

$$V_o = |A_d| V_d + |A_c| V_c = 100 \times 100 \mu\text{V} + 0.1 \times 1000 \mu\text{V}$$

$$\boxed{V_o = 10.1 \text{ mV}}$$

Ques

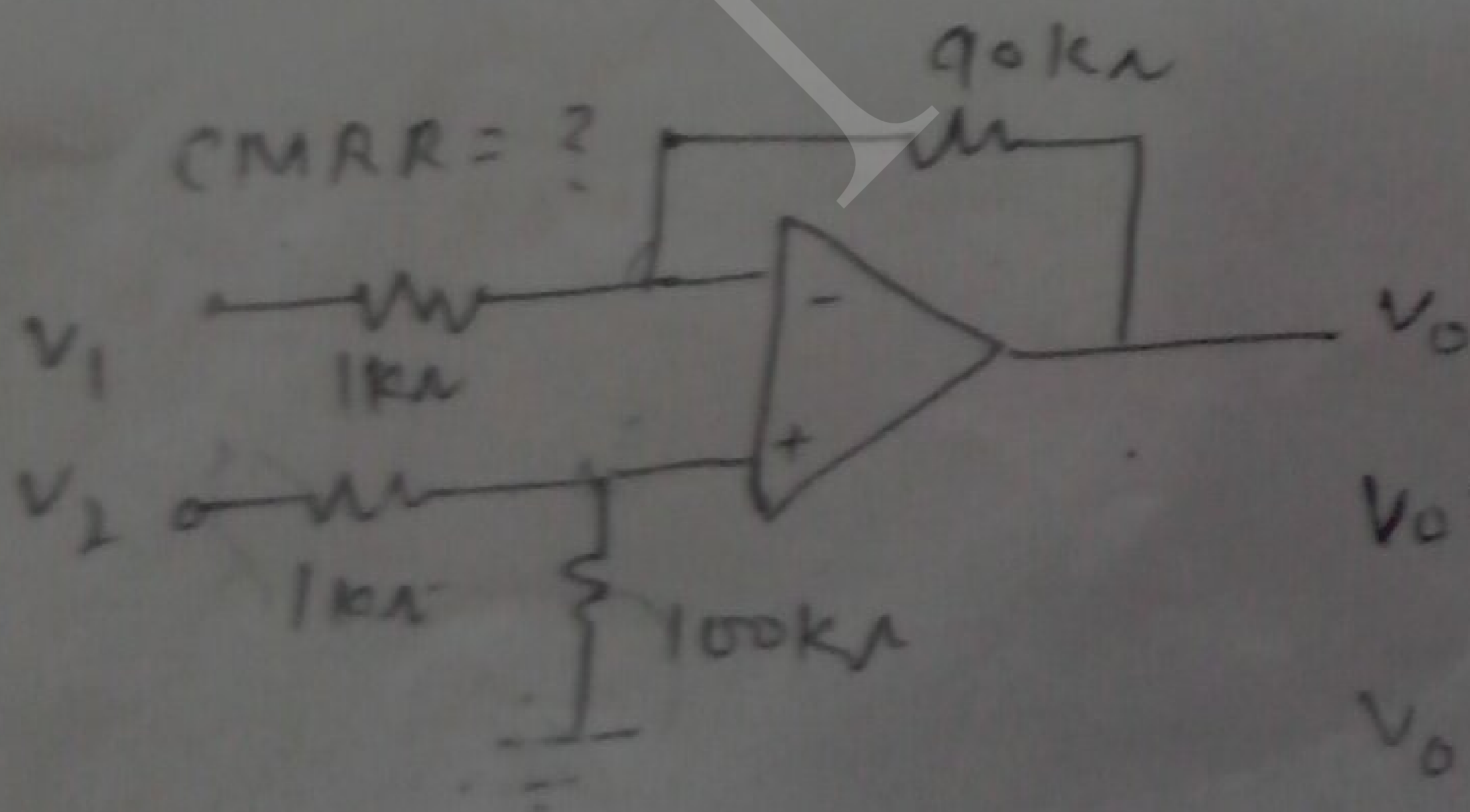

$$\text{CMRR} = \left| \frac{A_d}{A_c} \right|, \quad A_c = A_1 + A_2, \quad A_d = \frac{A_1 - A_2}{2}$$

$$V_o = -\frac{90}{1} V_1 + \left(1 + \frac{90}{1}\right) \frac{100}{(100+1)} V_2$$

$$V_o = -90 V_1 + \frac{(91) \times 100}{101} V_2$$

$$V_o = -90 V_1 + 90.09 V_2 \quad \text{--- (I)}$$

Comparing with standard Eq. $V_o = A_1 V_1 + A_2 V_2$ --- (II)


$$A_1 = -90, \quad A_2 = 90.09 \quad \text{then} \quad A_c = A_1 + A_2 = 109$$

$$A_d = \frac{A_1 - A_2}{2} = \frac{-180.09}{2} = -90.045$$

$$\text{CMRR} = \frac{|A_d|}{|A_c|} = \frac{1000.5}{109}$$

OP-AMP INTEGRATOR

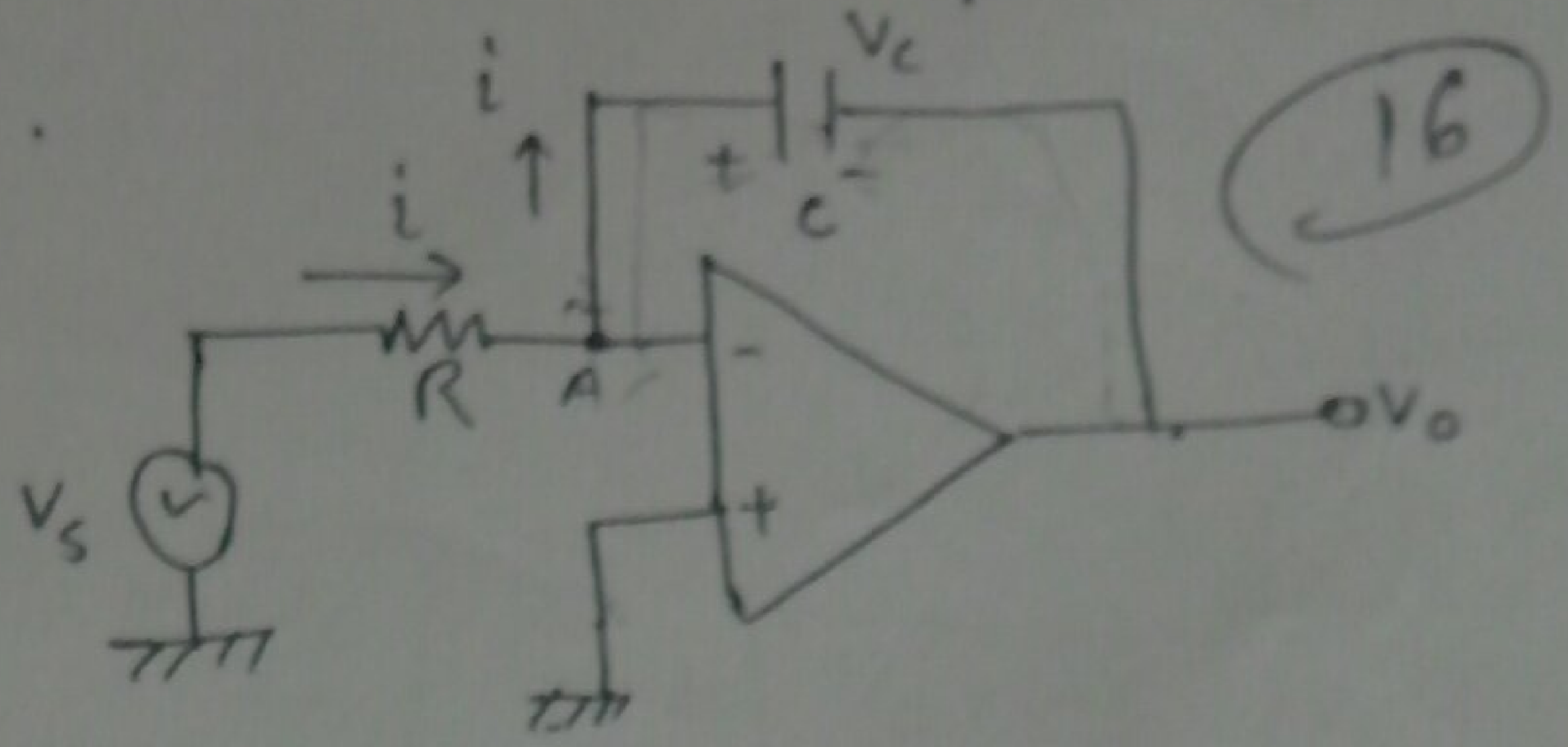For an integrator feedback is capacitor & series component is Resistor.



~~10kV at node A~~ $i = \frac{V_s}{R}$
 $V_c + V_o = 0$

~~10kV at node A~~ $V_o = -V_c$
 $= -\frac{1}{C} \int i dt$

$V_c = \frac{1}{C} \int i dt$
 Voltage across capacitor.

$V_o = -\frac{1}{C} \int \frac{V_s}{R} dt$


$V_o = -\frac{1}{RC} \int V_s dt$

$V_o = -\frac{1}{\tau} \int V_s dt$

$\tau = RC = \text{Time Constant}$

OP-Amp Differentiation

Current through capacitor

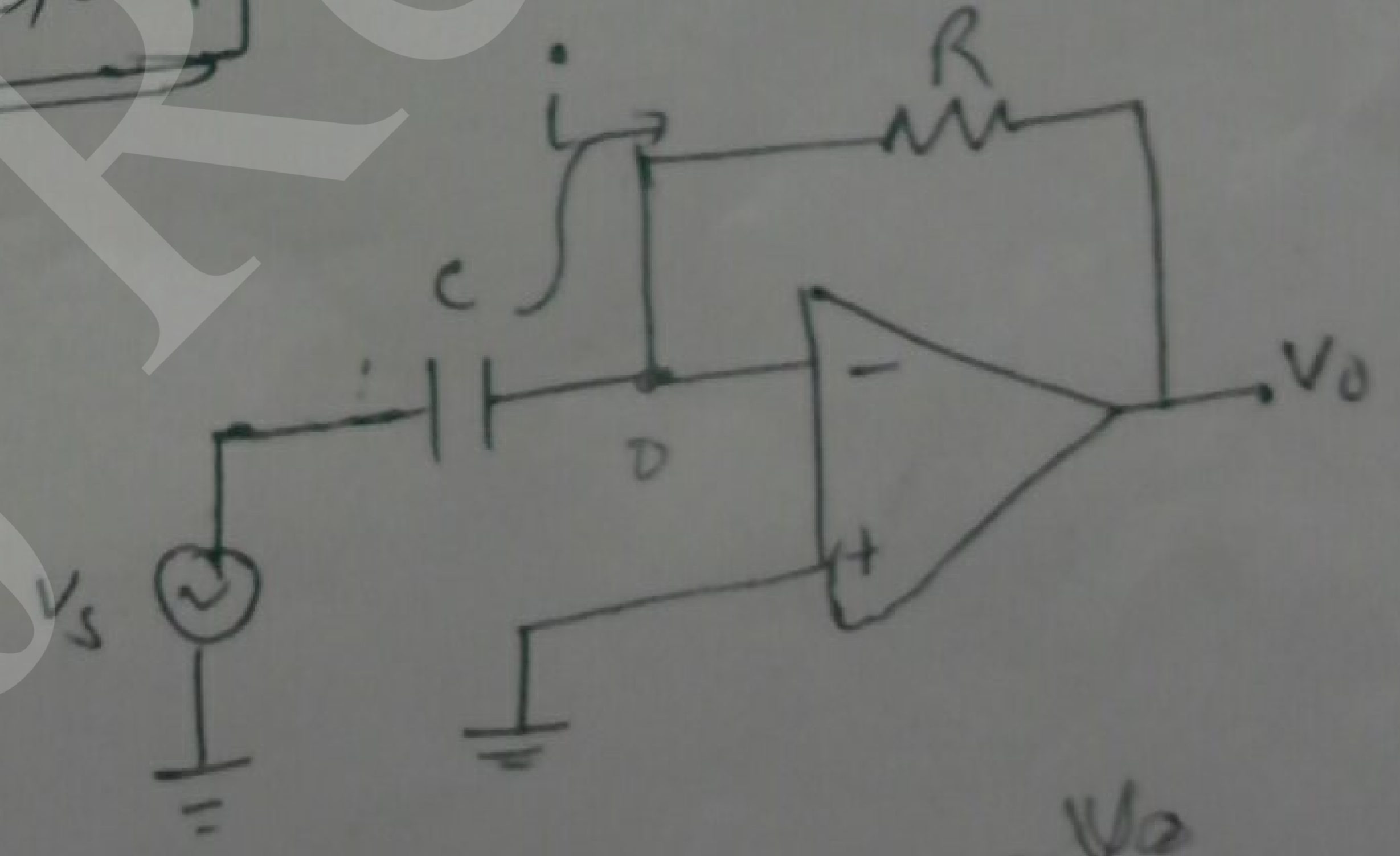

$i_c = C \frac{dV_s}{dt}$

$i_c R + V_o = 0$

$V_o = -i_c R$

$V_o = -C \frac{dV_s}{dt} R$

$V_o = -RC \frac{dV_s}{dt}$

$V_o = -\tau \frac{dV_s}{dt}$

$-i_c R - 0 = V_o$


$V_o = -i_c R$

$V_o = -\frac{dV_s}{dt} RC$

$RC \left(\frac{dV_s}{dt} \right)$

$V_o = -\tau \frac{dV_s}{dt}$

Op-Amp Differentiator with an Inductor

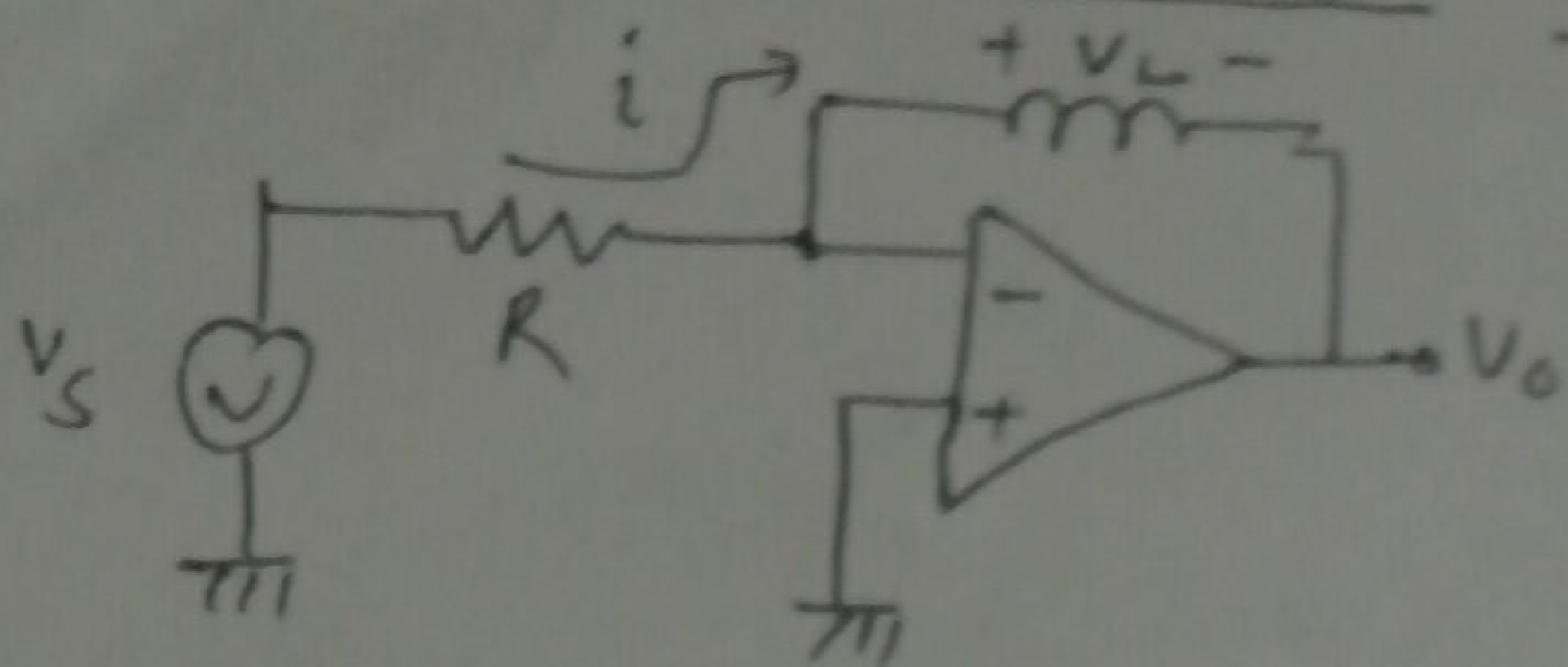

$$v_L = L \frac{di}{dt}$$


$$i = \frac{v_s}{R}, \quad v_o = -v_L = -L \frac{dv_s}{R dt}$$

$$v_o = -L \frac{d}{dt} \left(\frac{v_s}{R} \right)$$

$$v_o = -\tau \frac{dv_s}{dt} \quad \leftarrow \quad v_o = -\frac{L}{R} \frac{dv_s}{dt}$$

$\tau = L/R$ Time constant in R-L Network.

Ques Ideal Op-Amp. find v_o

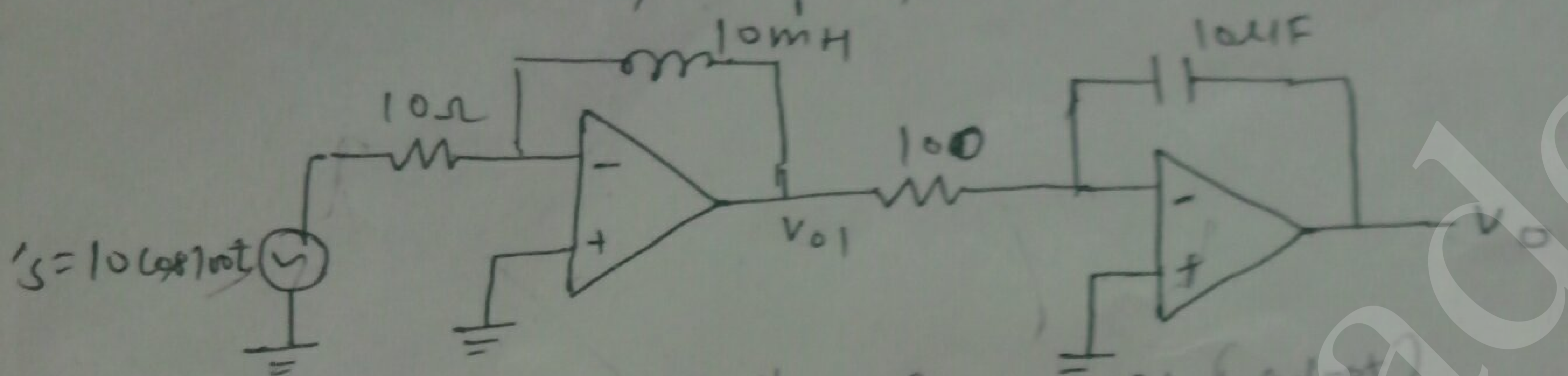


$$v_o = -L \frac{dv_s}{dt}$$

$$v_o = -L \frac{d}{dt} \left(\frac{v_s}{R} \right)$$

Ans $v_o = v_s$

INVERTING SUMMER also called adder.

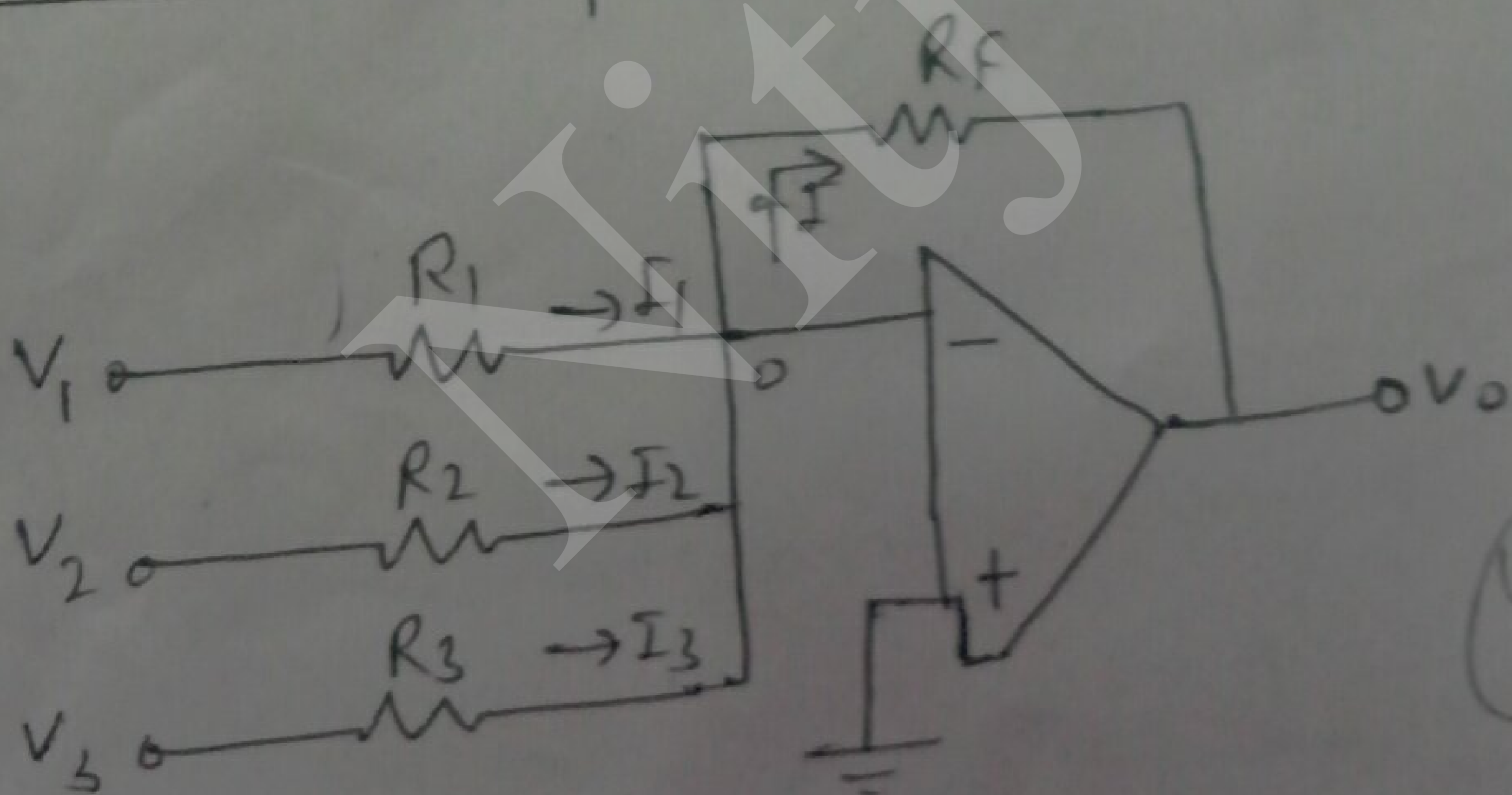

KCL

$$\frac{v_1 - 0}{R_1} + \frac{v_2 - 0}{R_2} + \frac{v_3 - 0}{R_3} = \frac{0 - v_o}{R_f}$$

$$v_o = - \left[\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right] R_f$$

OR

$$v_o = A_1 v_1 + A_2 v_2 + A_3 v_3$$

$$v_o = -\tau \frac{dv}{dt}$$

$v_o = -\frac{1}{10000 \times 10^{-6}} \int \sin 100t dt$

$\frac{+1}{10^{-3}} \int \cos 100t dt$

$\frac{\cos 100t}{100}$

$\frac{1 - \cos 100t}{100}$

If $R_1 = R_2 = R_3 = R_f$


(18)

$V_o = -(V_1 + V_2 + V_3) \rightarrow$ Inverting Summer

Non Inverting Summer

(18)

By applying superposition principle.

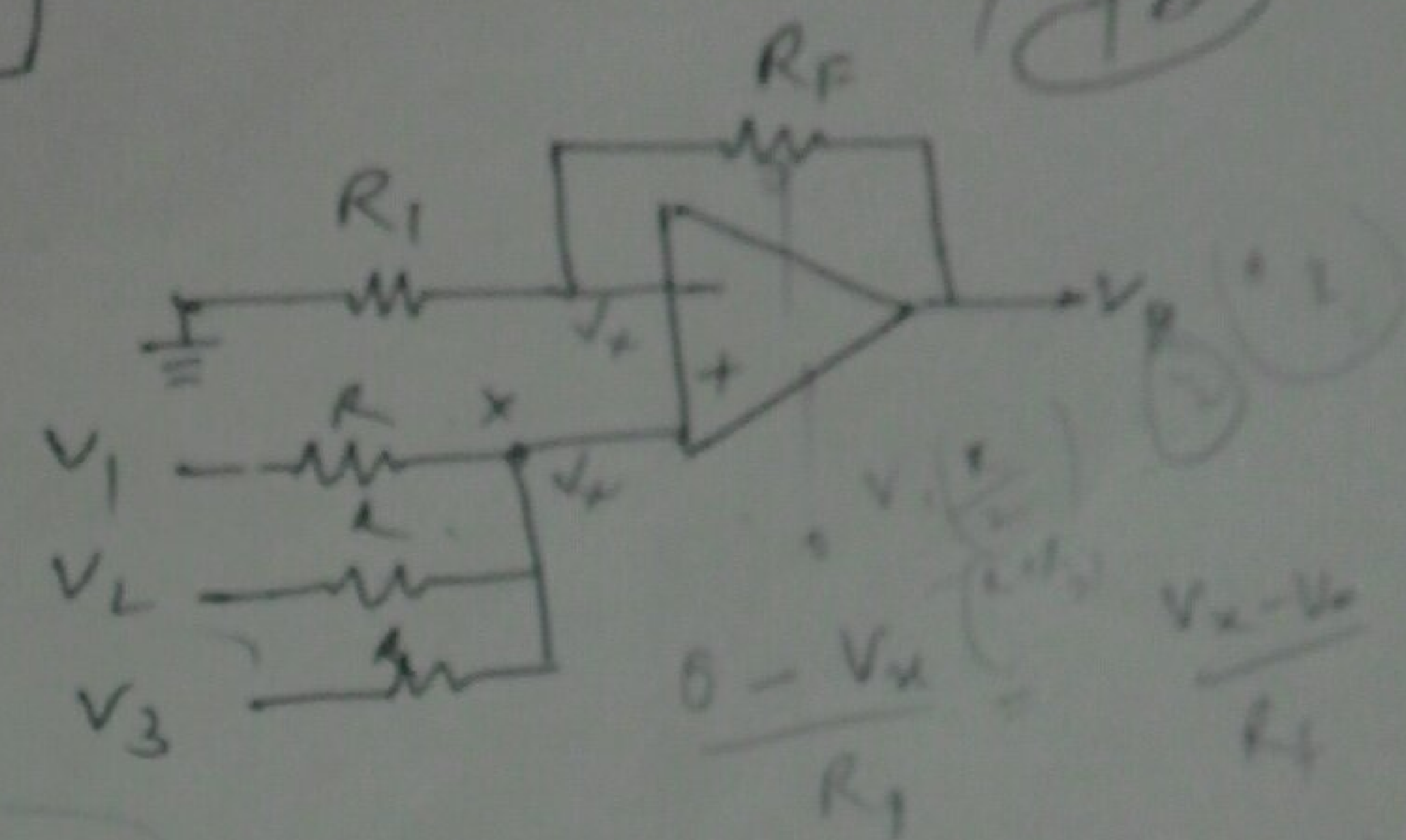

$V_o = (1 + \frac{R_f}{R_1}) V_n$

~~we get~~ $V_n = V_{n1} + V_{n2} + V_{n3}$

let V_2 & V_3 are grounded then

$V_{n1} = \frac{V_1 (R/2)}{R + R/2} = \frac{V_1}{3}$

let V_1 & V_3 are grounded

$V_{n2} = \frac{V_2 (R/2)}{R + R/2} = \frac{V_2}{3}$

let V_1 & V_2 are grounded

$V_{n3} = \frac{V_3 (R/2)}{R + R/2} = \frac{V_3}{3}$

$V_n = \frac{V_1}{3} + \frac{V_2}{3} + \frac{V_3}{3} = \frac{1}{3} (V_1 + V_2 + V_3)$

$V_o = (1 + \frac{R_f}{R_1}) \frac{1}{3} (V_1 + V_2 + V_3)$

Slew Rate (SR) or SR.

It is defined as the maximum rate at which the amplifier output can be changed in volt/μsec.

$SR = \frac{\Delta V_o}{\Delta t} \Big| \frac{\text{Volt}}{\mu\text{sec}}$

for Ideal $SR = \infty$

$SR = \left(\frac{\Delta V_o}{\Delta V_i} \right) \times \frac{\Delta V_i}{\Delta t}$
 $SR = |A_{vL}| \frac{\Delta V_i}{\Delta t}$

Slew Rate is also associated with the max^m operating input signal frequency as

$f \leq \frac{SR}{2\pi K} \text{ Hz}$
 $\omega \leq \frac{SR}{K}$

$K = |A_{vL}| \Delta V_i$