

LAKSHYA JEE

LAKSHYA KO HAR HAAL ME PAANA HAI



Electric Potential & Capacitance

-Er. Rohit Gupta



Today's GOALS!


Capacitors
&
Dielectrics



Kirchhoff's rules

①

Kirchhoff's junction rule.

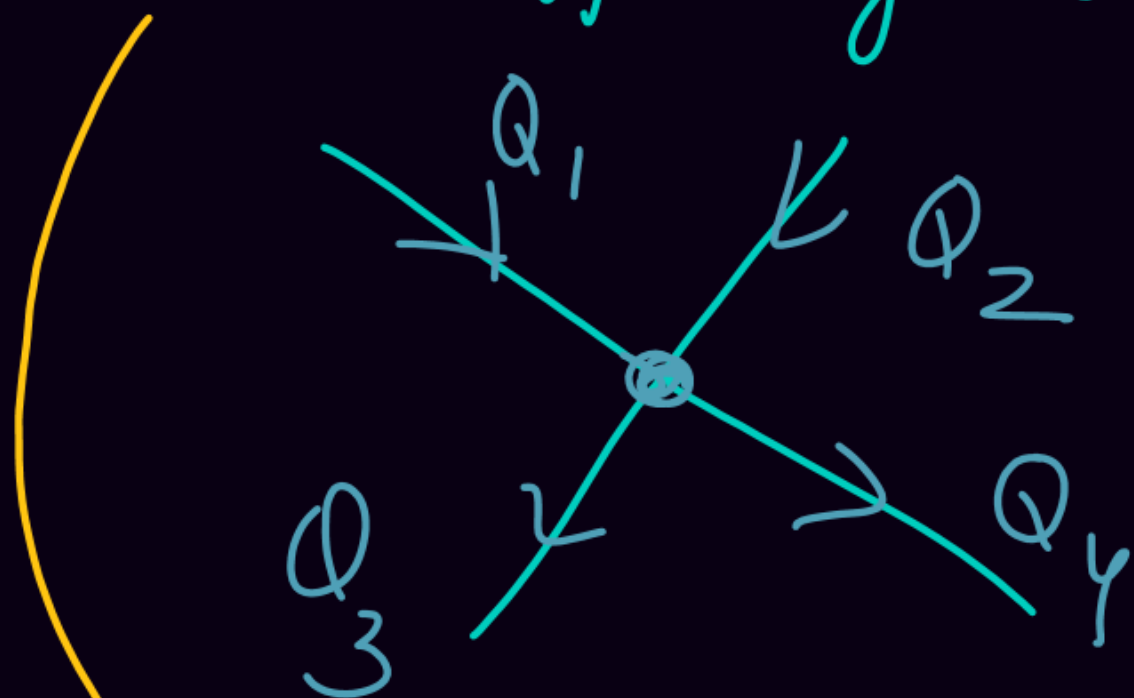

Charge rate = Current rate

$$Q_1 + Q_2 = Q_3 + Q_4$$

↳ Conservation of charge.


② Kirchhoff's loop rule (conservation of energy)

In a closed circuit net potential difference / drop is zero.

Electrostatic field is a conservative field.

This means the net work done in a closed loop is zero.

$$\Delta V = -\frac{W}{q} = 0$$

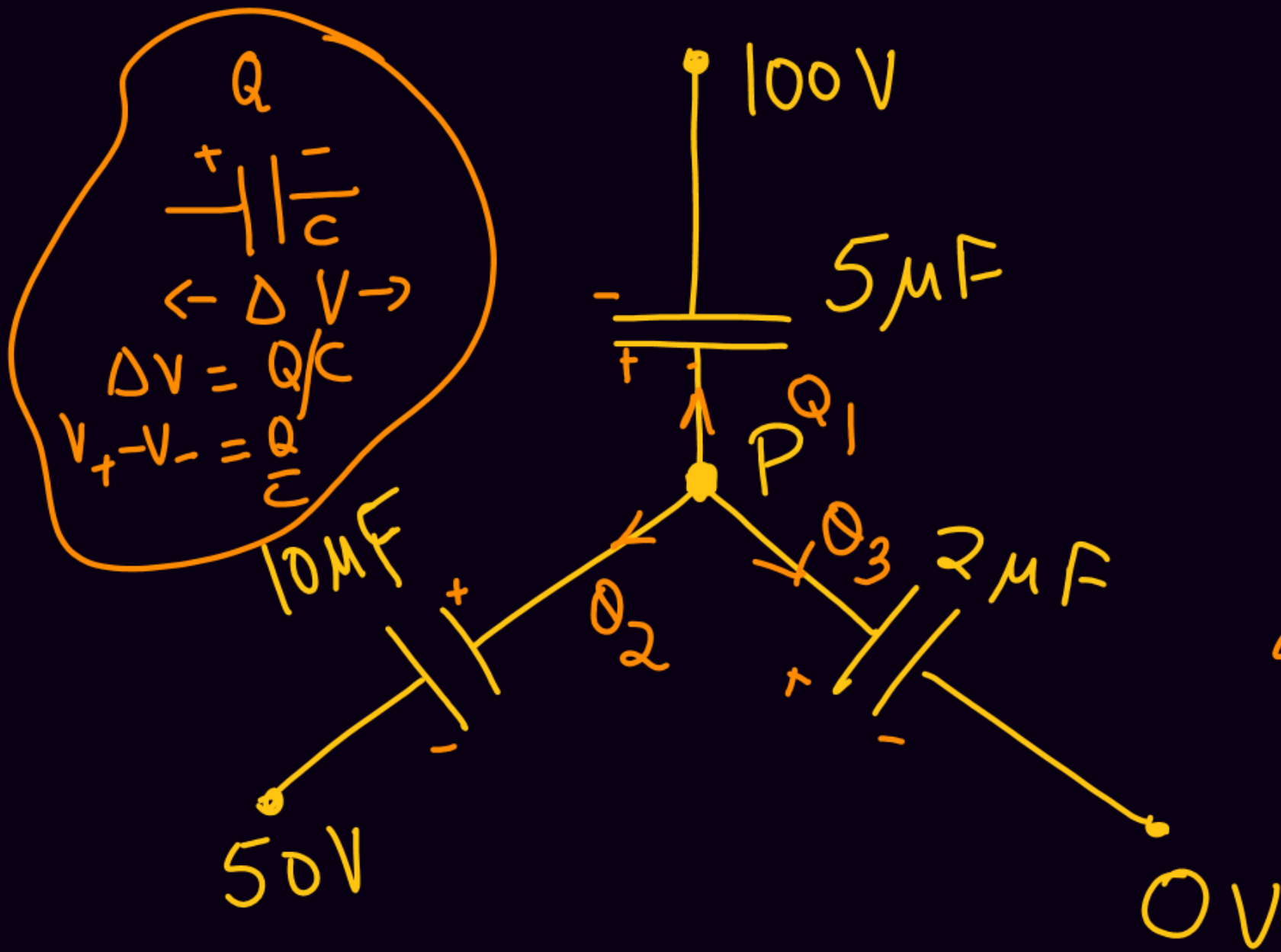

Find the potential of the junction.


$$Q_1 + Q_2 + Q_3 = 0$$

$$5(V_p - 100) + (V_p - 50)10 + (V_p - 0) \times 2 = 0$$

$$17V_p - 500 - 500 = 0$$

$$V_p = \frac{1000}{17} = 58.82 \text{ V}$$



Find the charge on all the capacitors?

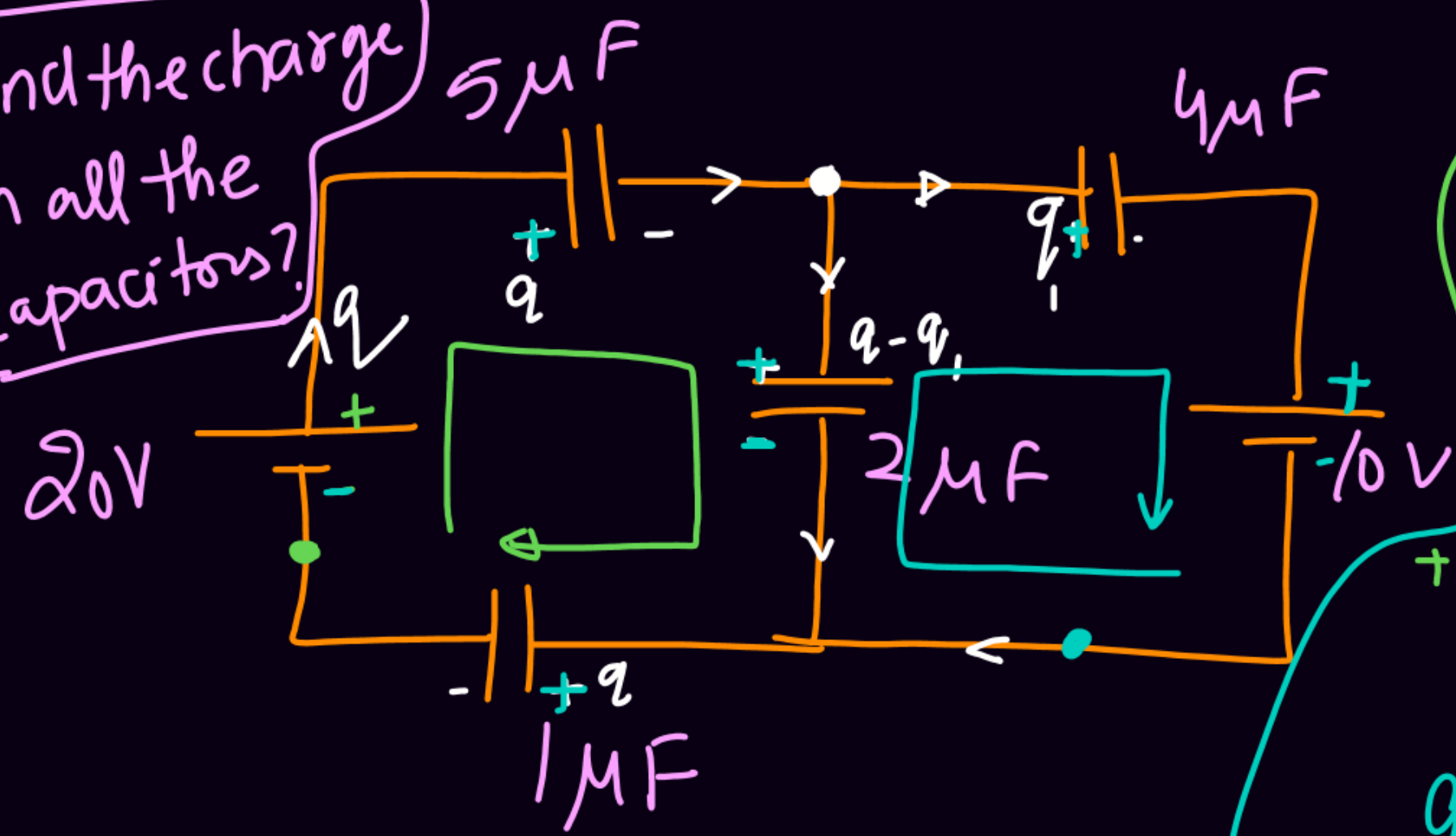

$$+20 - \frac{q}{5} - \frac{(q - q_1)}{2} - \frac{q}{1} = 0 \quad (1)$$

$$+ \frac{q - q_1}{2} - \frac{q_1}{4} - 10 = 0 \quad (2)$$


Sharing of charge / Common pot.

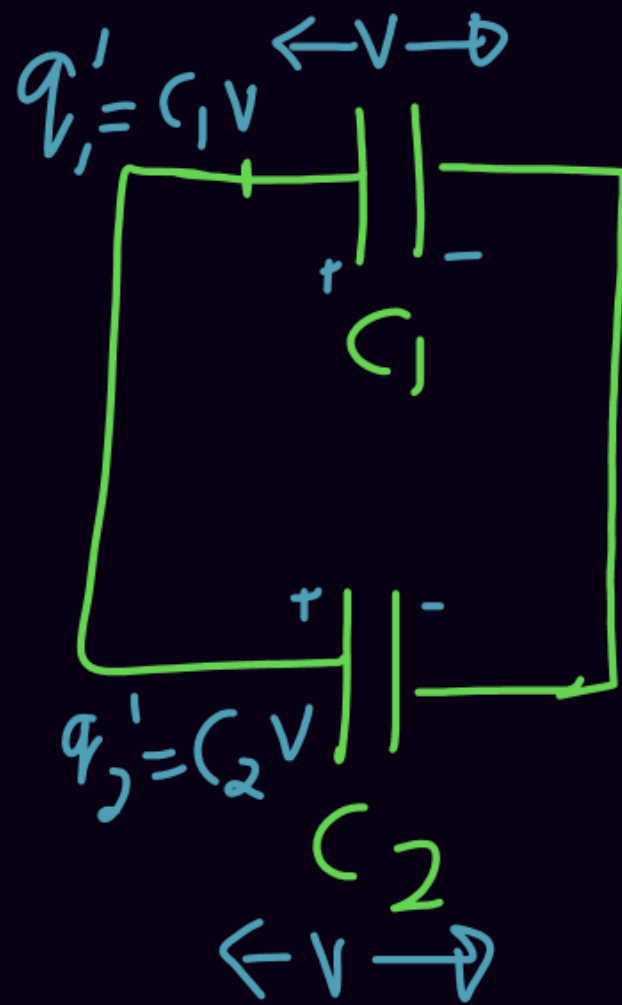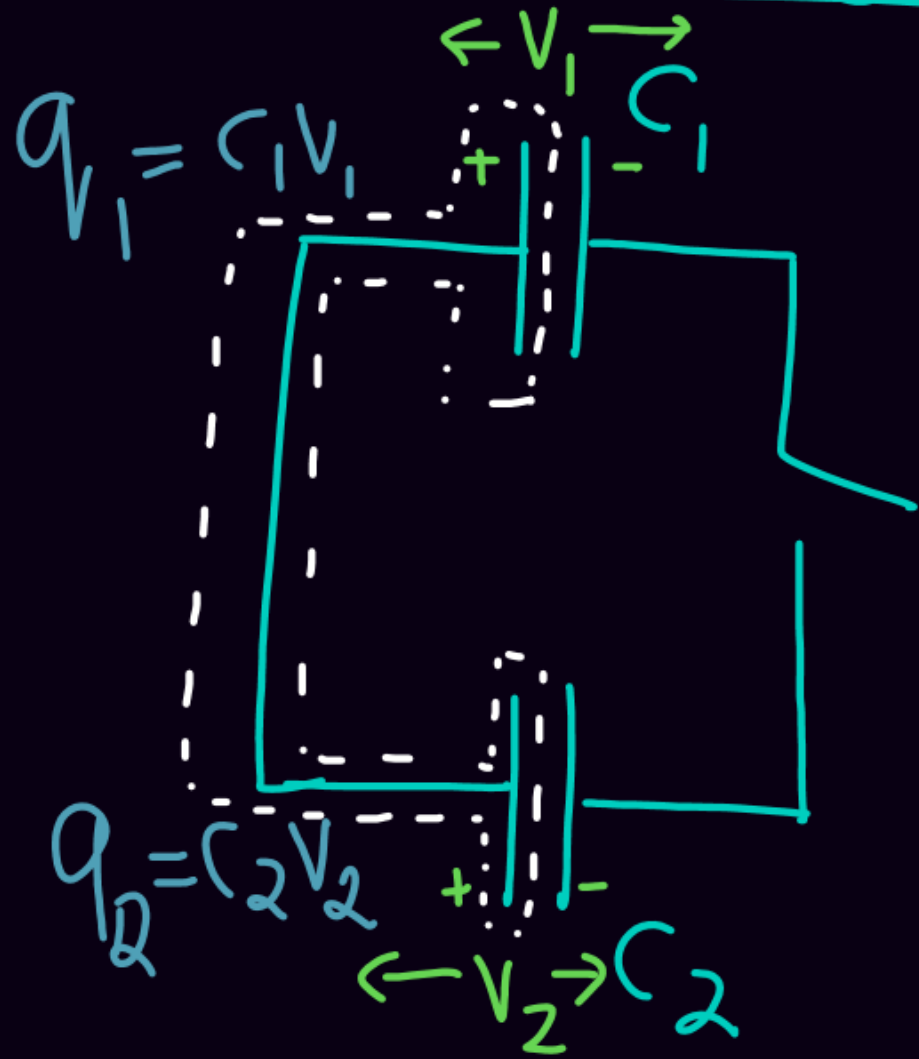

find the common potential after closing the switch?

$$q_1 + q_2 = q_1' + q_2'$$
$$C_1 V_1 + C_2 V_2 = C_1 V + C_2 V$$
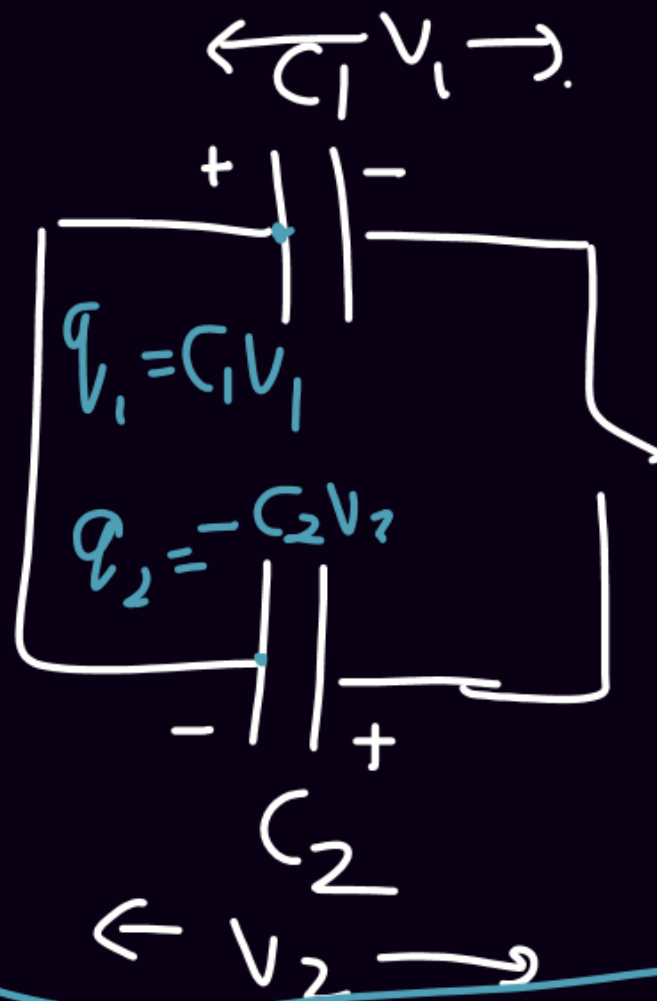
$$V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$




Two capacitors are charged & connected as shown.

find common pot. after closing the switch.

$$q_1 + q_2 = q_1' + q_2'$$

$$C_1 V_1 - C_2 V_2 = C_1 V + C_2 V$$

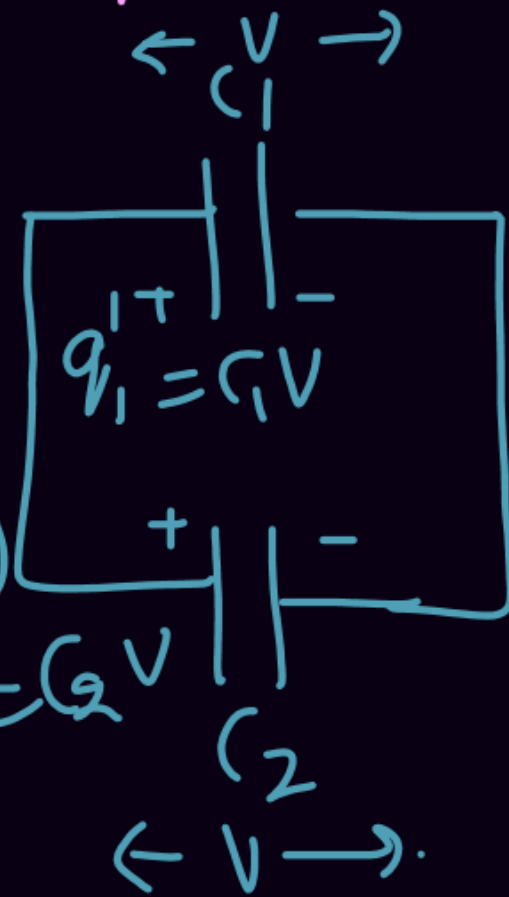

$$V = \frac{C_1 V_1 - C_2 V_2}{C_1 + C_2}$$

Two condensers of capacities C_1 and C_2 are connected in parallel and charged. Then the ratio of charge on C_1 to charge on C_2 is


1) $\frac{C_2}{C_1}$

2) $\left(\frac{C_2}{C_1}\right)^2$

3) $\frac{C_1}{C_2}$

4) $\left(\frac{C_1}{C_2}\right)^2$

Condenser \equiv Capacitor.

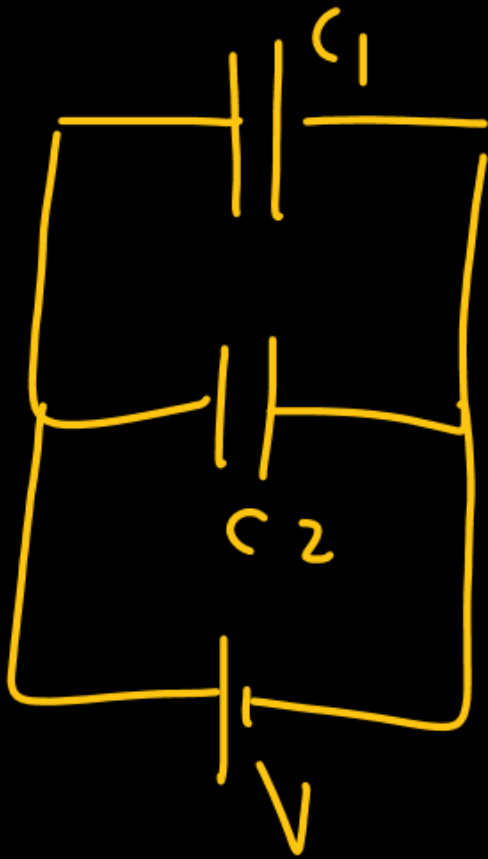

$$q_1 = C_1 V$$

$$q_2 = C_2 V$$

$$\frac{q_1}{q_2} = \frac{C_1}{C_2}$$




Two identical parallel plate capacitors are joined in series to 100 V battery. Now a dielectric constant ($K = 4$) is introduced between the plates of second capacitor. The potential differences on capacitors are

1) 60 V, 40 V

2) 70 V, 30 V

3) 75 V, 25 V

4) 80 V, 20 V

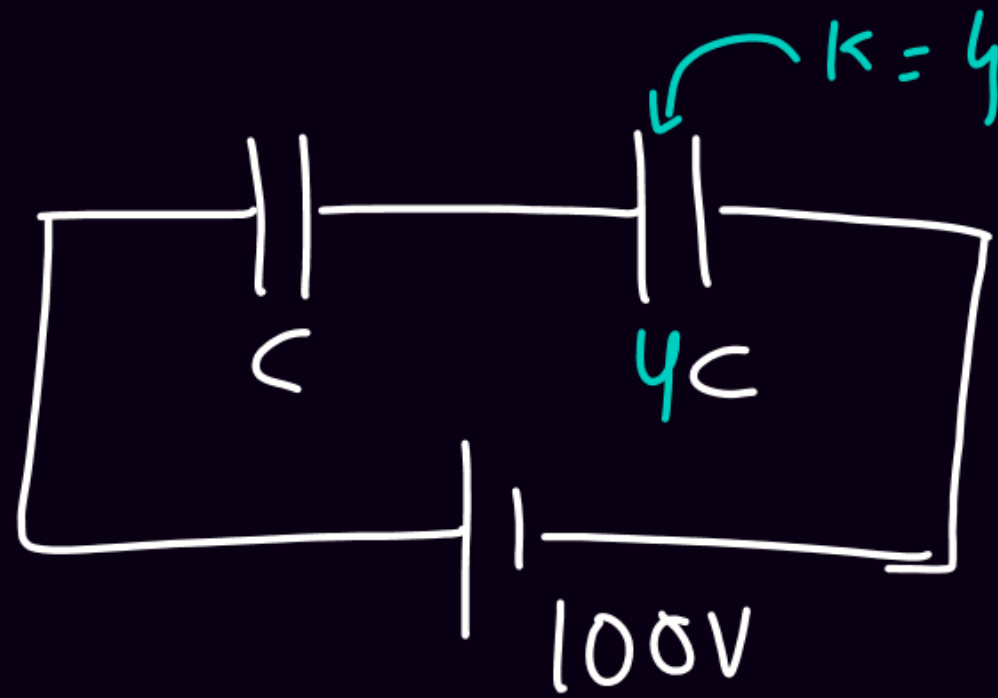

$$V_C = \frac{4C \times 100}{4C + C} = 80V$$



$$V_{C_1} = \frac{V C_2}{C_1 + C_2}$$

The work done in increasing the potential difference across the plates of a capacitor from 4 V to 6 V is W . The further work done in increasing the potential difference from 6 V to 8 V is

1) W

2) $5W/7$

~~3) $7W/5$~~

4) $2W/5$

$$\Delta U = \frac{1}{2} C (V_2^2 - V_1^2) = W$$

$$W = \frac{1}{2} C (6^2 - 4^2)$$

$$\frac{W'}{\frac{1}{2} C (8^2 - 6^2)}$$

$$= \frac{36 - 16}{64 - 36} = \frac{20}{28} = \frac{5}{7}$$

$$W' = \frac{7W}{5}$$


Three condensers of capacities $3 \mu\text{F}$, $4 \mu\text{F}$ and $5 \mu\text{F}$ are connected in series and a constant potential is applied between the ends of the combination. Their potentials are in the ratio of

1) $5 : 4 : 3$

2) $3 : 4 : 5$

3) $4 : 5 : 3$

~~4) $20 : 15 : 12$~~

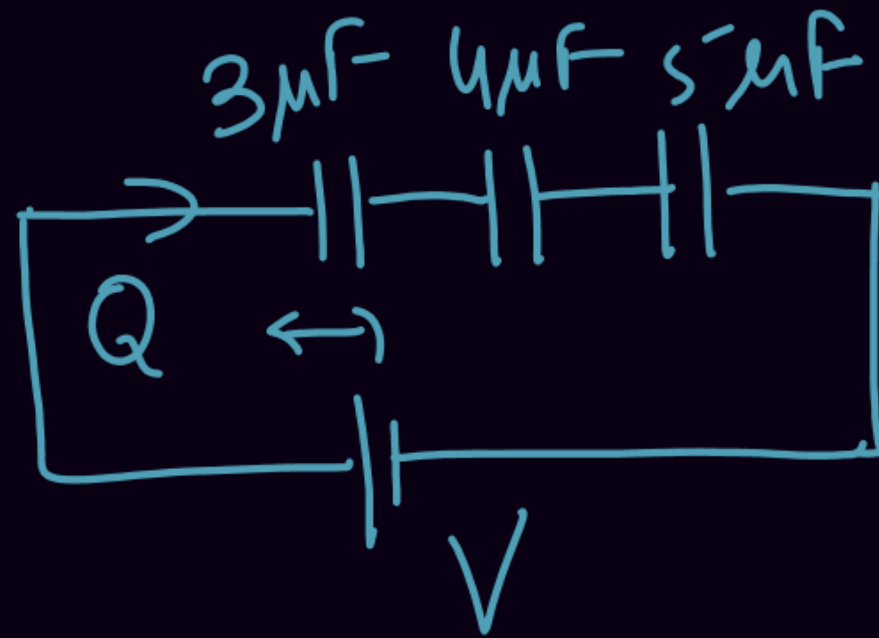

$$V_3 = \frac{Q}{3}$$

$$V_4 = \frac{Q}{4}$$

$$V_5 = \frac{Q}{5}$$

$$V_3 : V_4 : V_5 = \frac{Q}{3} : \frac{Q}{4} : \frac{Q}{5}$$

$$= \underline{20 : 15 : 12}$$


The radius of the circular plates of a parallel plate condenser is r_1 . Air is there as dielectric. The distance between the plates if its capacitance is equal to that of an isolated sphere of radius r is

~~1) $r_1^2 / 4r$~~

2) r^2 / r_1

3) r / r_1

4) $r^2 / 4$

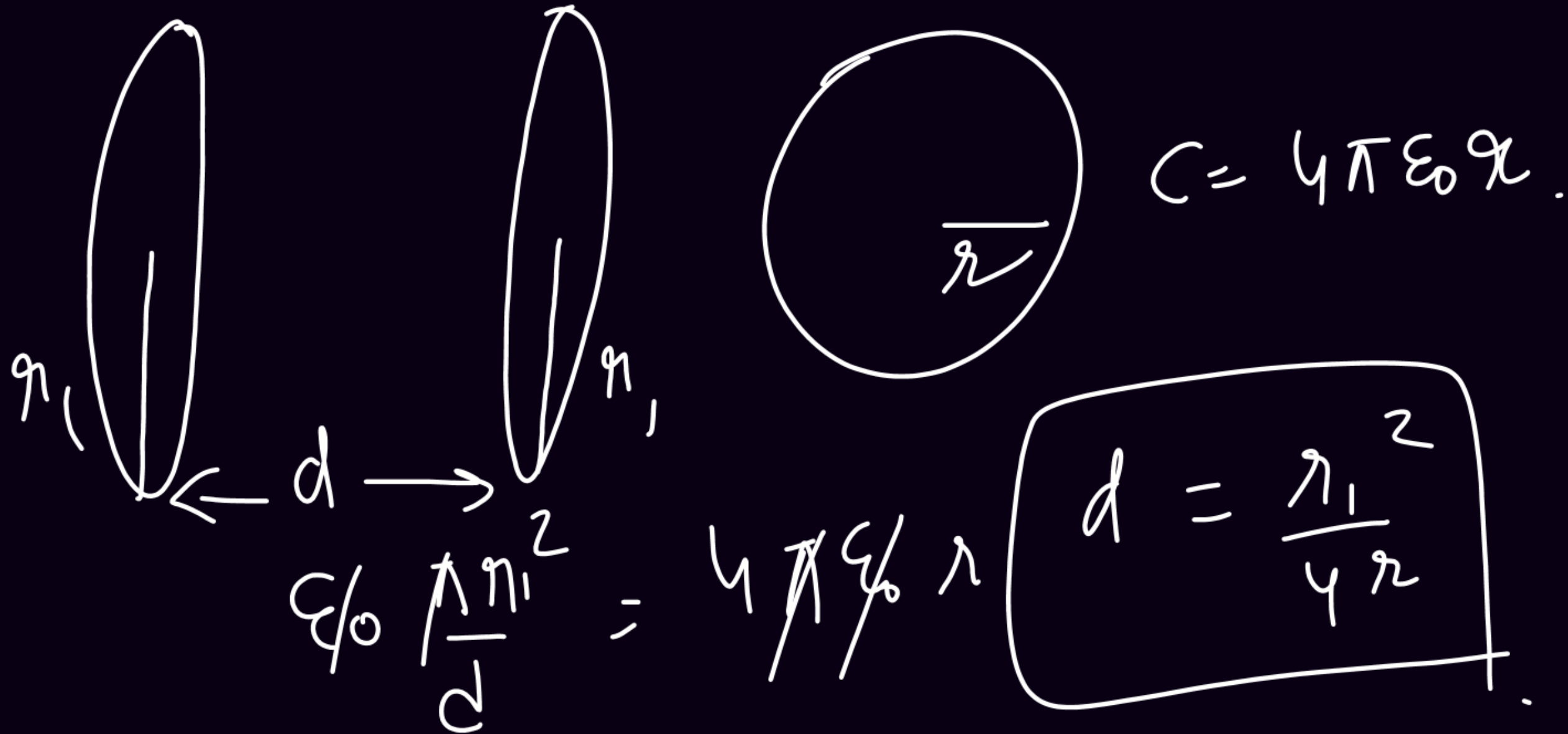


Three condensers each of capacity $6 \mu\text{F}$ are available. The effective capacity that cannot be obtained by combining them all is

1) $18 \mu\text{F}$


2) $9 \mu\text{F}$

3) $4 \mu\text{F}$



~~4) $8 \mu\text{F}$~~

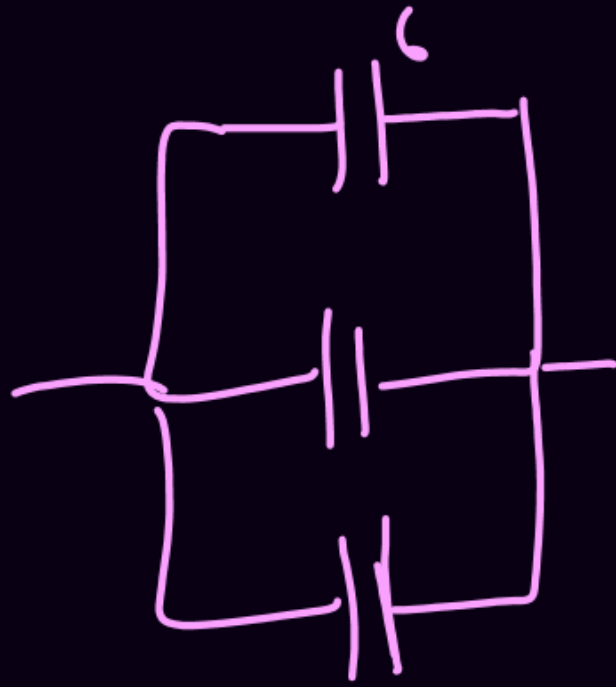

$$C = 18 \mu\text{F}$$

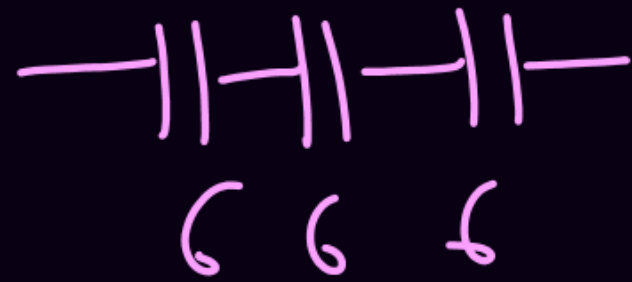

$$C = \frac{6}{3} = 2 \mu\text{F}$$

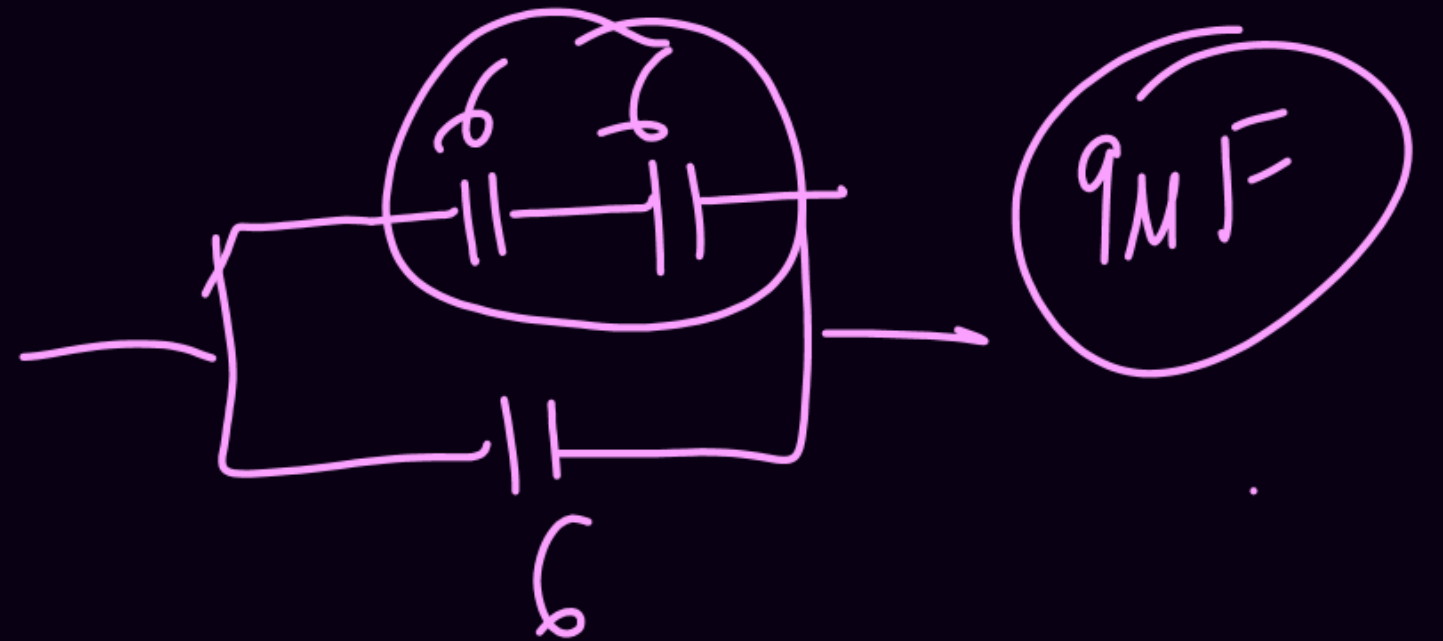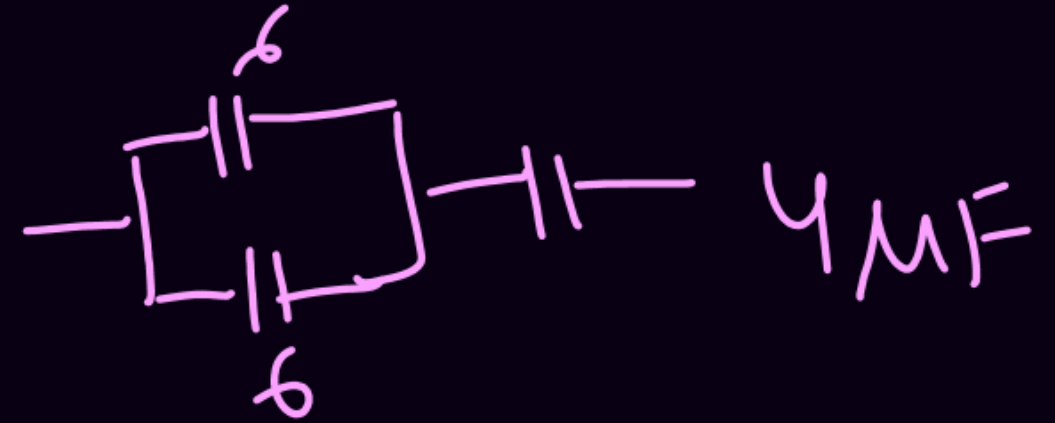


The capacity of a parallel plate condenser with air medium is 60 μF having distance of separation d . If the space between the plates is filled with two slabs each of thickness $d/2$ and dielectric constants 4 and 8, the effective capacity becomes

1) 160 μF

~~2) 320 μF~~

3) 640 μF

4) 360 μF

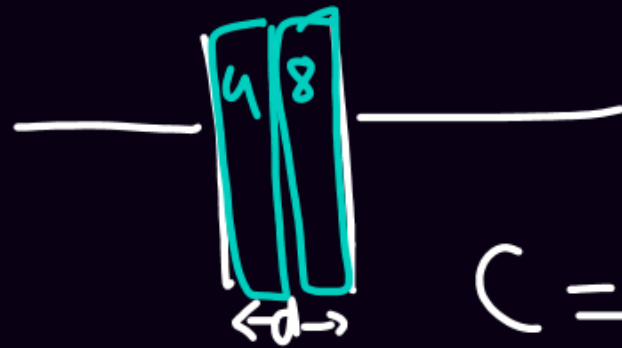


$$C = 60 \mu\text{F}$$

$$C = \frac{\epsilon_0 A}{\frac{d}{2 \times 4} + \frac{d}{2 \times 8}}$$

$$= \frac{\epsilon_0 A}{\frac{d}{2 \times 4} \left(1 + \frac{1}{2}\right)}$$

$$= \frac{16 \epsilon_0 A}{3d}$$

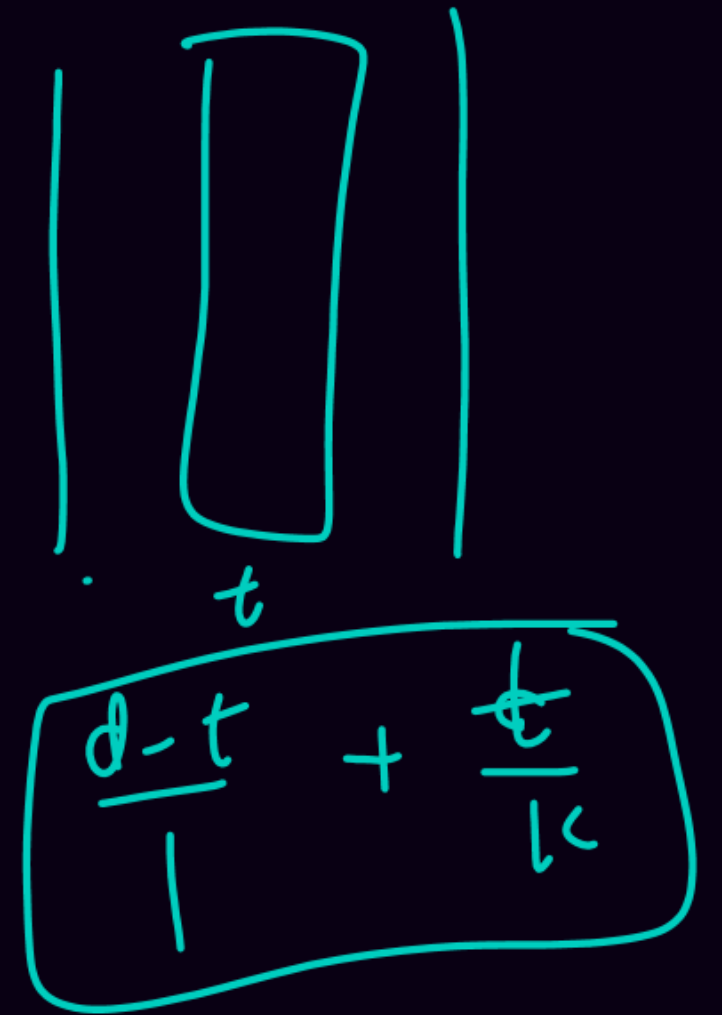

$$= \frac{16 \times 60}{3} = 320 \mu\text{F}$$


Two condensers of capacities C_1 and C_2 charged to potentials V_1 and V_2 are connected in two ways as shown in the figure. The ratio of loss of energies in the case (i) to case (ii) is

1) $\frac{V_1 - V_2}{V_1 + V_2}$

2) $\frac{(V_1 - V_2)^2}{(V_1 + V_2)^2}$

3) $\frac{V_1^2 - V_2^2}{V_1^2 + V_2^2}$

4) $\frac{(V_1 + V_2)^2}{(V_1 - V_2)^2}$

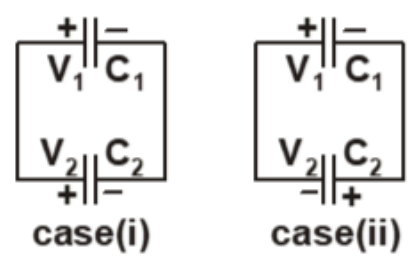

A parallel plate capacitor with air as medium between the plates has a capacitance $10 \mu\text{F}$. The area of the capacitor is divided into two equal halves and filled with two media having dielectric constants 2 and 4. The capacitance of the system will be

1) $10 \mu\text{F}$

2) $20 \mu\text{F}$

3) $30 \mu\text{F}$

4) $40 \mu\text{F}$

Thank You Lakshyians