
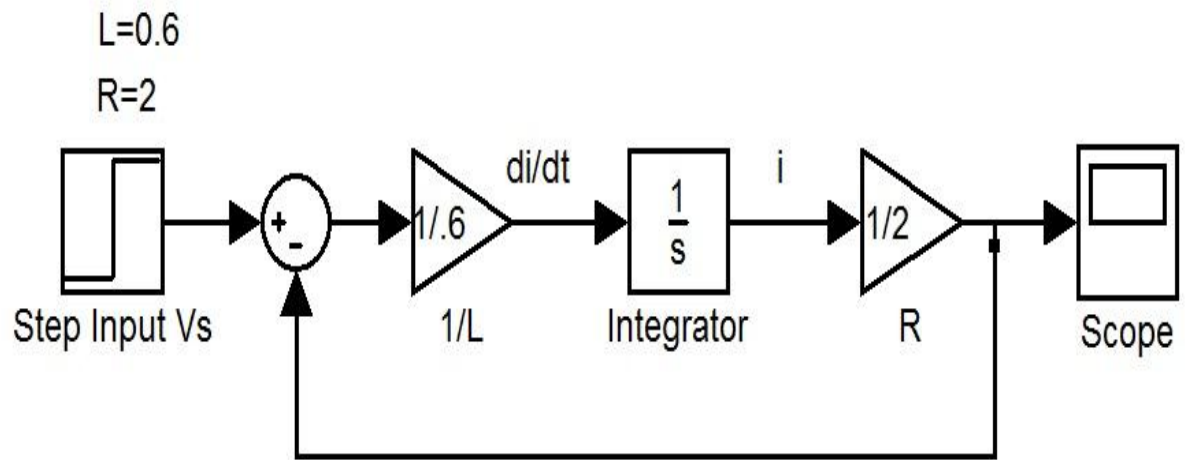


Aim: To Simulate Series RL Circuit.

Circuit Diagram:

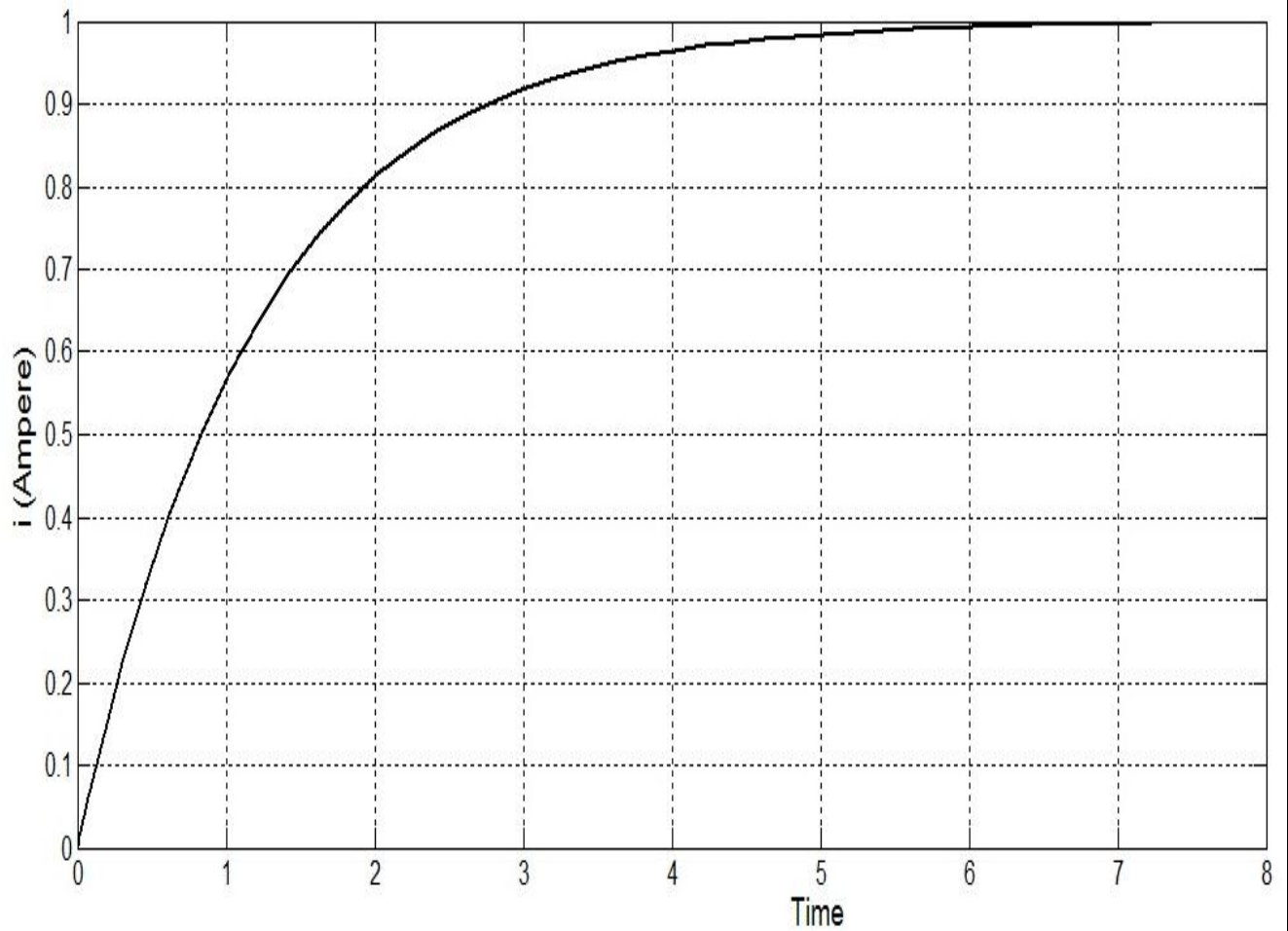


Output:




Aim: To Simulate Series RC Circuit.

Circuit Diagram:

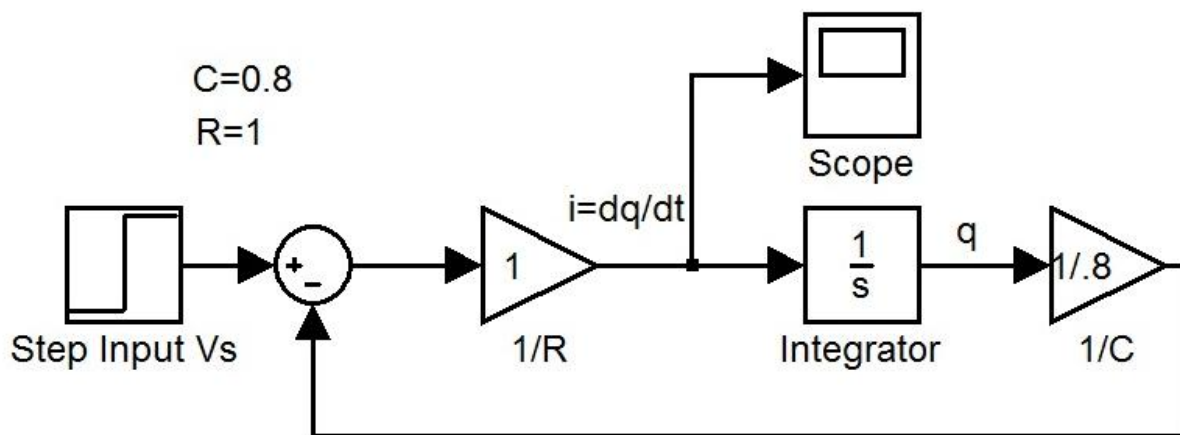


Output:

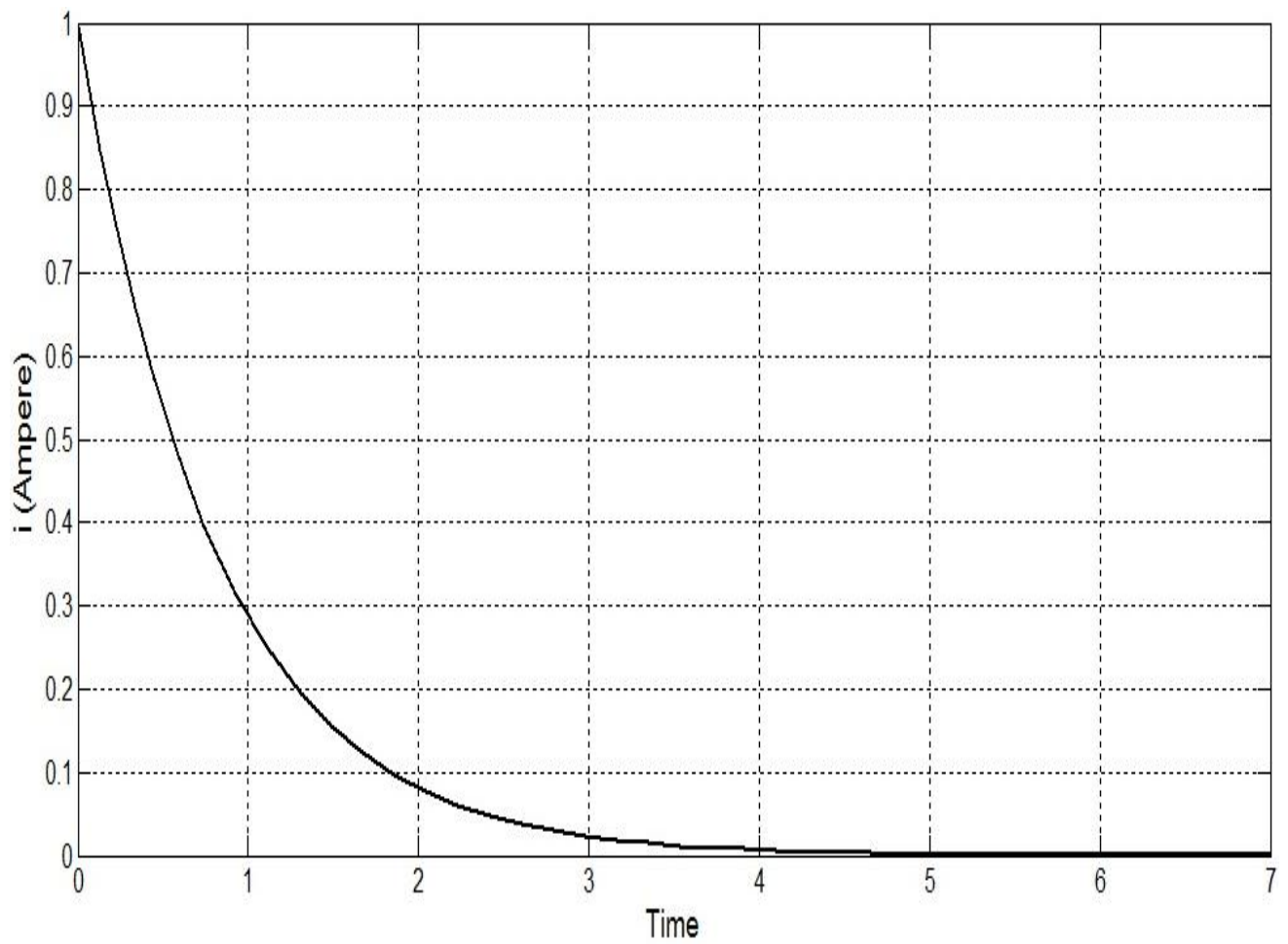


Aim: To Simulate Series RLC Circuit.

Circuit Diagram:

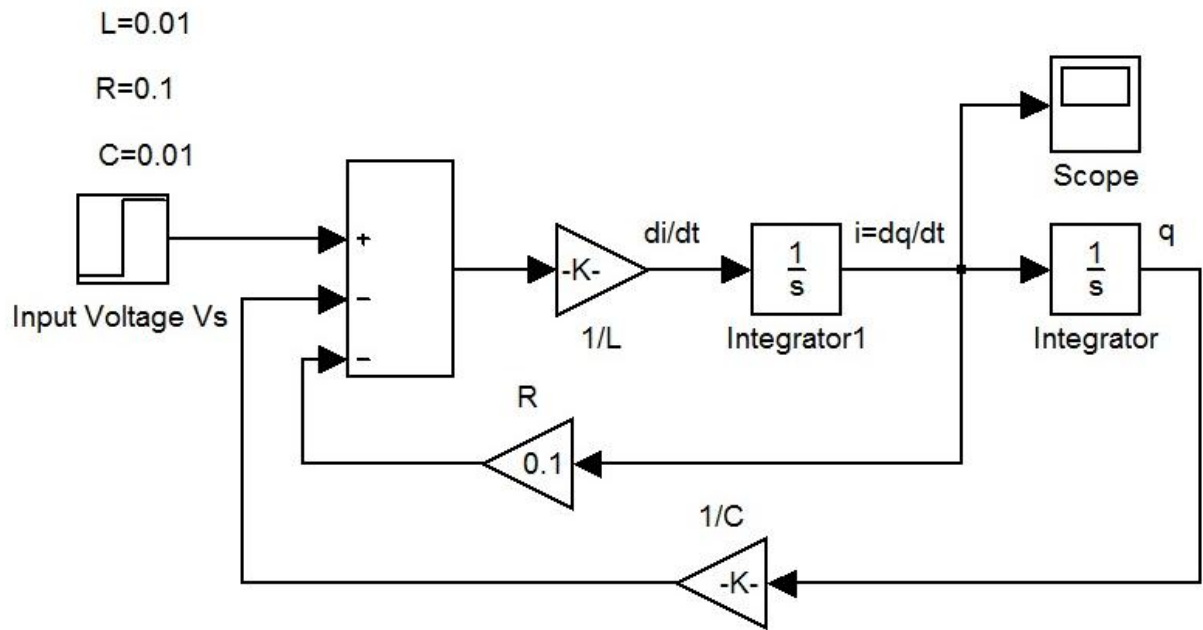

Output:

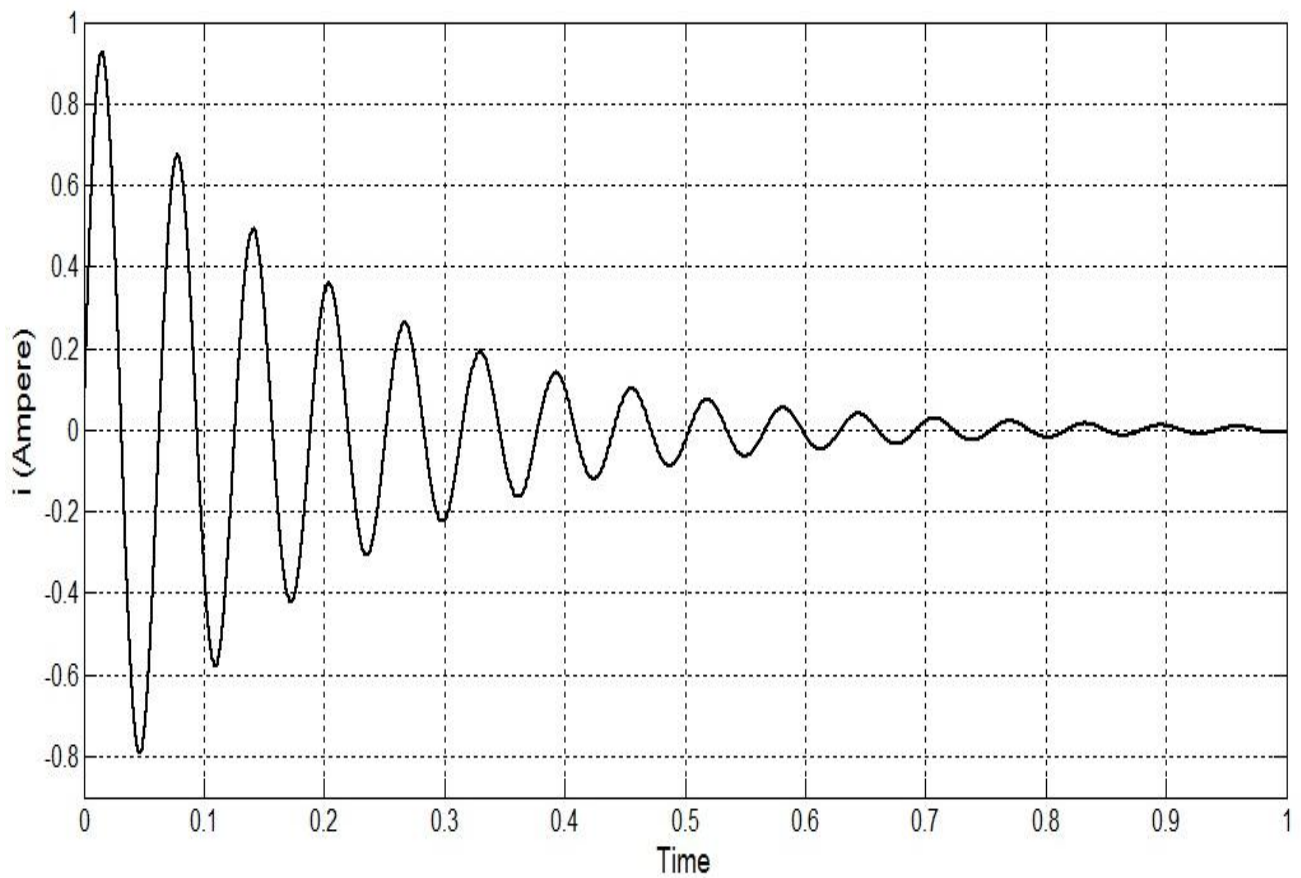

Aim: To analysis performance of Short Transmission line by using MATLAB.

Program:

```
clc
clear all
%SHORT TRANSMISSION LINE%
Pr=input('Receiving End Power(MW): ');
Vr=input('Receiving End Voltage(KV): ');
pfr=input('Receiving End Power Factor: ');
r=input('Resistance per Km(ohm): ');
x=input('Reactance per Km(ohm): ');
L=input('Total Length of Line(Km): ');
f=input('Supply Frequency(Hz): ');

%TRANSMISSION LINE PARAMETER%
R=(r*L)
X=(x*L)

%RECEIVING END VOLTAGE%
Vrph=(Vr/sqrt(3))
Ir=Pr/(3*Vrph*pfr)
phi=acos(pfr)      %  $\cos^{-1}\phi$  %
sphi=sin(phi)     %  $\sin\phi$  %
Irnw=abs(Ir)*(pfr-((1*j)*sphi))

% VOLTAGE REGULATION%
A=1
B=R+(j*X)
C=0
D=1
```

$$V_s = (A * V_{rph}) + (B * I_{rnew})$$

$$\text{VolgReg} = ((\text{abs}(V_s) - V_{rph}) / V_{rph}) * 100$$

% EFFICIENCY %

$$I_s = I_{rnew}$$

$$u = \text{angle}(V_s)$$

$$v = \text{angle}(I_s)$$

$$\text{pfs} = \cos(u - v)$$

$$V_{snew} = \sqrt{3} * \text{abs}(V_s)$$

$$P_s = \sqrt{3} * V_{snew} * \text{abs}(I_s) * \text{pfs}$$

$$\text{Efficiency} = (P_r / P_s) * 100$$

Output:

Receiving End Power(MW): 12.75

Receiving End Voltage(KV): 33

Receiving End Power Factor: 0.85

Resistance per Km(ohm): 0.24

Reactance per Km(ohm): 0.65

Total Length of Line(Km): 8

Supply Frequency(Hz): 50

$$R = 1.9200$$

$$X = 5.2000$$

$$V_{rph} = 19.0526$$

$$I_r = 0.2624$$

$$\text{phi} = 0.5548$$

$$\text{sphi} = 0.5268$$

$$I_{rnew} = 0.2231 - 0.1382i$$

$$A = 1$$

$$B = 1.9200 + 5.2000i$$

$$C = 0$$

$$D = 1$$

$$V_s = 20.1997 + 0.8945i$$

$$\text{VolgReg} = 6.1249$$

$$I_s = 0.2231 - 0.1382i$$

$$u = 0.0443$$

$$v = -0.5548$$

$$\text{pfs} = 0.8259$$


$$V_{\text{snew}} = 35.0212$$

$$P_s = 13.1467$$



$$\text{Efficiency} = 96.9826$$

Aim: To simulate balanced 3 wire system.

Circuit Diagram:

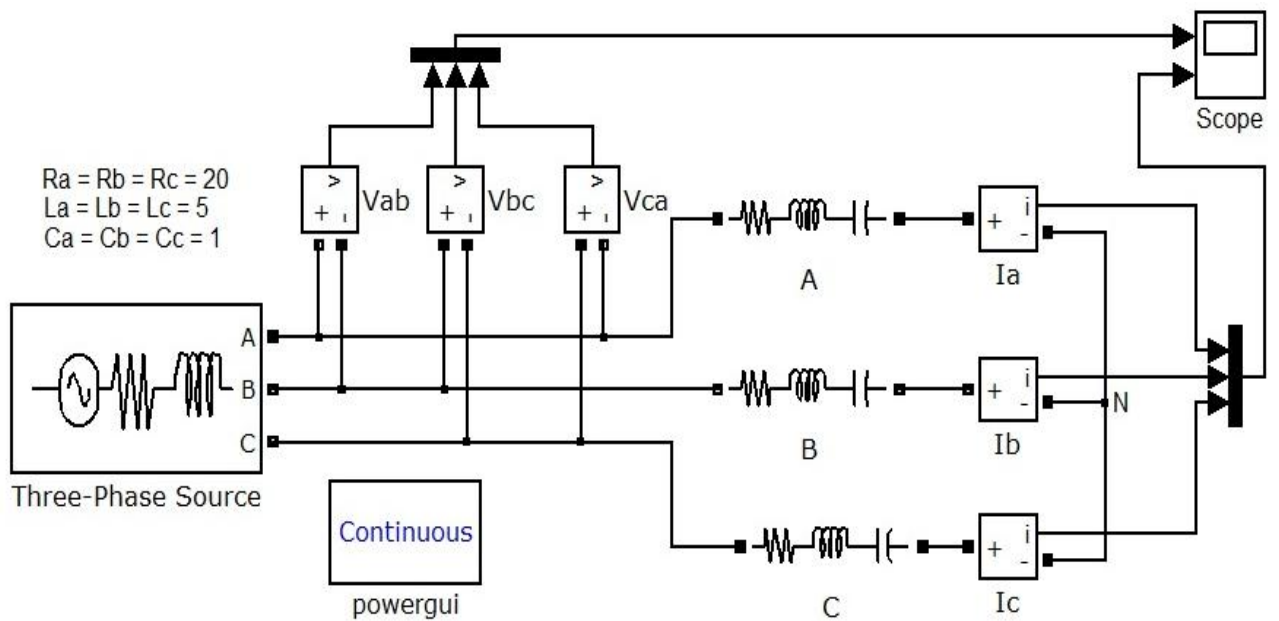


Output:

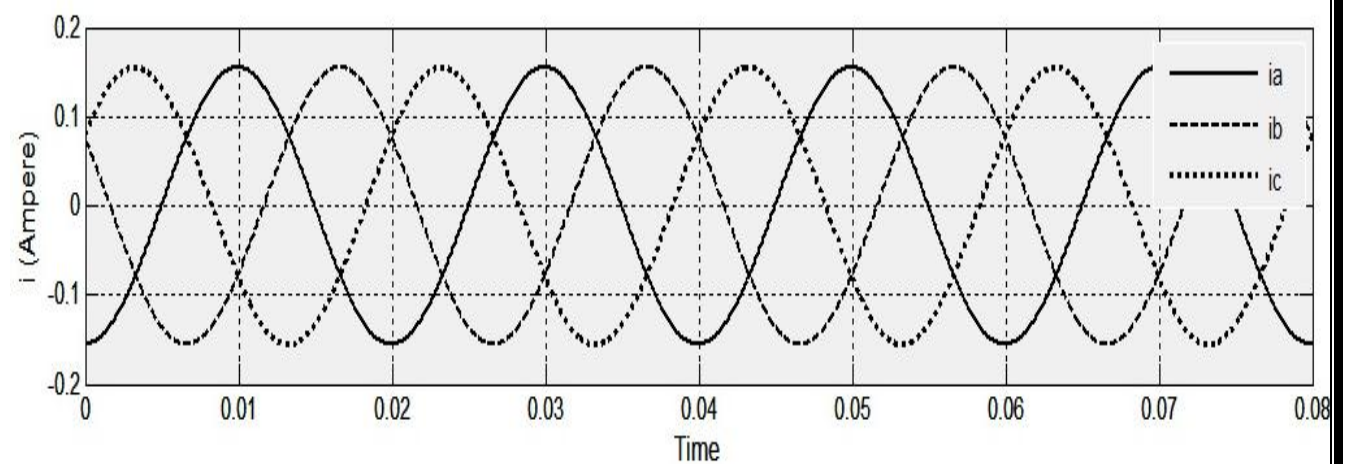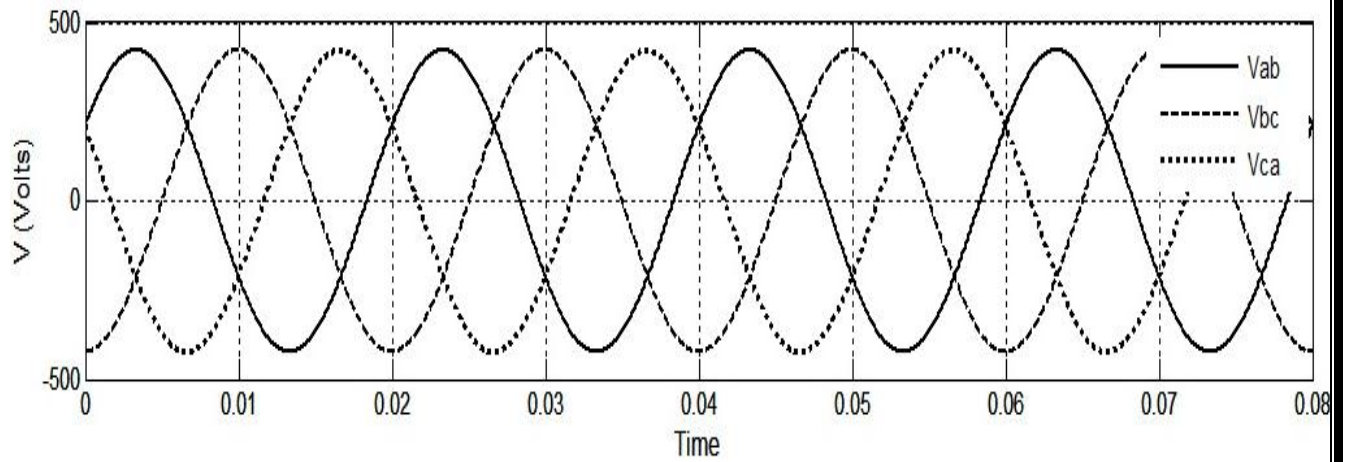

Aim: To simulate unbalanced 3 wire system.

Circuit Diagram:

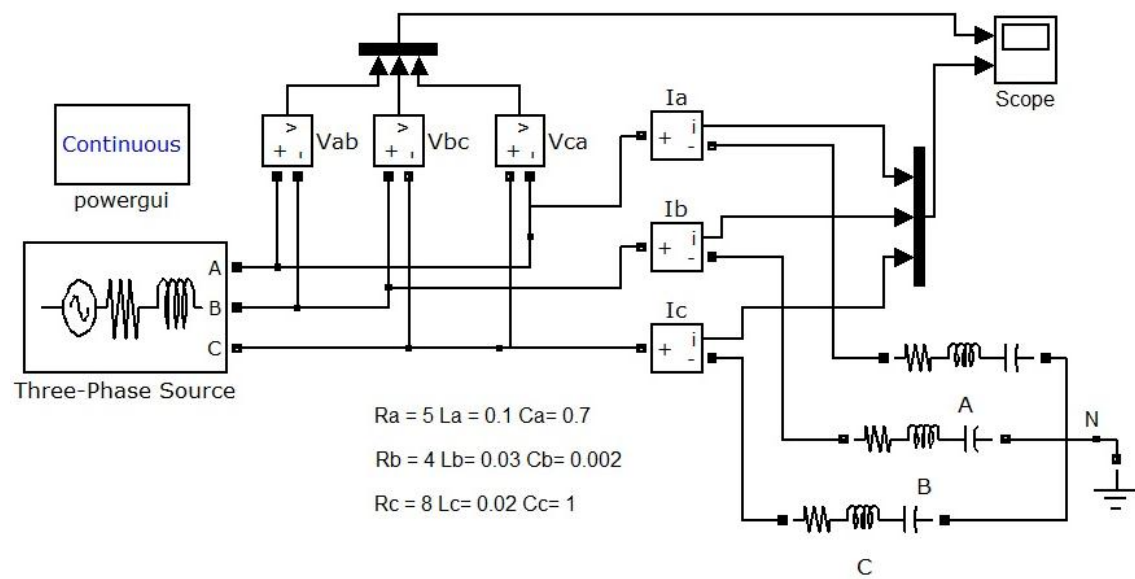

Output:

