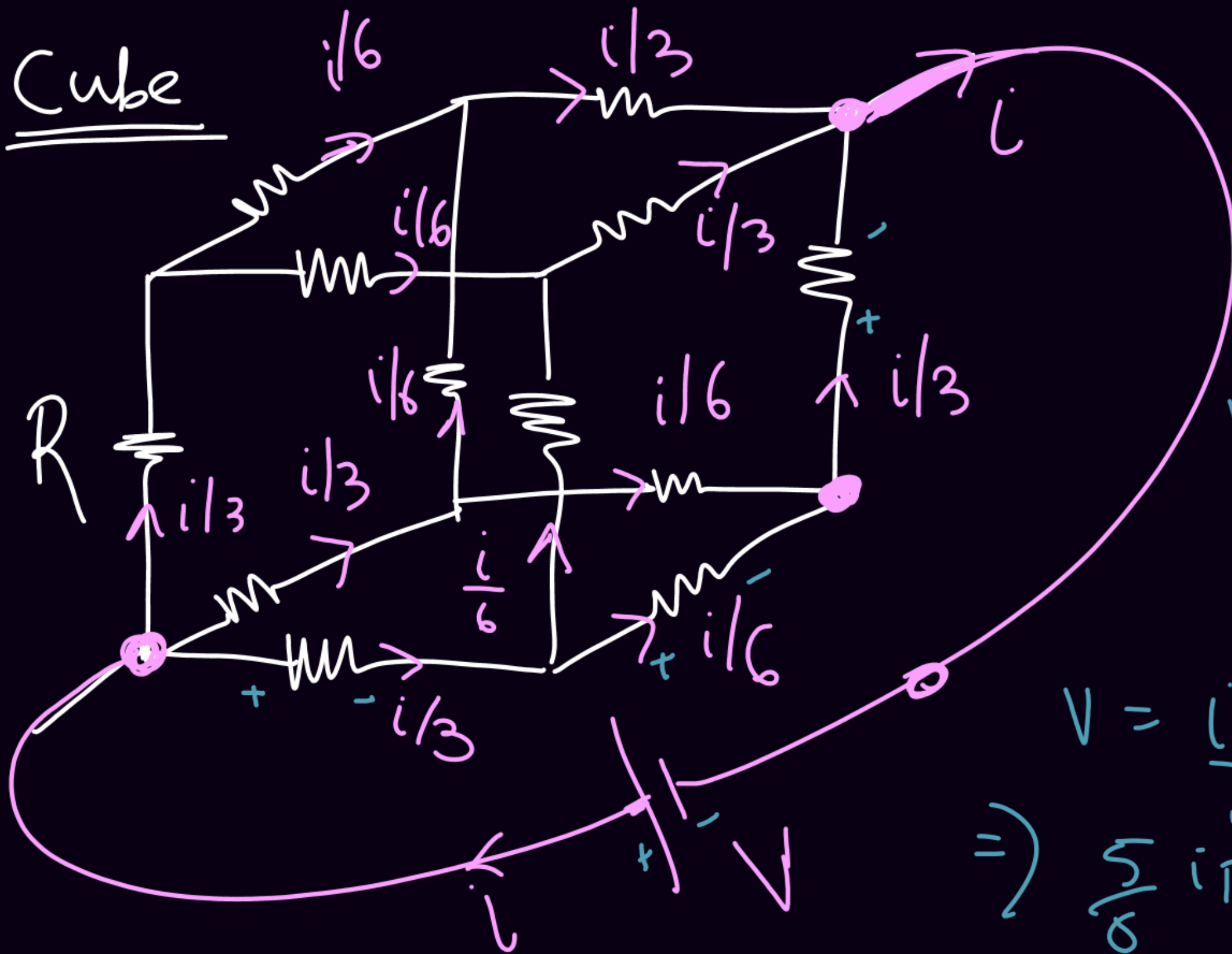


Electric Potential  
&  
Capacitance  
By Rohit Gupta

Today's Goal  
Grouping of Capacitors  
&  
Resistors





$$R_{eq} = \frac{V}{i}$$

$$V - \frac{iR}{3} - \frac{i}{6}R - \frac{i}{3}R = 0$$

$$V = \frac{iR}{3} \left( 1 + \frac{1}{2} + 1 \right)$$

$$\Rightarrow \frac{V}{i} = \frac{5R}{3} = \frac{10R}{6}$$

# Wheatstone bridge

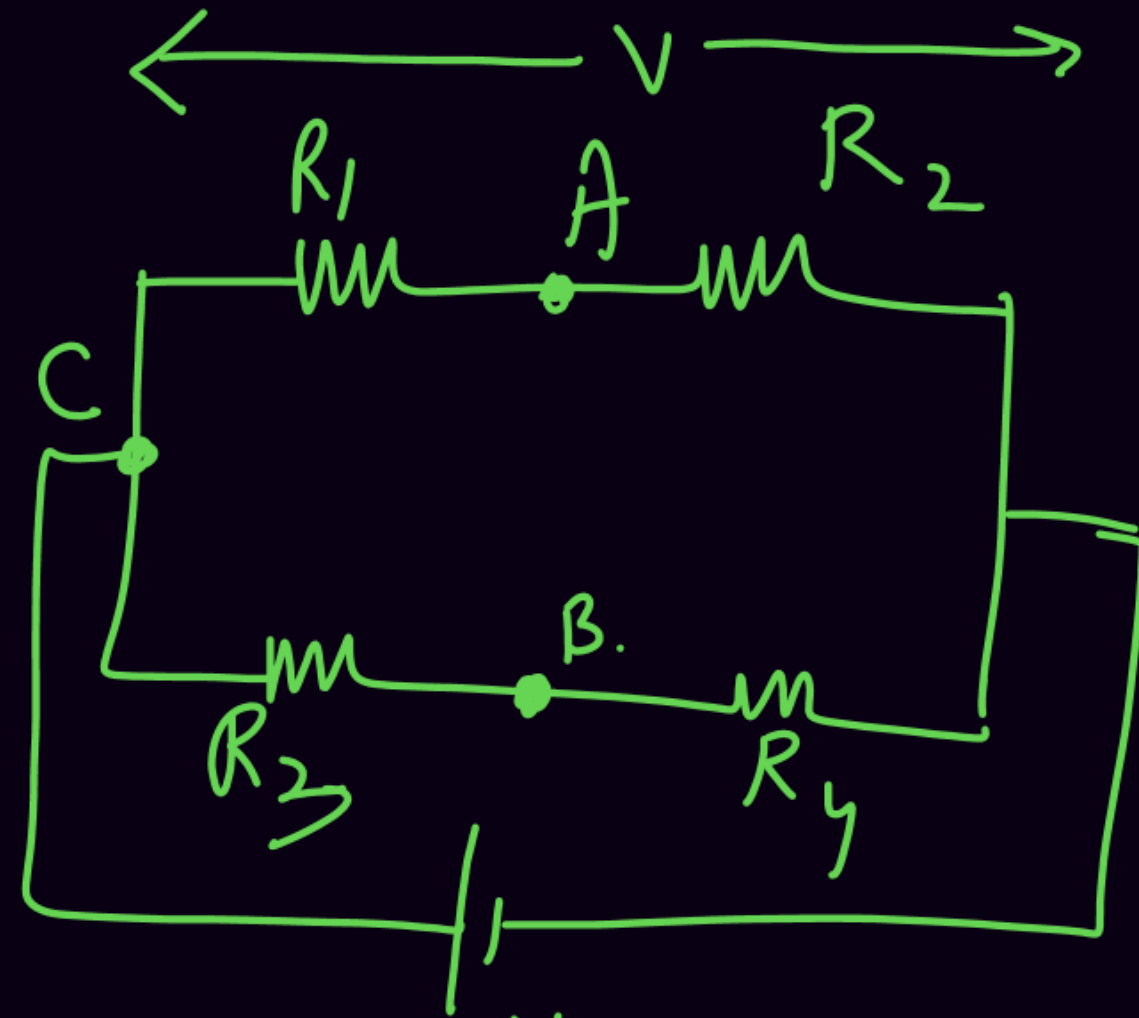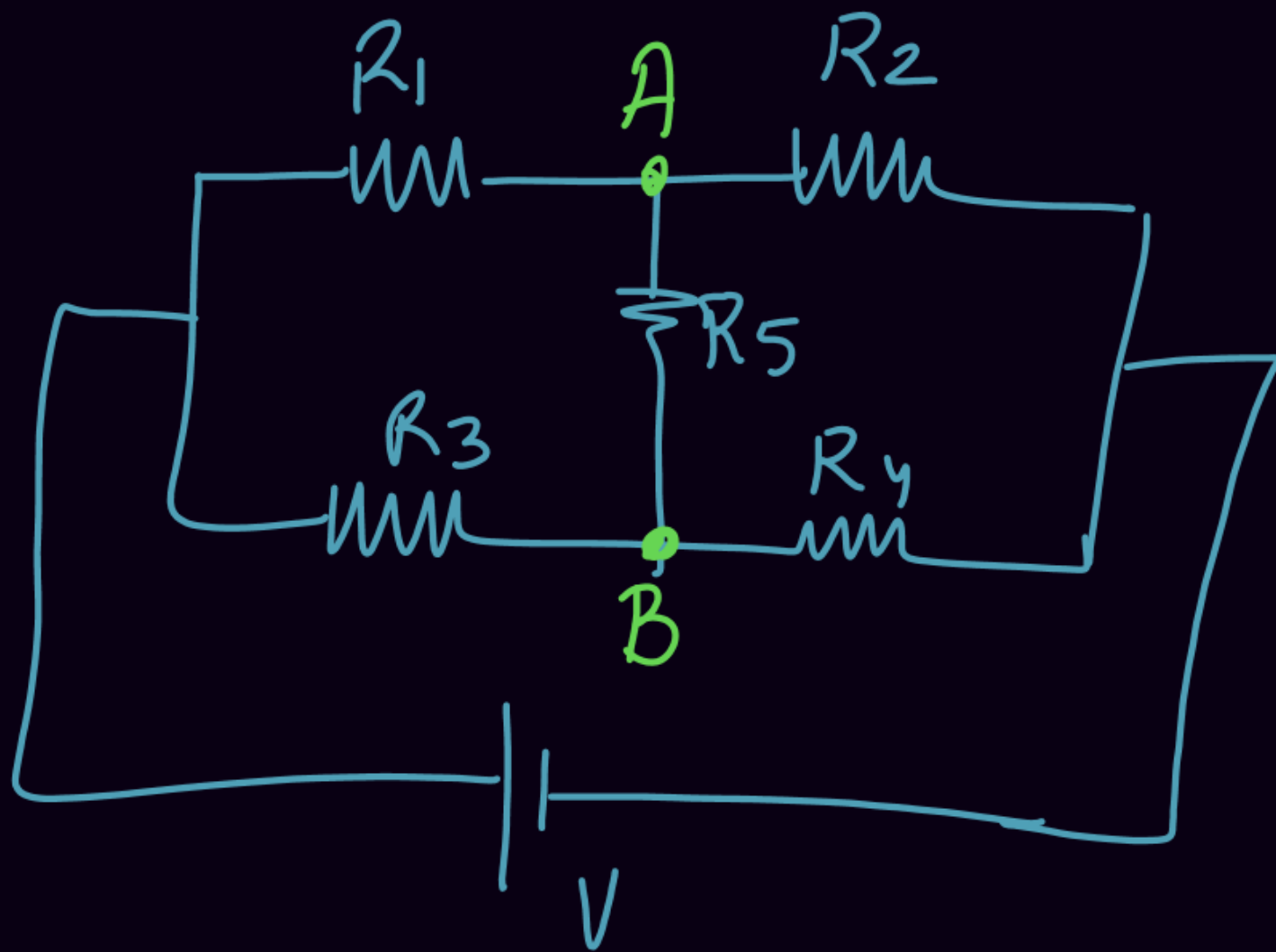

$$V_C - V_A = \frac{R_1 V}{R_1 + R_2}$$

$$V_C - V_B = \frac{R_3 V}{R_3 + R_4}$$

If  $V_A = V_B$  then

$$V_C - V_A = V_C - V_B$$


$$\frac{R_1 \cancel{V}}{R_1 + R_2} = \frac{R_3 \cancel{V}}{R_3 + R_4}$$

$$\frac{R_1 + R_2}{R_1} = \frac{R_3 + R_4}{R_3}$$


$$\cancel{1} + \frac{R_2}{R_1} = \cancel{1} + \frac{R_4}{R_3}$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

# \* Short circuit



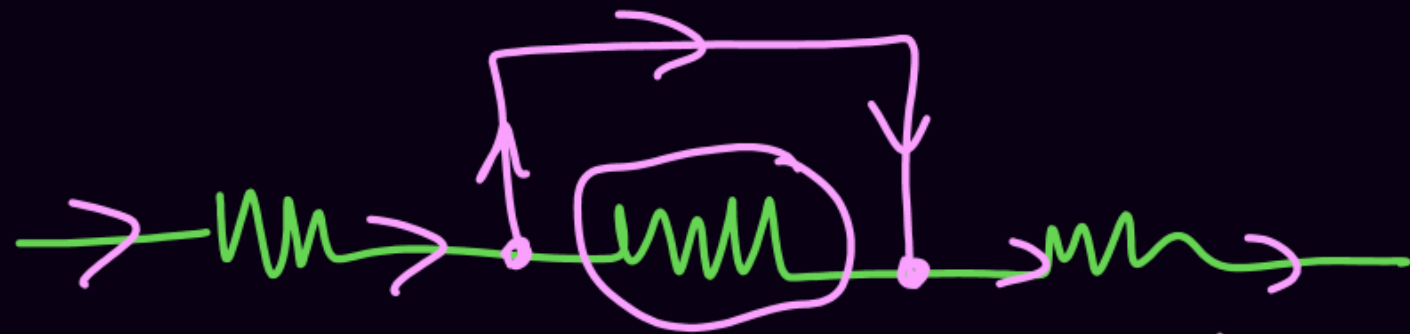


Short circuit

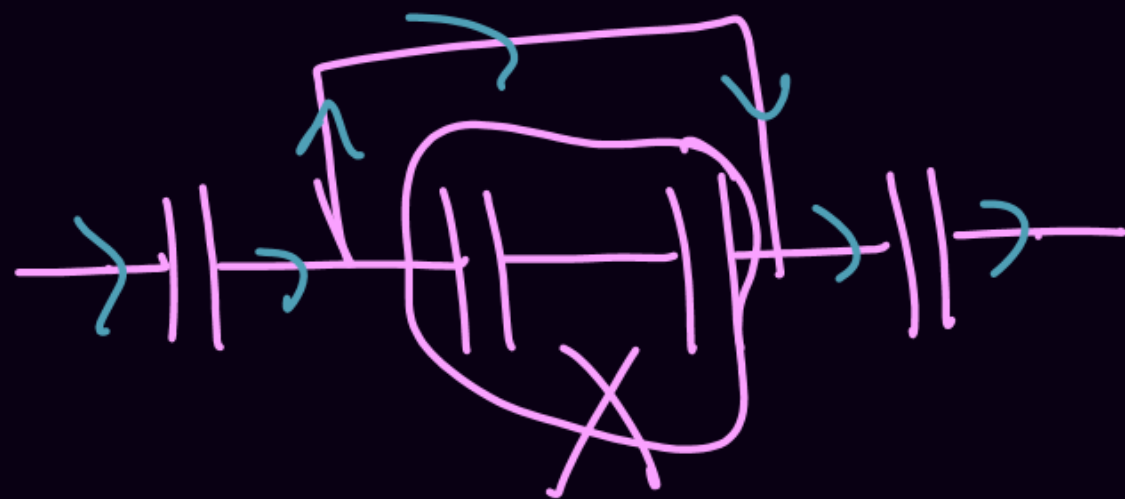

/

\* Junction open

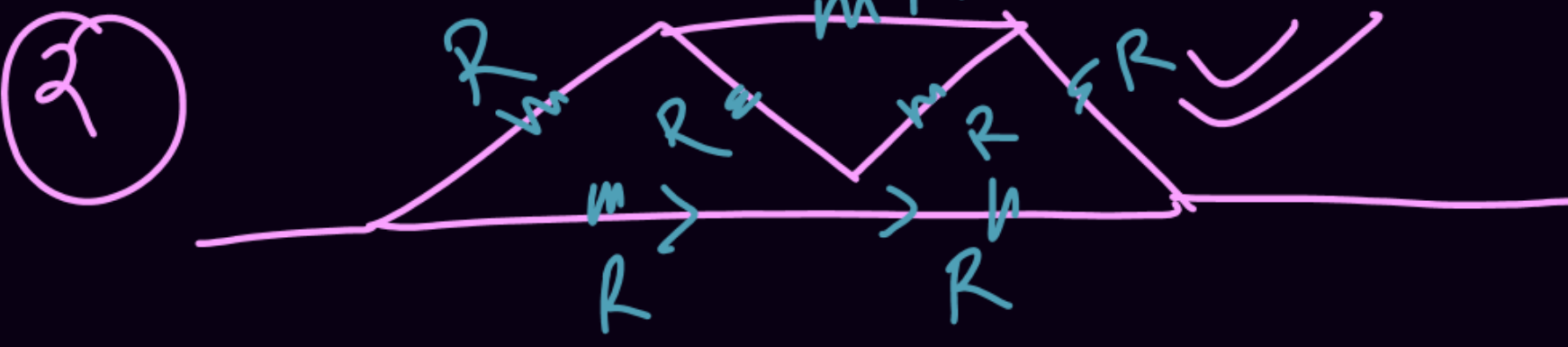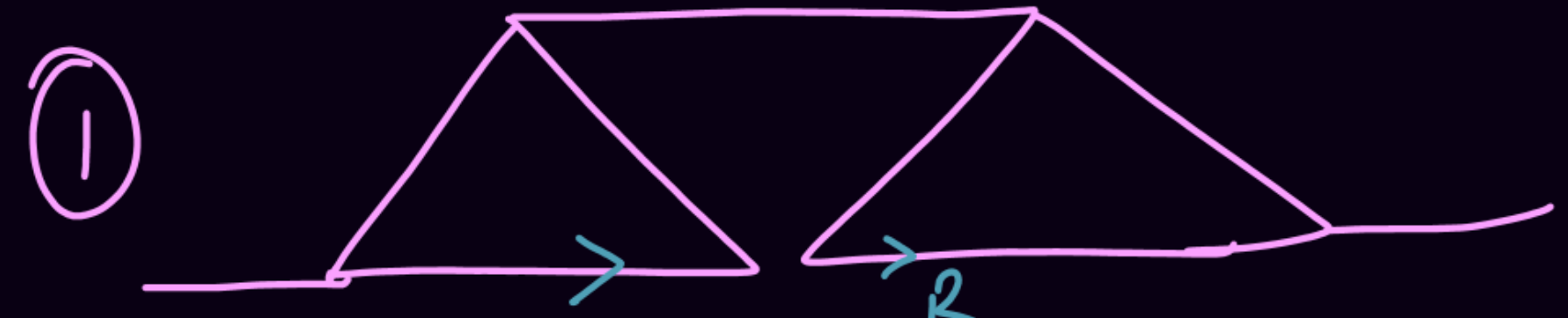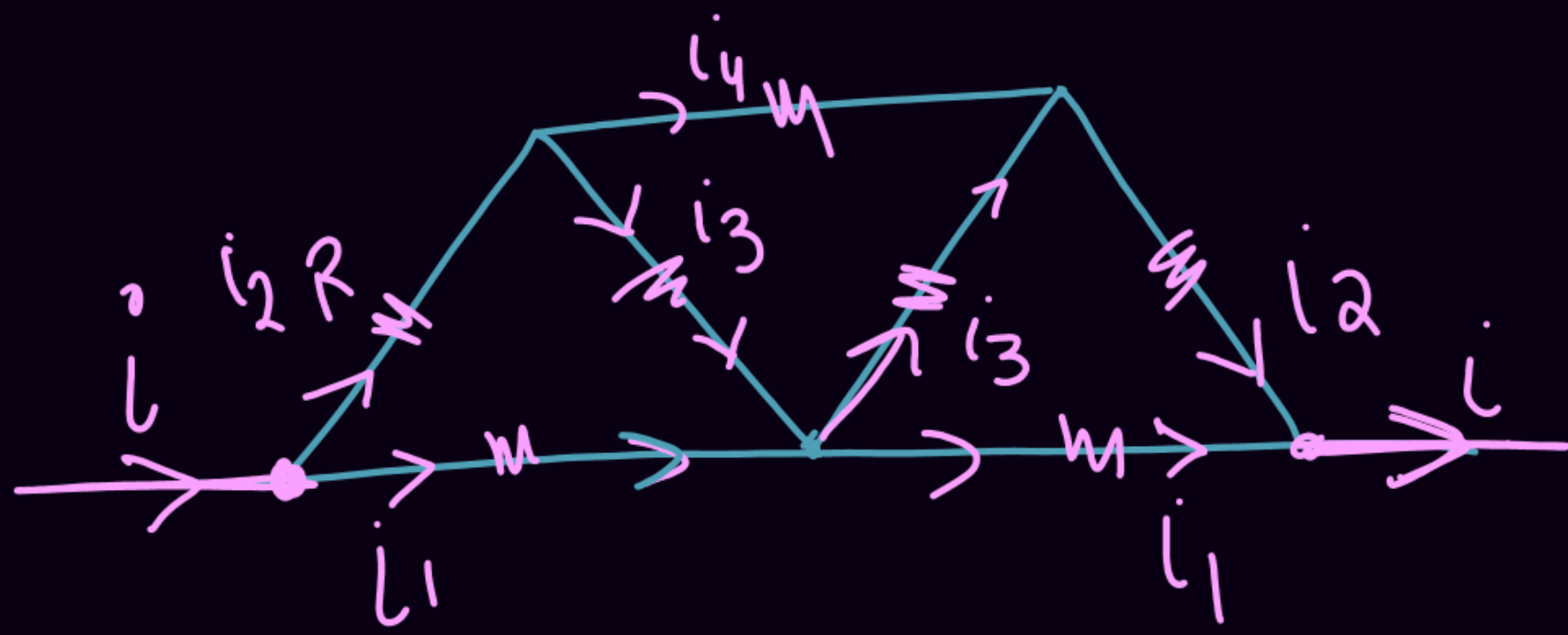




$$\left( \frac{2R}{3} + 2R \right) \parallel 2R.$$

$$\frac{8R}{3} \parallel 2R$$




$$\frac{8R \times 2R}{3}$$

$$\frac{8R}{3} + 2R.$$
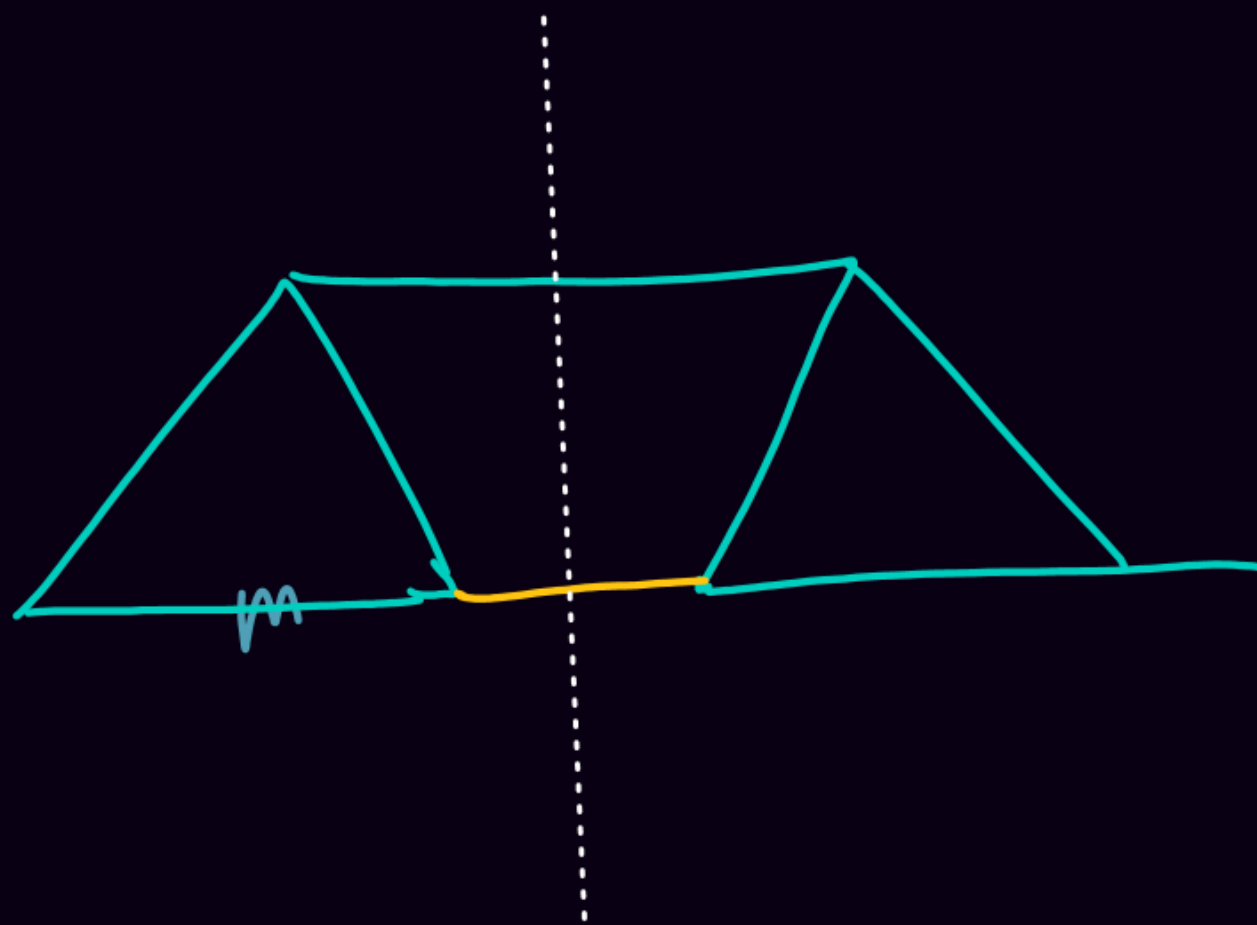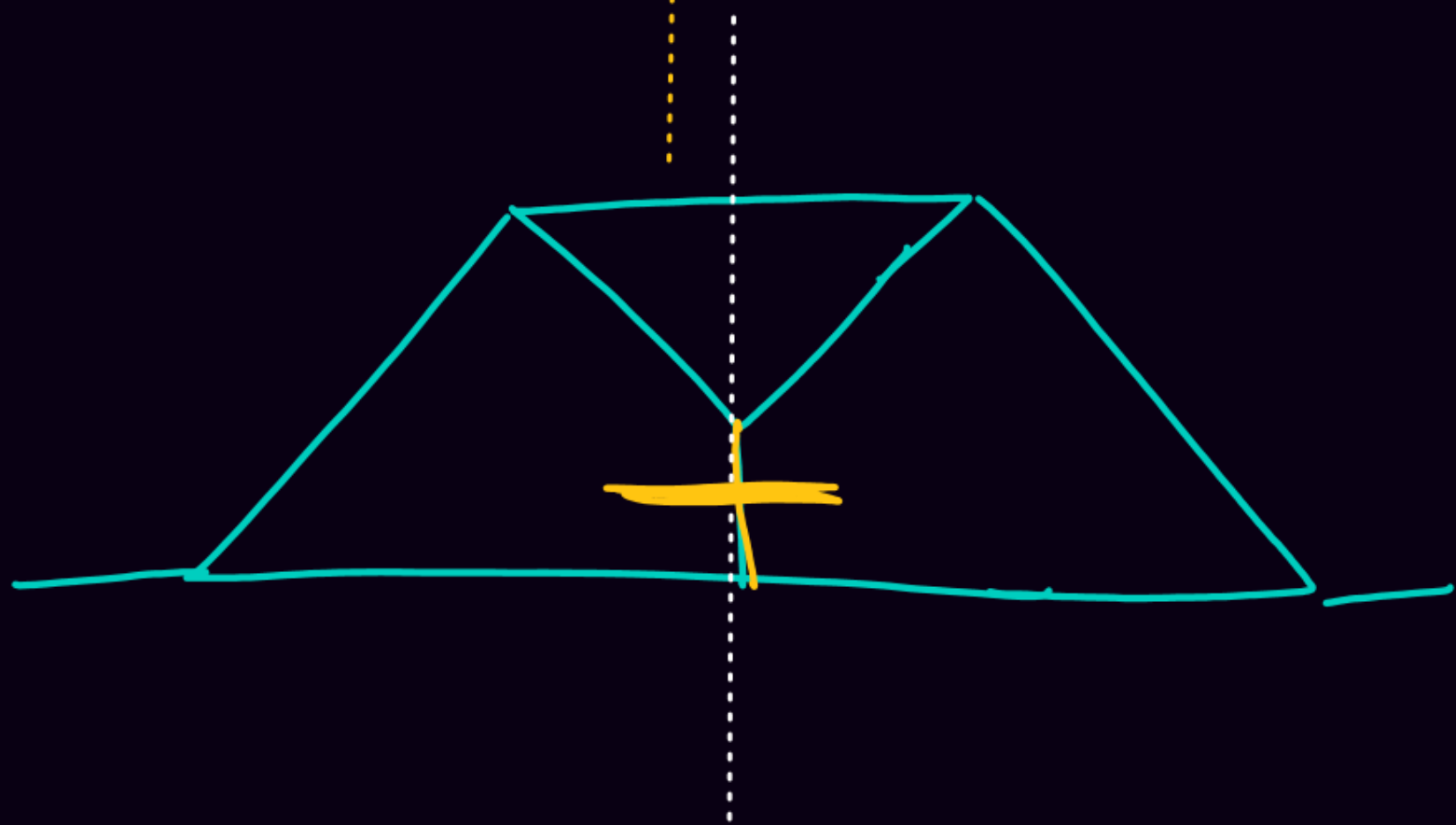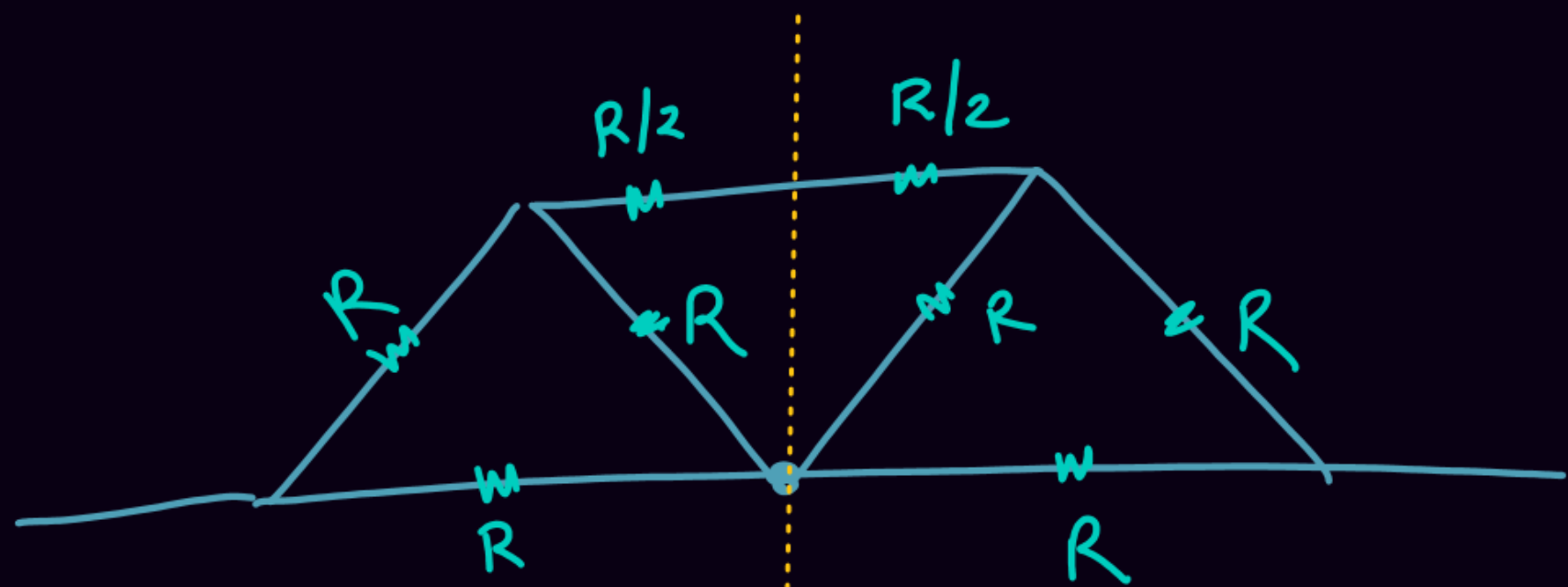
$$\Rightarrow \frac{16}{4} R = \frac{8R}{7}$$








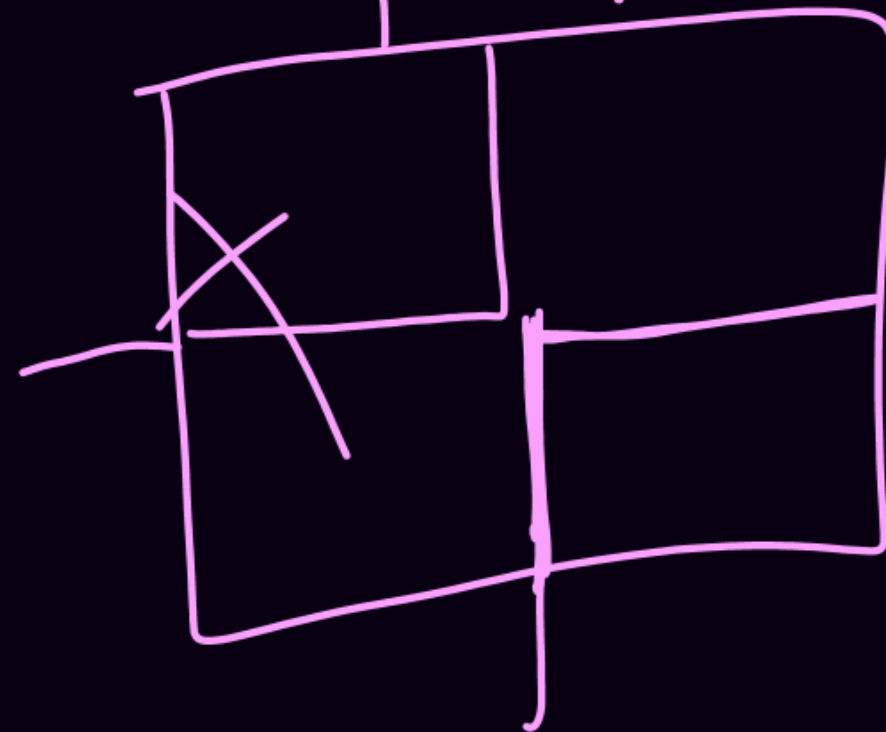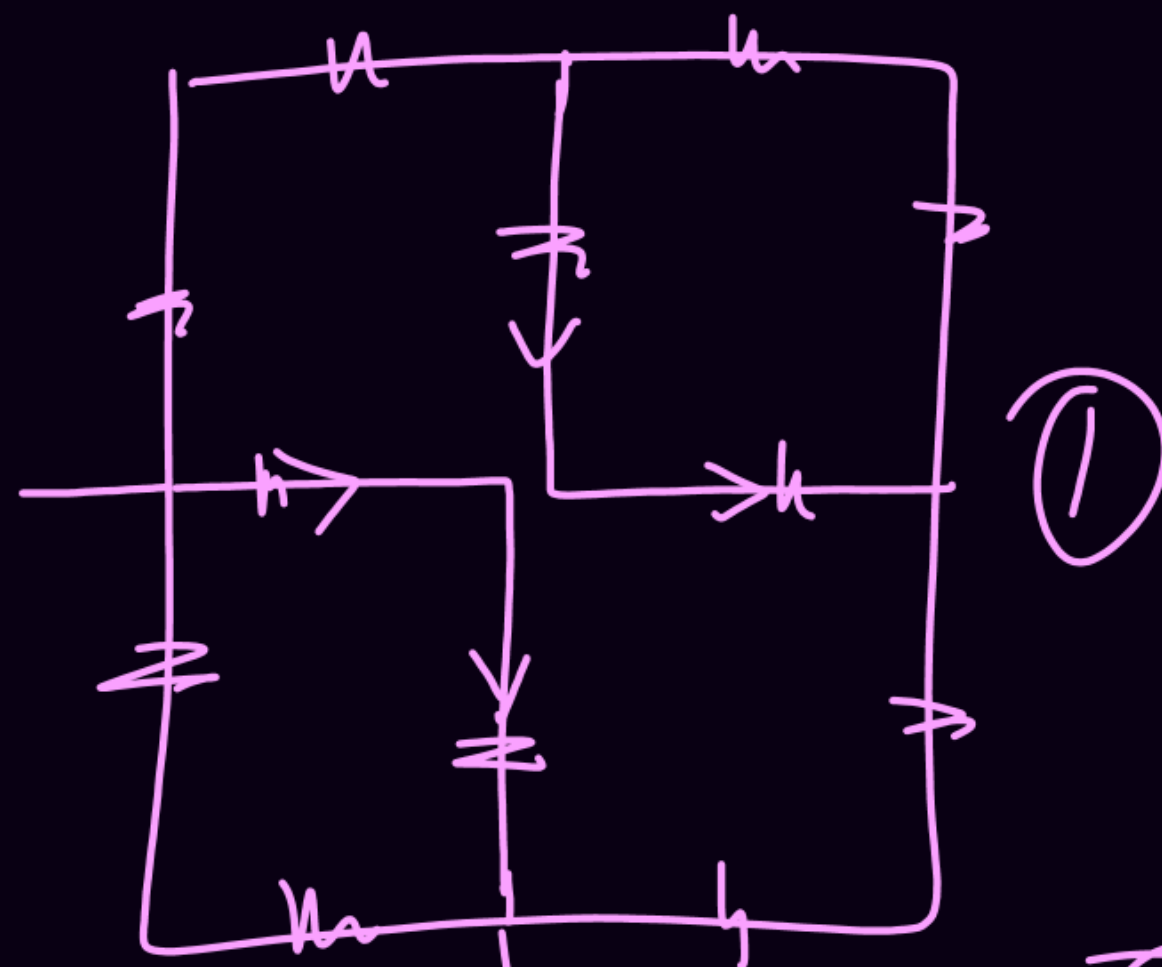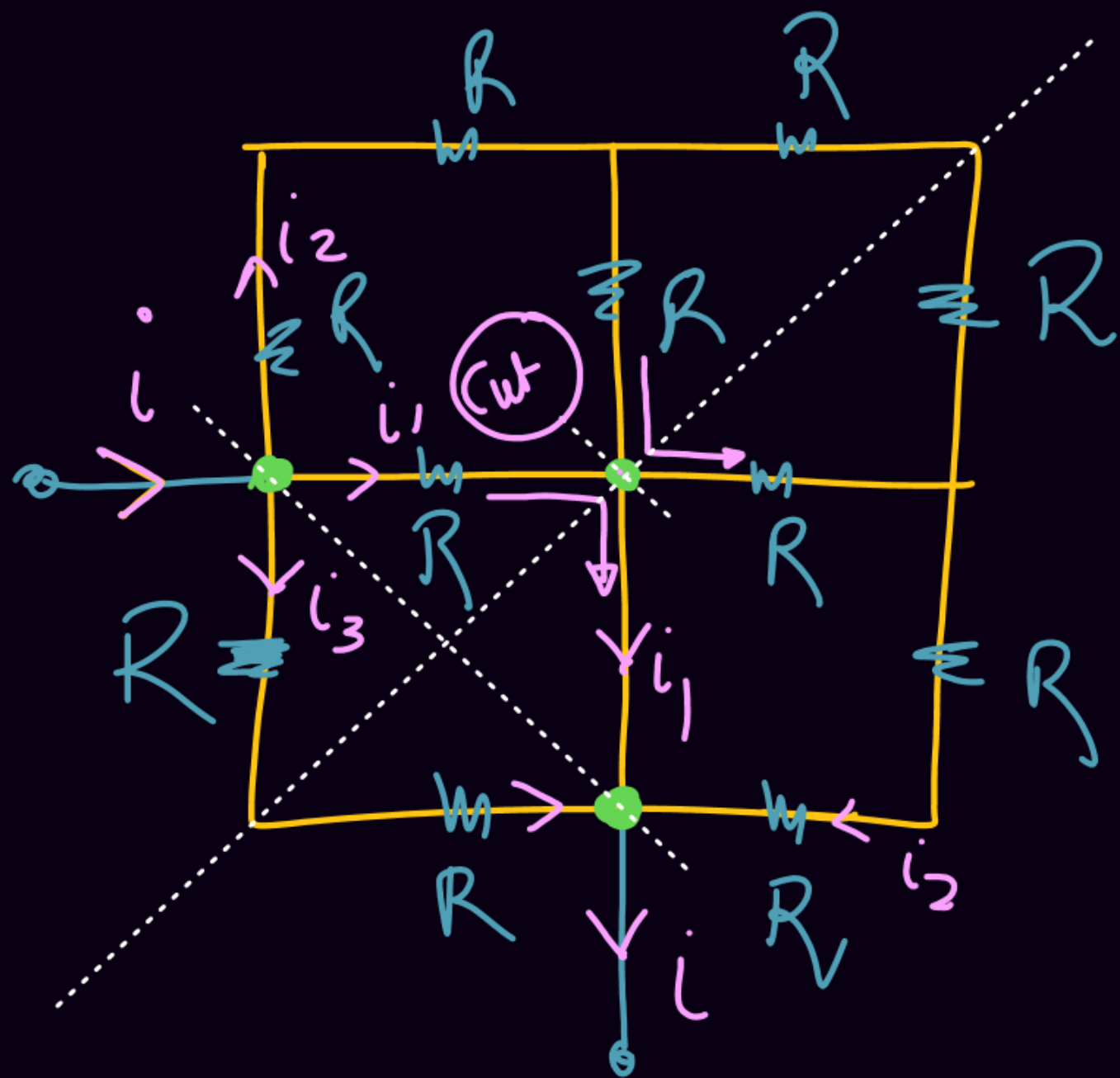





(1)

(2)

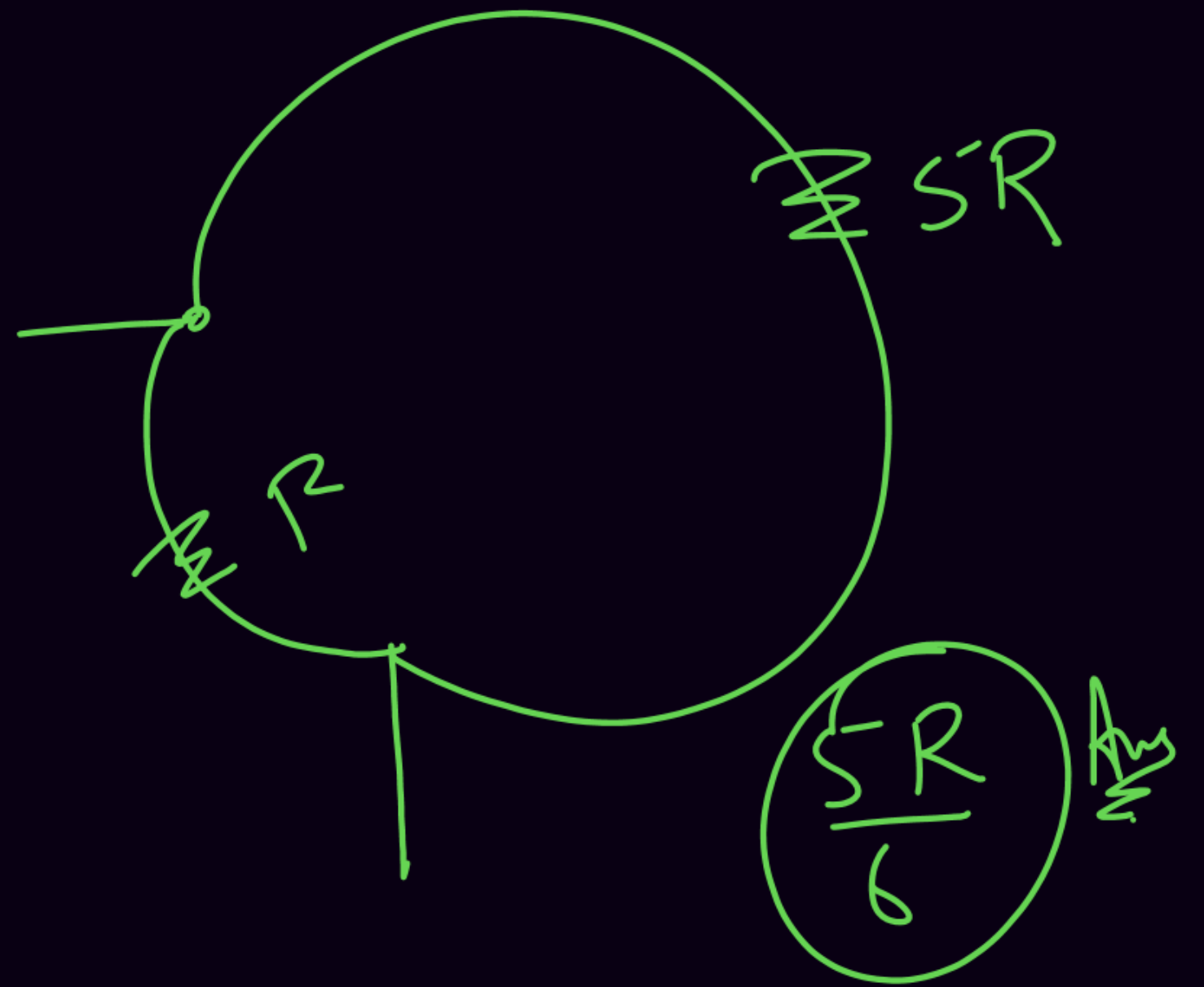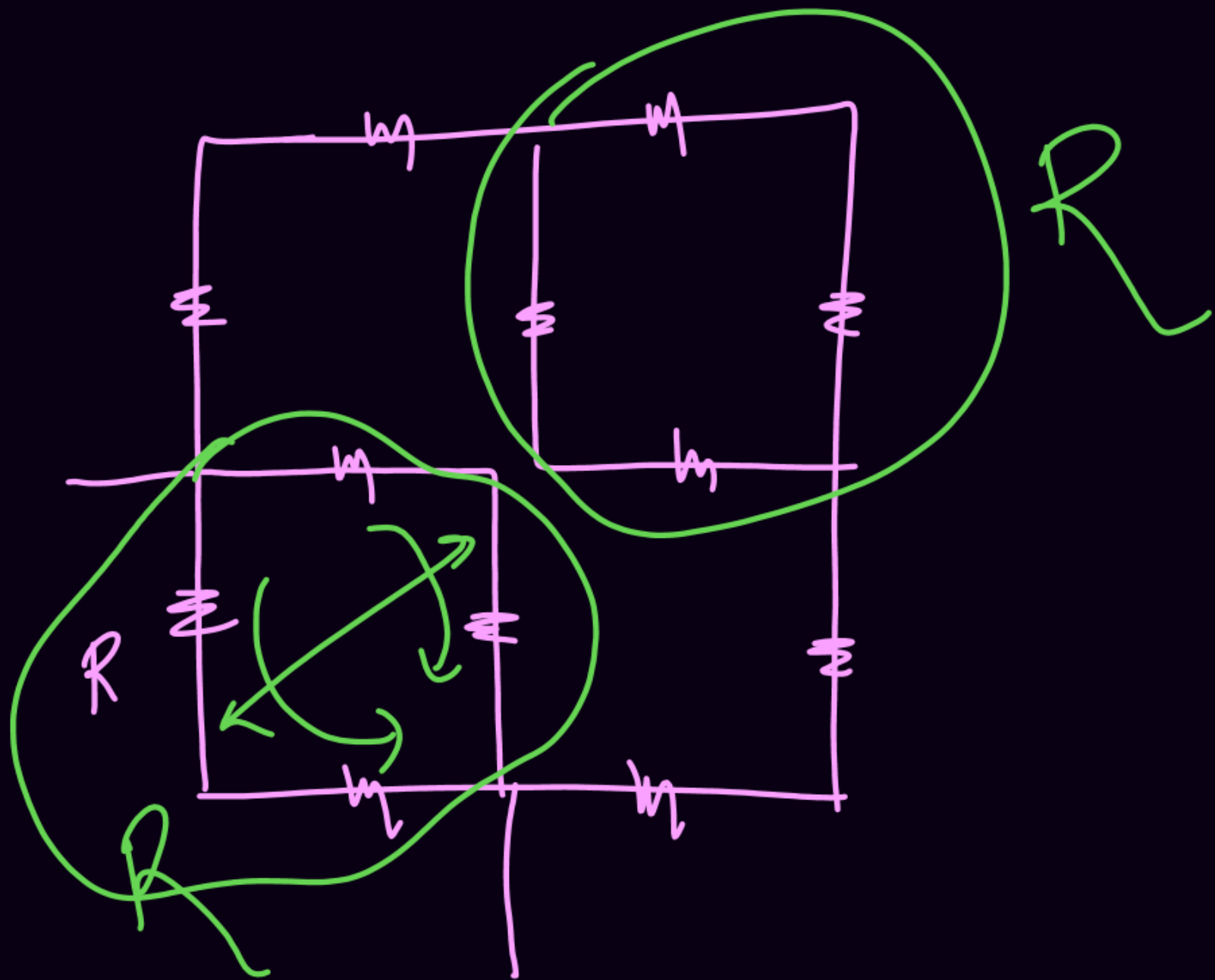


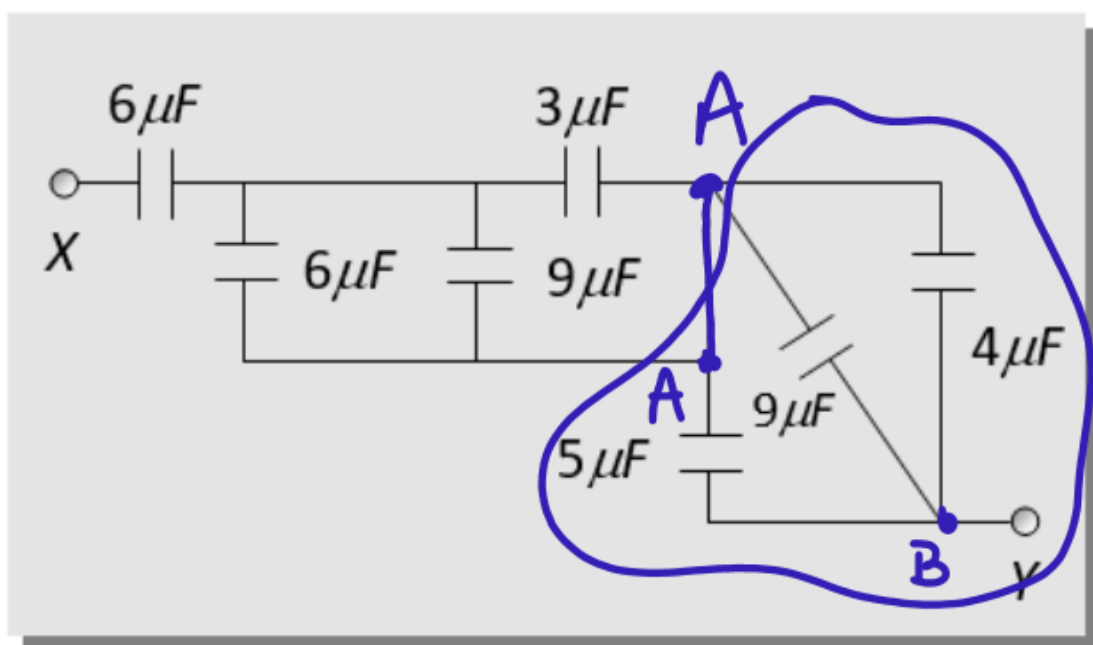

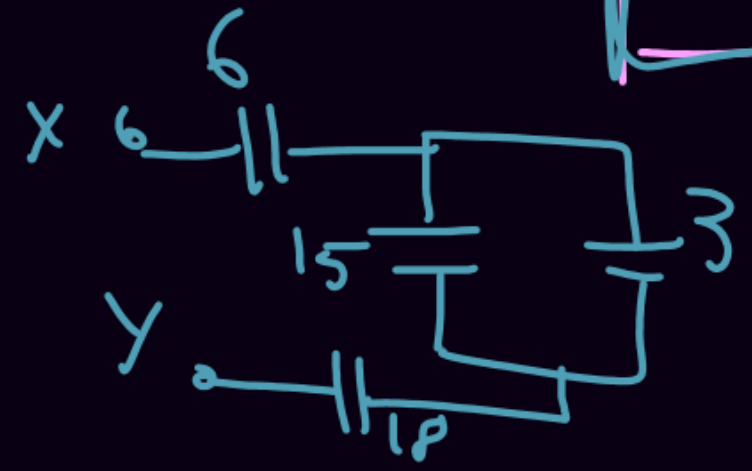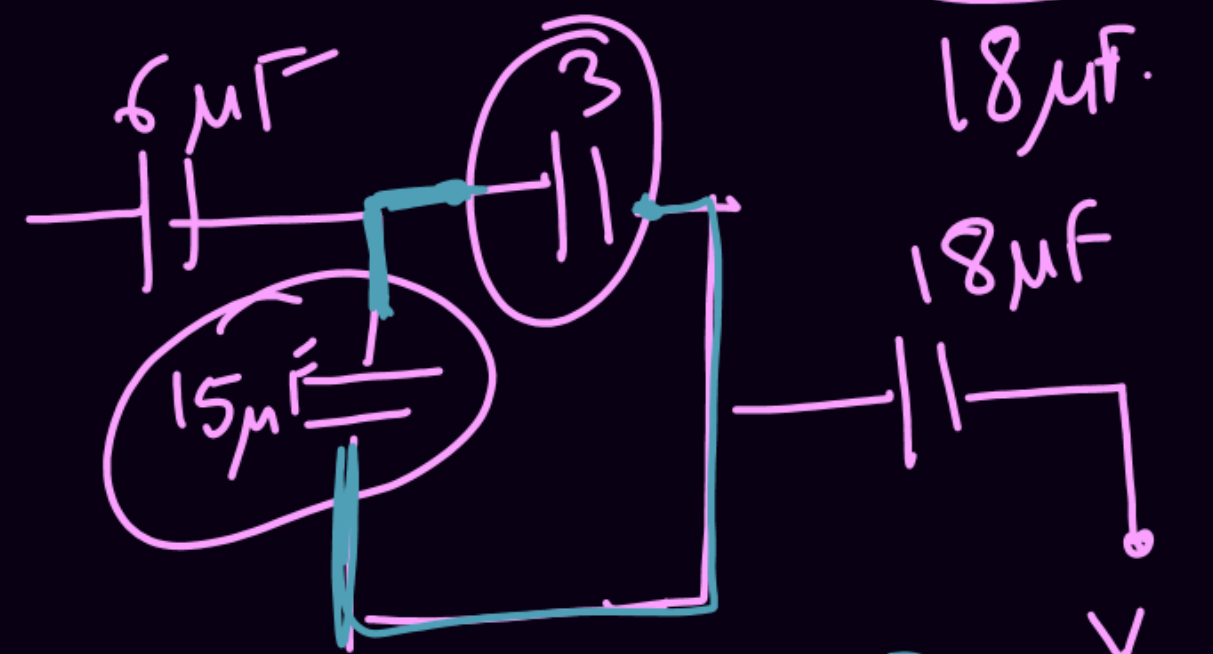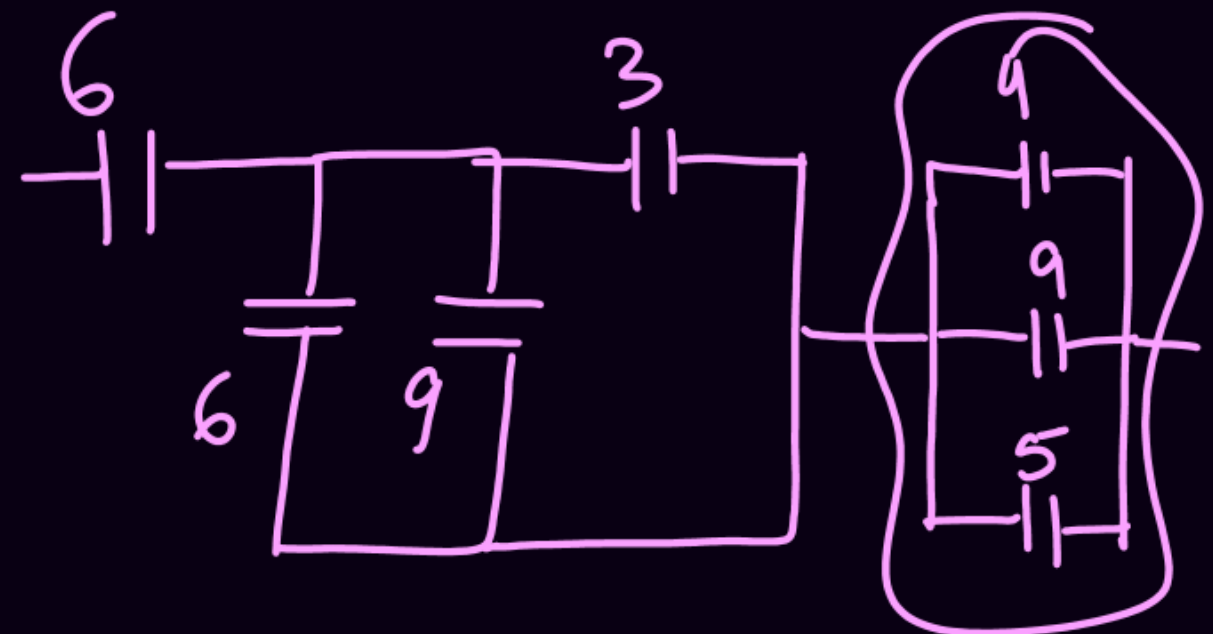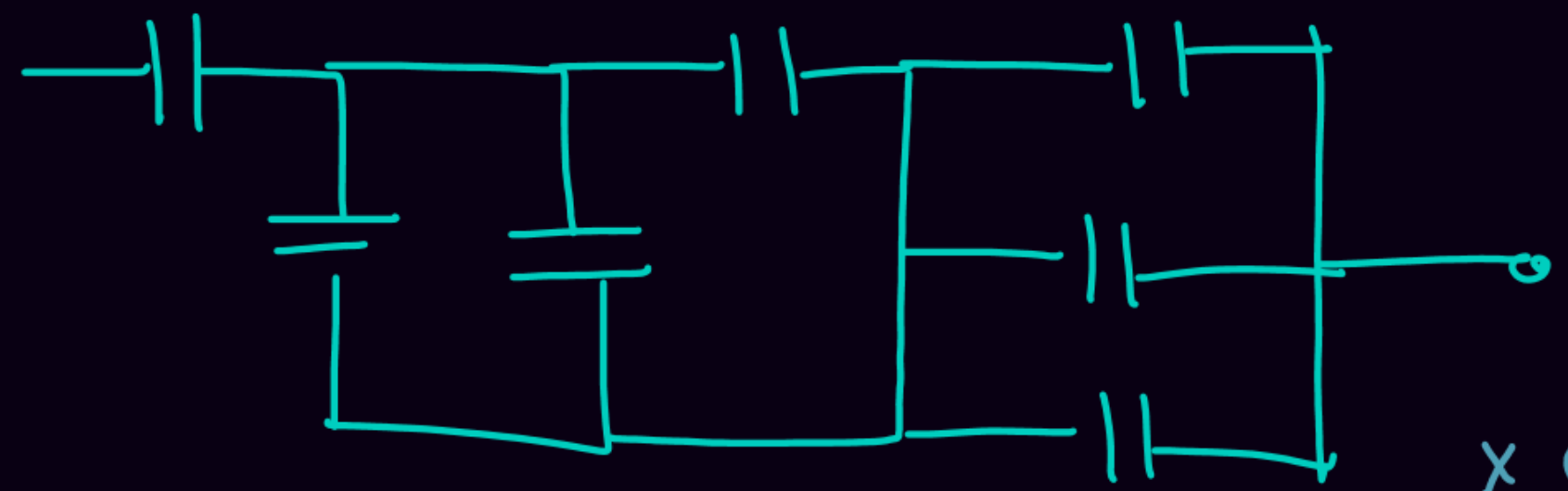
- ~~(a)  $3.6\mu F$~~
- (b)  $6\mu F$
- (c)  $1.5\mu F$
- (d)  $9\mu F$



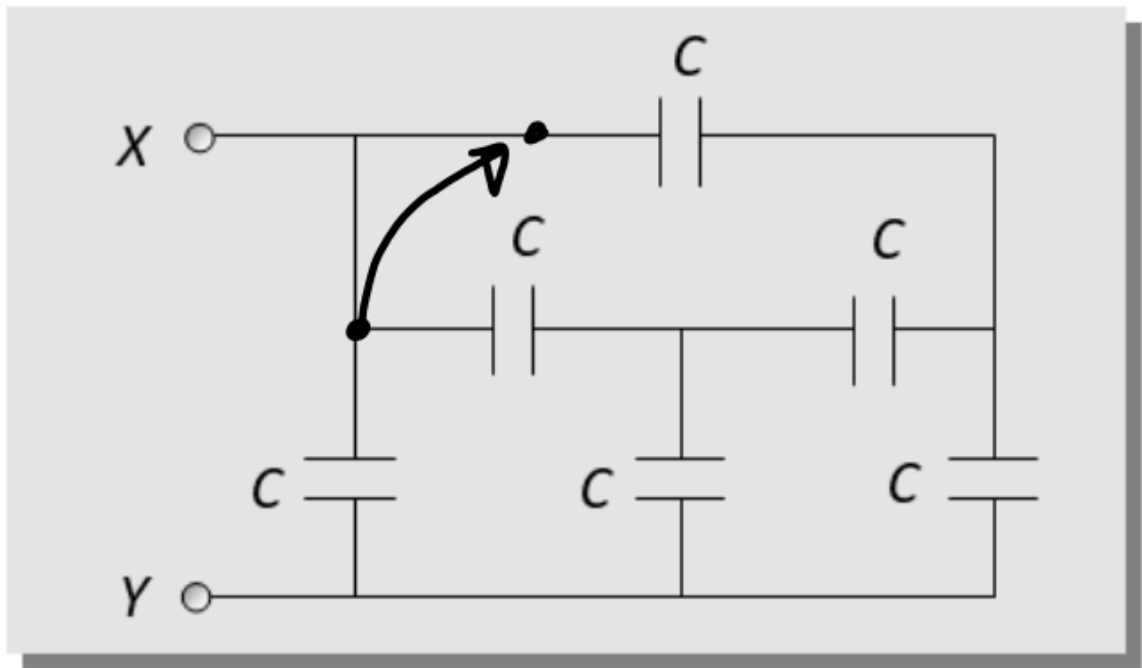
$$\frac{9 \times 18}{9 + 18} = \frac{18}{3} = 3.6$$




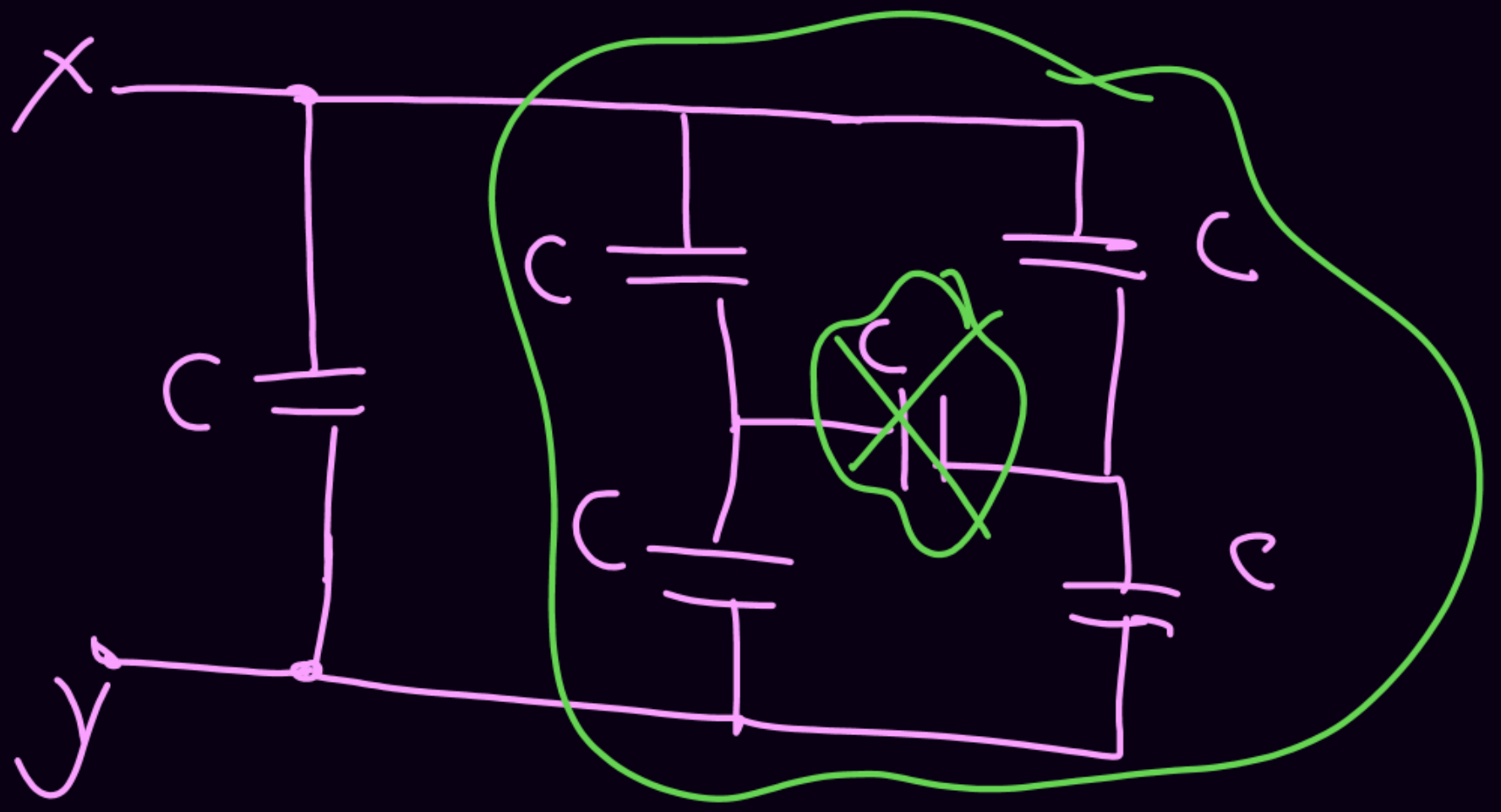- (a)  $C/2$
- (b)  $C$
- ~~(c)  $2C$~~
- (d)  $6C$



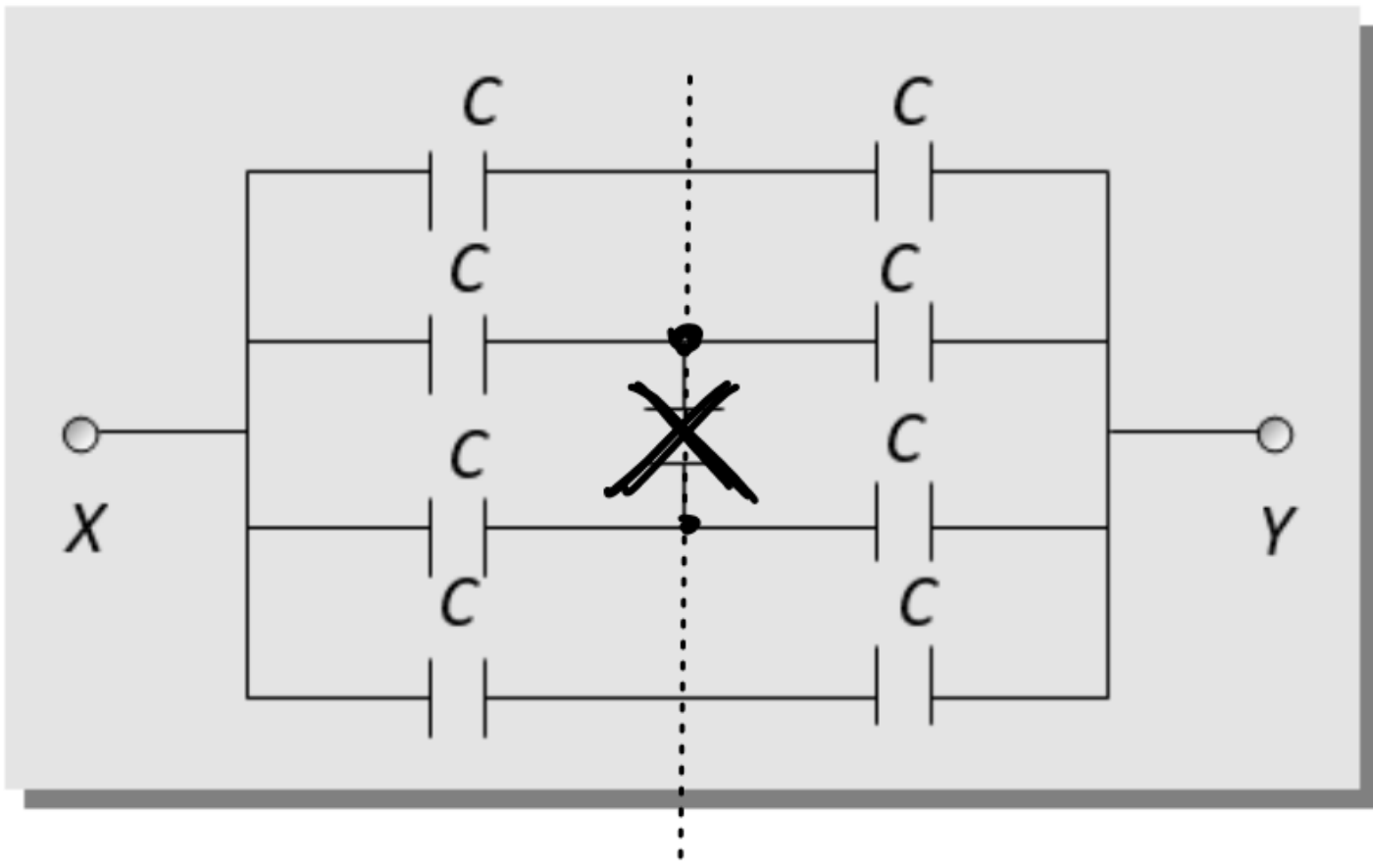

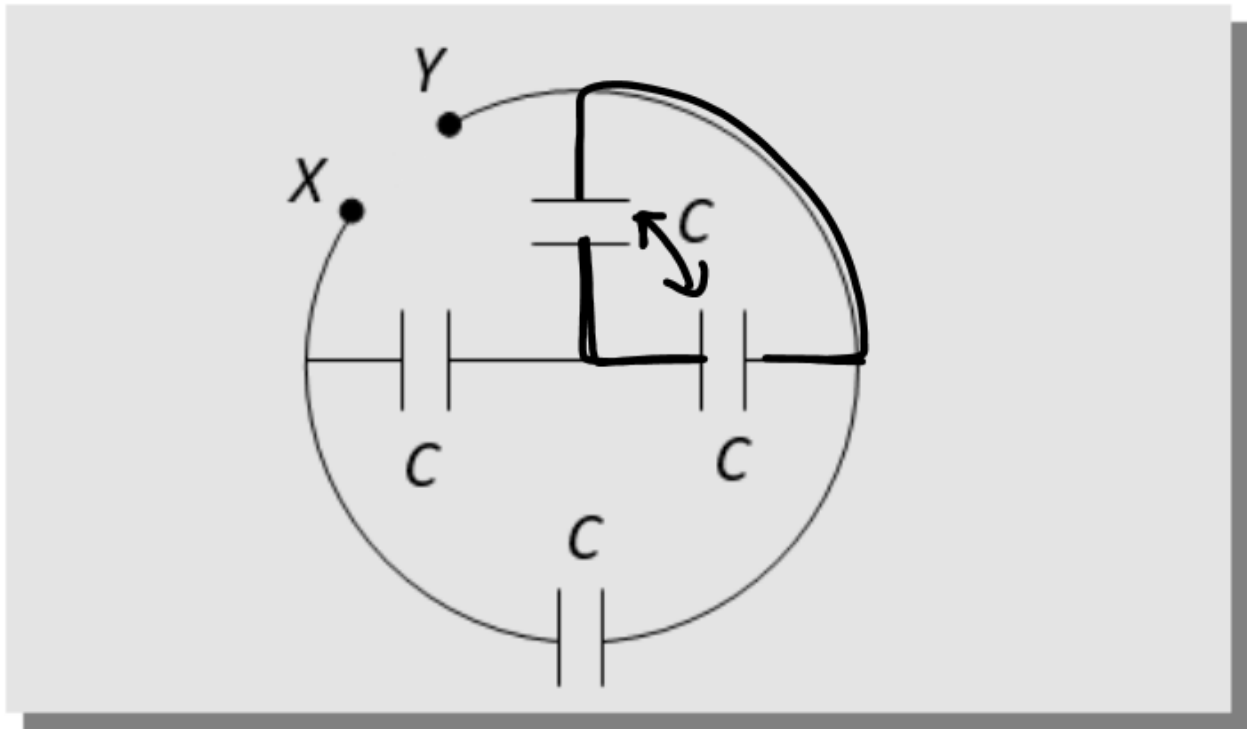- (a)  $C$
- (b)  $C/2$
- ~~(c)  $2C$~~
- (d)  $3C$





~~(a)~~  $\frac{5}{3}C$


(b)  $\frac{2}{3}C$

(c)  $C$

(d)  $2C$

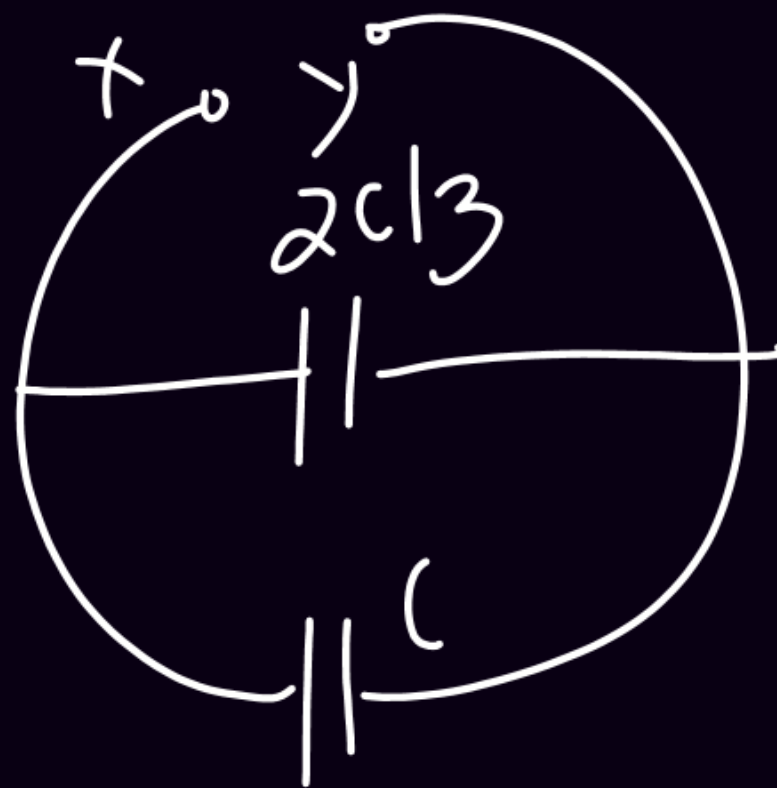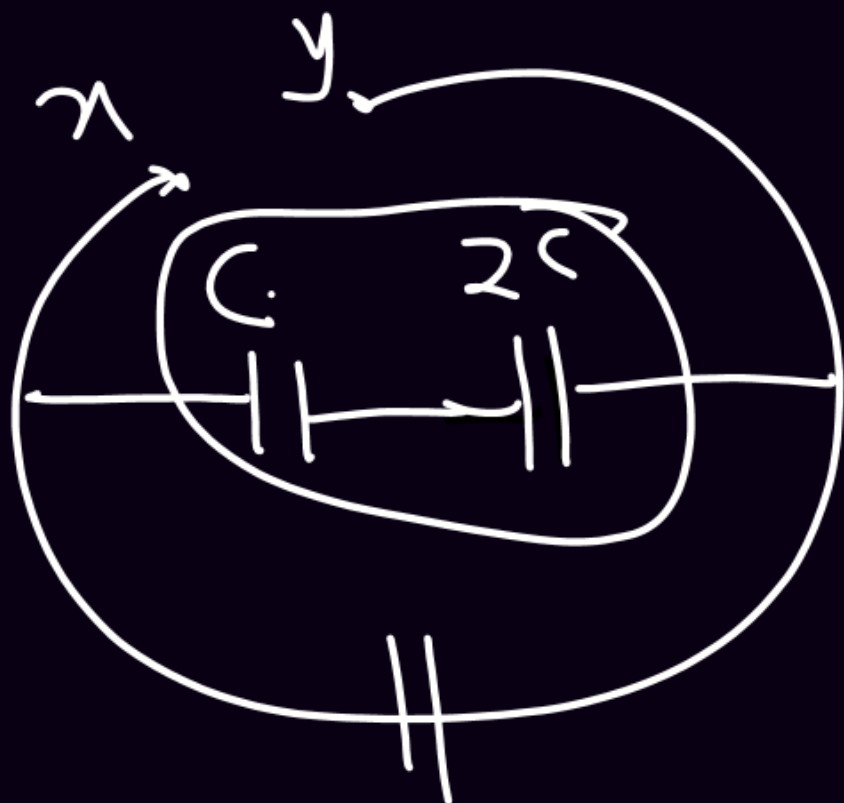

$\frac{2C}{3} + C = \frac{5C}{3}$

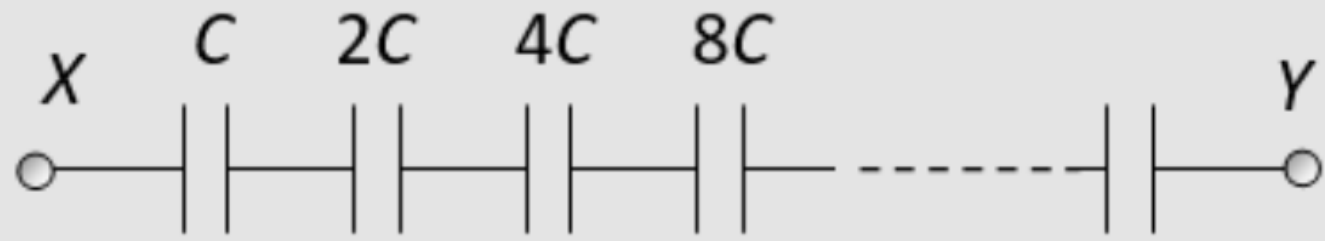

(a) C

~~(b) C/2~~

(c) 2C

(d)  $\infty$

$$S_{\infty} = \frac{a}{1-r} \quad \left( \begin{array}{l} a=1 \\ r=\frac{1}{2} \end{array} \right)$$

$$= \frac{1}{1-\frac{1}{2}}$$


$$= \frac{2}{2-1}$$

$$= 2$$


$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{2C} + \frac{1}{4C} + \frac{1}{8C} + \dots$$

$$= \frac{1}{C} \left( 1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots \right)$$

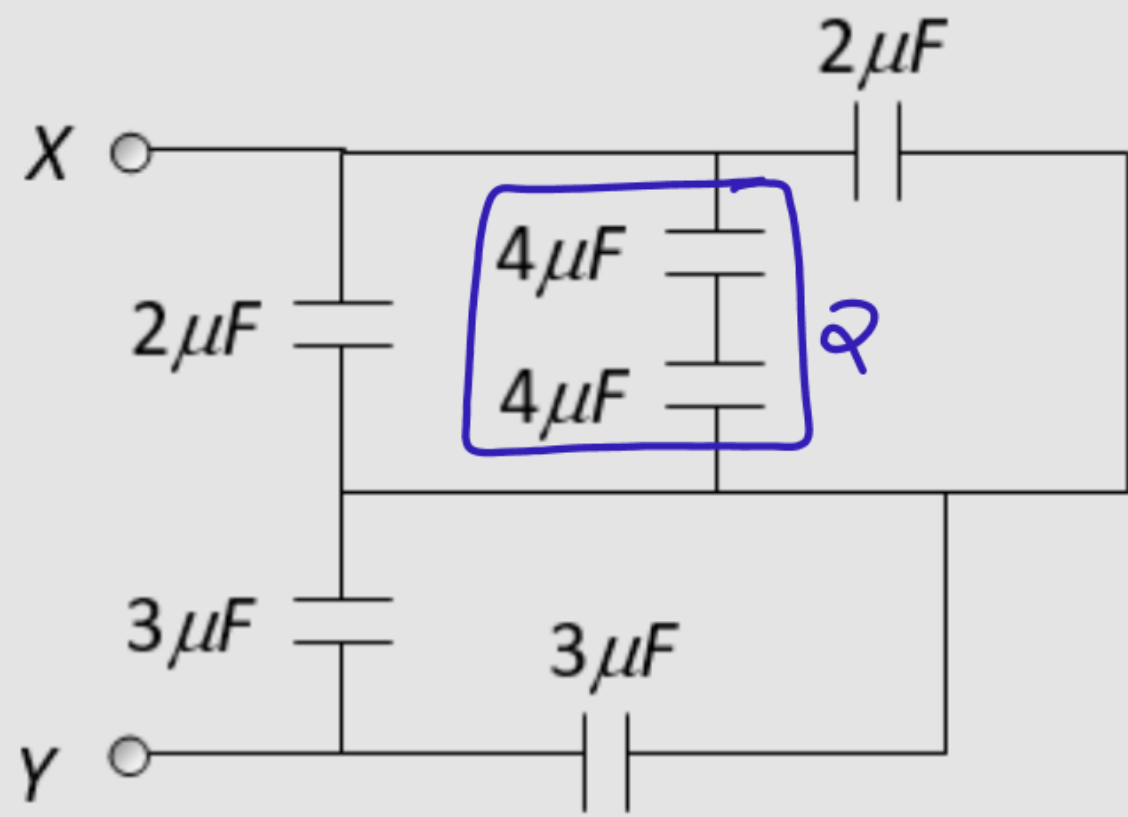
$$\frac{1}{C_{eq}} = \frac{2}{C} \Rightarrow C_{eq} = C/2$$



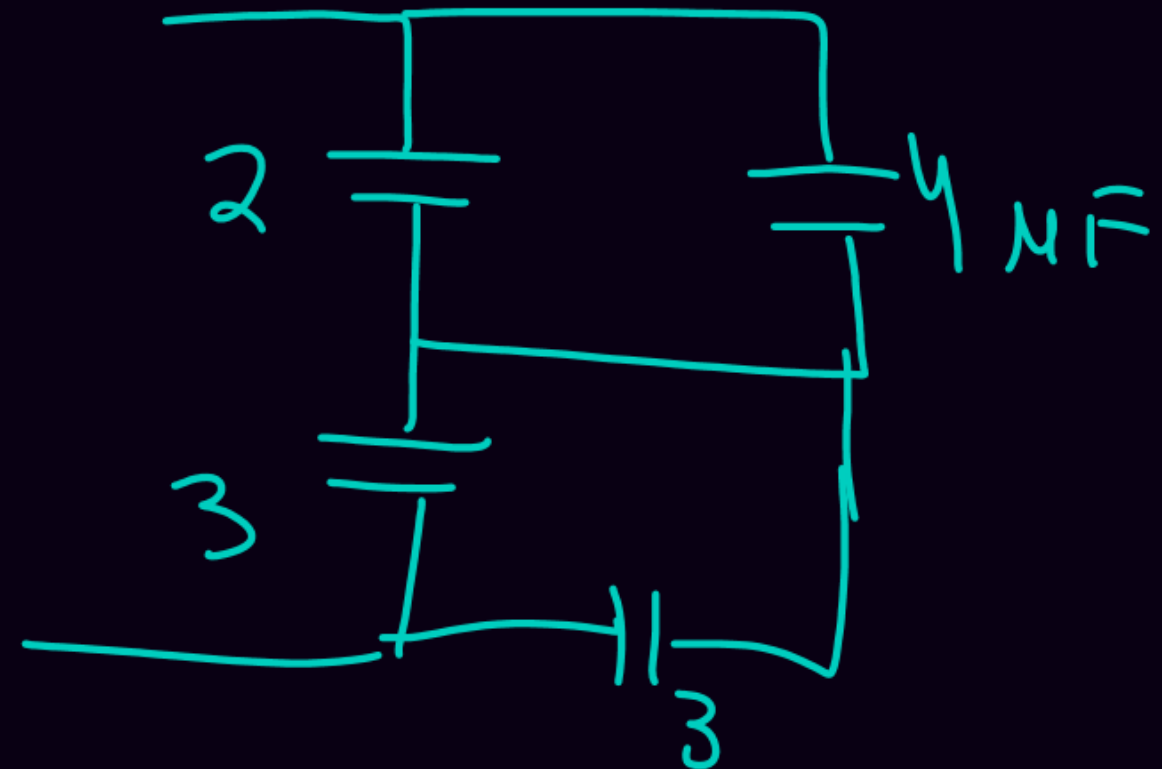- (a)  $17/6\mu F$
- (b)  $12/17\mu F$
- (c)  $6/5\mu F$
- ~~(d)  $3\mu F$~~





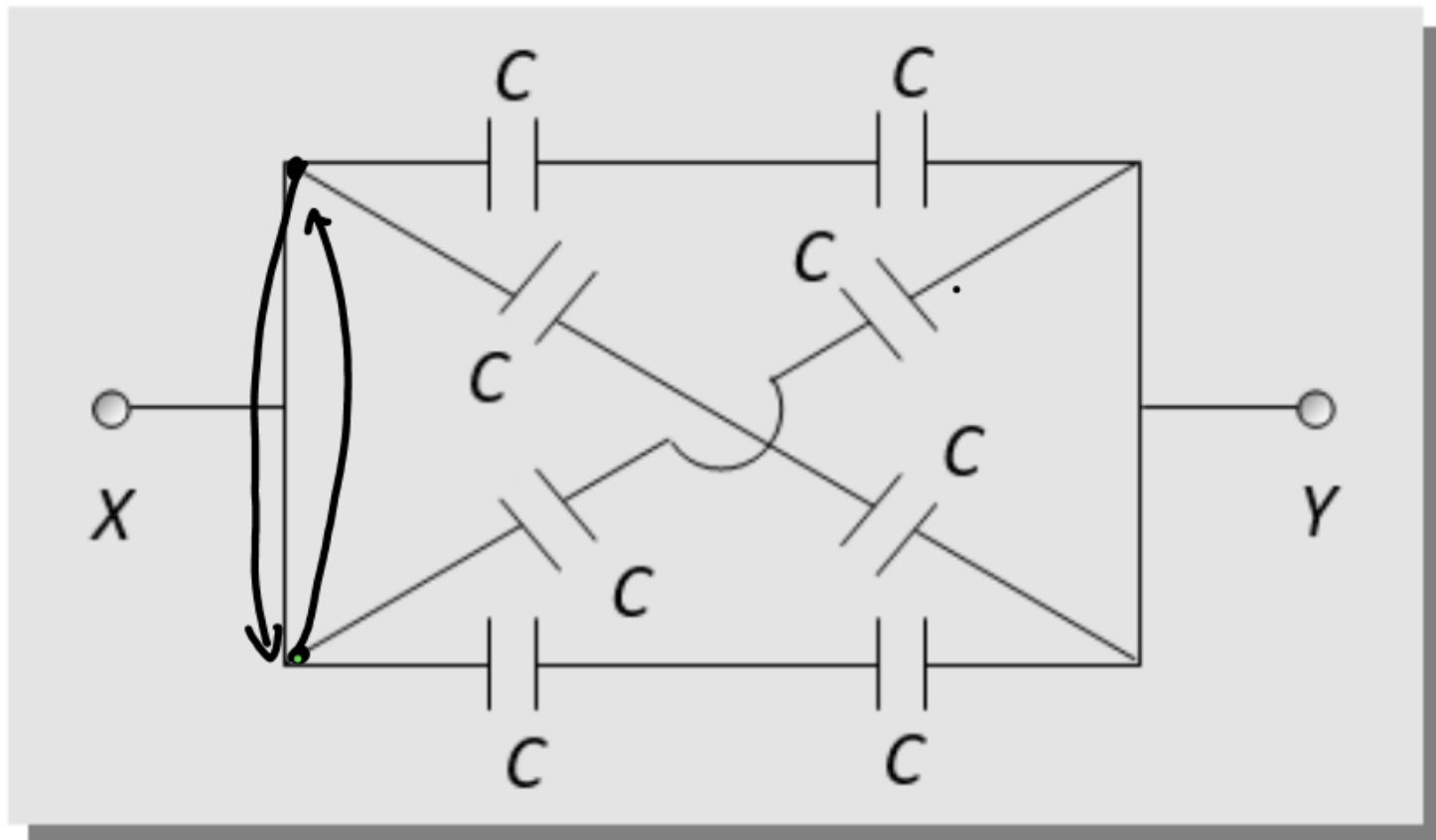



(a)  $C$

~~(b)  $2C$~~


(c)  $3C$

(d)  $4C$

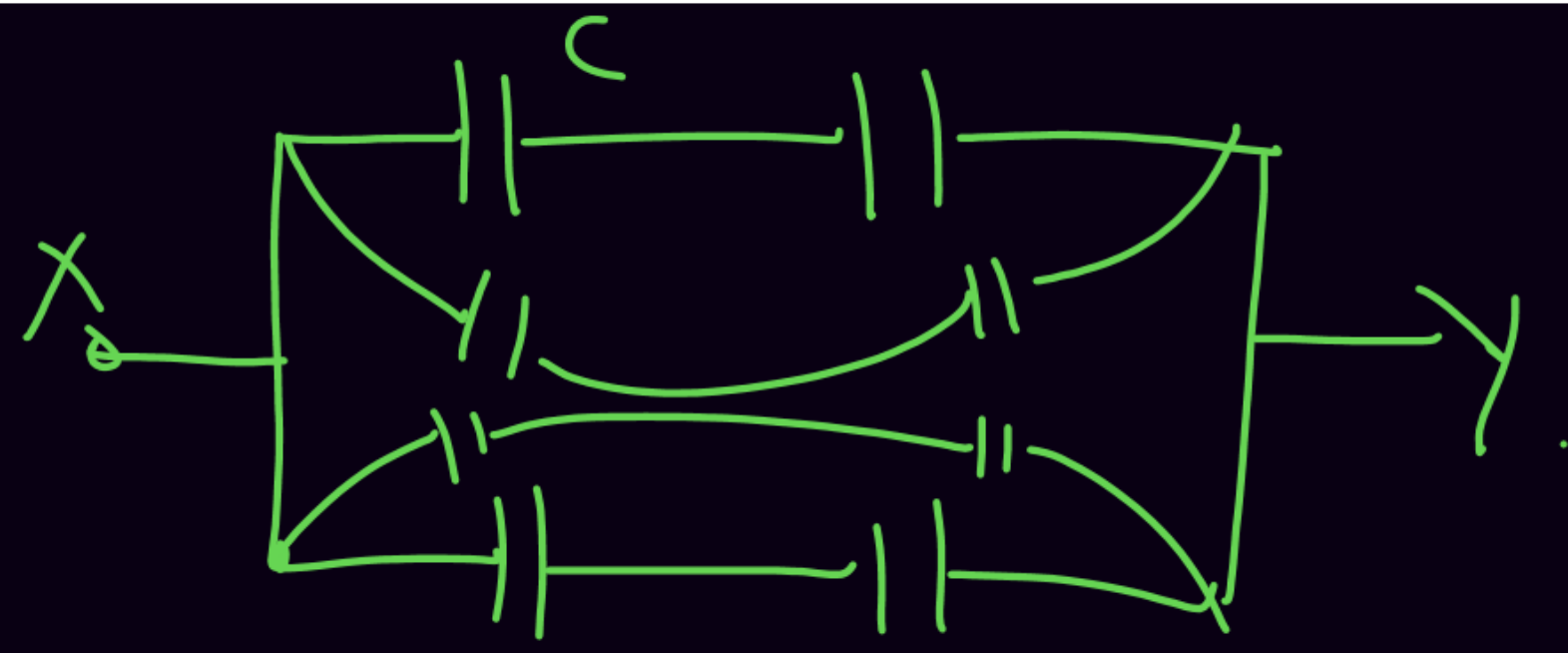

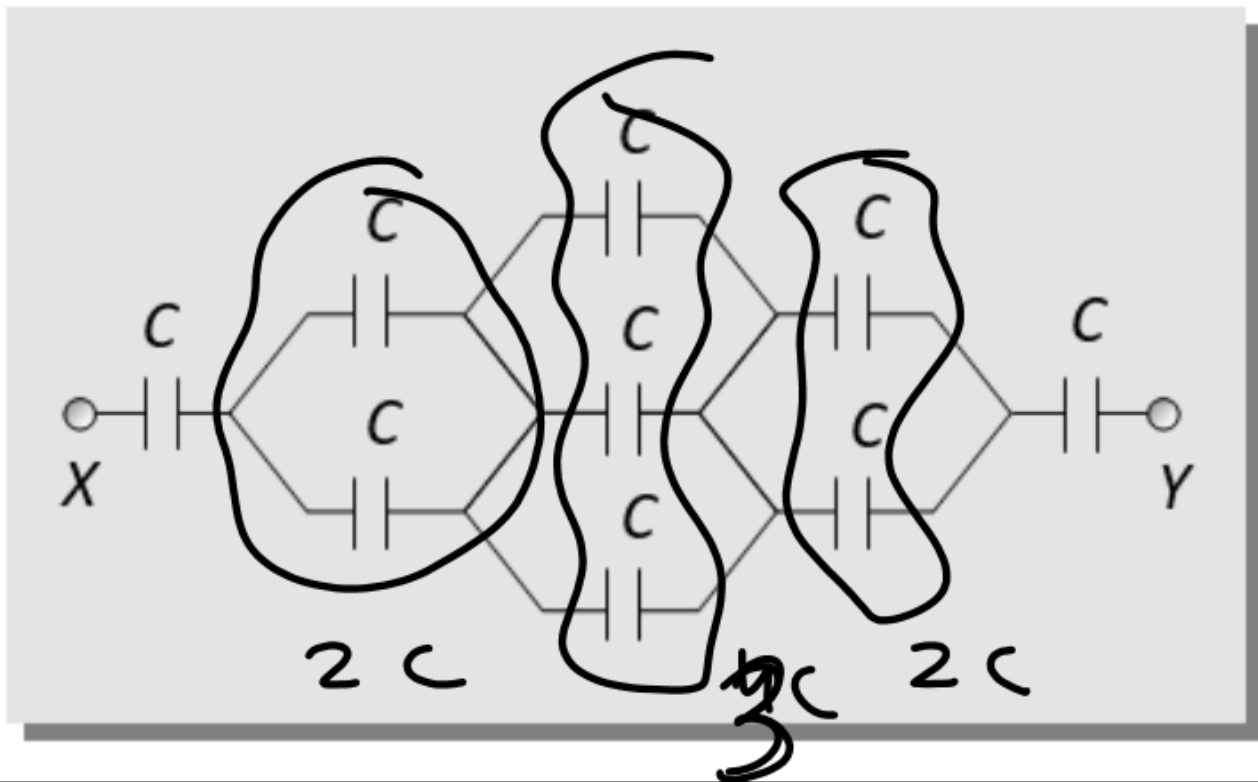

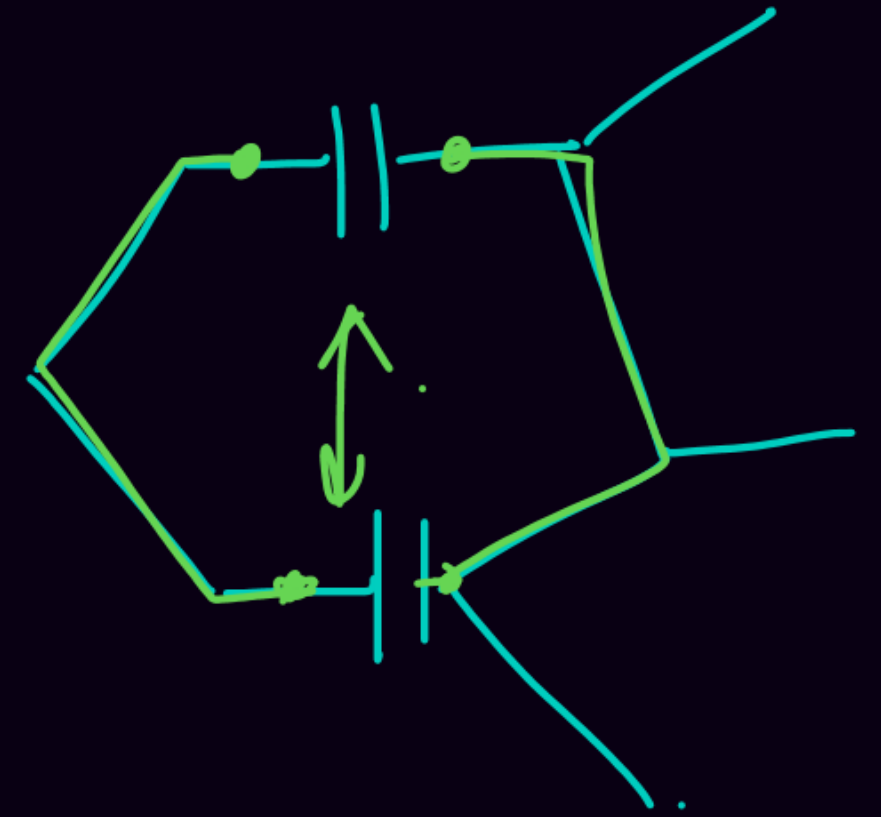- (a)  $C/10$
- (b)  $10C/3$
- ~~(c)  $3C/10$~~
- (d)  $9C$




$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{2C} + \frac{1}{3C} + \frac{1}{2C} + \frac{1}{C}$$


$$\frac{1}{C} \left( 1 + \frac{1}{2} + \frac{1}{3} + \frac{1}{2} + 1 \right)$$

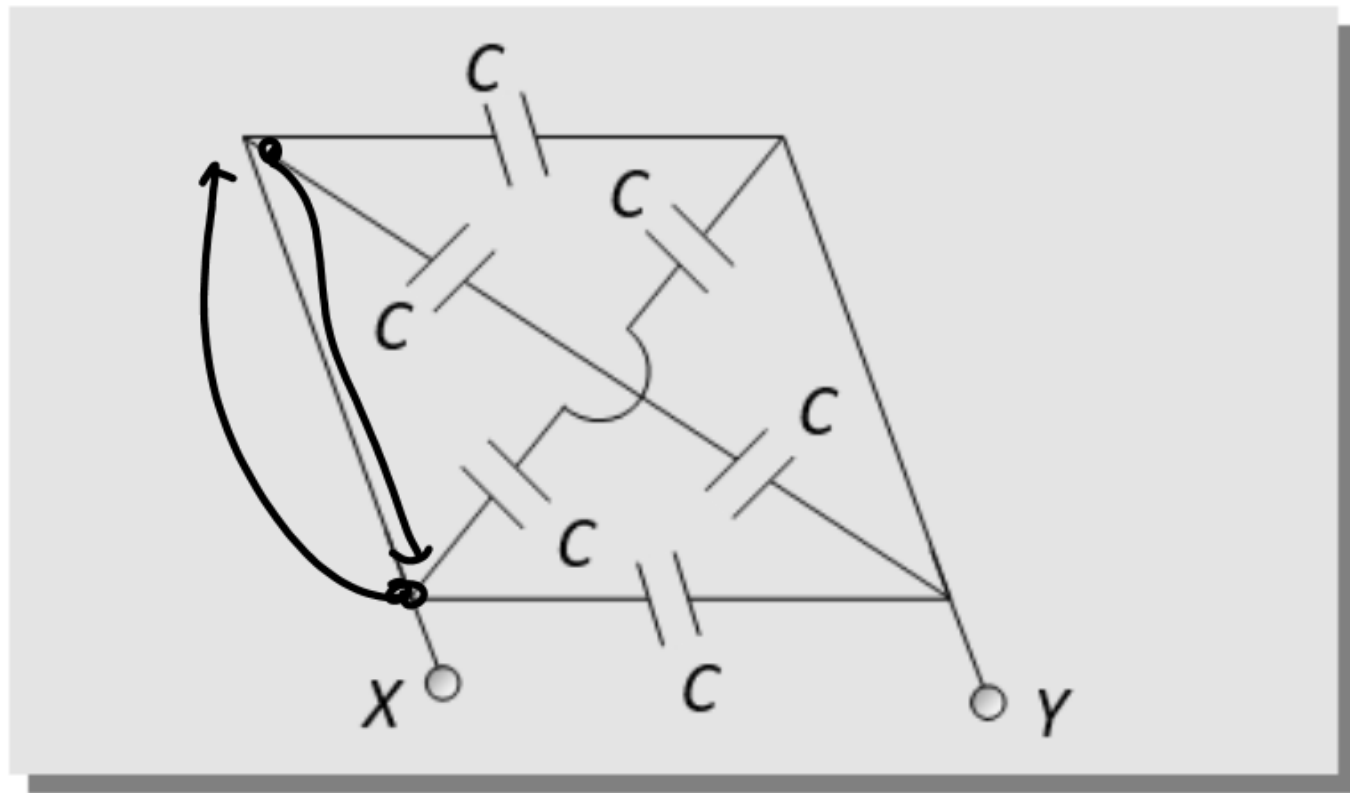
$$\frac{1}{C} \left( 3 + \frac{1}{3} \right) \Rightarrow C_{eq} = \frac{3C}{10}$$





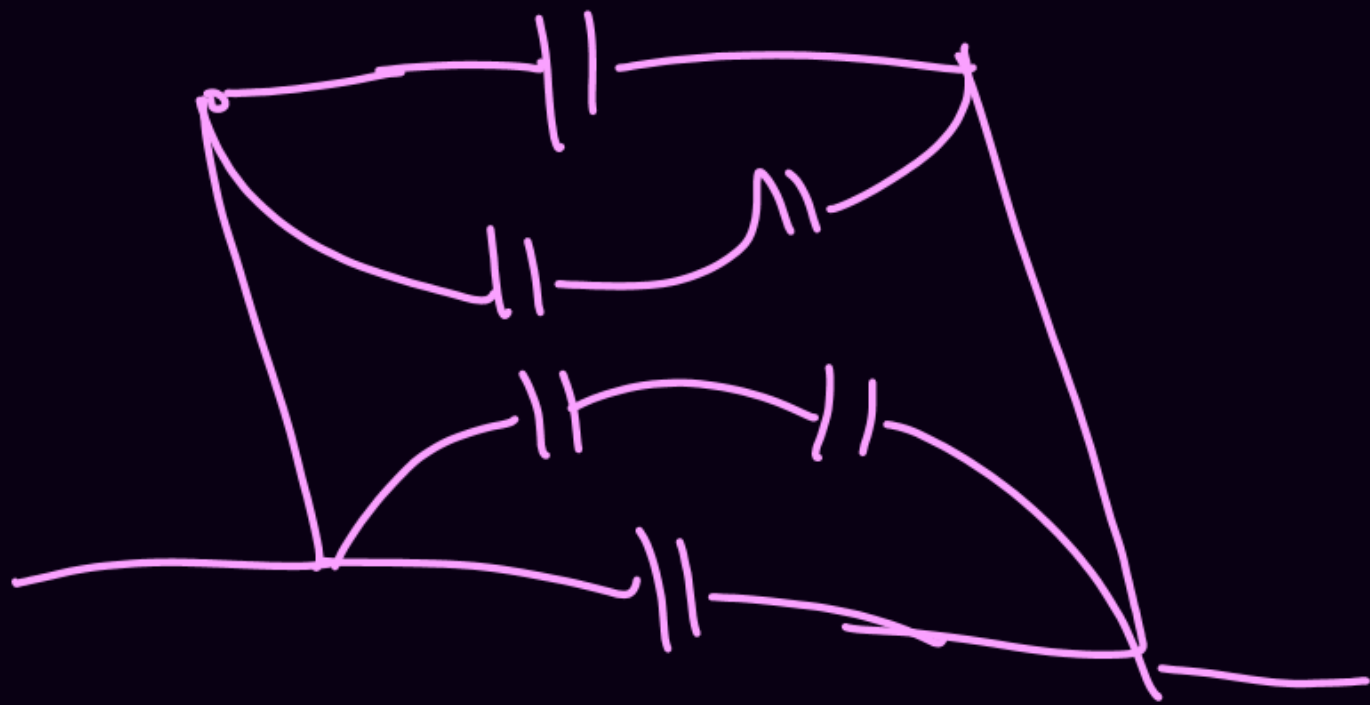- (a)  $C$
- (b)  $2C$
- (c)  $3C$
- (d)  $4C$



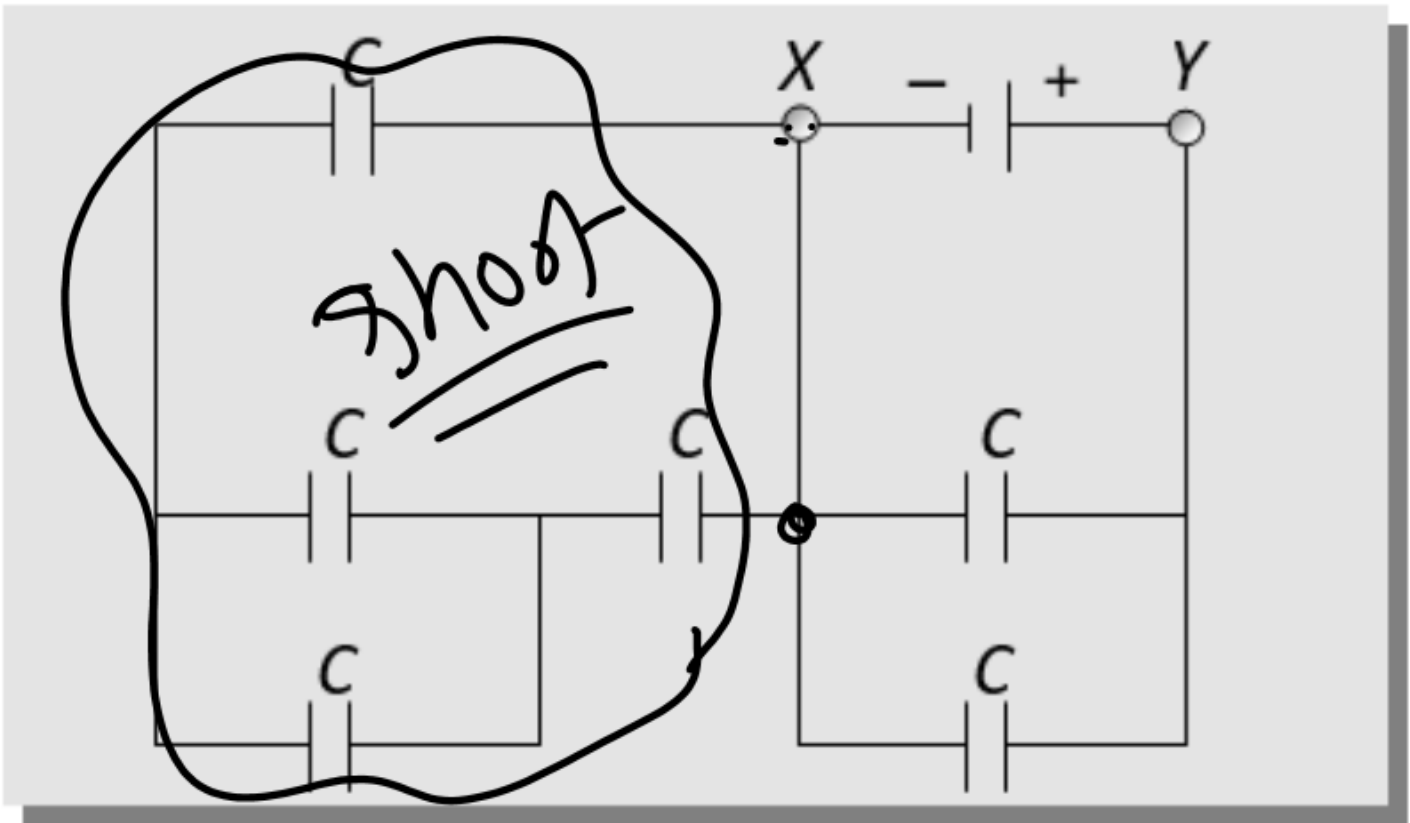


(a)  $6C$


(b)  $5C$

(c)  $3C$

~~(d)  $2C$~~

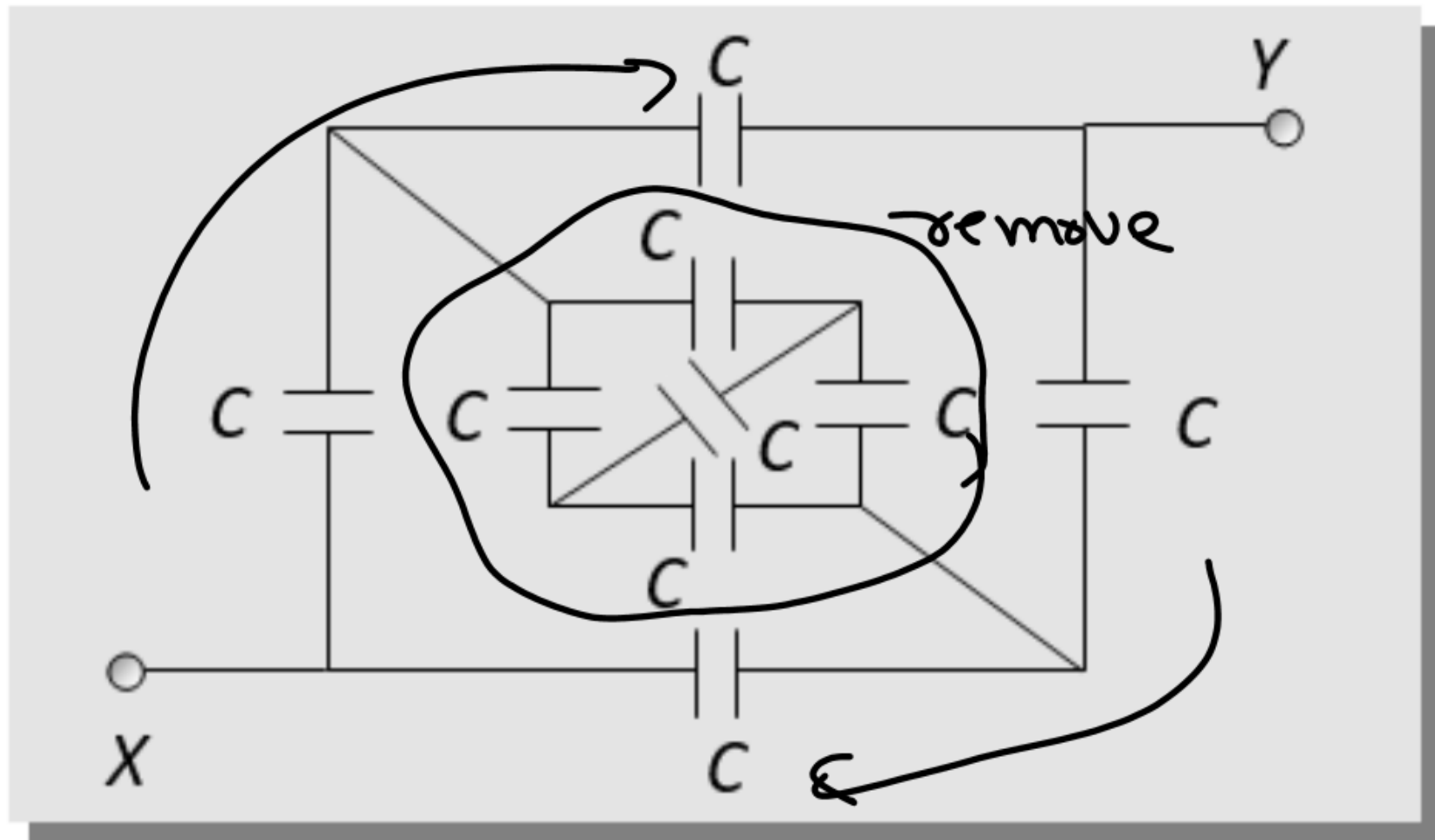

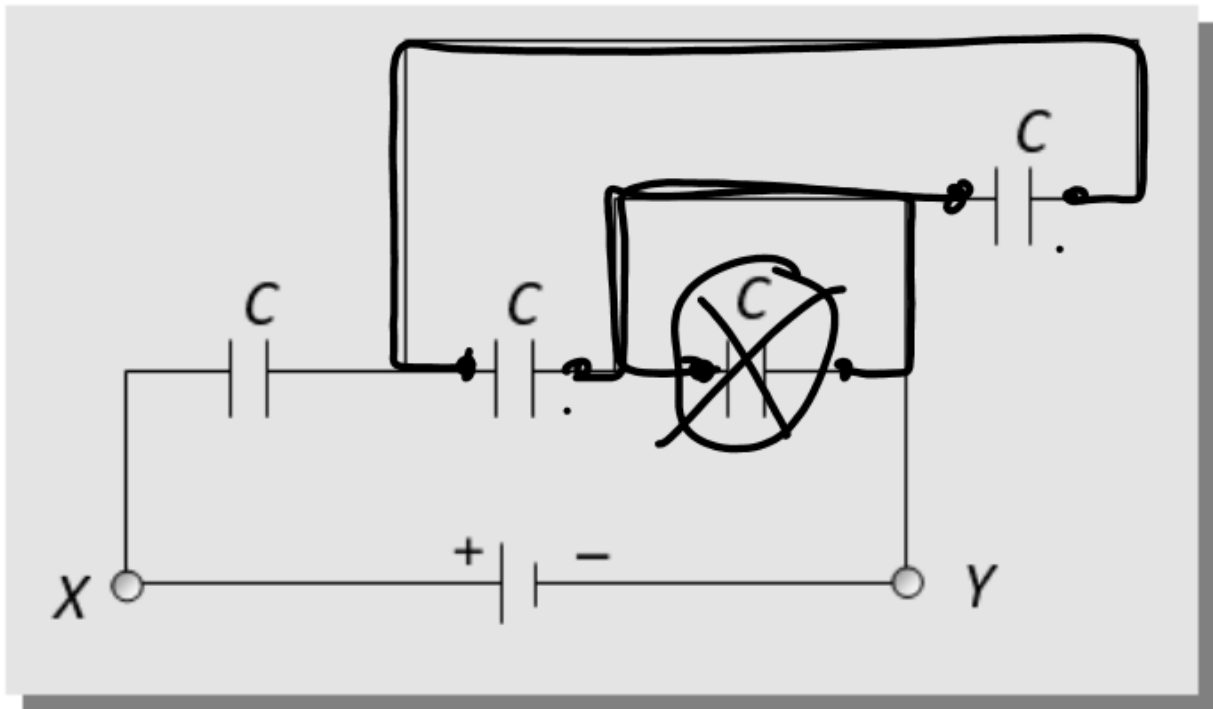- ~~(a)  $C$~~
- (b)  $4C$
- (c)  $6C$
- (d)  $0$




(a)  $C$

(b)  $2C$


(c)  $3C$

~~(d)  $2C/3$~~

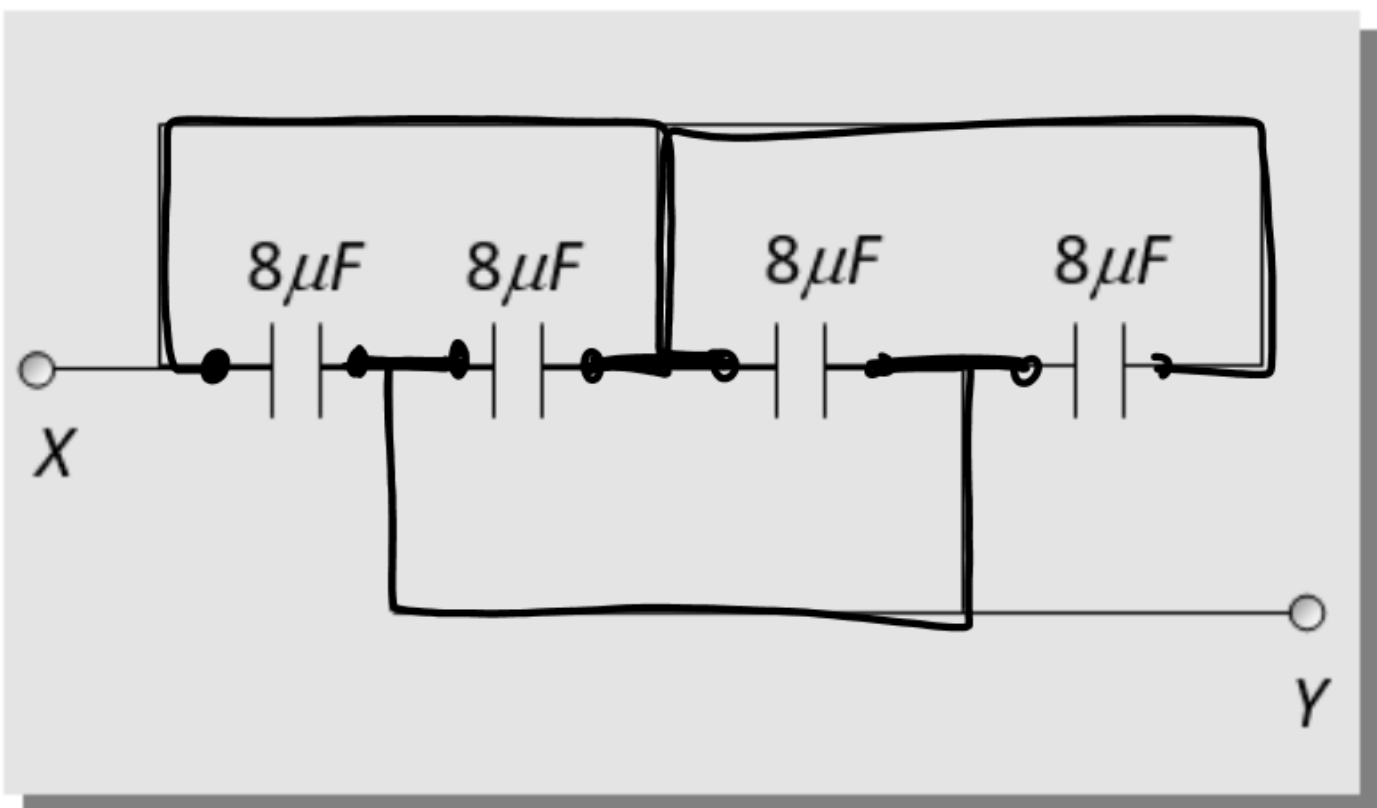

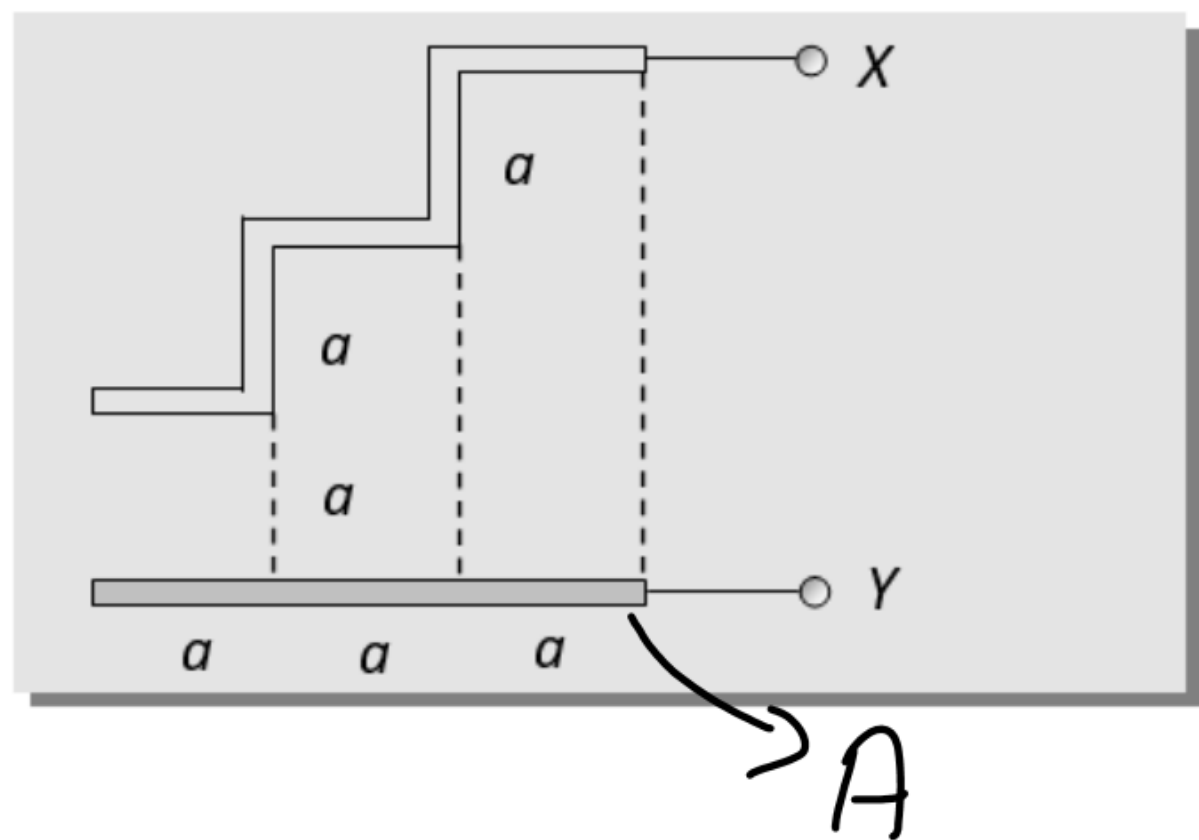- ~~(a)  $32\mu F$~~
- (b)  $2\mu F$
- (c)  $8\mu F$
- (d)  $16\mu F$







(a)  $\frac{10\epsilon_0 A}{5a}$

(b)  $\frac{9\epsilon_0 A}{7a}$

(c)  $\frac{11\epsilon_0 A}{18a}$

(d)  $\frac{12\epsilon_0 A}{18a}$

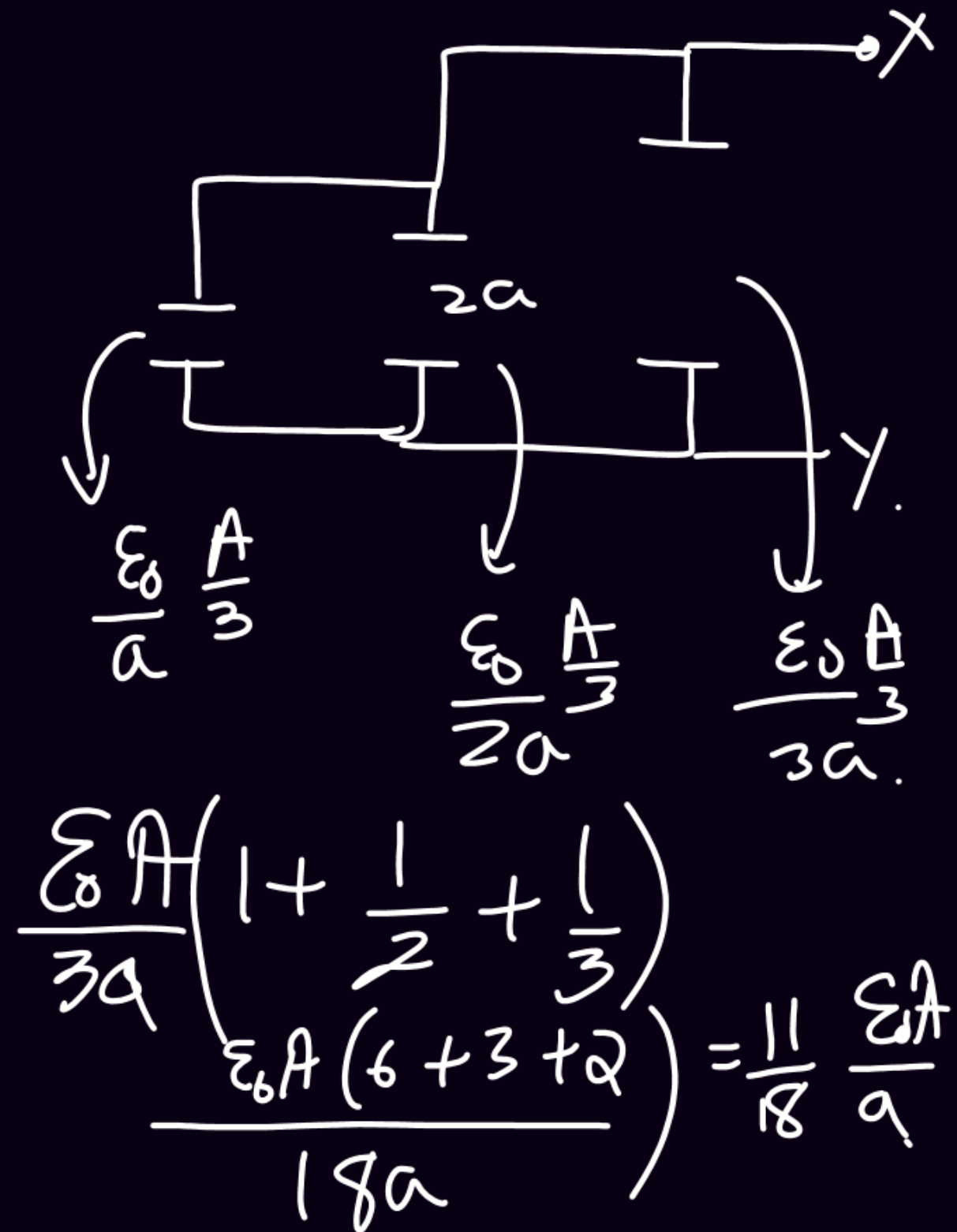

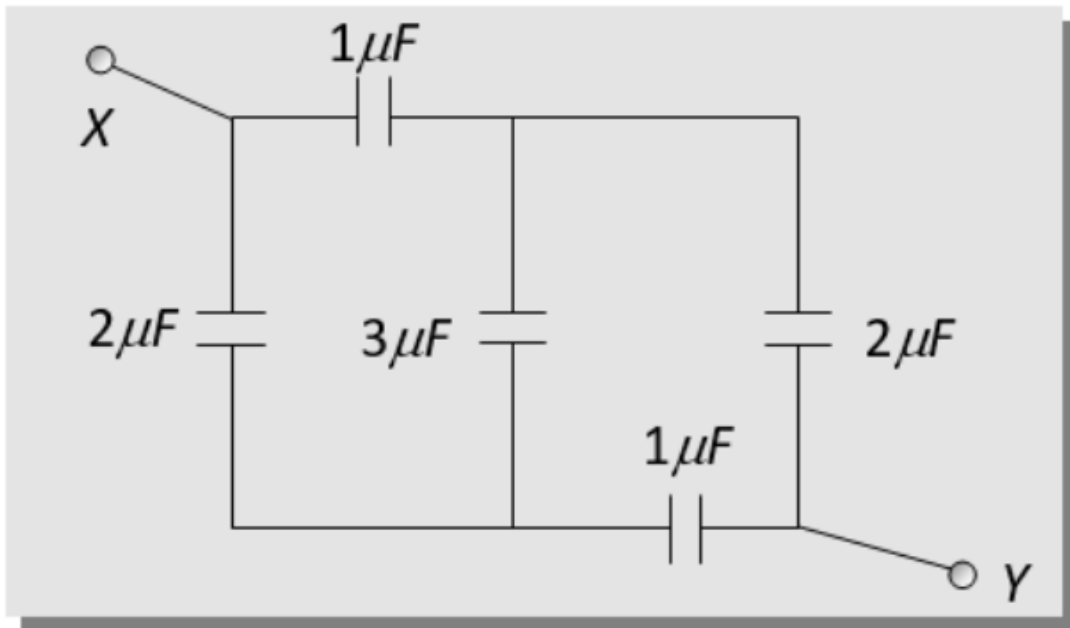


(a)  $\frac{19}{56}\ \mu\text{F}$

(b)  $\frac{64}{11}\ \mu\text{F}$

(c)  $\frac{56}{11}\ \mu\text{F}$


(d)  $\frac{9}{37}\ \mu\text{F}$

$$= \frac{13}{9}\ \mu\text{F}$$

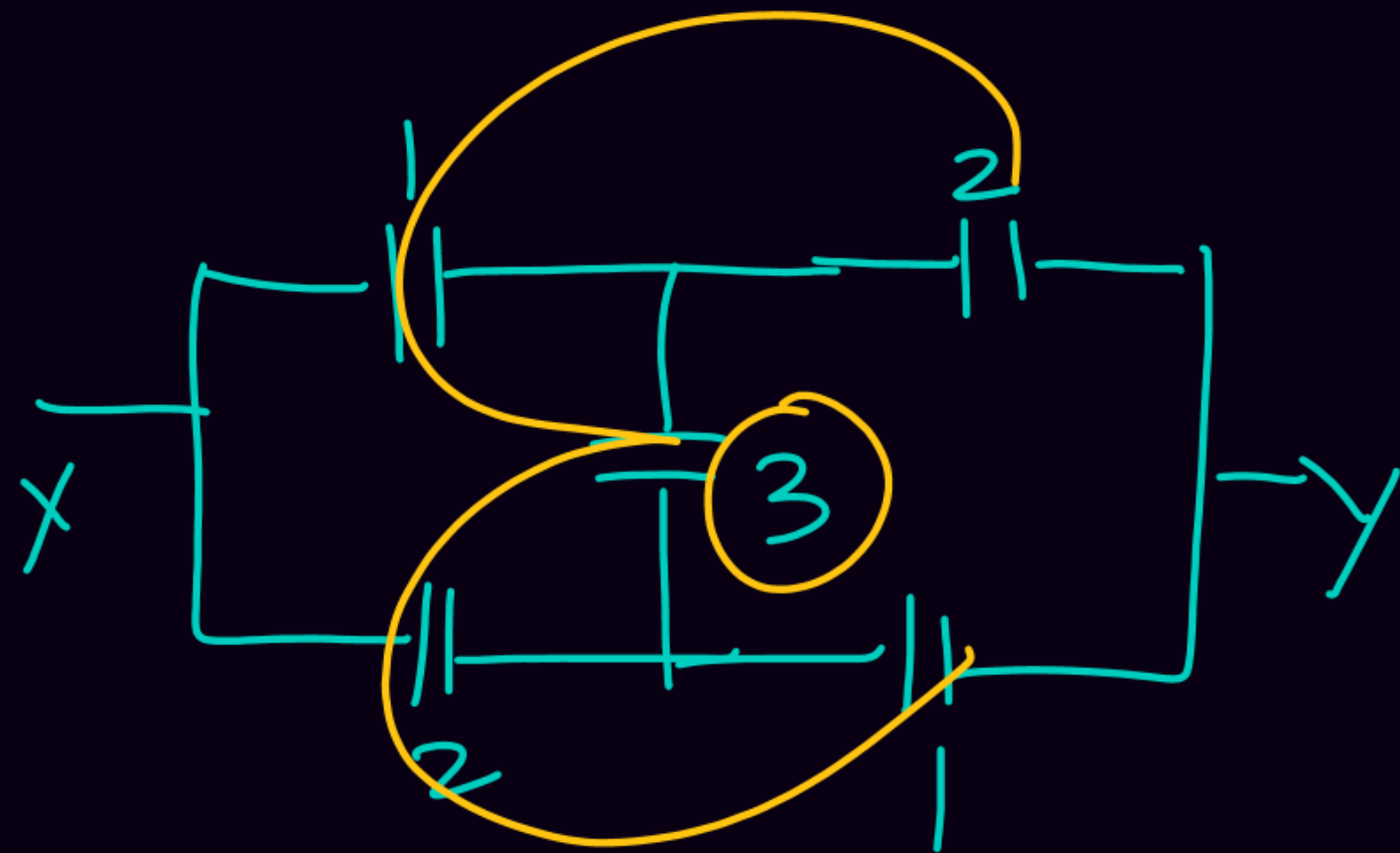

$$C_{eq} = \frac{2 \times 1 + 1 \times 3 + 3 \times 2 + 2 \times 1}{1 + 2 + 2 \times 3}$$

$$= \frac{2 + 3 + 6 + 2}{1 + 2 + 6}$$

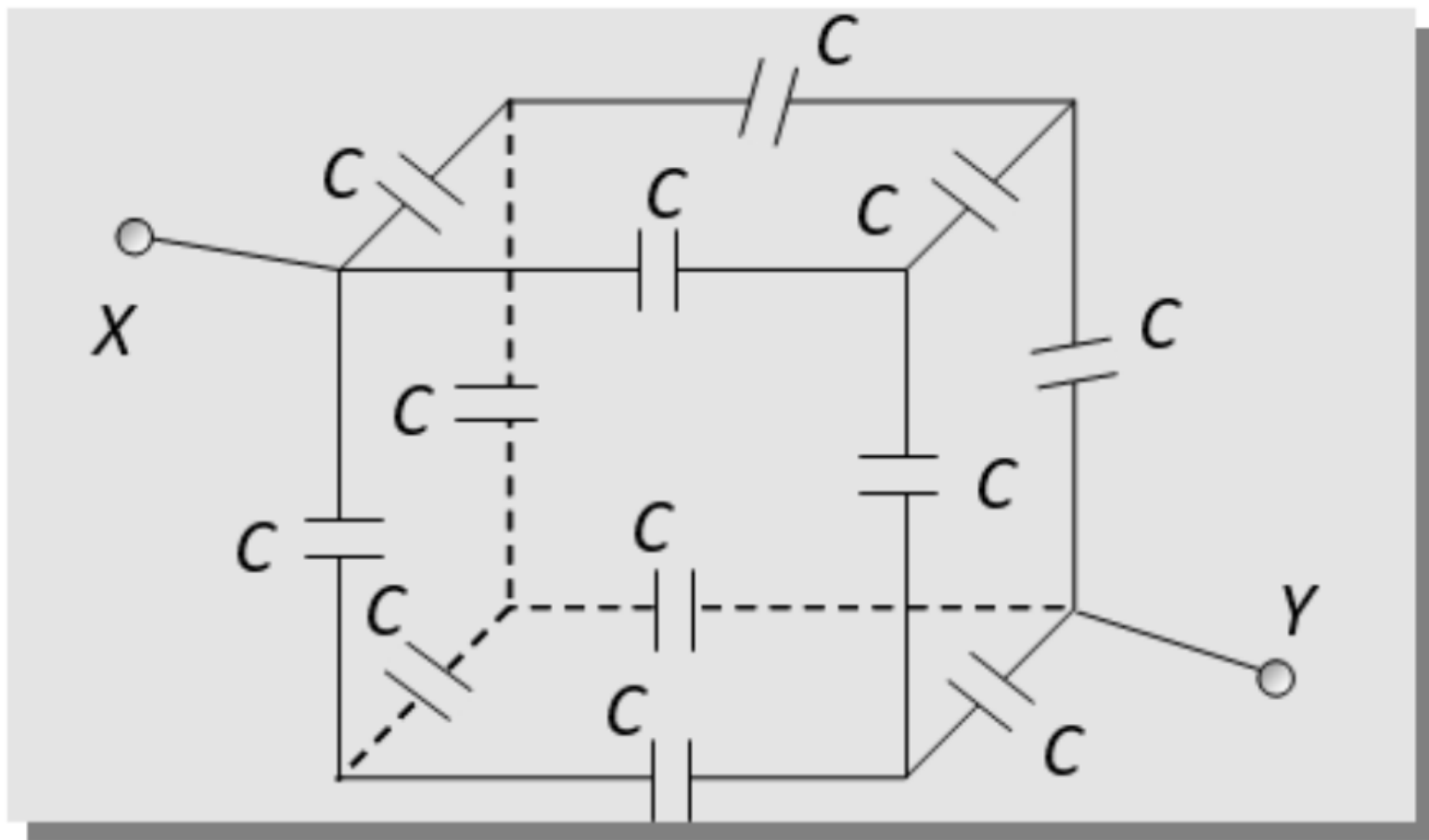


(a)  $\frac{5}{6}C$

(b)  $\frac{C}{6}$

(c)  $\frac{C}{5}$


~~(d)~~  $\frac{6C}{5}$



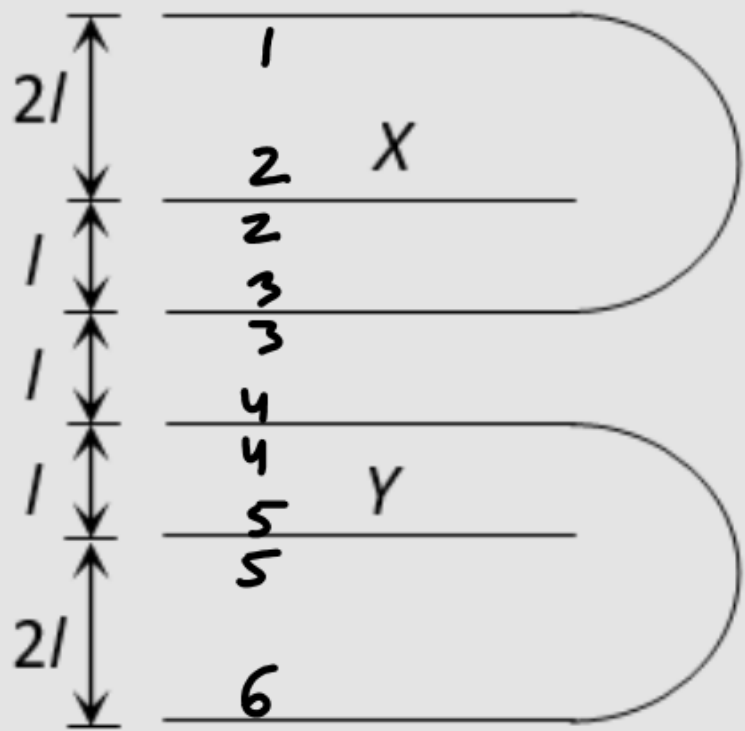

- ~~(a)  $\frac{3C}{7}$~~
- (b)  $\frac{7C}{3}$
- (c)  $5C$
- (d)  $2C$


$$C = \frac{\epsilon_0 A}{L}$$

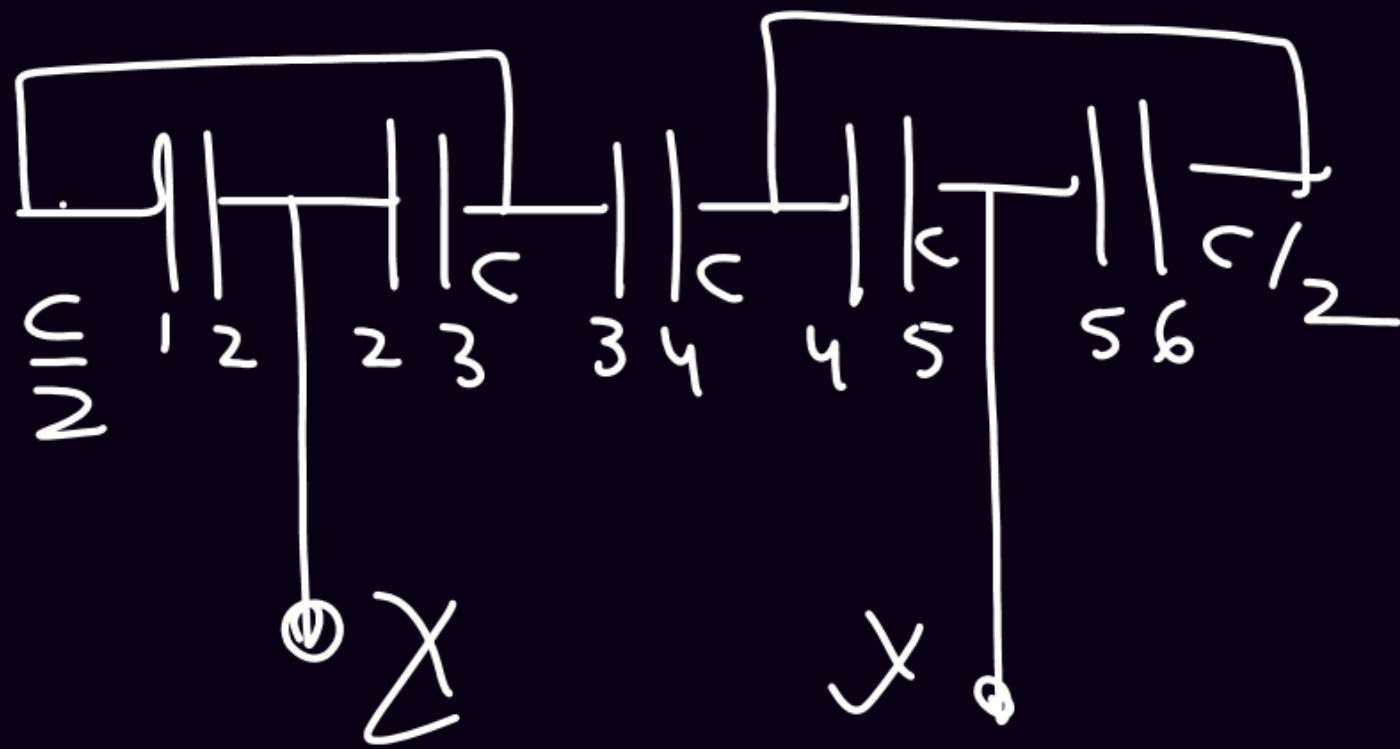

$$\frac{C}{2} + C = \frac{3C}{2}$$

$$\frac{1}{C_{eq}} = \frac{2}{3C} + \frac{2}{3C} + \frac{1}{C}$$
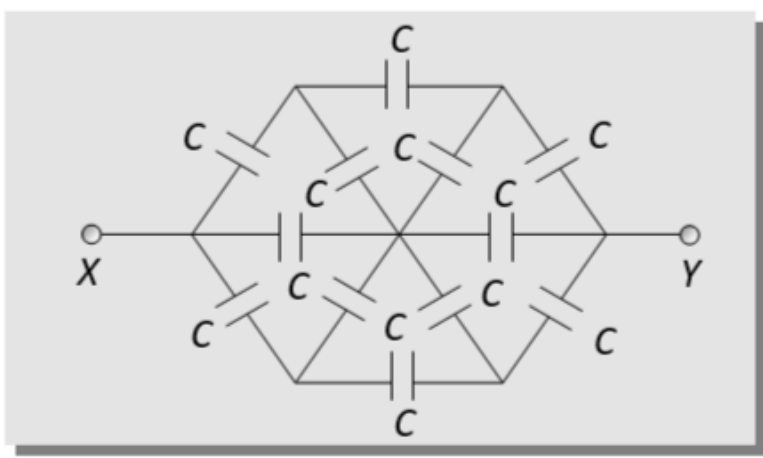
$$C_{eq} = \frac{4}{3C} + \frac{1}{C} = \frac{4+3}{3C}$$




(a)  $\frac{4C}{5}$


(b)  $\frac{5C}{4}$

(c)  $12 C$

(d)  $\frac{C}{12}$

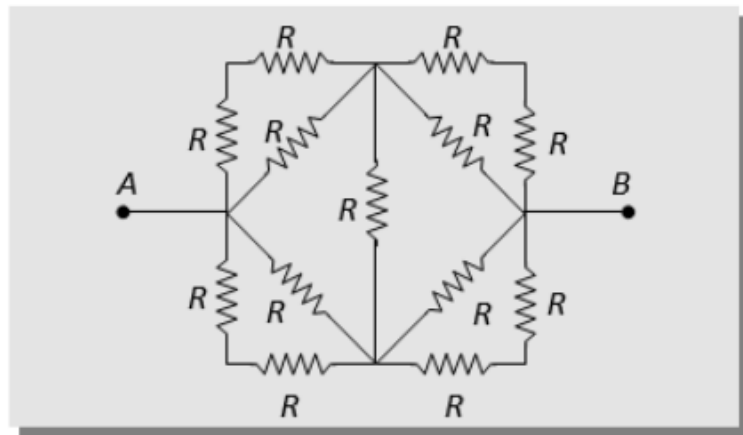

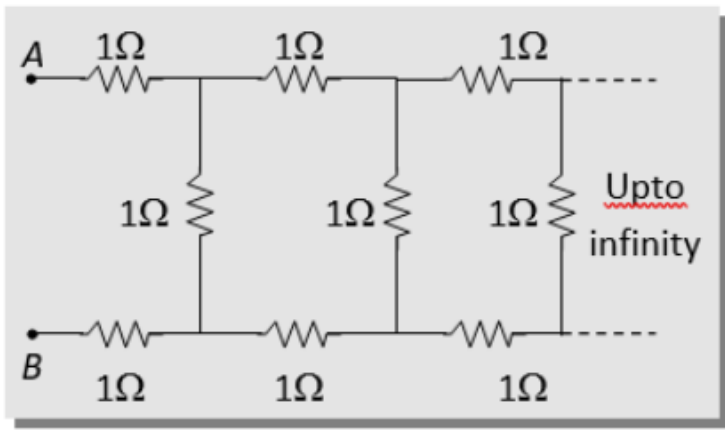- (a)  $2R\Omega$
- (b)  $\frac{4R}{3}\Omega$
- (c)  $\frac{2R}{3}\Omega$
- (d)  $R\Omega$




(a)  $(\sqrt{3} - 1)$

(b)  $(1 - \sqrt{3})$

(c)  $(1 + \sqrt{3})$

(d)  $(2 + \sqrt{3})$



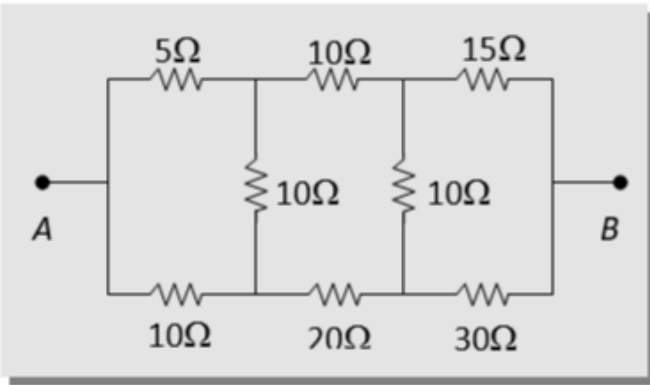


(a)  $20\ \Omega$


(b)  $30\ \Omega$

(c)  $90\ \Omega$

(d)  $110\ \Omega$

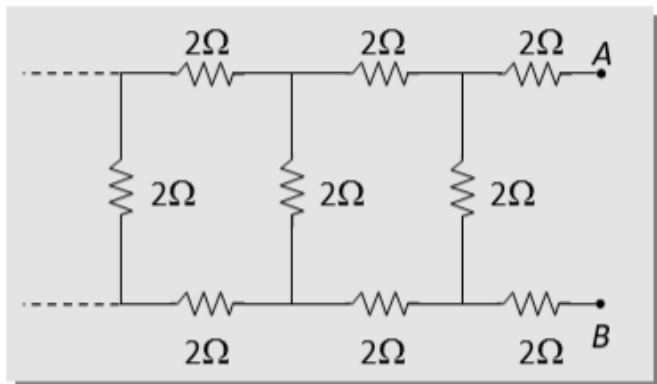

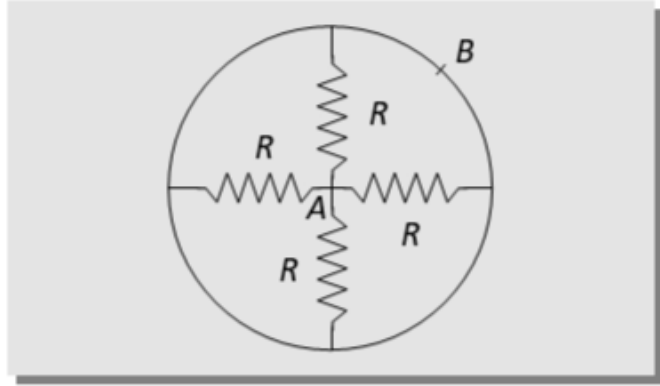- (a) Less than  $4\ \Omega$
- (b)  $4\ \Omega$
- (c) More than  $4\ \Omega$  but less than  $12\ \Omega$
- (d)  $12\ \Omega$




(a)  $\frac{R}{4}$

(b)  $4R$

(c)  $\frac{3R}{4}$

(d)  $\frac{4R}{3}$

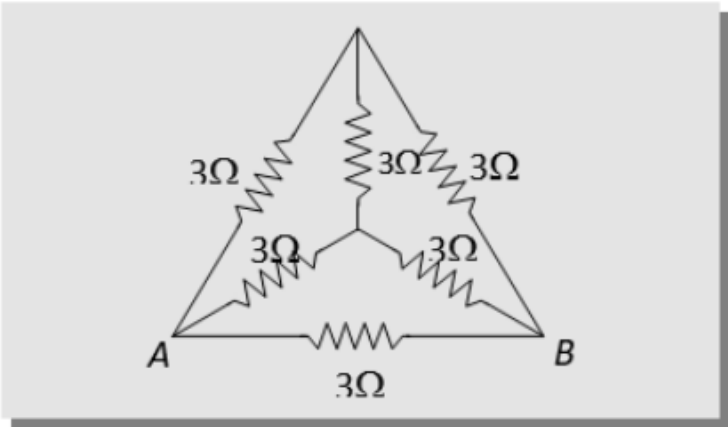


(a) 4 ohms


(b) 2 ohms

(c) 1 ohm

(d)  $\frac{6}{4}$  ohm

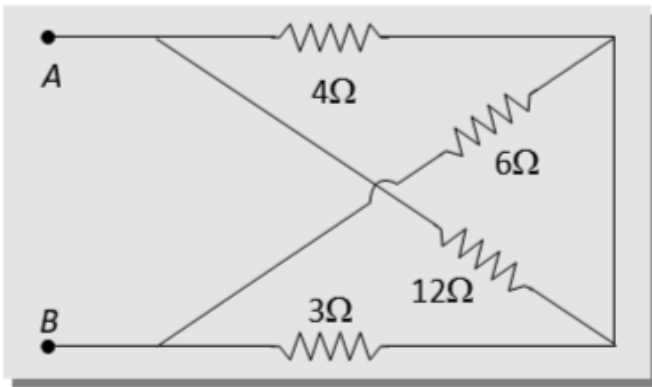

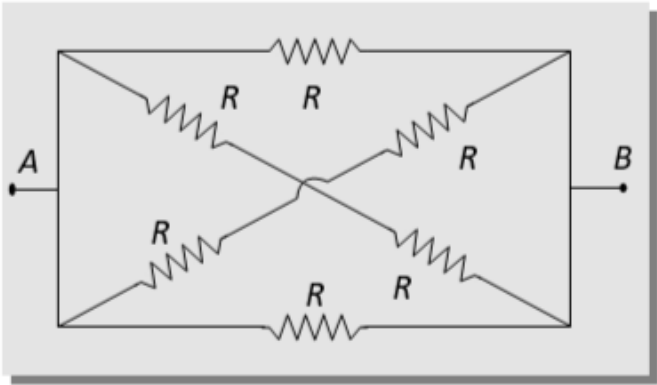- (a)  $6 \Omega$
- (b)  $16 \Omega$
- (c)  $7 \Omega$
- (d)  $5 \Omega$




(a)  $R$


(b)  $\frac{R}{3}$

(c)  $3R$

(d)  $4R$

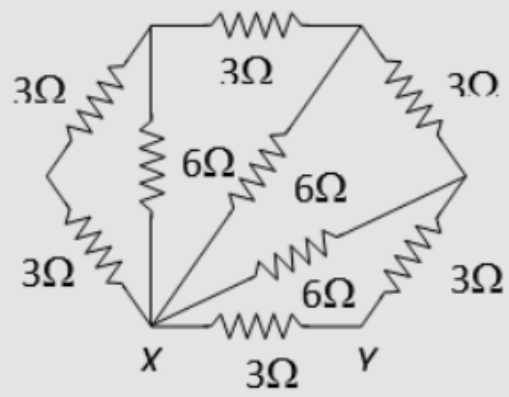


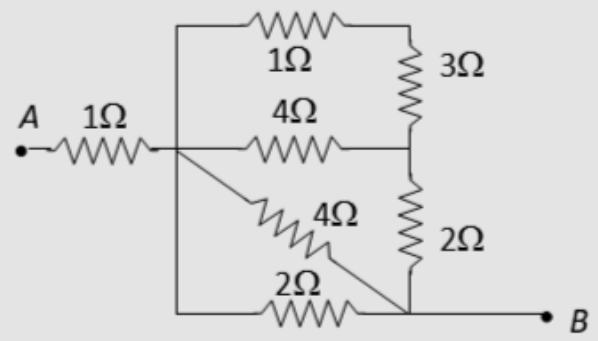- (a)  $4 \Omega$
- (b)  $2 \Omega$
- (c)  $8 \Omega$
- (d)  $16 \Omega$



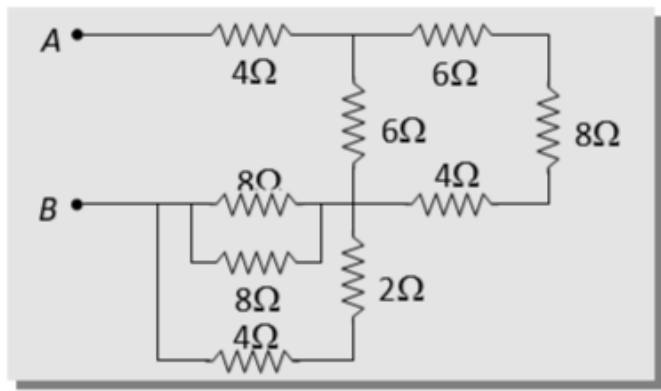- (a)  $1\Omega$
- (b)  $2\Omega$
- (c)  $3\Omega$
- (d)  $4\Omega$






(a)  $4\ \Omega$

(b)  $6\ \Omega$

(c)  $10.9\ \Omega$

(d)  $12.6\ \Omega$

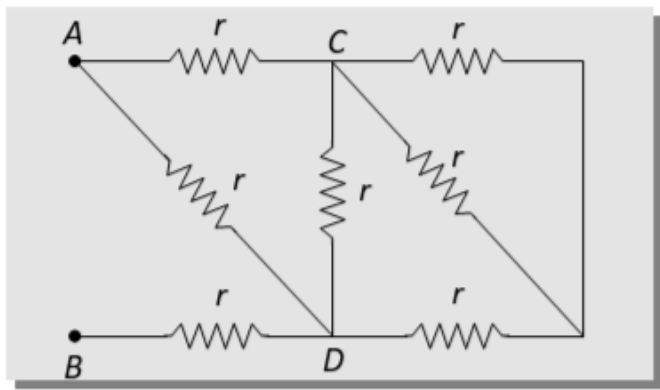


(a)  $\frac{13}{9}r$

(b)  $\frac{11}{5}r$

(c)  $\frac{5}{12}r$

(d)  $\frac{21}{13}r$

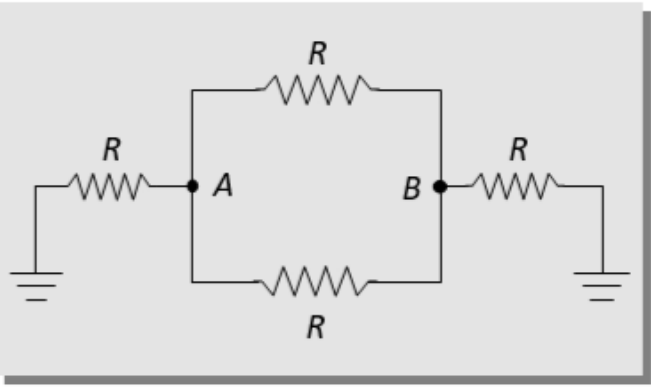


(a)  $\frac{R}{2}$

(b)  $\frac{2R}{5}$

(c)  $\frac{3R}{5}$

(d)  $\frac{R}{3}$

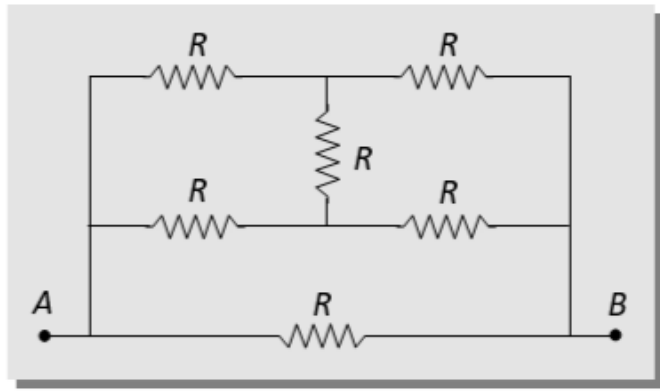


(a)  $\frac{R}{2}$


(b)  $R$

(c)  $2R$


(d)  $4R$

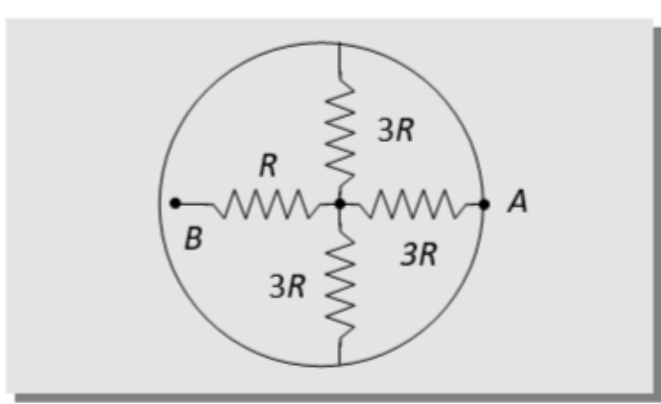

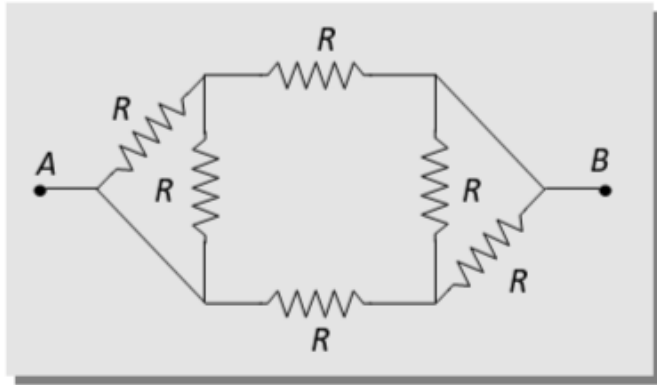- (a)  $2R$
- (b)  $4R$
- (c)  $7R$
- (d)  $10R$



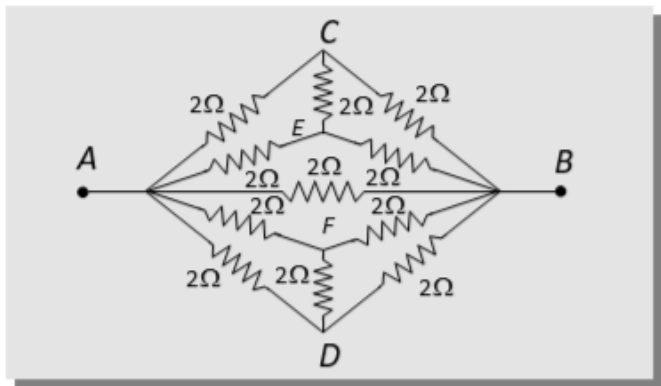- (a)  $\frac{3}{4}R$
- (b)  $\frac{5}{3}R$
- (c)  $\frac{7}{5}R$
- (d)  $R$



(a)  $2\Omega$

(b)  $\frac{2}{3}\Omega$

(c)  $\frac{3}{4}\Omega$

(d)  $\frac{4}{3}\Omega$

Thank You