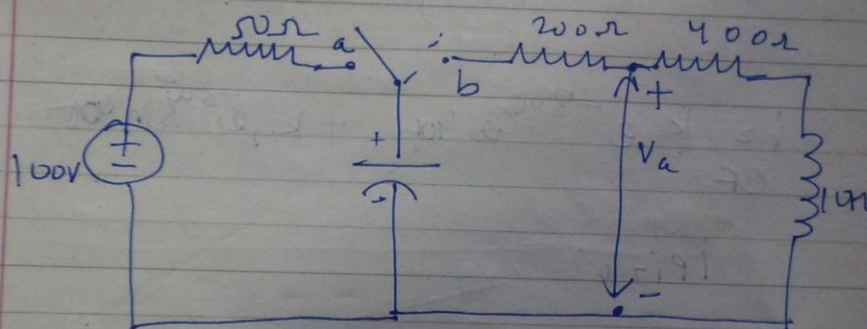


### III Semester Electrical circuit Analysis


- ① The switch in the circuit shown in fig 1 has been in position 'a' for a long time. At  $t=0$  the switch is moved instantaneously to position 'b'. Find  $V_a$  and  $dV_a/dt$ .



$$V(0^-) = 100V, V(0^+) = 100$$

$$i_L(0^-) = i_L(0^+) = 0$$

$$t > 0$$

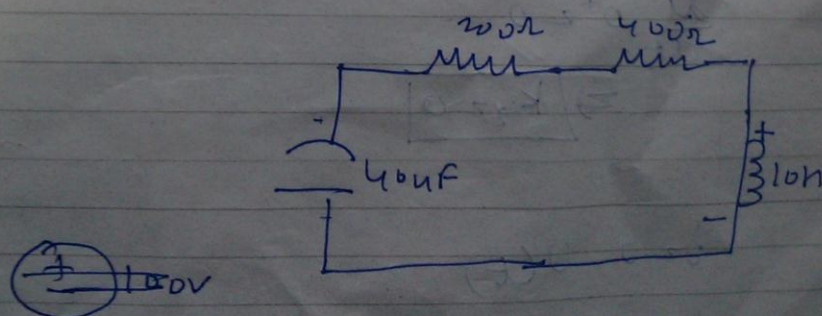

$$\frac{1}{C} \int i_c dt + 10 \frac{di}{dt} + 600i = 0$$

$$\frac{di}{dt} = 0$$

$$2500i + 600 \frac{di}{dt} + 10 \frac{d^2i}{dt^2} = 0$$

$$10p^2 + 600p + 2500 = 0$$

$$i = K_1 e^{-30t} \cos 40t + K_2 e^{-30t} \sin 40t$$

$$i(0) = 0$$

$$i = K_1 e^{-30t} \cos 40t + K_2 e^{-30t} \sin 40t$$

$$i(0) = 0 \Rightarrow \boxed{K_1 = 0}$$

$$\frac{di}{dt} = 0$$

$$\Rightarrow \boxed{K_2 = 0}$$

$$i = 0 \quad V(t)$$

$$\underline{i(0) = 0}$$


$$V_a(0^+) = V_c = 100V$$



$$V_C = 0$$

$$\frac{dV_C}{dt} = 0$$

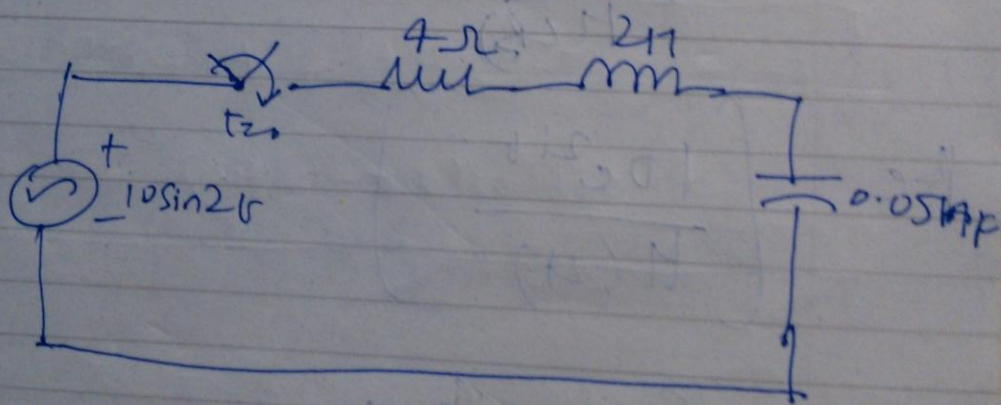- ② The series RLC circuit shown in Fig 2 is excited at  $t = 0$  by the sinusoidal source and the capacitor is initially uncharged. Determine the current  $i(t)$  for  $t > 0$  using time domain analysis.



$$t = 0^-, V_C = 0, V_C(0^+) = 0$$

$$i_L(0^-) = i_L(0^+) = 0$$

$$10 \sin 2t \angle 4^\circ + 2 \frac{di}{dt} + 20 \int dt$$

$$\frac{di}{dt} \cos t = 20$$

$$20 \cos t = \frac{di}{dt} + 2 \frac{d^2 i}{dt^2} + 20i$$

$$2D^2 + 4D + 20 = 20 \cos t$$

$$D^2 + 2D + 10 = 10 \cos 2t$$

$$CF = k_1 e^{-5 \cos 3t} + k_2 e^{5 \sin 3t}$$

$$R = \frac{K(s)}{H(s)}$$

$$Re \left[ \frac{10e^{2it}}{H(2i)} \right]$$

$$Re \left[ \frac{10e^{2it}}{6+2i} \right]$$

$$Re \left[ \frac{e^{2it} (60 - 20i)}{40} \right]$$



$$\text{Re} \left[ \frac{1}{40} \left[ 60e^{2it} - 2ie^{2it} \right] \right]$$

$$\frac{60}{40} \cos 2t + \frac{20}{60} \sin 2t$$

$$1.58 - 0.5i$$

$$= 1.581 \angle -18.4$$

$$\text{Re} \left[ 1.581 e^{(2it - 18.43t)} \right]$$

$$= 1.581 \cos(2t - 18.43) = \text{PI}$$

$$i^2 \left[ K_1 e^{-t} \cos 2t + K_2 e^{-t} \sin 2t \right]$$

$$+ 1.581 \cos(2t - 18.43)$$

$$i(0^+) = K_1 + 1.581 \cos(-18.43) = 0$$

$$K_1 \approx -1.5$$


$$\frac{di}{dt} = -k_1 e^{-t} \cos 3t + k_1 e^{-t} (3)(-\sin 3t) \\ - k_2 e^{-t} \sin 3t + k_2 e^{-t} (3)(\cos 3t) \\ + (1.581 \times 2) (\sin(2t - 18.43))$$

$$0 = k_1 + 3k_2 + 1 + 1 \\ k_2 = -1$$

$$i = -1.5 e^{-t} \cos 3t + (-1.1) e^{-t} \sin 3t \\ + 1.581 \cos(2t - 18.43)$$

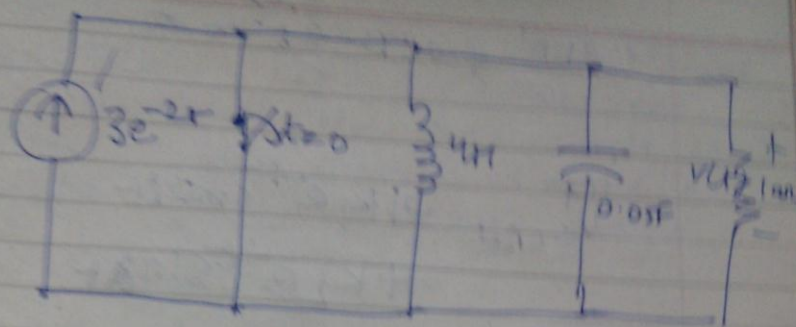③ In the RL circuit shown in Fig 3, source is applied at  $t=0$ . Determine the voltage  $v(t)$  for  $t > 0$ . Use time domain analysis.






$$v_L(0^-) = v_L(0^+) = 0 \text{ V}$$

$$i_L(0^-) = i_L(0^+) = 0$$

$$t > 0$$

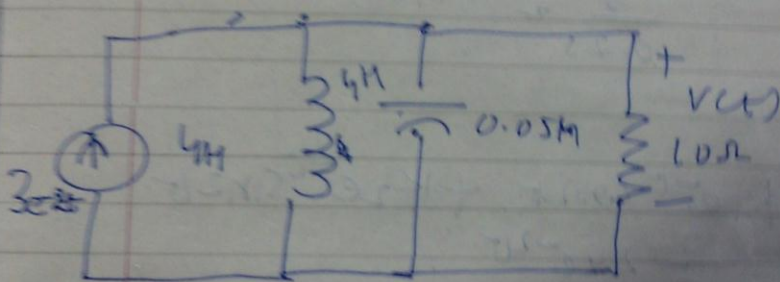

$$0.05 \frac{dv_C}{dt} + \frac{v_C}{10} + 0.25 \int v_L dt = 3e^{-2t}$$

$$\Rightarrow 3e^{-2t}$$

$$\frac{dv_C(0^+)}{dt} = \frac{3}{0.05} = 60 \text{ V/s}$$

$$0.05 \frac{d^2 v_C}{dt^2} + \frac{1}{10} \frac{dv_C}{dt} + 0.25 v_C = -6e^{-2t}$$

$$0.010 + 0.010 + \frac{0.25}{5} = 0$$

$$V_{CE} = k_1 e^{-t} \cos 2t + k_2 e^{-t} \sin 2t$$

$$P_{72} = \frac{6 \text{ V} \times (0.5 \text{ V} - 0.5 \text{ V})}{H(2)}$$

$$= \frac{6}{0.25} = -24 e^{-2t}$$

$$V_{CE} = k_1 e^{-t} \cos 2t + k_2 e^{-t} \sin 2t - 24 e^{-2t}$$

$$0 = k_1 - 24$$

$$k_1 = 24 \quad \text{Differentiating again}$$


$$k_2 = 24$$

$$24 e^{-t} [\cos 2t + \sin 2t] - 24 e^{-2t}$$

$$V_{CE} = 24 e^{-t} [\cos 2t + \sin 2t - e^{-t}]$$



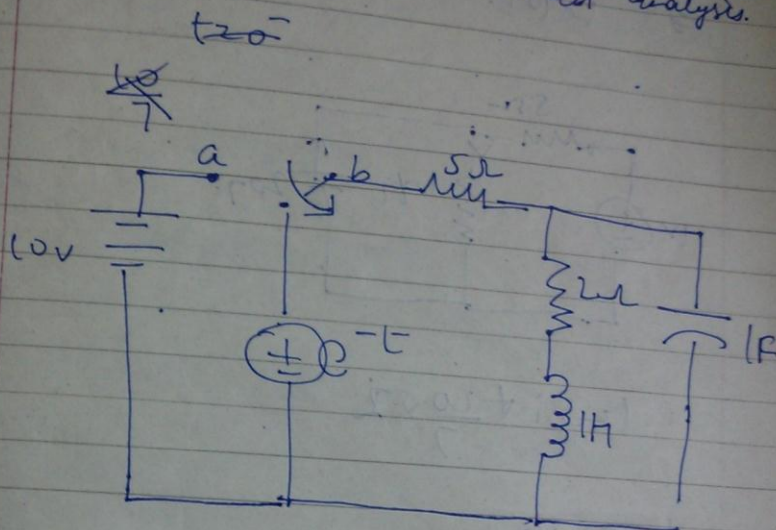4 In the network of fig 4, switch is changed from 'a' to 'b' at  $t=0$ , steady state being achieved before  $t=0$ . Find an expression for the current through the inductor for  $t > 0$  using time domain analysis.




$t=0^-$

$$\frac{10A}{7} = i_L(0^-) = i_L(0^+)$$


$$V_C(0^-) = \frac{20A}{7} = V_C(0^+)$$

$t > 0$

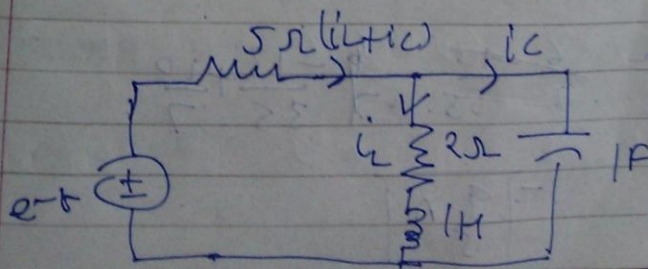

$$e^{-t} \left( 5i(1) + 2i + L \frac{di}{dt} \right) = 0 \quad (1)$$

$$\Rightarrow i_c(0^+)$$

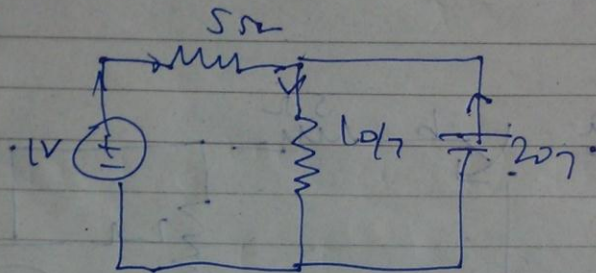

$$12.5i + \frac{10}{7} \times 2$$

$$12.5i + \frac{20}{7}$$

$$5i = 1 - \frac{20}{7}$$

$$i = \frac{-13}{35}$$

$$\Rightarrow i_c = \frac{6 - 13}{35} = \frac{-7}{35} = -\frac{1}{5}$$

$$\Rightarrow \frac{9}{5} \text{ A}$$



8 ②

$$\int i c dt = 2iL + \frac{diL}{dt}$$

$$\frac{2diL}{dt} + \frac{d^2iL}{dt^2} - i c z_0 (Li)$$

$$H(s) = \begin{vmatrix} D+7 & 5 \\ D^2+20 & -1 \end{vmatrix}$$

$$50^2 + 11D - 17 = 0$$

$$-1.1 + 0.43i$$

$$iL(t) = k_1 e^{-1.1t} \cos(0.43t) + k_2 e^{-1.1t} \sin(0.43t)$$

$$H(s) = \begin{vmatrix} 6 & 5 \\ 1 & -1 \end{vmatrix} \quad -6 + 5s - 1$$

$$P = \frac{-1}{-1} = 1$$

$$iL(0^+) = \frac{10}{7} A$$

$$\frac{di_L}{dt}(0^+) = \frac{10}{7} \times 0 A$$

$$i_L = k_1 e^{-1.1t} \cos(0.43t) + k_2 e^{-1.1t} \sin(0.43t) + e^{-t}$$

$$\frac{10}{7} = k_1 + 1$$

$$k_1 = 3/7$$

$$\begin{aligned} \frac{di_L}{dt} = & -1.1 k_1 e^{-1.1t} \cos(0.43t) \\ & + k_2 e^{-1.1t} \times (0.43) (\sin - 0.43t) \\ & - e^{-t} - 1.1 k_2 e^{-1.1t} \sin(0.43t) \end{aligned}$$

$$+ k_2 e^{-1.1t} (0.43t) (\cos 0.43t)$$

$$0.43 k_2 - 1 - 1.1 k_1 = 0$$

$$0.43 k_2 = 1.1 k_1 + 1$$



$$P = \frac{-1}{-1} = 1$$

$$iL(0^+) = \frac{10}{7} A$$

$$\frac{di_L}{dt}(0^+) = \frac{10}{7} \times 0 A$$

$$i_L = k_1 e^{-1.1t} \cos(0.43t) + k_2 e^{-1.1t} \sin(0.43t) + e^{-t}$$

$$\frac{10}{7} = k_1 + 1$$

$$k_1 = 3/7$$

$$\begin{aligned} \frac{di_L}{dt} = & -1.1 k_1 e^{-1.1t} \cos(0.43t) \\ & + k_2 e^{-1.1t} \times (0.43) (\sin - 0.43t) \\ & - e^{-t} - 1.1 k_2 e^{-1.1t} \sin(0.43t) \end{aligned}$$

$$+ k_2 e^{-1.1t} (0.43t) (\cos 0.43t)$$

$$0.43 k_2 - 1 - 1.1 k_1 = 0$$



$$0.43 k_2 = 1.1 k_1 + 1$$

$$\underline{K_2 = 3.42}$$

$$i_L = \left[ \frac{3}{7} e^{-1.1t} \cos(0.43t) + 3.42 e^{-1.1t} \sin(0.43t) \right] u(t)$$

43t)

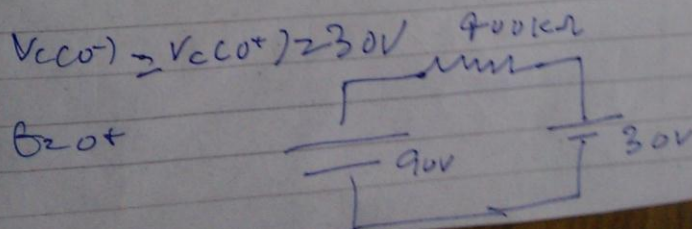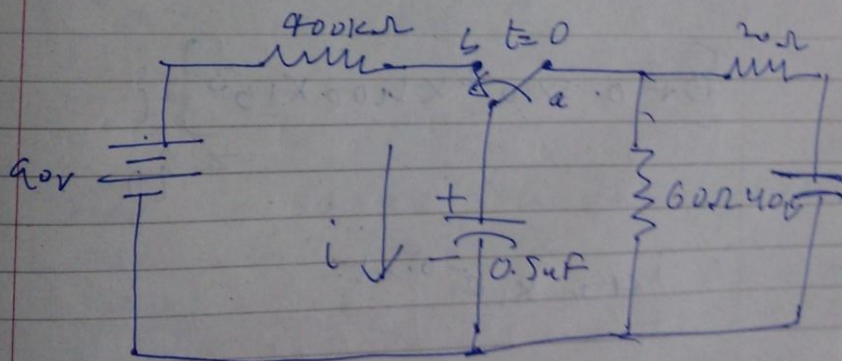5 The switch in the circuit shown in fig 5 has been in position a for a long time. At  $t=0$ , the switch is moved to position 'b'. Obtain an expression for  $v(t)$  &  $i(t)$  for  $t \geq 0$






$$V_C(0^-) = V_C(0^+) = 30V$$

$$i_{CC(0^+)} = 0.15mA$$

$$t > 0$$

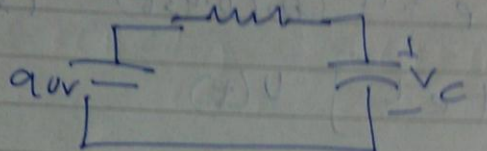

$$90 = (400 \times 10^3) i_C + V_C$$

$$90 = V_C + 400 \times 10^3 \frac{dV_C}{dt}$$

$$\left[ 1 + 0.5 \times 10^{-6} \times 400 \times 10^3 \right] \dot{V}_C = 90$$

$$i_{CF2} = K_1 e^{-0.2t}$$

PAGE: / /  
DATE: / /

$$PI = \frac{a_0}{0.2} = 450$$

$$V_C = 450 + K_1 e^{-0.2t}$$

$$V_C(0^+)$$


$$= 30 = 450 + K_1$$

$$K_1 = -420$$

$$V_C = 450 - 420 e^{-0.2t}$$

$$\boxed{C \frac{dV_C}{dt} = 4.2 \times 10^{-5} e^{-0.2t}}$$

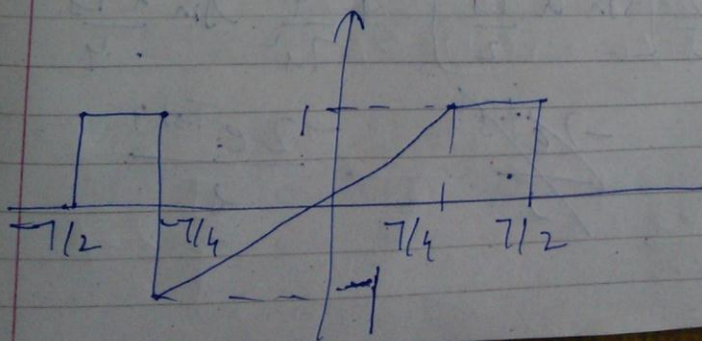6 Find the Laplace transform of waveforms shown in fig 6a and 6b.





$$f(t) = u(t + T/2) - 2u(t + T/4)$$

$$+ \frac{1}{T} u(t + T/4) \times 2T +$$

$$- \frac{2}{T} u(t - T/4) - u(t - T/2) \Rightarrow$$


$$F(s) = \frac{e^{T/2}}{s} - \frac{2e^{T/4}}{s} + \frac{2}{T} \left( \frac{1}{s^2} \right) e^{-T/4} - \frac{e^{-T/2}}{s} + \frac{2}{T} \left( \frac{1}{s^2} \right) e^{T/4}$$

$$\frac{1}{s} \left[ e^{T/2} - e^{T/4} \right] + \frac{2}{T} \left( \frac{1}{s^2} \right) \left[ e^{T/4} - e^{-T/4} \right]$$

$$= \frac{2}{s} \left[ \sin a \frac{T}{2} \right] + \frac{4}{T s^2} \sin \frac{h T}{4}$$

$$- \frac{2e^{T/4}}{s} - \frac{2e^{-T/4}}{s}$$

68

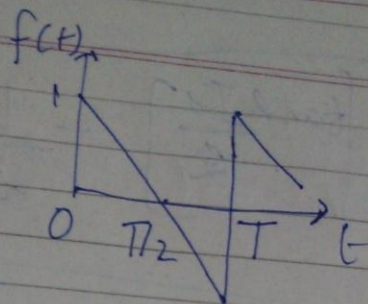

$$f(t) = u(t) - \frac{1}{T}r(t) + \frac{1}{T}r(t-T) + u(t-T)$$

44

$$F(s) = \frac{1}{s} - \frac{1}{s^2} + \frac{e^{-Ts}}{s^2} + \frac{e^{-Ts}}{s}$$

$e^{-Ts}$

$$F(s) = \frac{F_1(s)}{1 - e^{-Ts}}$$


$$\frac{\frac{1}{s} [1 + e^{-Ts}] - \frac{1}{s^2} [1 - e^{-Ts}]}{1 - e^{-Ts}}$$

$$= \frac{1}{s} \left[ \frac{1 + e^{-Ts}}{1 - e^{-Ts}} \right] - \frac{1}{s^2} \left[ \frac{1 - e^{-Ts}}{1 - e^{-Ts}} \right]$$




$$\frac{1}{s} \left[ \frac{\tanh \frac{Ts}{2}}{2} \right] = \frac{1}{s^2}$$

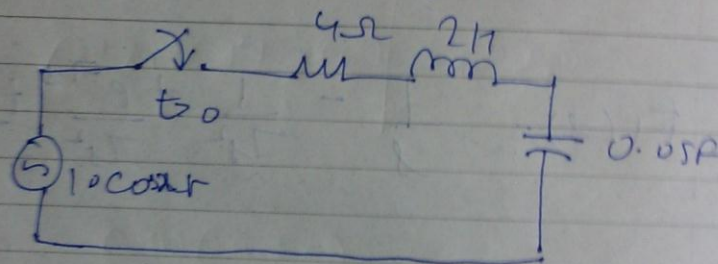1 Determine  $i(t)$  in the circuit shown in Fig 7 use Laplace transform method.




$t=0^-$

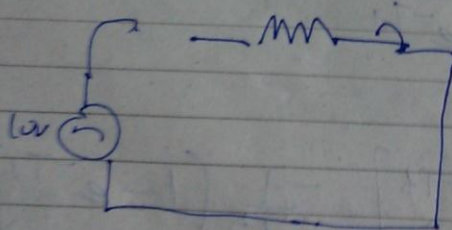


$$V_C(0^-) = V_C(0^+) = 0V$$


$$i_L(0^-) = i_L(0^+) = 0A$$

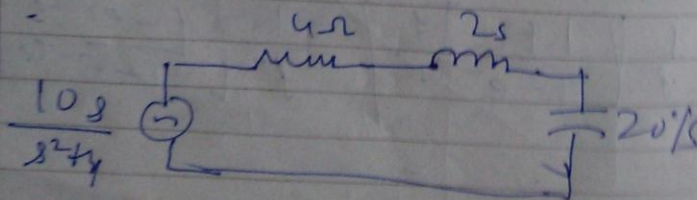

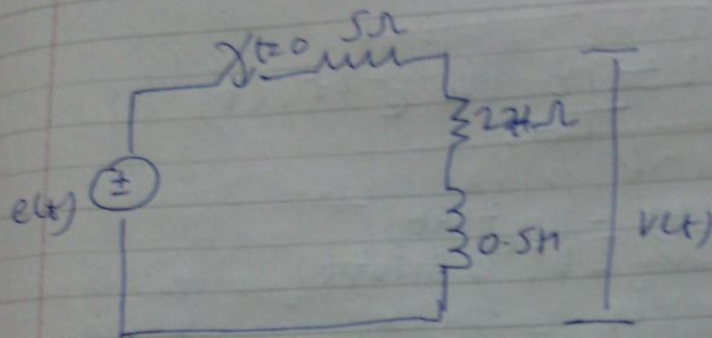12. In the network shown, find  $V(t)$  using convolution integral theorem if  $e(t) = 3e^{-2t} V(t)$



in Laplace

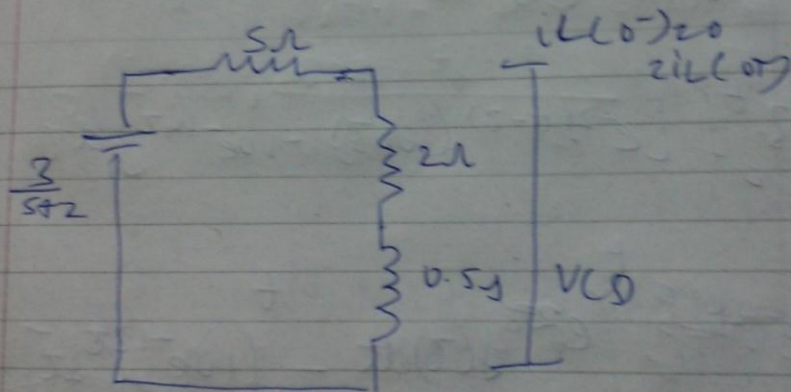

$$V(s) = \left( \frac{\frac{3}{s+2}}{5 + 0.5s} \right) \times (2 + 0.5s)$$

$$= \frac{3(0.5s + 2)}{(7 + 0.5s)(s + 2)} = \frac{s + 4}{(14 + s)(s + 2)}$$



$$3 \left( \frac{s+4}{14+s} \right) \cdot \left( \frac{1}{s+2} \right)$$

$\swarrow f_1(s)$        $\searrow e^{-2t}$   
 $\searrow e^{-2t}$        $\swarrow f_2(s)$

$$3 \left( 1 - \frac{10}{14+s} \right) \cdot e^{-2t}$$

$\downarrow$   
 $g(t) - 10e^{-14t}$        $\swarrow f_1(t)$

By applying convolution theorem

$$3 \int_0^t [e^{2(t-\tau)} (g(\tau) - 10e^{-14\tau})] d\tau$$

$$3e^{-2t} \left[ \int_0^t e^{2\tau} g(\tau) d\tau - \int_0^t 10e^{-12\tau} d\tau \right]$$

$$3e^{-2t} \left[ 1 + \frac{5}{6} e^{-12t} - \frac{5}{6} \right]$$

$$3e^{-2t} \left[ \frac{1}{6} + 5e^{-12t} \right]$$

$$\frac{3e^{-2t}}{6} [1 + 5e^{-12t}]$$

$$\frac{3}{6} [e^{-2t} + 5e^{-14t}]$$

$$= \frac{1}{2} [e^{-2t} + 5e^{-14t}]$$

(13) The impulse response of a network is given by  $h(t) = 2\delta(t) - 4e^{-3t}u(t)$ . Find the current response of the network for a voltage excitation  $v(t) = 7e^{-2t}u(t)$  using C.T.

$$h(t) = i(t) = 2\delta(t) - 4e^{-3t}$$

$$v(s) \cdot i(s) = 1(s)$$

By applying convolution integral theorem

$$i(t) = \int_0^t 7e^{-2(t-\tau)} u(t-\tau) [2\delta(\tau) - 4e^{-3\tau}u(\tau)] d\tau$$

$$= 7e^{-2t} \left[ \int_0^t e^{2\tau} \cdot 2\delta(\tau) d\tau - \int_0^t 4e^{-\tau} d\tau \right]$$

$$= 7e^{-2t} \left[ 2 - \left[ \frac{4e^{-\tau}}{-1} - \frac{4}{-1} \right] \right]$$



$$7e^{-2t} \left[ 2 + 4e^{-t} - 4 \right]$$

$$7e^{-2t} \left[ 4e^{-t} - 2 \right]$$

$$\boxed{28e^{-3t} - 14e^{-2t}} = i(t)$$

14 Using IVT and FVT, find the values of  $p(0)$  and  $f(\infty)$ , wherever applicable

$$(i) F(s) = \frac{2s^3 - s^2 - 3s - 5}{s^3 + 6s^2 + 10s}$$

$$f(0) = \lim_{s \rightarrow \infty} sF(s)$$

$$f(\infty) = \lim_{s \rightarrow 0} sF(s)$$

$$sF(s) = \frac{s(2s^3 - s^2 - 3s - 5)}{s(s^2 + 6s + 10)}$$

$$= \frac{2s^3 - s^2 - 3s - 5}{s^2 + 6s + 10}$$

$$= -\frac{5}{6} \text{ FVT}$$

$$\underline{15} \text{ V}$$

IVT not applicable as degree is same

$$(ii) F(s) = \frac{8s-2}{s^2+1}$$

$$\lim_{s \rightarrow \infty} F(s) = \frac{s^2 \left[ 8 - \frac{2}{s} \right]}{s^2 \left[ 1 + \frac{1}{s^2} \right]}$$

$$= 8 = IVT$$

$$\lim_{s \rightarrow 0} F(s) = \frac{8s^2 - 2s}{s^2 + 1} = 0$$

$$15 \quad V(s) = \frac{3s(s+1)}{(s+2)(s^2+2s+2)}$$

$$= \frac{3s(s+1)}{(s+2)(s-(-1+i))(s-(-1-i))}$$



$$K(-1+i) = \frac{3 \times \sqrt{2} \angle 135^\circ \times 1 \angle 90^\circ}{\sqrt{2} \angle 45^\circ \times 2 \angle 90^\circ}$$

$$= 1.5i$$

$$\Rightarrow K(-1-i) = -1.5i$$

$$K(-2) = 3 \times \left[ \frac{1 \angle 180^\circ \times 2 \angle 180^\circ}{2} \right]$$

$$= \underline{\underline{3}}$$

$$\Rightarrow v(t) = 3 \cdot e^{-2t} + 1.5i e^{(-1+i)t} - 1.5i e^{(-1-i)t}$$

